

# 11080 BDC

## Intelligently Controlling Brushed DC Motors

# Objectives

- Further your understanding of brushed DC motors and how to control them
- Understanding Pulse Width Modulation
- Familiarize you with a couple of Microchip's development tools
- Show you an application of brushed DC motor control

# Agenda

1. Brushed DC Motor Basics
  - A). Principles of Operation
  - B). 4 Types of BDCMs
  
2. Motor Control
  - A). Drive Topologies
  - B). CCP ( PWM Mode )
  - C). Speed Measuring
  - D). ECCP ( Enhanced PWM )

# Brushed DC Motor Basics


# Principles of Operation

1. Stator
2. Rotor / Armature
3. Brushes and Commutator


# Stator

- Generates a stationary magnetic field that surrounds the rotor, this field is generated by either:

permanent magnets

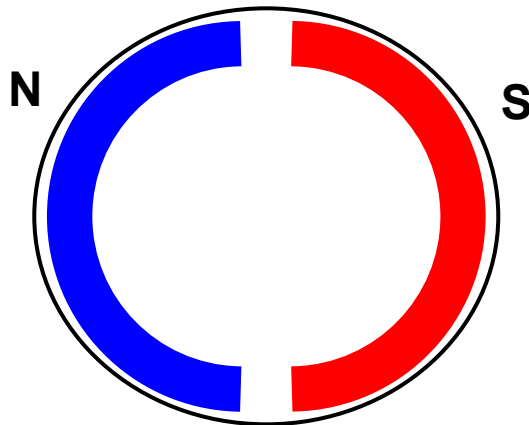


electromagnetic windings

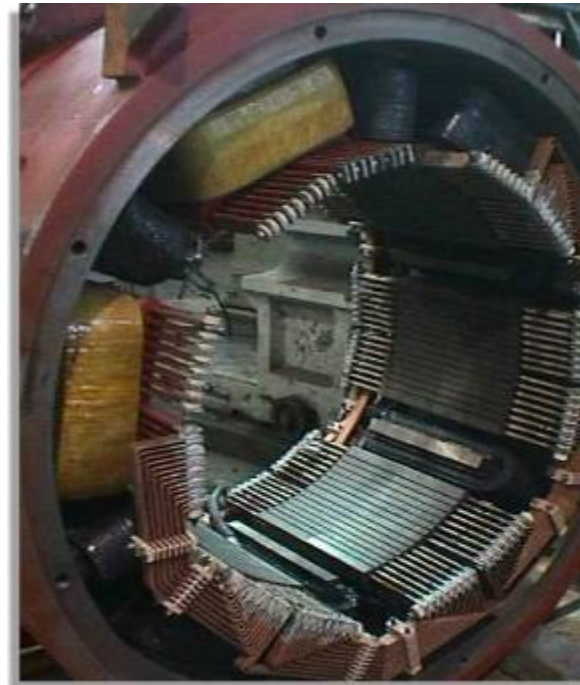

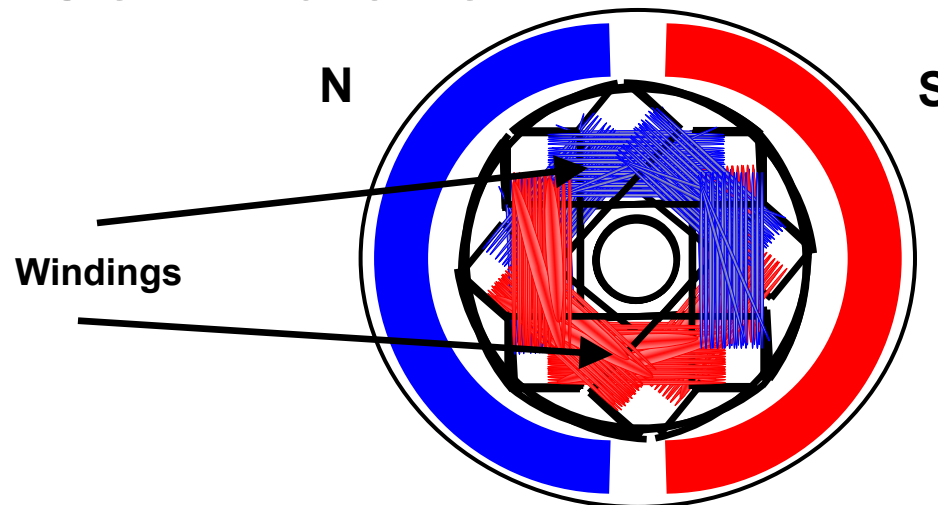
# Rotor

- Also known as the Armature
- Made up of one or more windings
- Commutation




# Brushes and Commutator

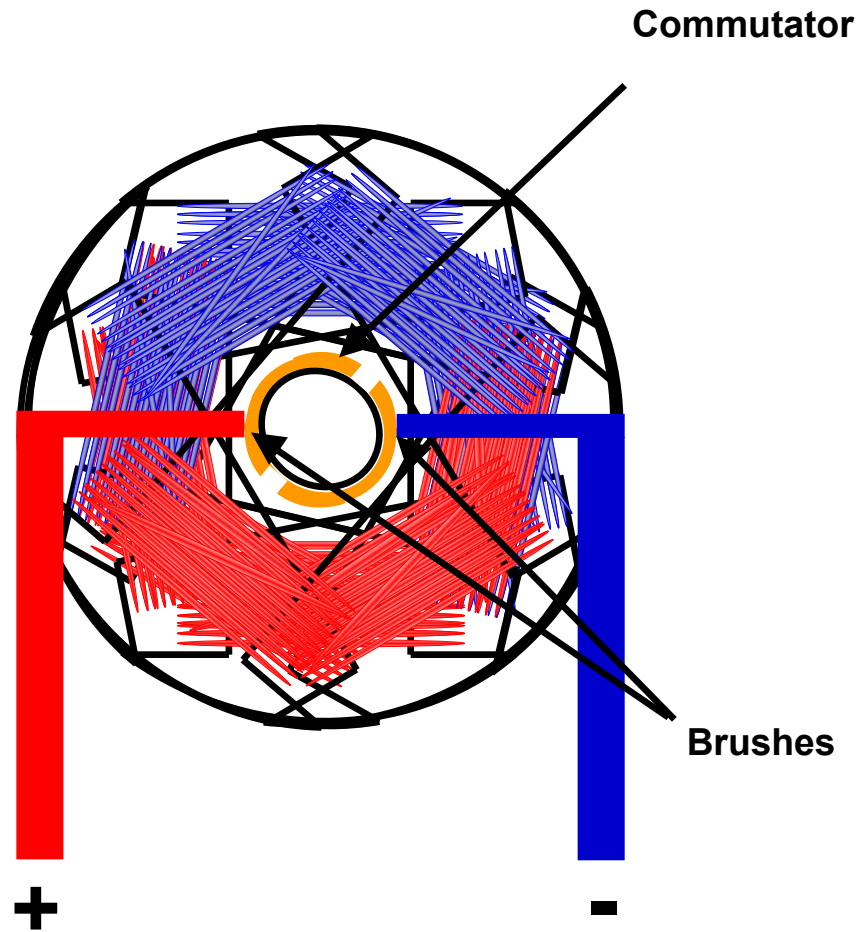



# Brushed DC Motor

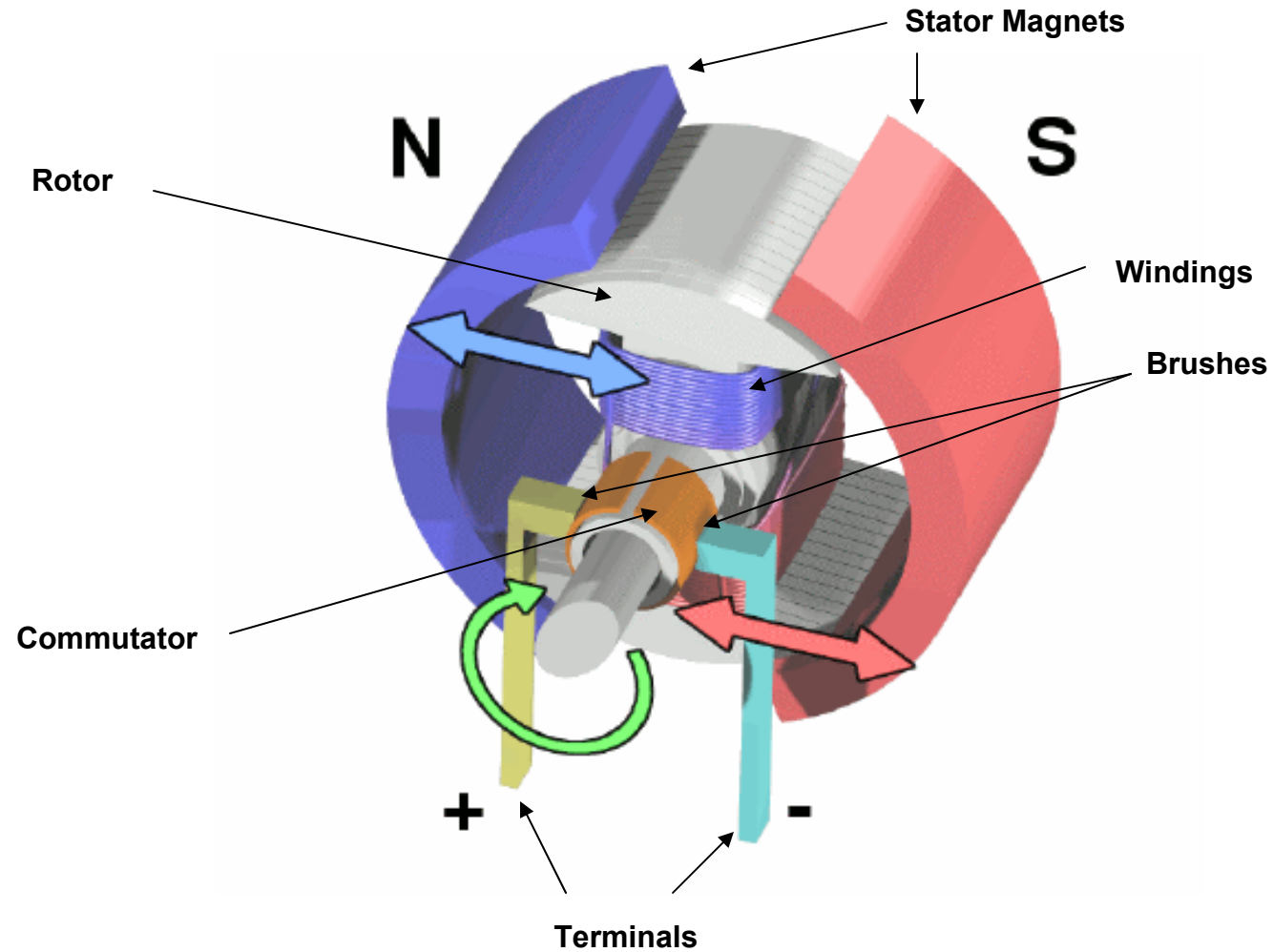


# Four Types of BDCMs


1. Permanent Magnet
2. Shunt - wound
3. Series - wound
4. Compound - wound
  - Shunt + Series
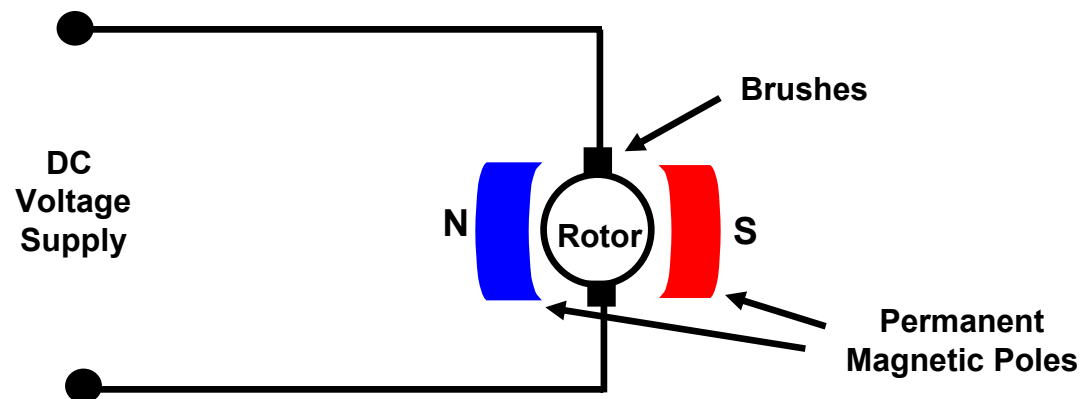
# Permanent Magnet (PMDC)

- Most common
- Used in fractional horsepower applications  
Examples: Toys, RC app., Slot cars, Appliances, etc...
- More cost effective than wound stators
- Torque, limited b/c of stator field
  - Good low end ( low speed ) torque
  - Limited high end ( high speed ) torque
- Responds very quickly to voltage changes due to constant stator field ( good speed control )
- **Drawback, Magnets lose their magnetic properties over time**



# Shunt-Wound (SHWDC)

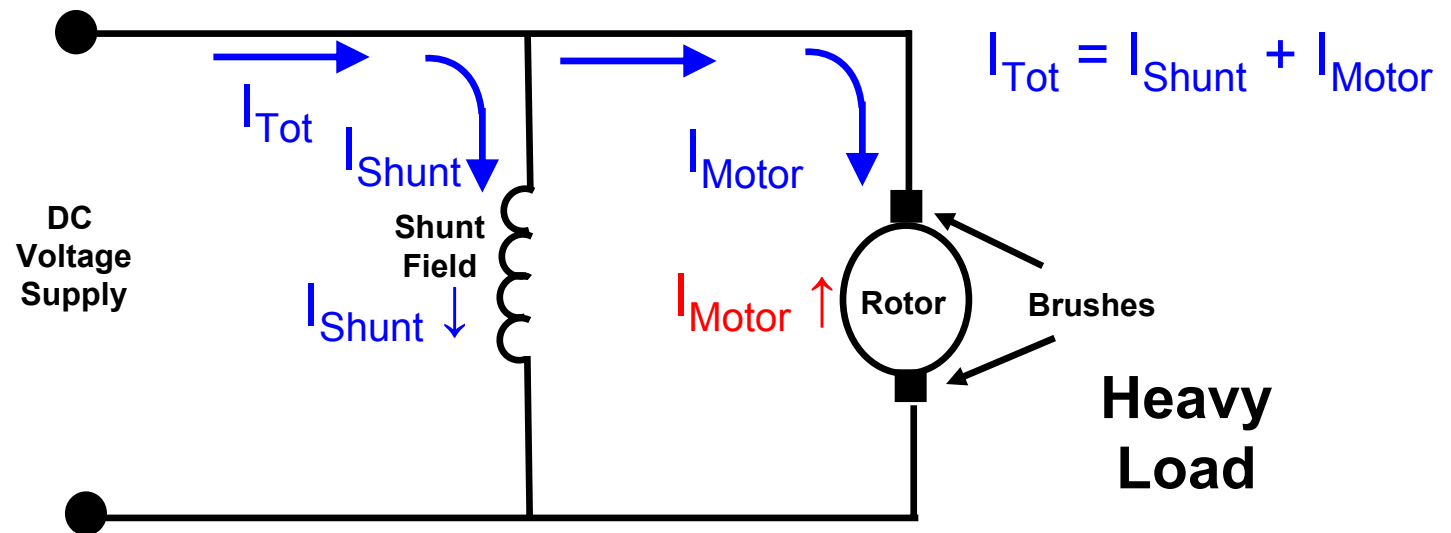


- As  $V_{Supply} \uparrow$ ,  $I_{Tot} \uparrow$ , speed  $\uparrow$ , stator/rotor field  $\uparrow$ , thus Torque  $\downarrow$
- As motor load  $\uparrow$ ,  $I_{Motor} \uparrow$ ,  $I_{Shunt} \downarrow$ , stator field  $\downarrow$ , rotor field  $\uparrow$ , speed  $\downarrow$ , thus Torque  $\uparrow$


# Shunt-Wound
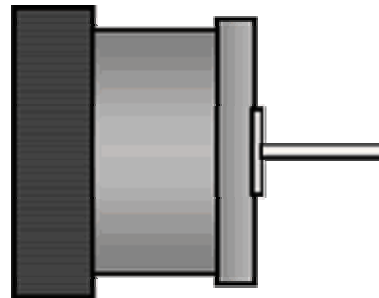
## (SHWDC)

- Decreasing torque at high speed
- At low speed, higher more consistent torque
- Excellent speed control
- Typically used in Industrial and automotive applications
- No loss of magnetism over time as with PMDC motors
- More expensive than PMDC motors
- Motor Runaway, if the shunt current goes to zero



# Series-Wound (SWDC)

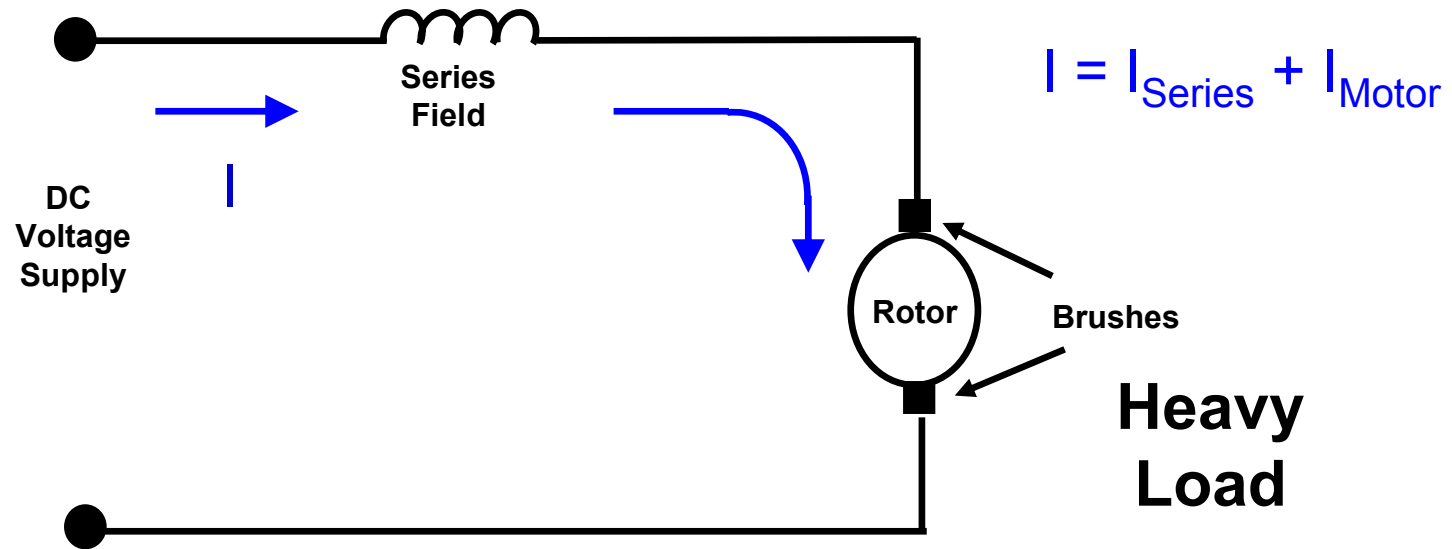


- As  $V_{\text{Supply}} \uparrow$ ,  $I \uparrow$ , Stator/Rotor field  $\uparrow$ , speed  $\uparrow$ , thus torque  $\downarrow$
- As motor load  $\uparrow$ ,  $I \uparrow$ , Stator/Rotor field  $\uparrow$ , speed  $\downarrow$ , thus torque  $\uparrow$

# Series-Wound

## (SWDC)

- Great slow speed torque ( low end )
  - But, as load is removed, speed increases sharply
- Ideally suited for heavy loads, examples: cranes and winches
  
- Poor high speed torque ( high end )
- More expensive than PMDC
- Poor speed control due to the series stator field
- Motor Runaway, if the series field is shorted

# Compound-Wound (CWDC)

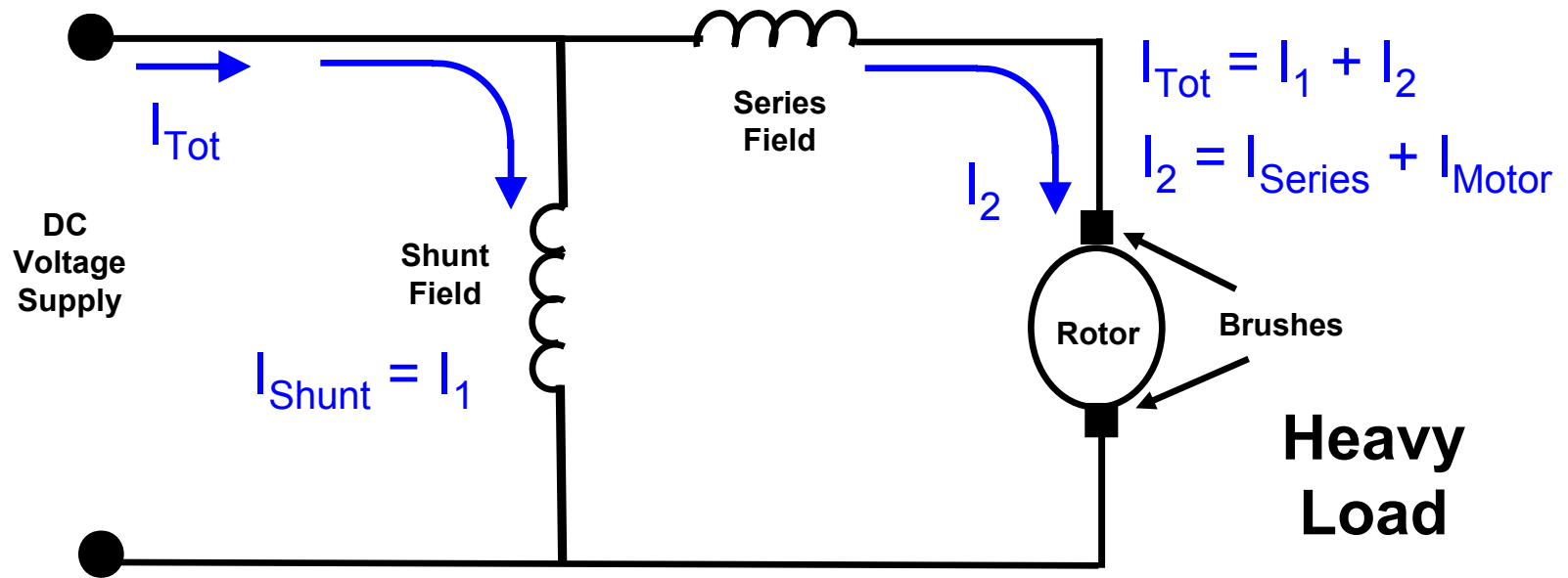


- As motor load  $\uparrow$ ,  $I_{Shunt} \downarrow$ , shunt field  $\downarrow$ ,  $I_2 \uparrow$ , Series field/Rotor field  $\uparrow$ , speed  $\downarrow$ , thus torque  $\uparrow$



# Compound-Wound (CWDC)

- Has the performance properties of both SHWDC and SWDC motors
- High torque at low speed w/ heavy loads, SHWDC motors
- Great speed control, SWDC motors
- Great for Industrial and automotive applications, example: generators
- Motor Runaway, less likely b/c shunt current must go to zero and series field must short
- More expensive than PMDC, SHWDC, and SWDC

# Performance Comparison

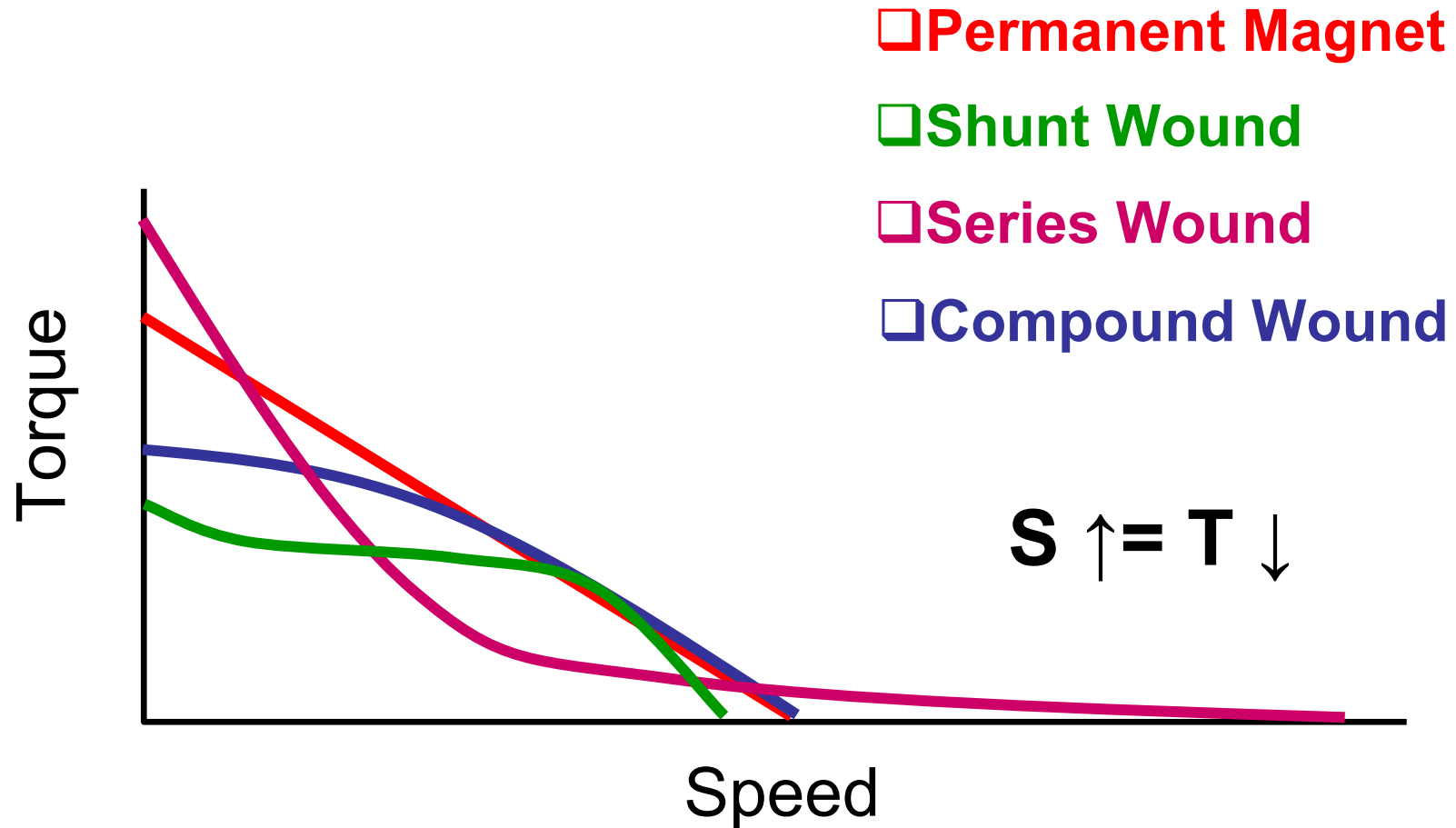


# Motor Control

# Motor Control Topologies

- Chopper
  - Low Side Drive
  - High Side Drive
- Half Bridge
  - Low Side Drive
  - High Side Drive
- Full Bridge (H-Bridge)


# Chopper

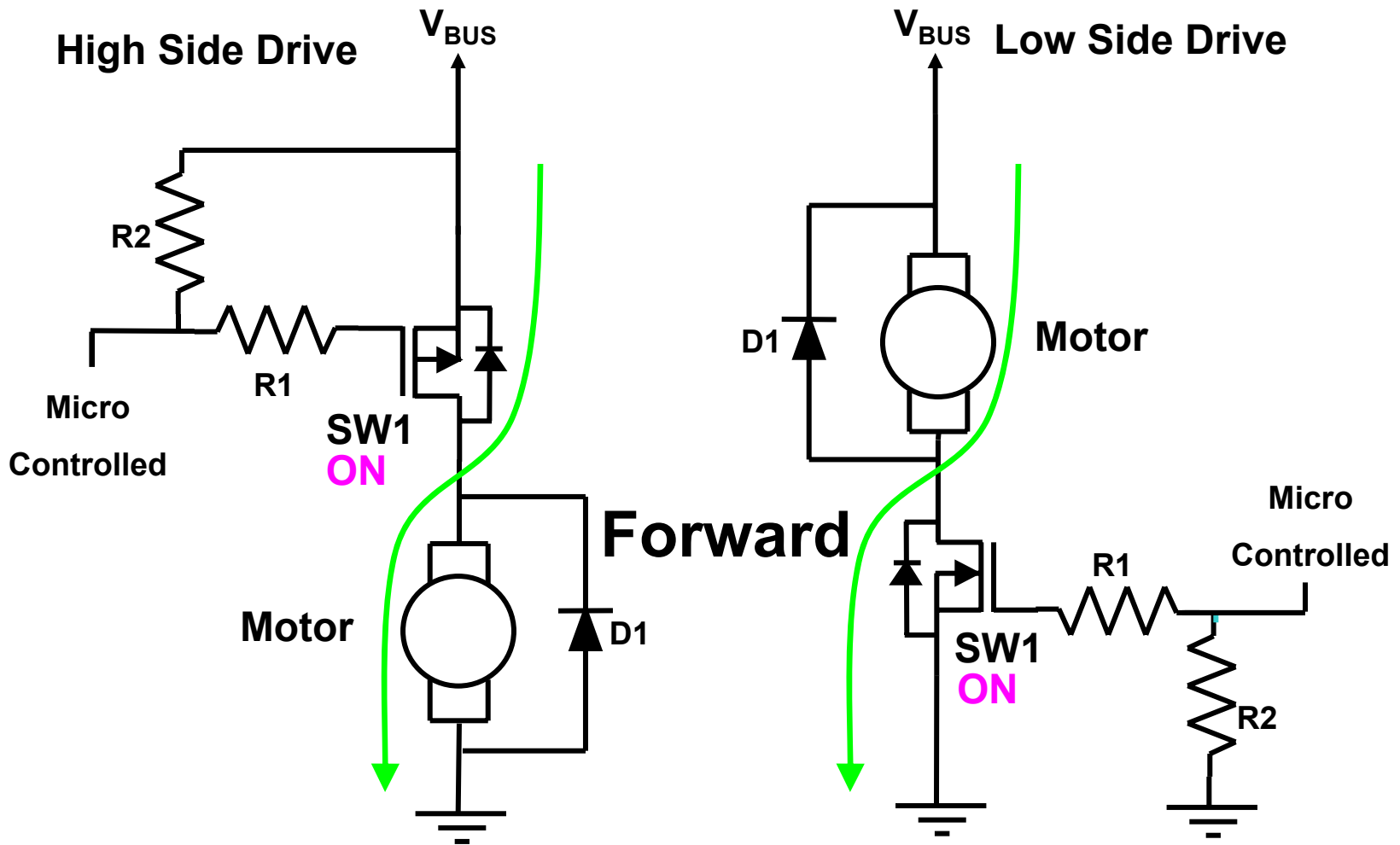


# Chopper

- Example: Fan controller
- Advantages
  - Simplest drive circuit for driving the switch
  - Less expensive, 1 MOSFET
- Safety ( High side drive )
- Disadvantages of the Chopper Topology
  - Can only go forward
  - No braking

# Half Bridge

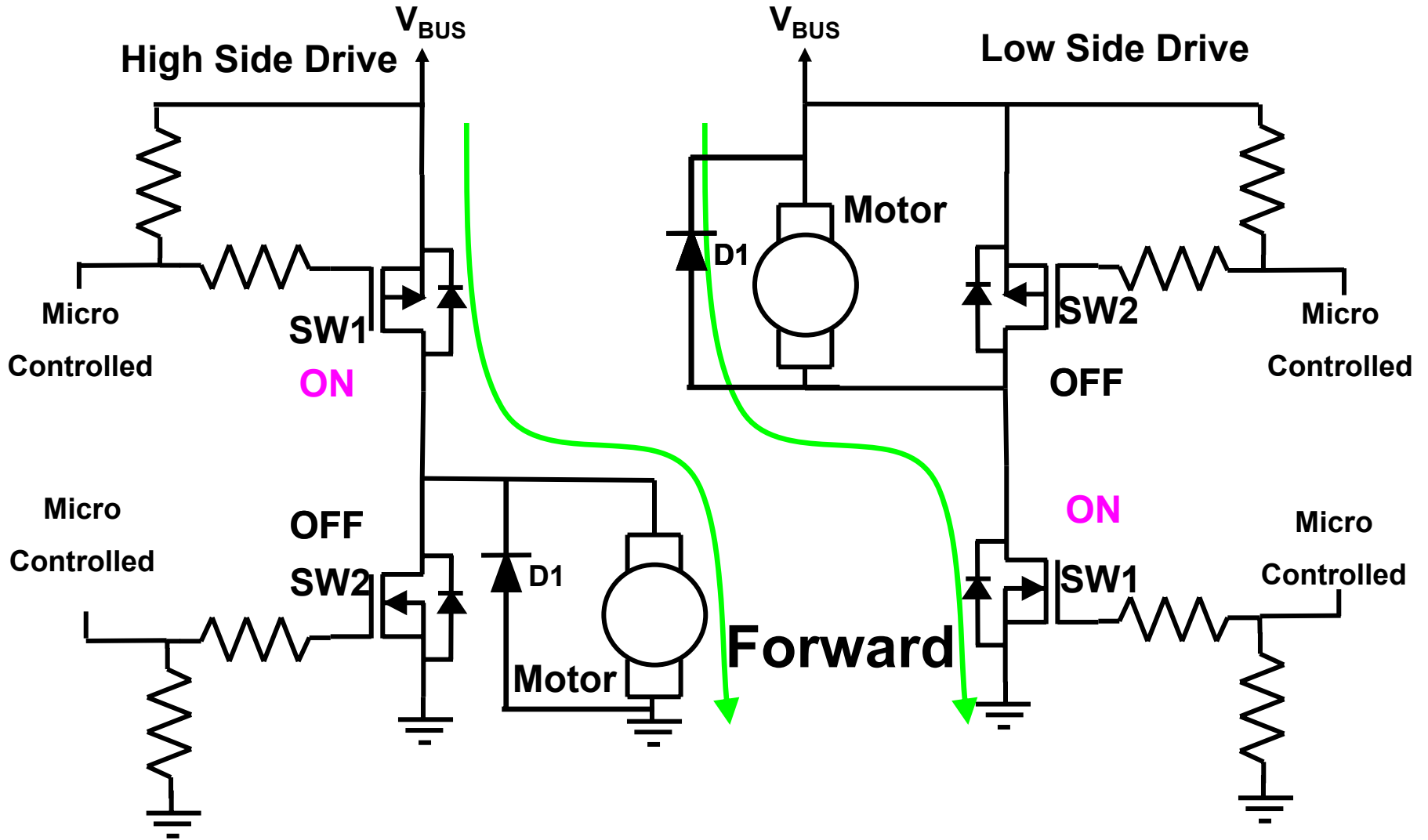


# Half Bridge

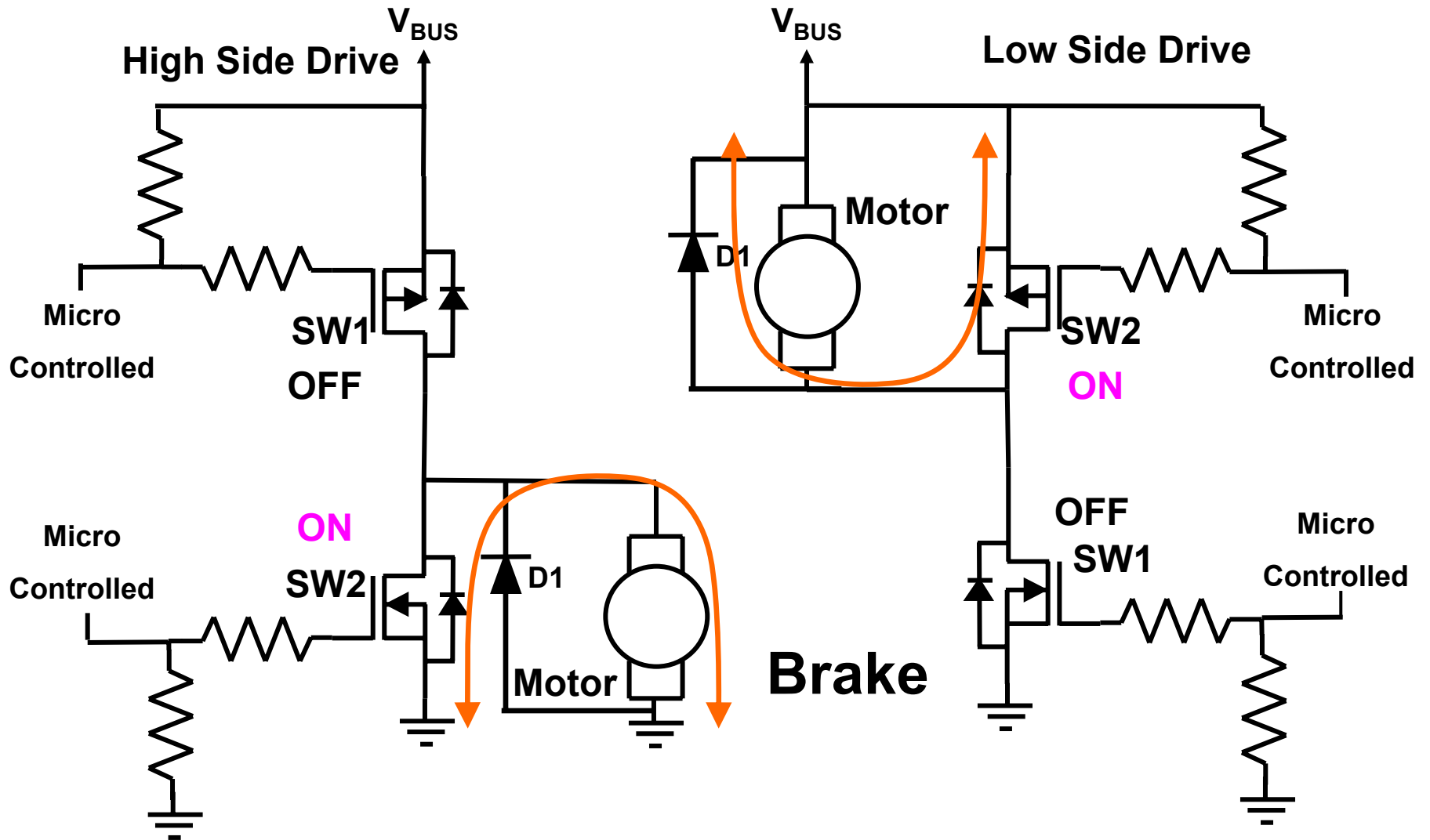




# Half Bridge

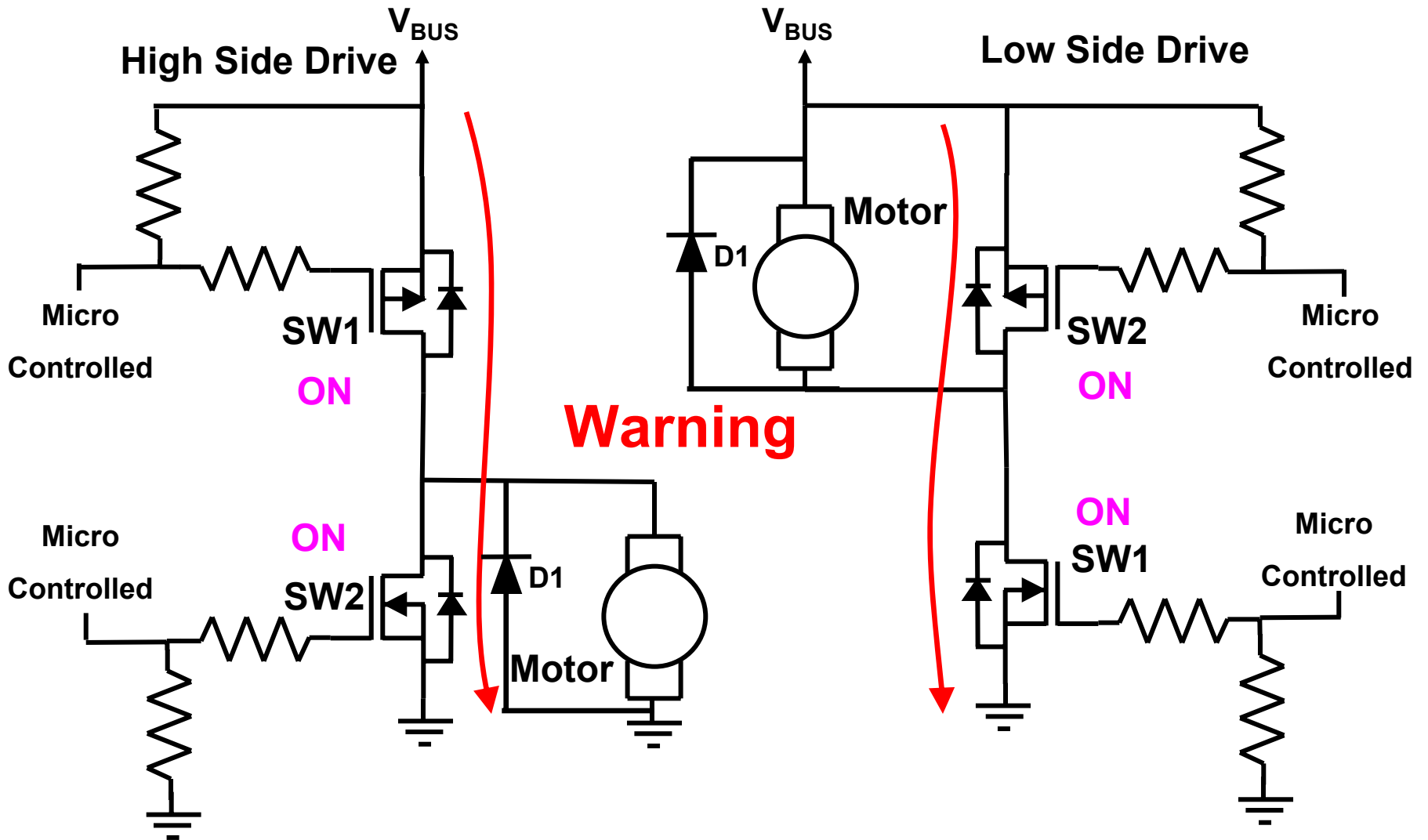


# Half Bridge

- Example: Slot car
- Advantages
  - Ability to brake the motor
  - Safety (High Side Drive)
- Disadvantages
  - Can only go forward
  - More parts, 2 outputs to control
  - Can have both the N-channel and P-channel on at the same time


# Full Bridge

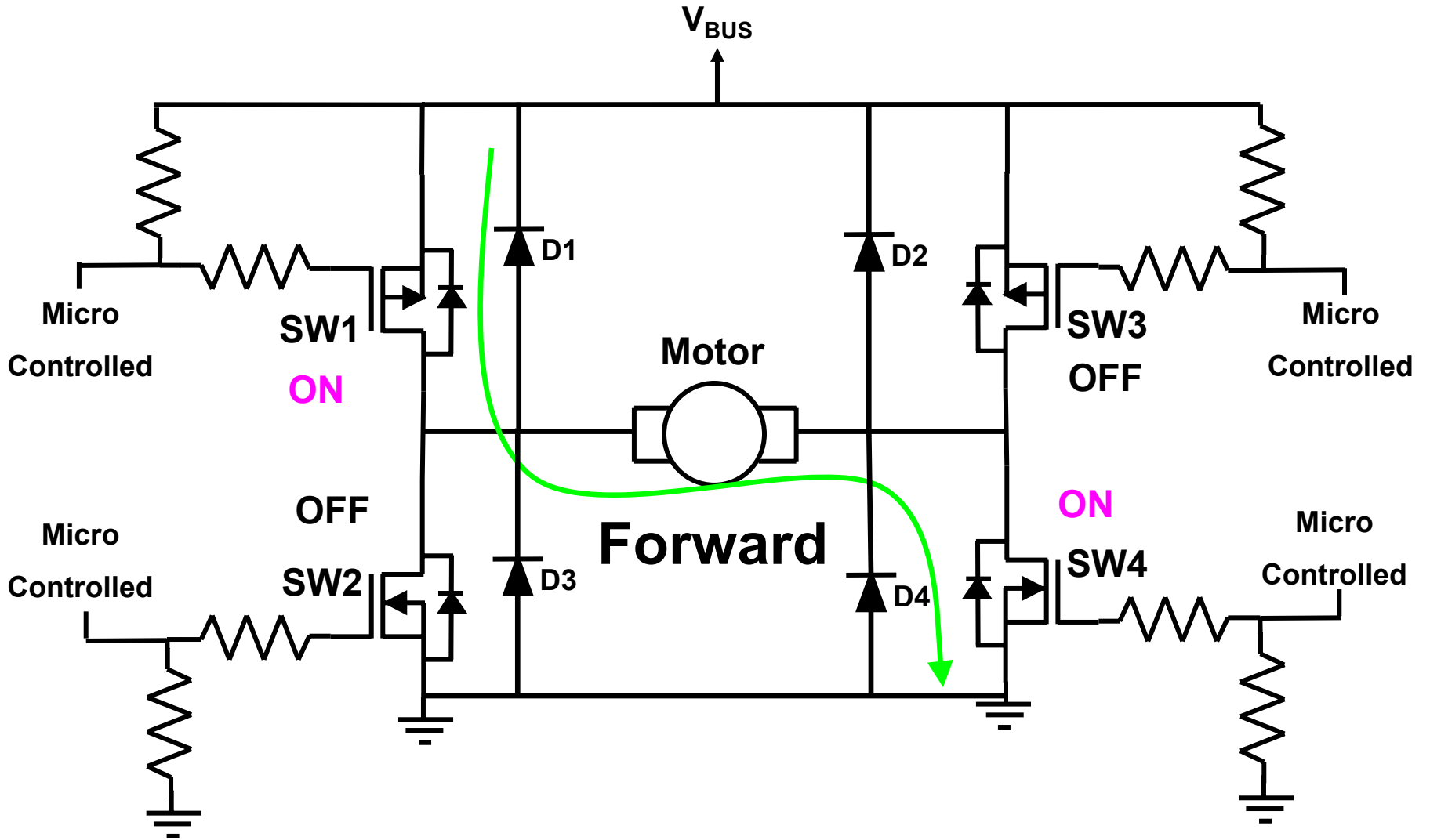


# Full Bridge

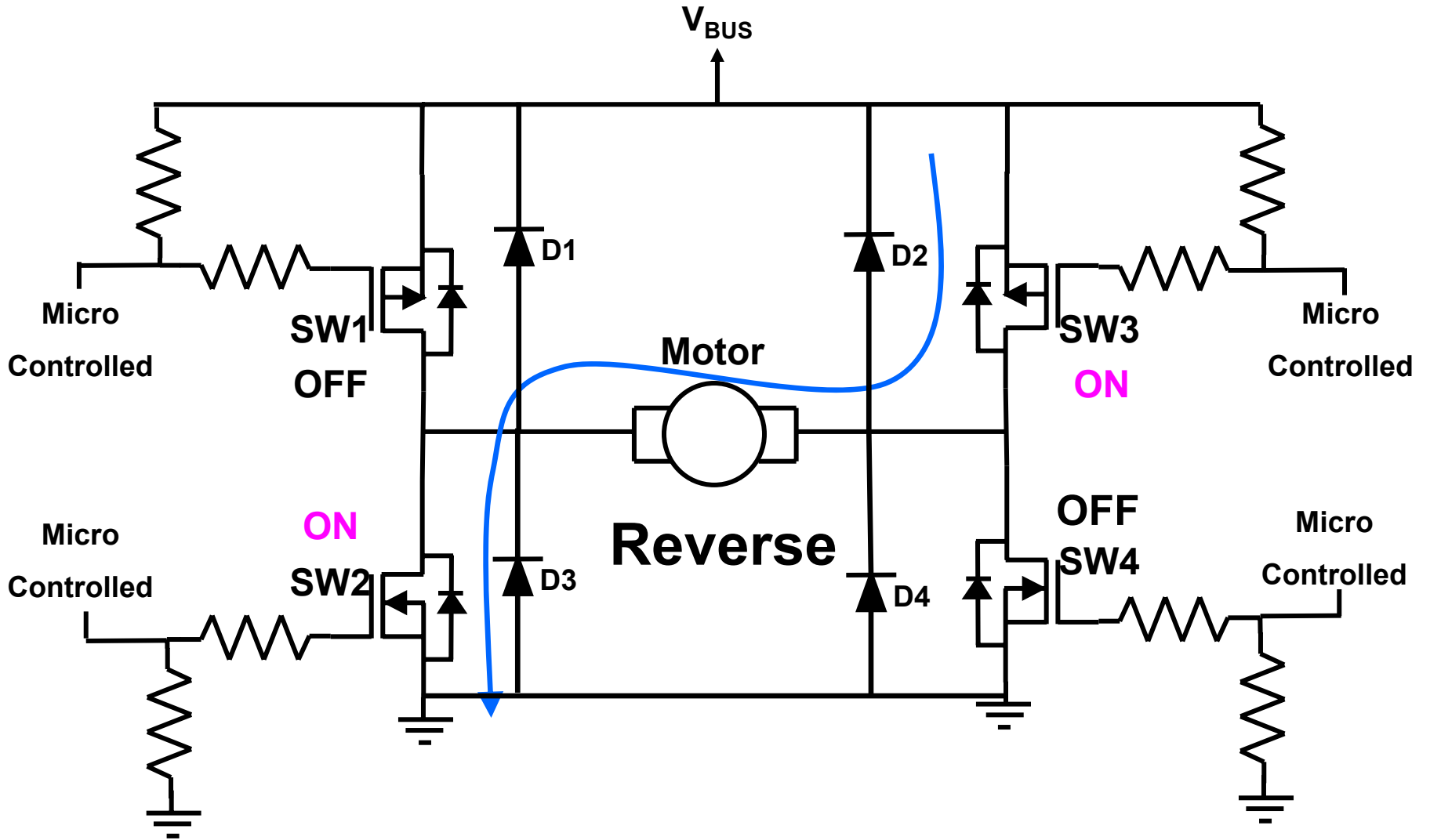

# Full Bridge

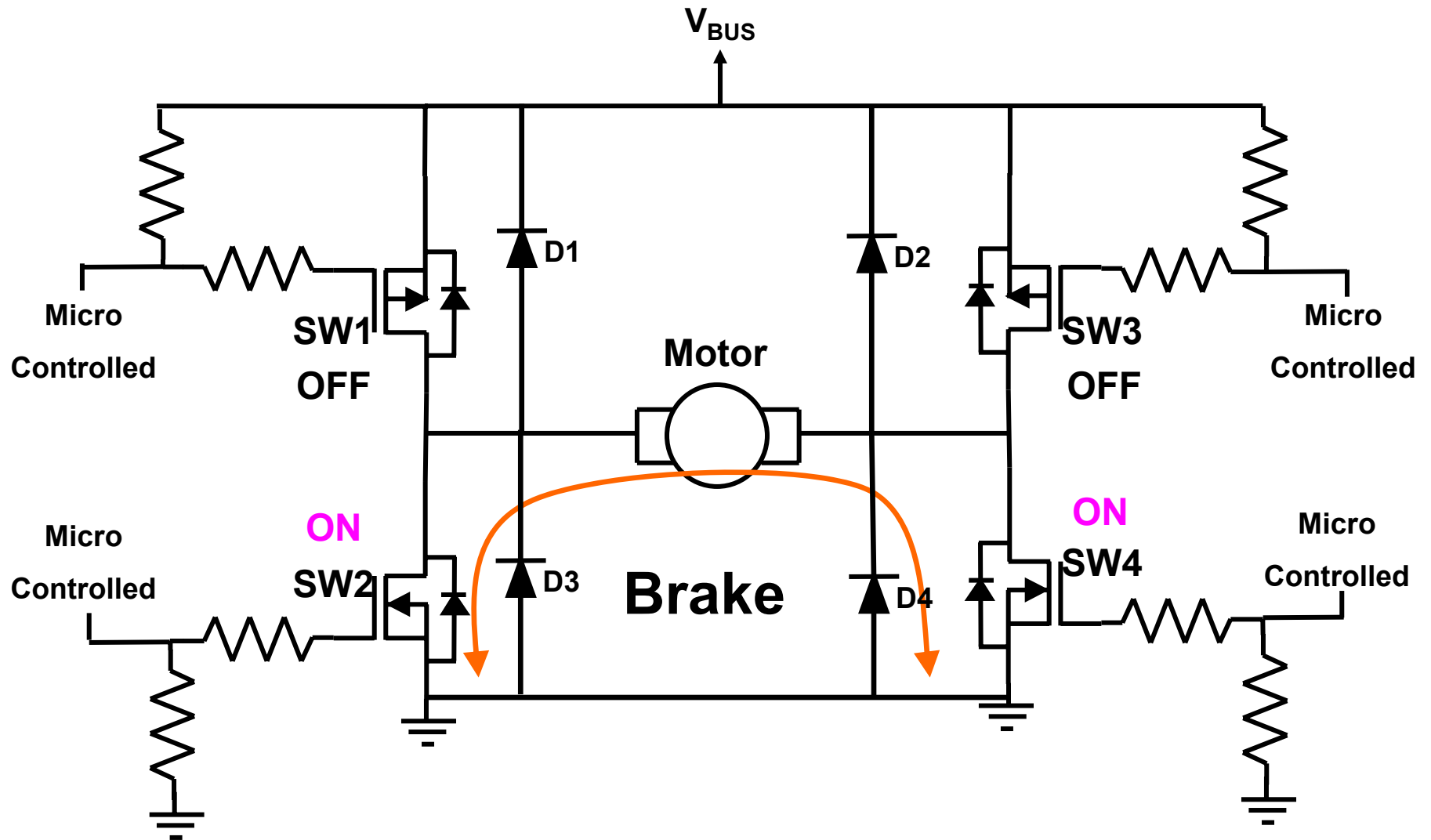

# Full Bridge

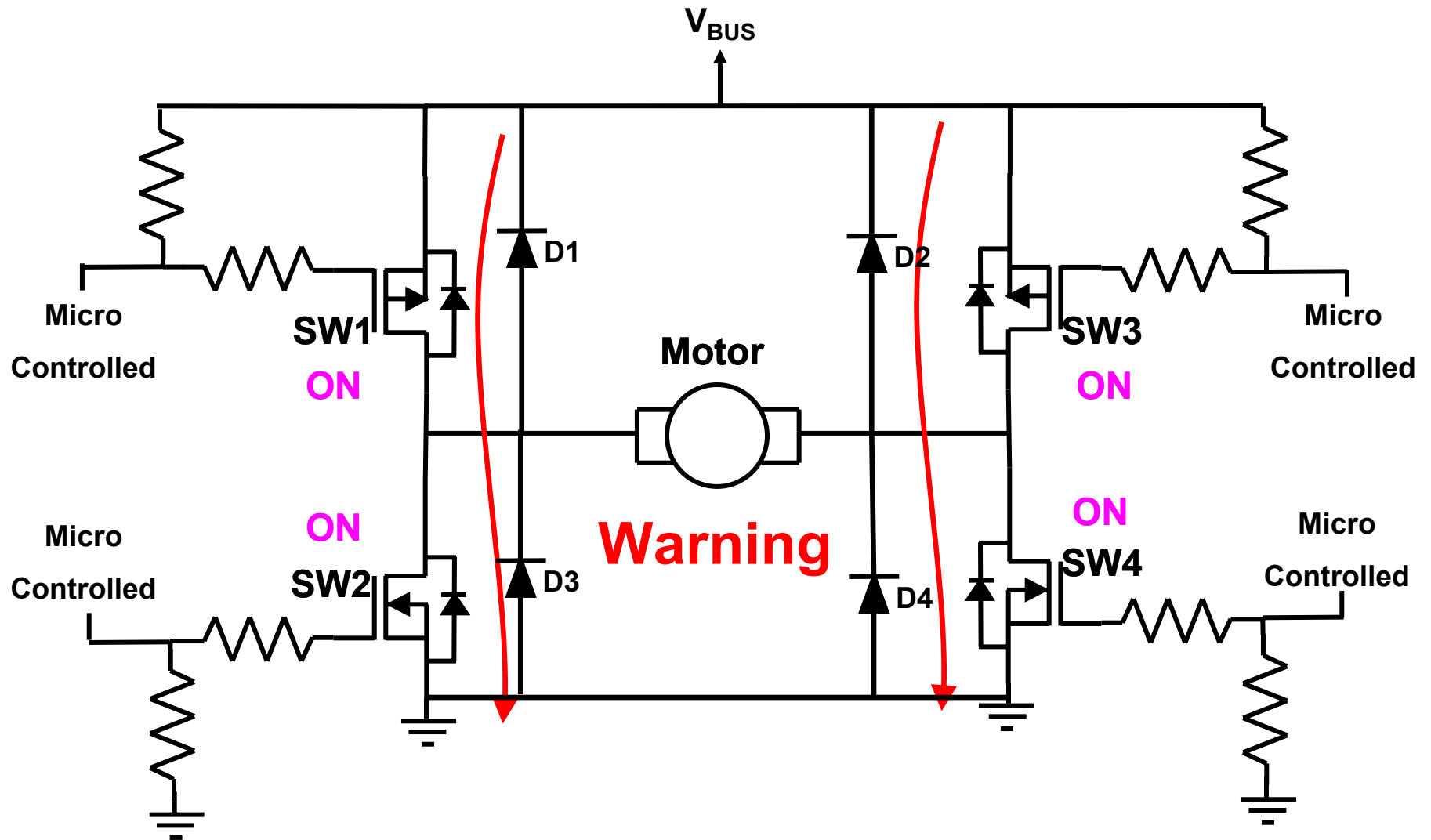

# Full Bridge

- Example: Cordless drill
- Advantages
  - Ability to drive the motor in reverse & brake
  - Safety ( High side drive )
- Disadvantages of the Full Bridge Topology
  - Most complicated
  - 4 outputs to control
  - Can have all N-channels and P-channels on at the same time

# Topology Review

- Chopper
  - Example: Fan control
  - Simplest, only one output to control
  - Fewest features
- Half Bridge
  - Example: Slot cars
  - More complex than the Chopper
  - Adds the Braking feature
- Full Bridge
  - Example: Cordless drill
  - Most complicated
  - Adds the features of Braking and Reverse



# Motor Control


How do we control the speed of a  
Brushed DC Motor?

# PWM


( Pulse Width Modulation )

- We control the speed by varying the voltage across the motor
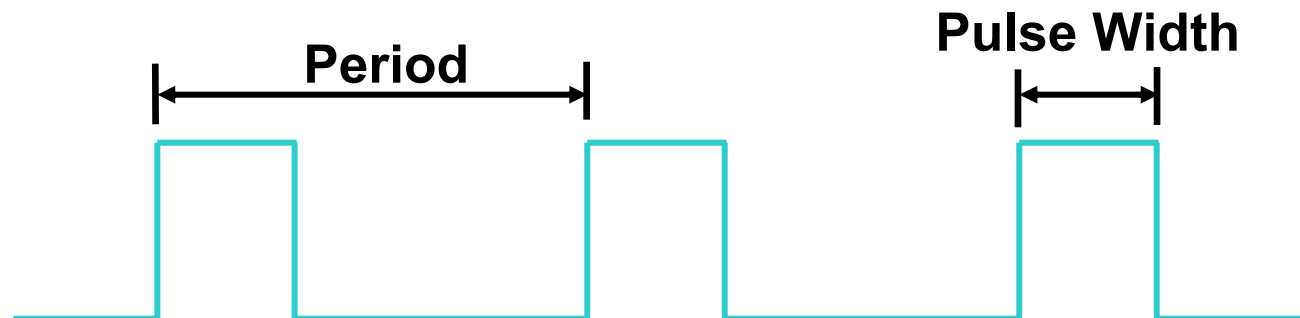
$$\begin{aligned} \text{Voltage Across Motor}_{\text{Avg.Volt}} &= \text{Voltage}_{\text{Supply}} \bullet \text{Duty Cycle} \\ &= VDD \bullet (\text{Pulse Width} / \text{Period}) \end{aligned}$$



# PWM

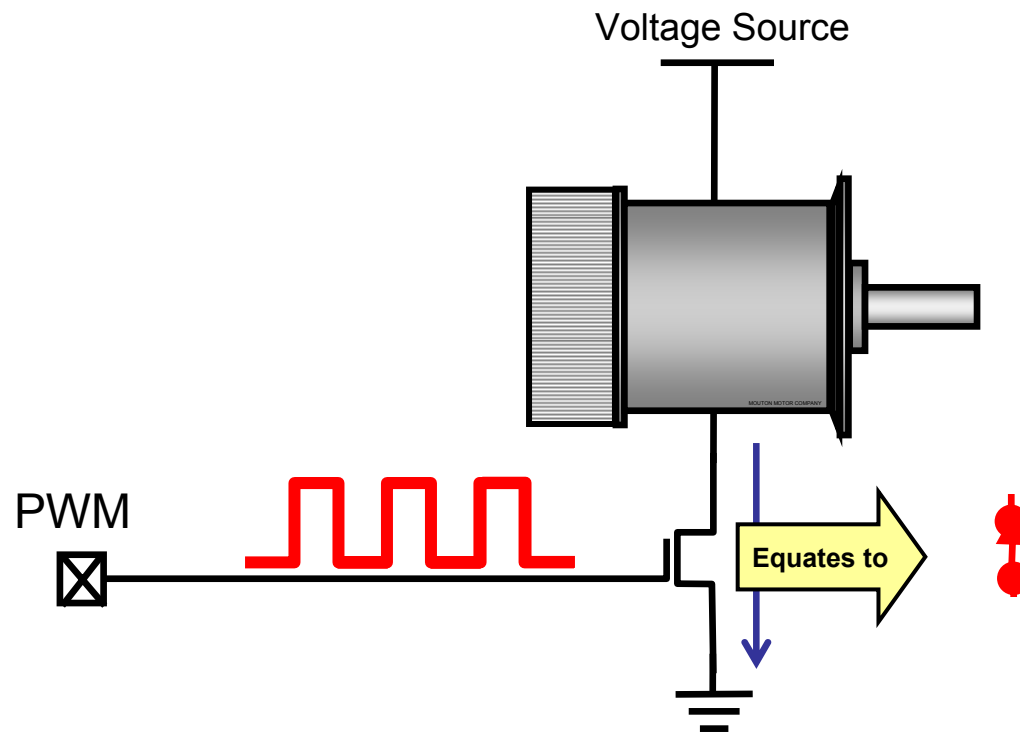


# Motor Control

- Brushed DC Motor acts like an Inductor
  - Current doesn't change instantaneously
  - As inductance increases, the slower the current changes


$$V(t) = L \bullet di/dt$$

- Voltage across motor is directly proportional to RPM
  - 100%RPM = 100% Duty cycle


# Motor Control

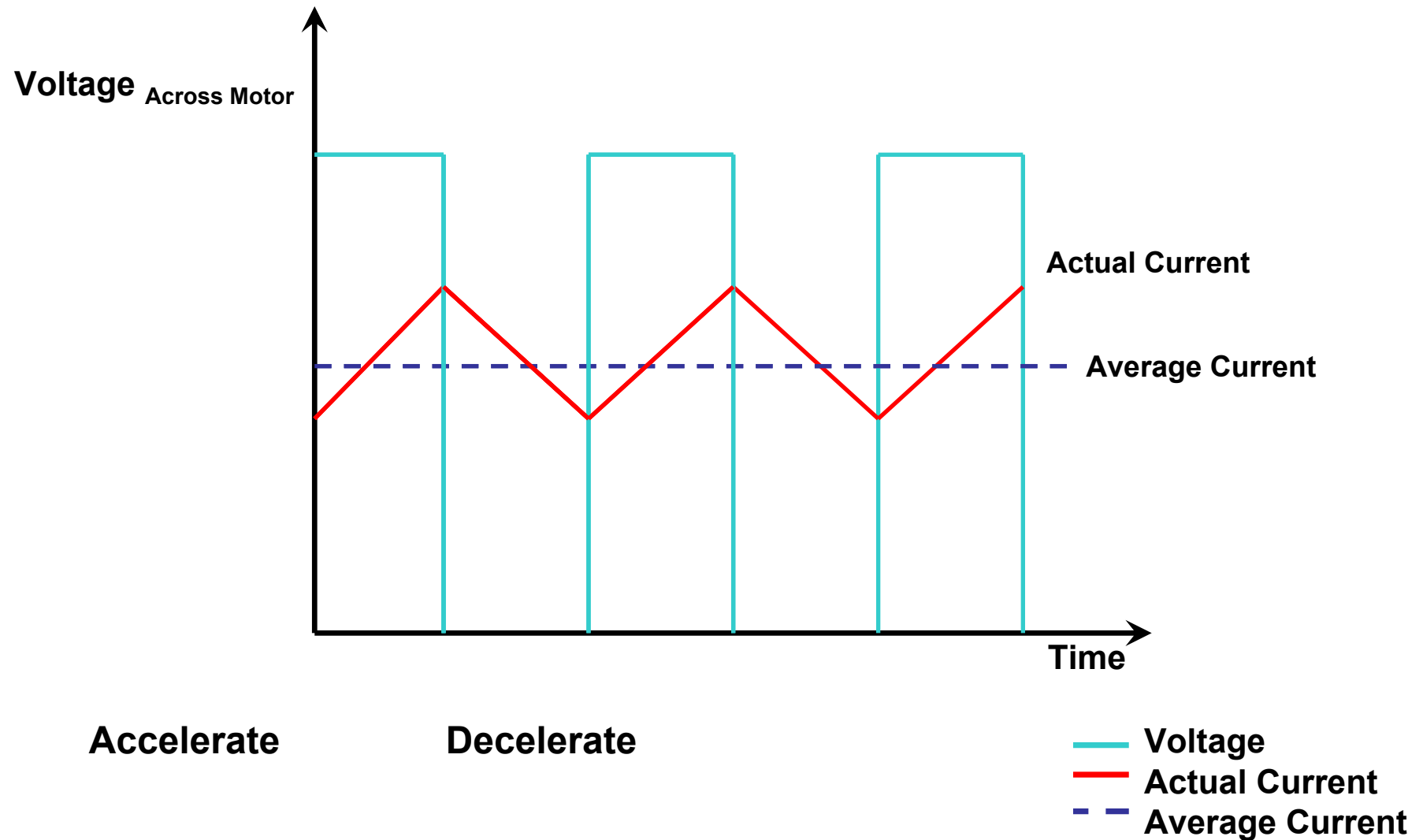


# Motor Control

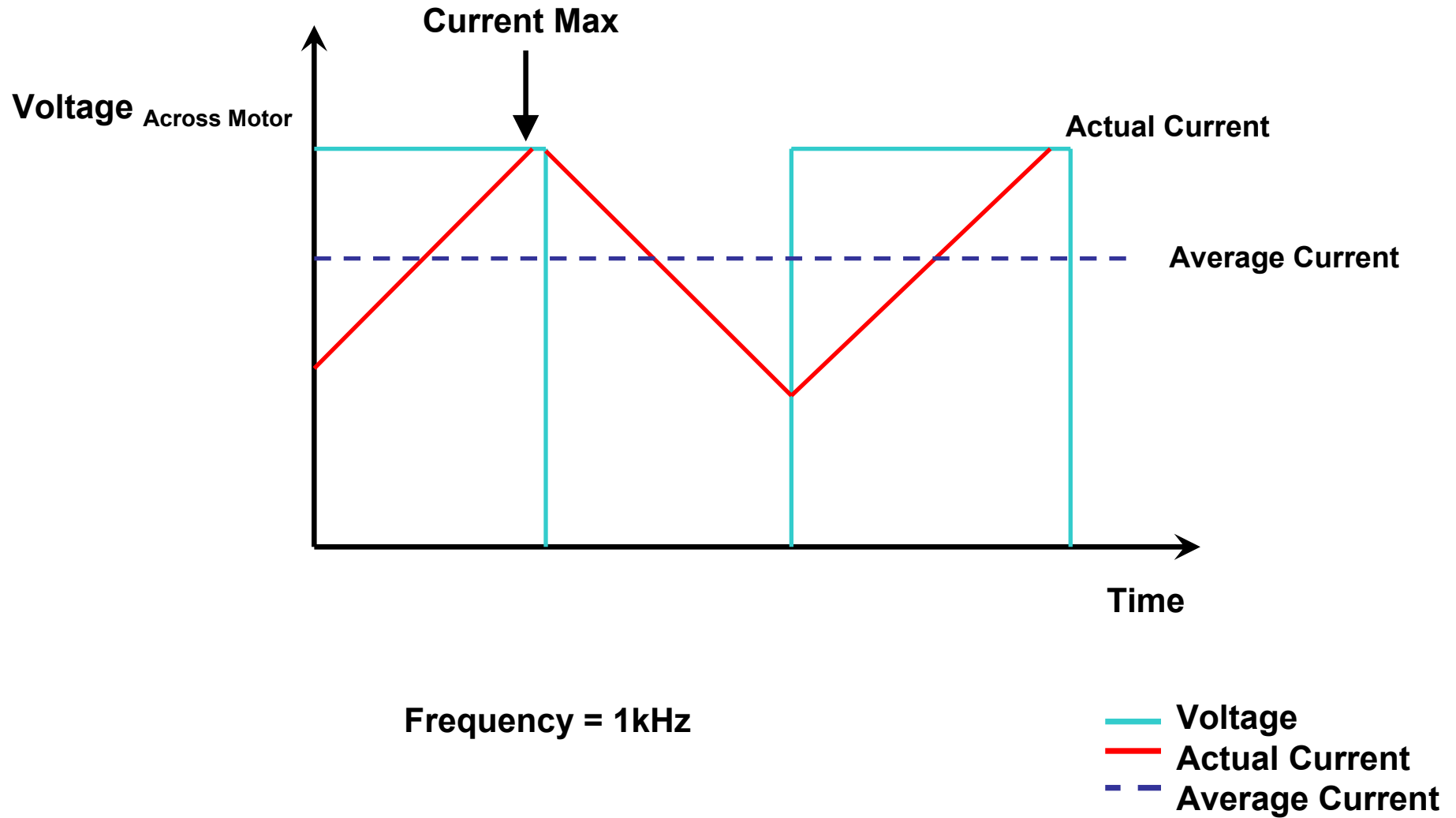

# Motor Control

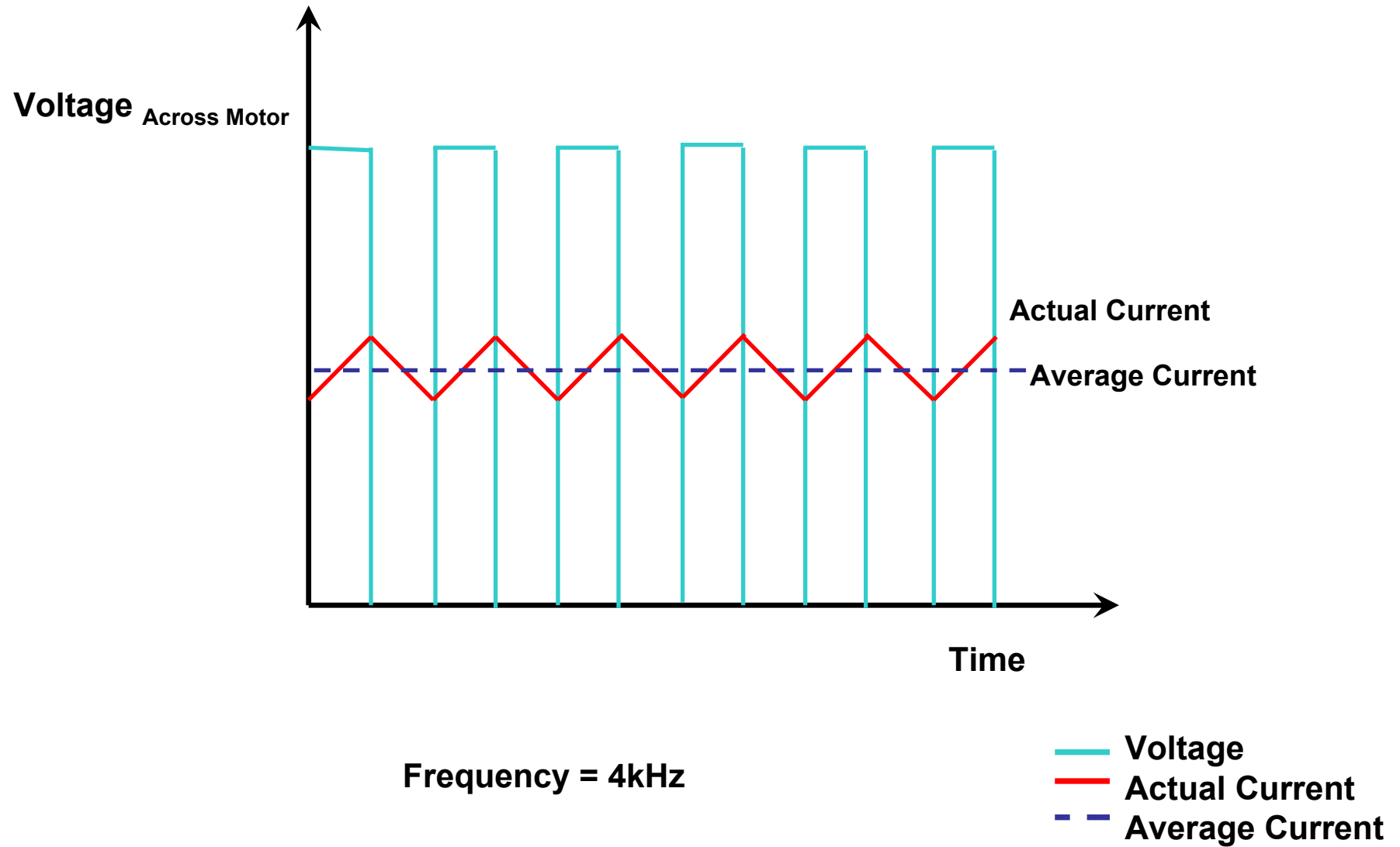

# Motor Control

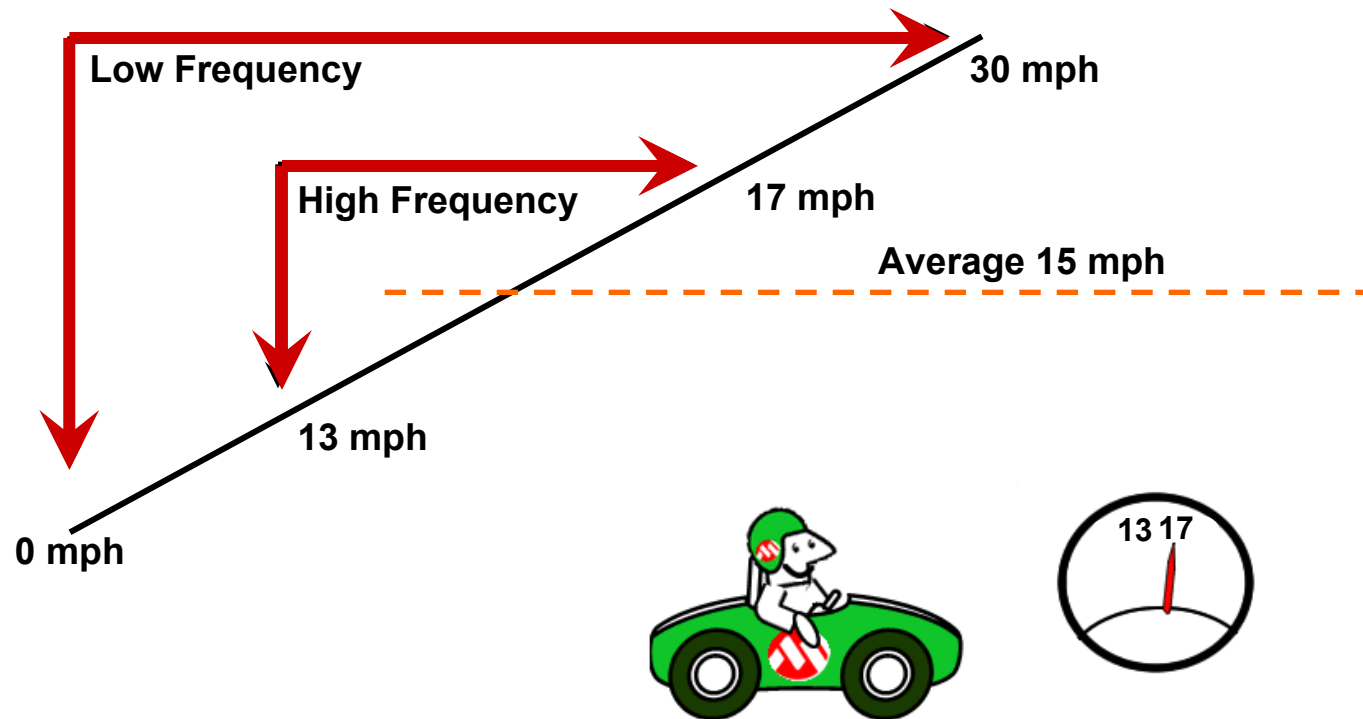


**So, is a higher frequency better?**




# Motor Control

## MOSFET Drive Circuit

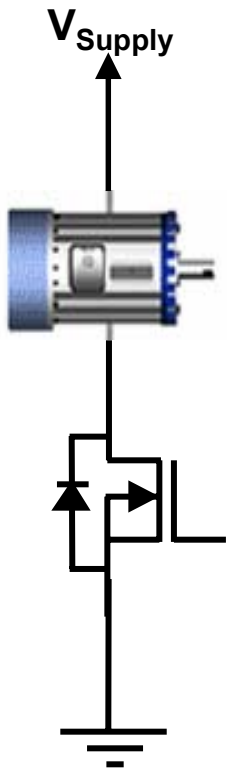

MOSFET dissipates more heat

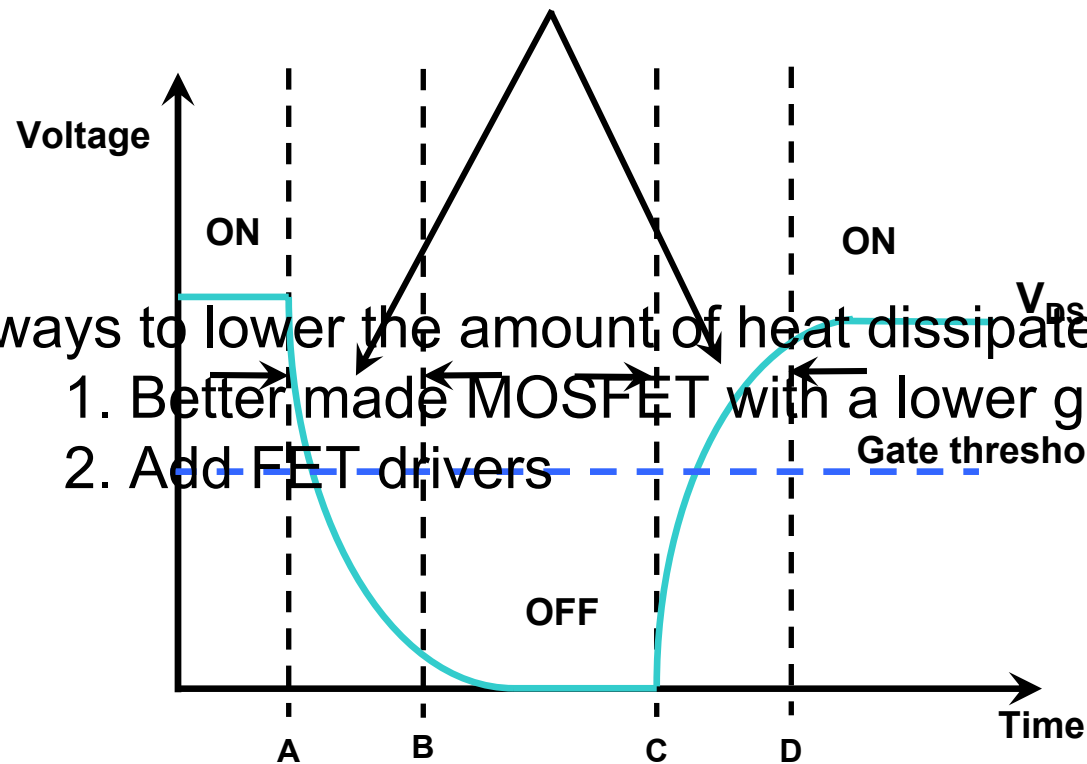

- 2 ways to lower the amount of heat dissipated:
  1. Better made MOSFET with a lower gate charge
  2. Add FET drivers

# Deciding on a PWM Frequency

- **2 considerations when choosing PWM frequency**
  - 1). Heat dissipated in the MOSFETs**
    - Switching speed
  - 2). Responsiveness of the motor**
    - A motor responds faster to changes in duty cycle at higher frequencies
  - 3). Sound generated by the motor**
    - Motor whines at 20Hz to 4kHz range
    - To avoid motor whine set frequency above 4kHz
  - 4). Speed at which the motor is operating**
    - At lower speeds you want a higher frequency, constant torque


# CCP

# Capture/Compare/PWM

# CCP Module

- What is it?  
The Capture/Compare/PWM module is a peripheral which allows the user to time and control different events
- What does it consist of?
  - Capture mode: allows timing of an events duration
  - Compare mode: allows the user to trigger an external event when a predetermined amount of time has expired
  - PWM mode: generates a pulse-width modulated signal of varying freq. and duty cycle on a single output
    - ▶ TMR2
    - ▶ PR2
    - ▶ CCPR1L
    - ▶ CCP1CON

# Hardware PWM

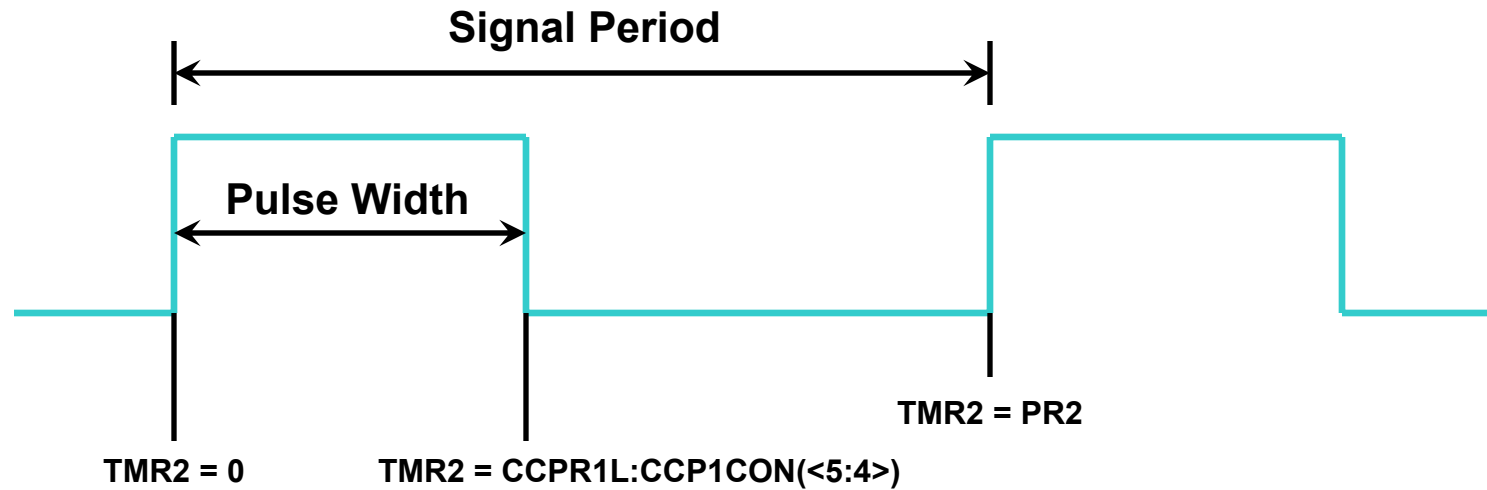

## Equations

$$\text{Period}_{PWM}(\text{seconds}) = (PR2 + 1) \cdot 4 \cdot T_{osc} \cdot TMR2 \text{ Prescaler}$$


$$\text{Duty Cycle}_{PWM}(\text{ratio}) = (CCPR1L:CCP1CON\langle 5:4 \rangle) / 4 ( PR2 + 1 )$$

# Lab 1

## Hardware PWM
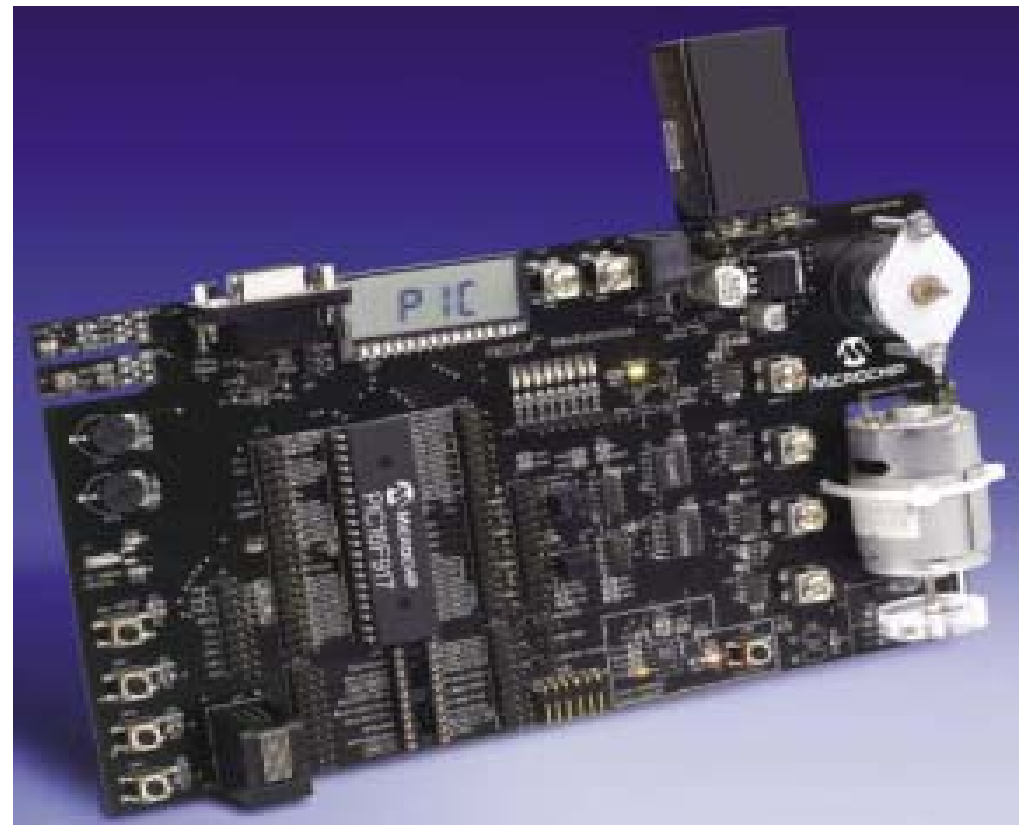
# Lab 1

- Use CCP to create a Hardware PWM
- Vary Duty Cycle via POT1
- Increase Frequency
- Vary the Duty Cycle and observe effects on motor



# Back EMF



# Back EMF

What is it?

- It is the Electro-Motive Force (EMF) or electrical kickback that results from a coil ( rotor ) turning inside a magnetic field ( stator ) and is sensed as a voltage


$$V_{\text{sensed}} = I_L \bullet R_{\text{motor}} + \epsilon$$

$V_{\text{sensed}}$  = Voltage Sensed


$I_L$  = Leakage Current

$R_{\text{motor}}$  = Motor Resistance


$\epsilon$  = Back EMF

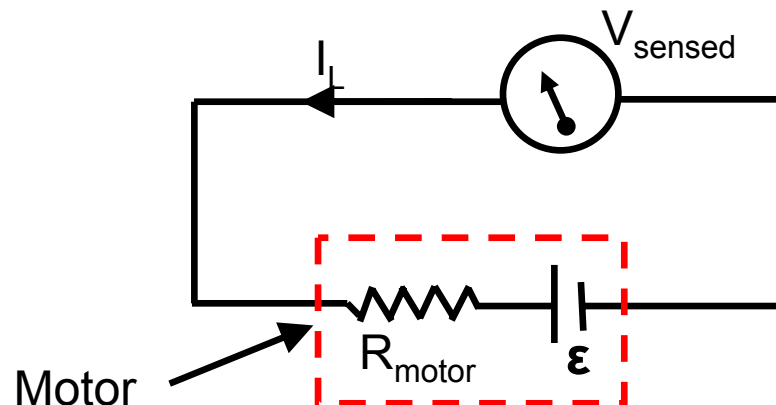

# Back EMF

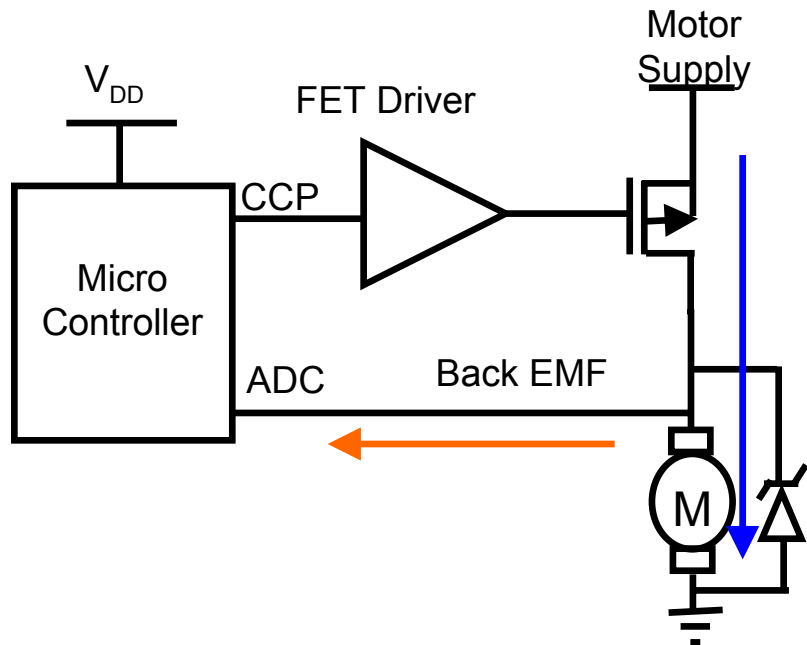


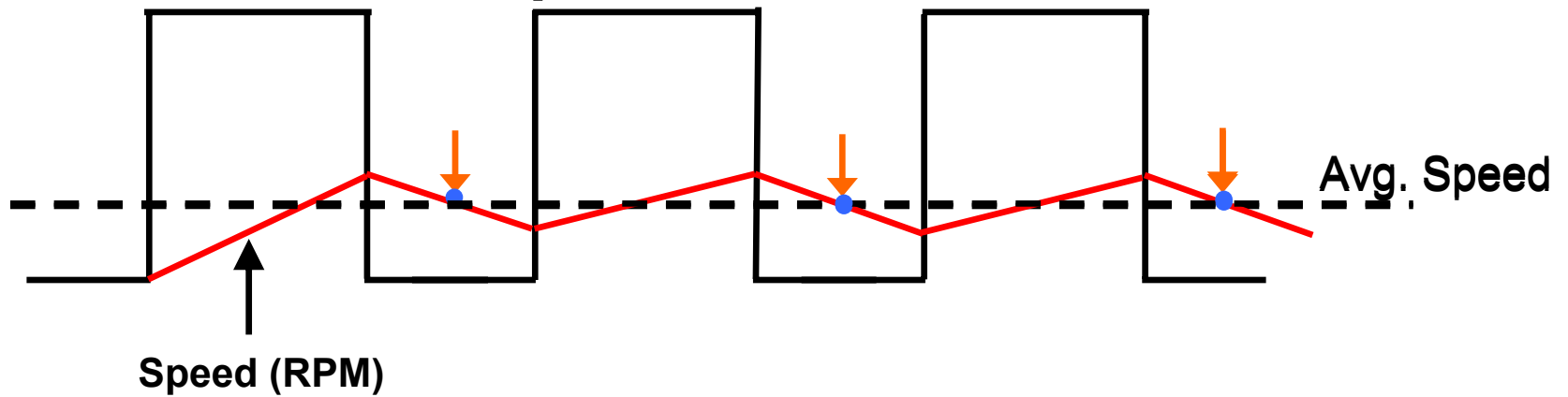- V on,  $I_{Motor}$  flows, RPM  $\uparrow$ , MFw building
- V off,  $I_{Motor}$  off, MFw collapse, RPM  $\downarrow$ ,  $\epsilon$   $\downarrow$



# Lab 2
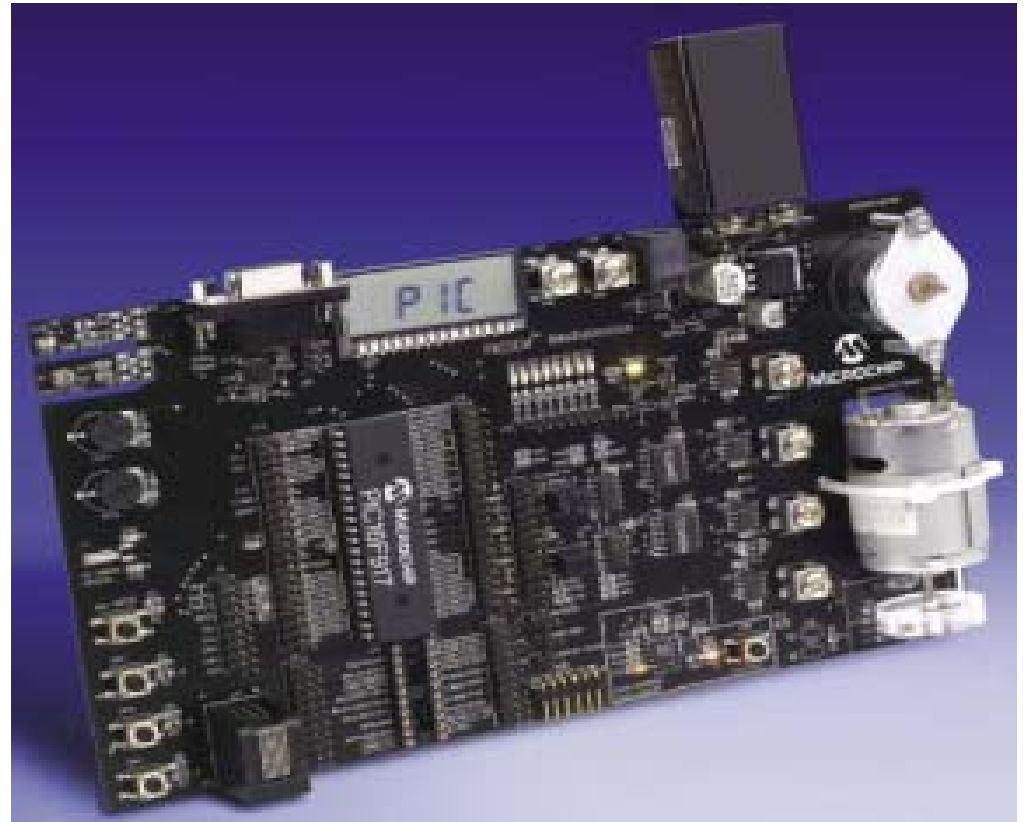
## Brushed DC Motor Control with Back EMF Feedback




# Lab 2


- Use CCP to create a Hardware PWM
- Use the ADC to measure Back EMF off the motor
- Vary the motor speed via POT1

# Optical Encoder

# Rotary Encoder

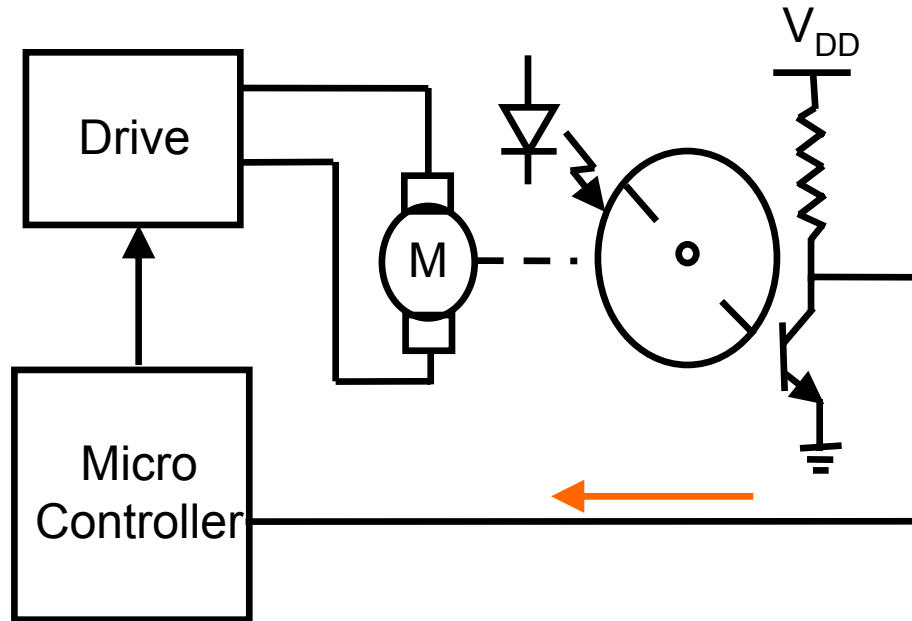


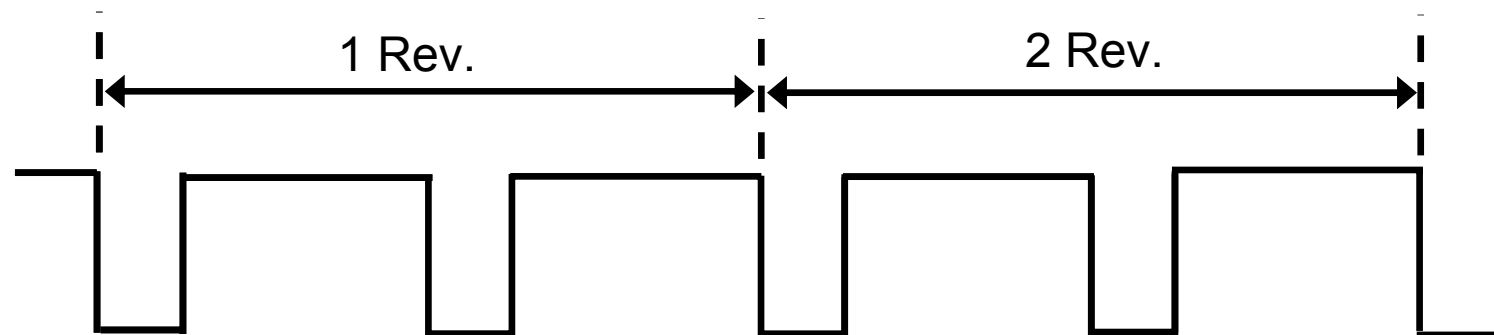- As the LED shines through the disc, the Photo transistor acts as a switch and closes allowing a '0' to be read
- Therefore, the time between every other rising edges of pulse correspond to the speed of motor



# Lab 3
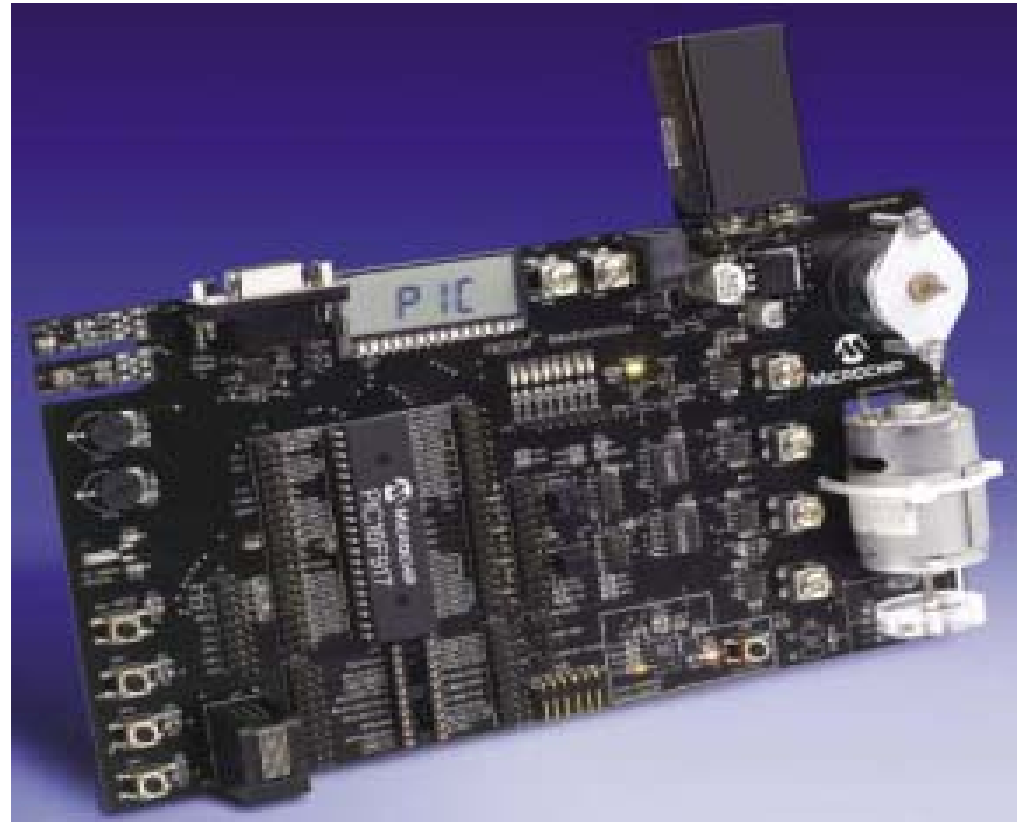
## Brushed DC Motor Control with Optical Encoder Feedback



# Lab 3

- Use CCP to create a Hardware PWM
- Use Optical Encoder to measure time of motor rotation
- Vary the motor speed via POT1



# Positives and Negatives

- Measuring motor speed using Back EMF
  - Positive: - Can sense speed faster
    - Low cost, Fewer parts
  - Negative: - Can't sense while motor is on thus, not as accurate
- Measuring motor speed using Optical Encoder
  - Positive: - No signal calibration thus, more accurate
  - Negative: - Can be affected by other light sources
    - Limited by the time it takes to complete 1 rev.
    - Higher cost, more parts and code maybe more involved

# **ECCP**

## **(Enhanced Compare/Capture/PWM)**

# ECCP Module

- What is it?  
The Enhanced Capture/Compare/PWM module is a peripheral which allows the user to time and control different events
- What does it consist of?
  - Capture mode: allows timing of an events duration
  - Compare mode: allows the user to trigger an external event when a predetermined amount of time has expired
  - PWM mode: generates a pulse-width modulated signal of varying freq. and duty cycle


# Enhanced PWM Modes

- The Enhanced PWM Mode can generate a PWM signal on up to four different output pins
  - ▶ Four different PWM Output modes:
    - Single PWM
    - Half-Bridge PWM
    - Full-Bridge PWM, Forward mode
    - Full-Bridge PWM, Reverse mode
  - ▶ Auto-Shutdown Mode
  - ▶ Auto-Restart Mode
  - ▶ Programmable Dead-Band Delay Mode
  - ▶ Pulse Steering Mode

# PWM Output Modes

- Single PWM
  - Generates a pulse-width modulated signal of varying freq. and duty cycle on a single output


Microcontroller

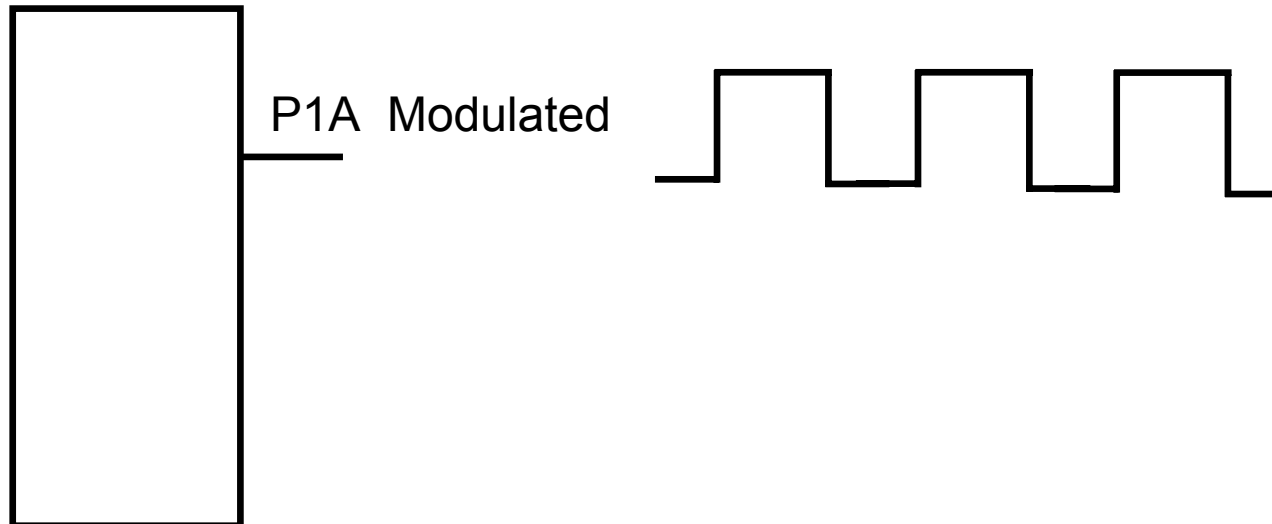

# PWM Output Modes

- Half-Bridge PWM
  - Generates a PWM signal on two outputs


Microcontroller

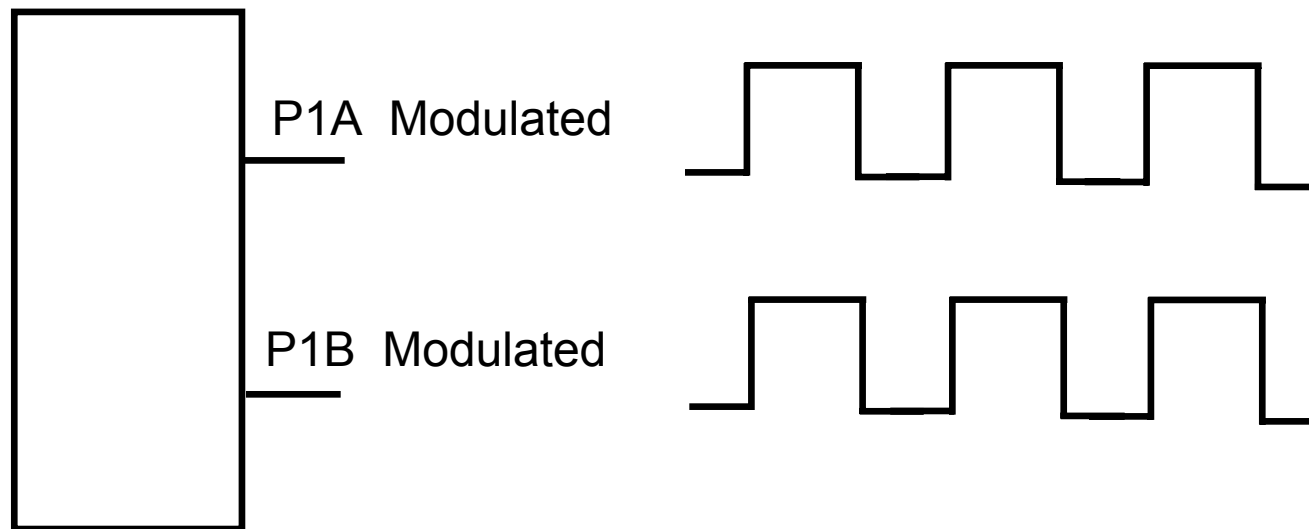
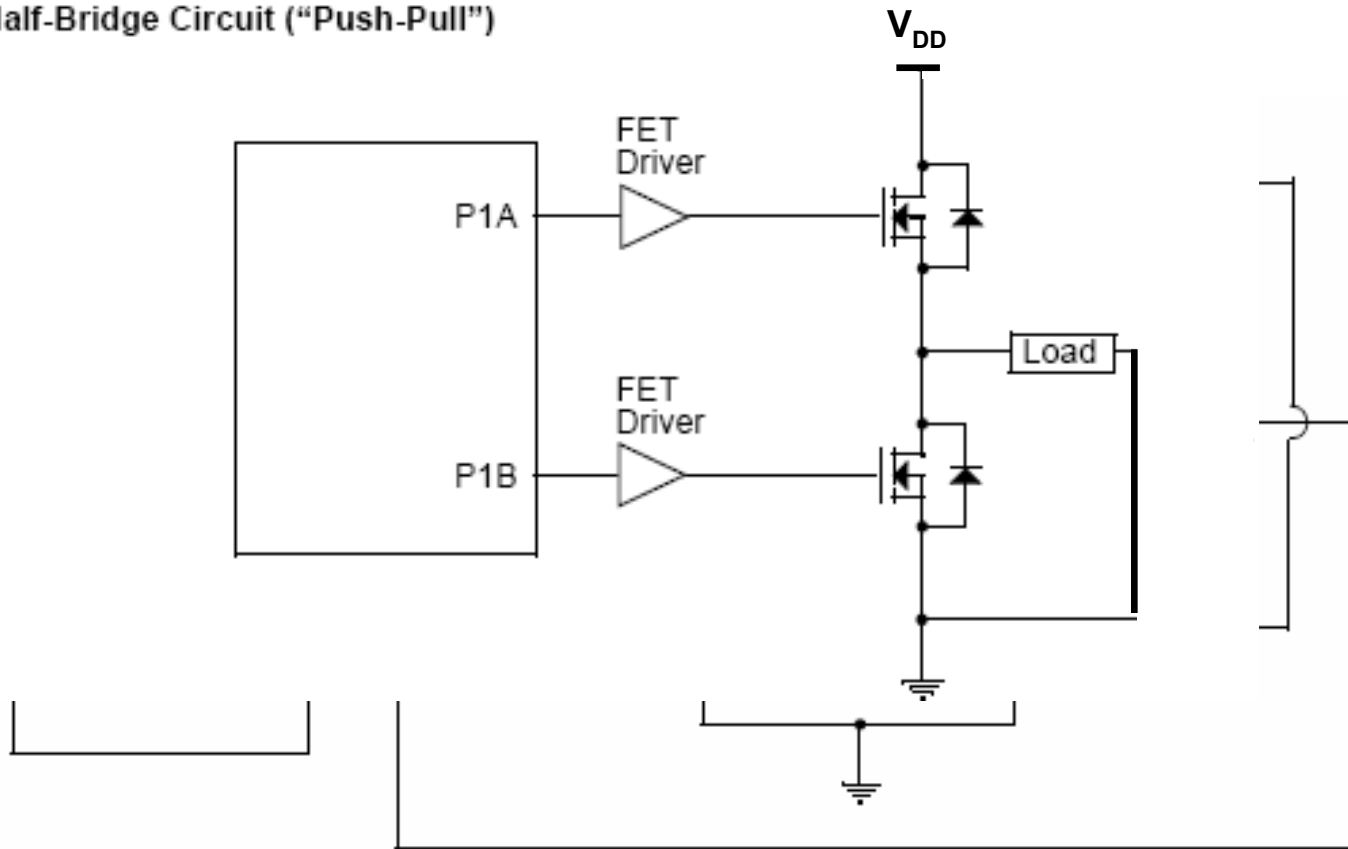
# PWM Output Modes


- Application examples:

Standard Half-Bridge Circuit ("Push-Pull")


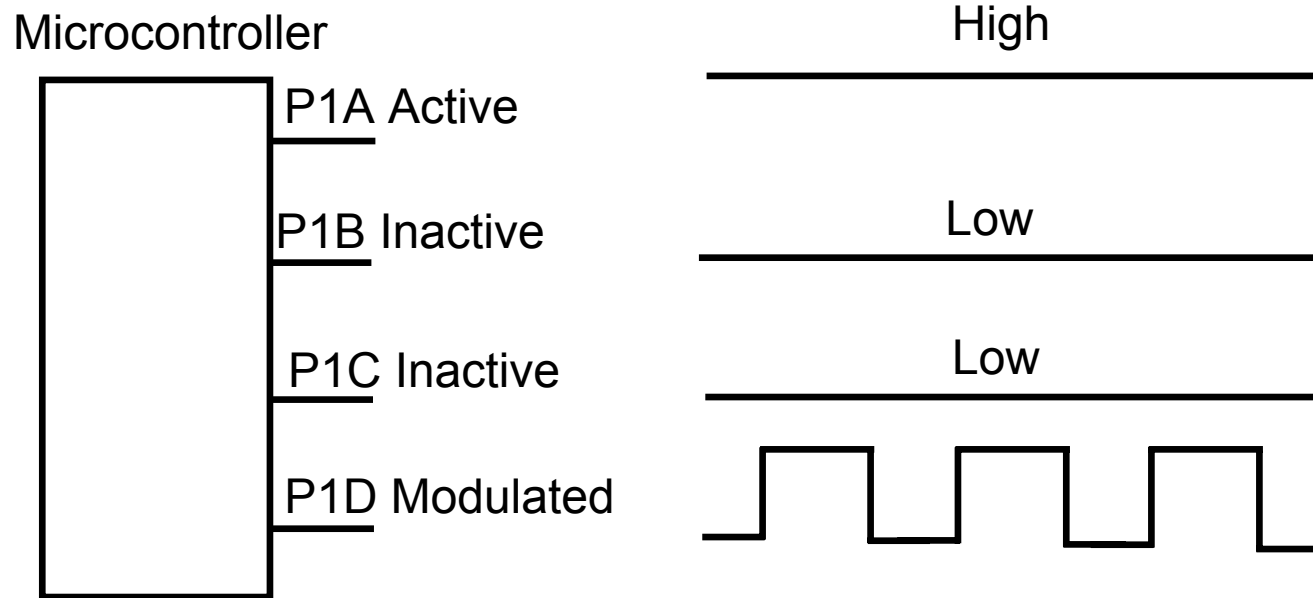
# PWM Output Modes


- Full-Bridge PWM, Forward Mode
  - All four pins are used as outputs





# PWM Output Modes


- Example:

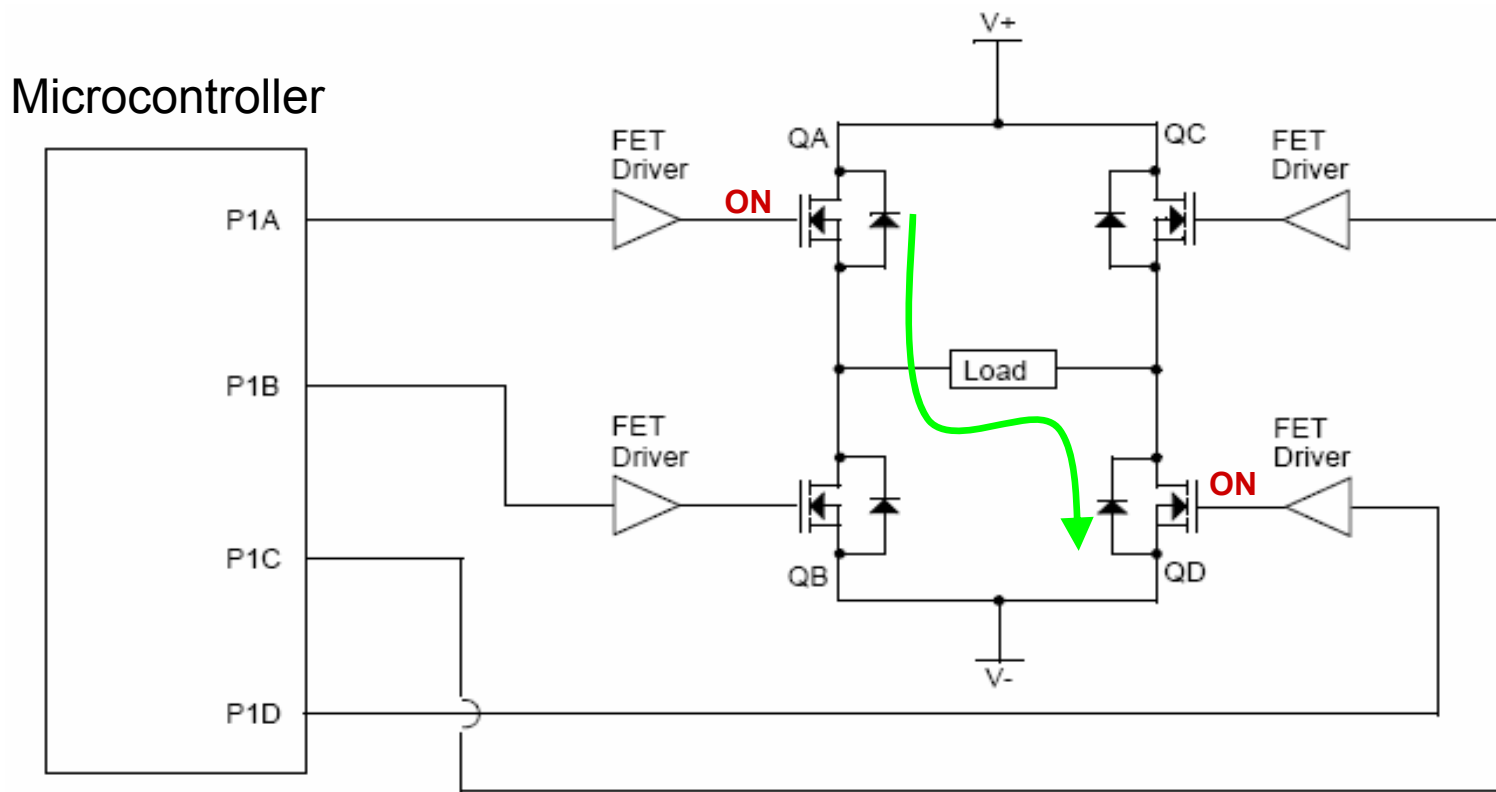

# PWM Output Modes


- Full-Bridge PWM, Reverse Mode
  - All four pins are used as outputs

Microcontroller

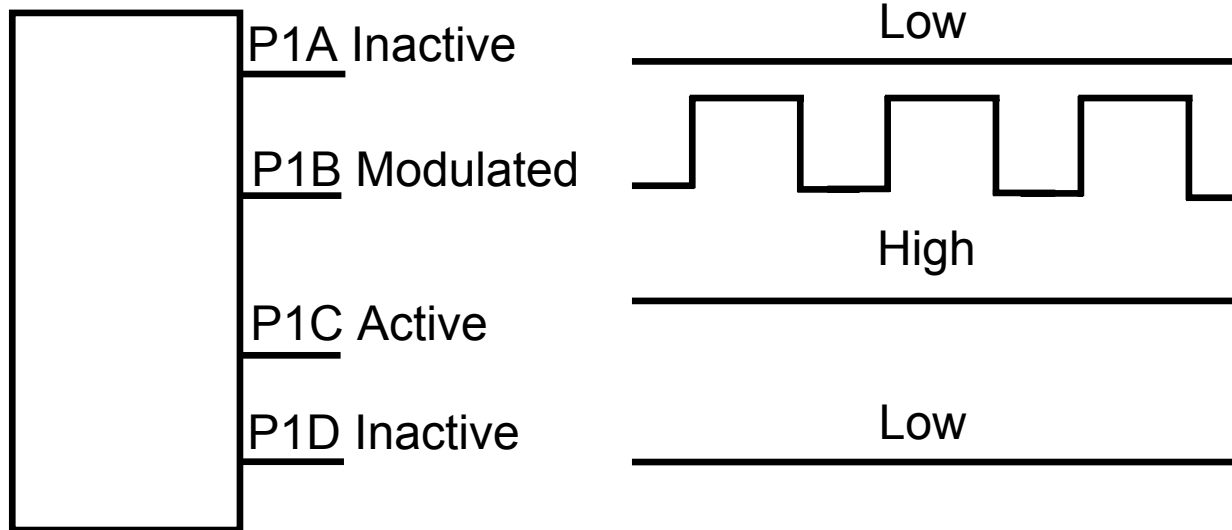

# PWM Output Modes

- Example:

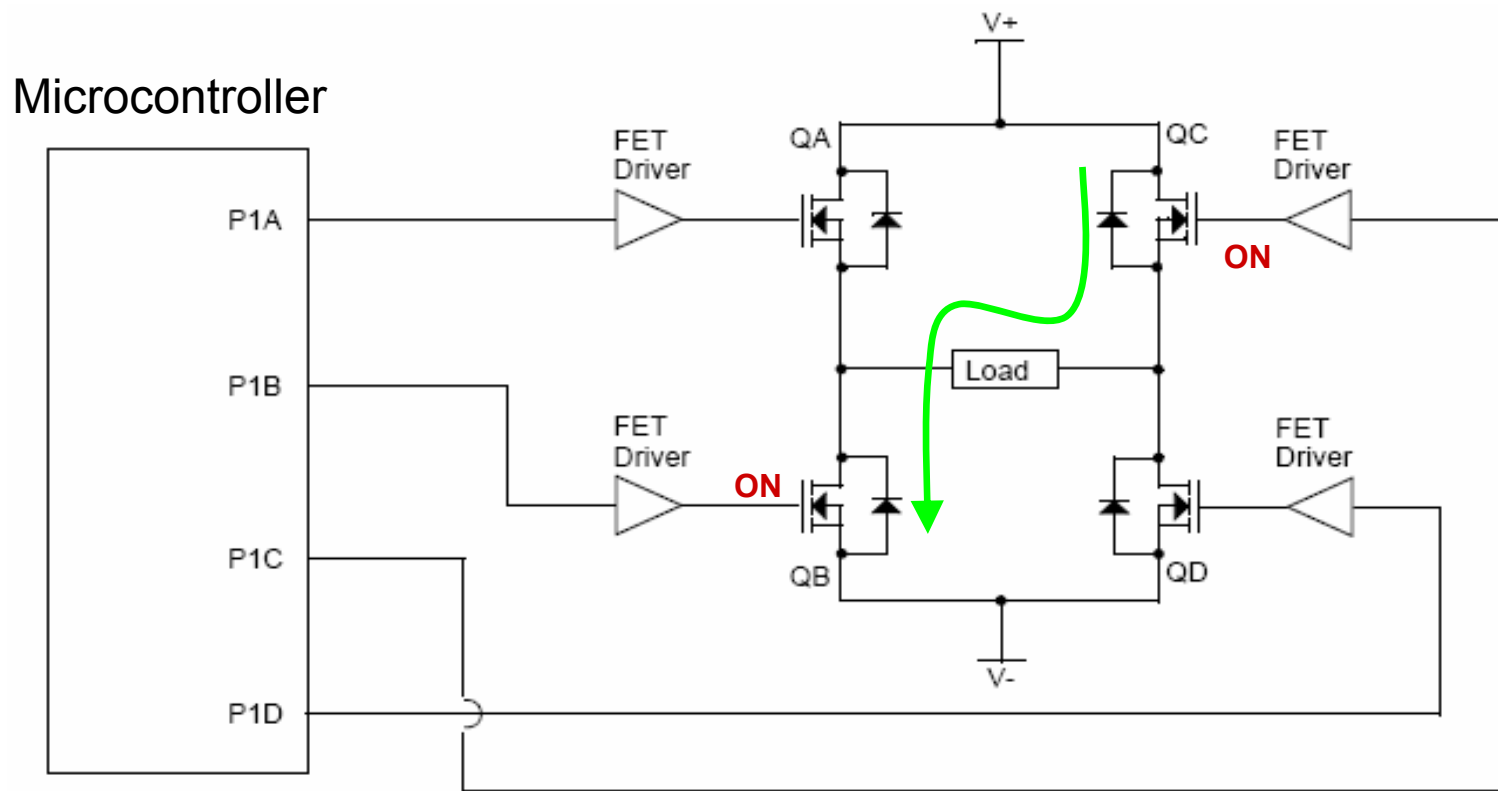


# Lab 4

## Brushed DC Motor Control Using the Enhanced PWM to change motor direction

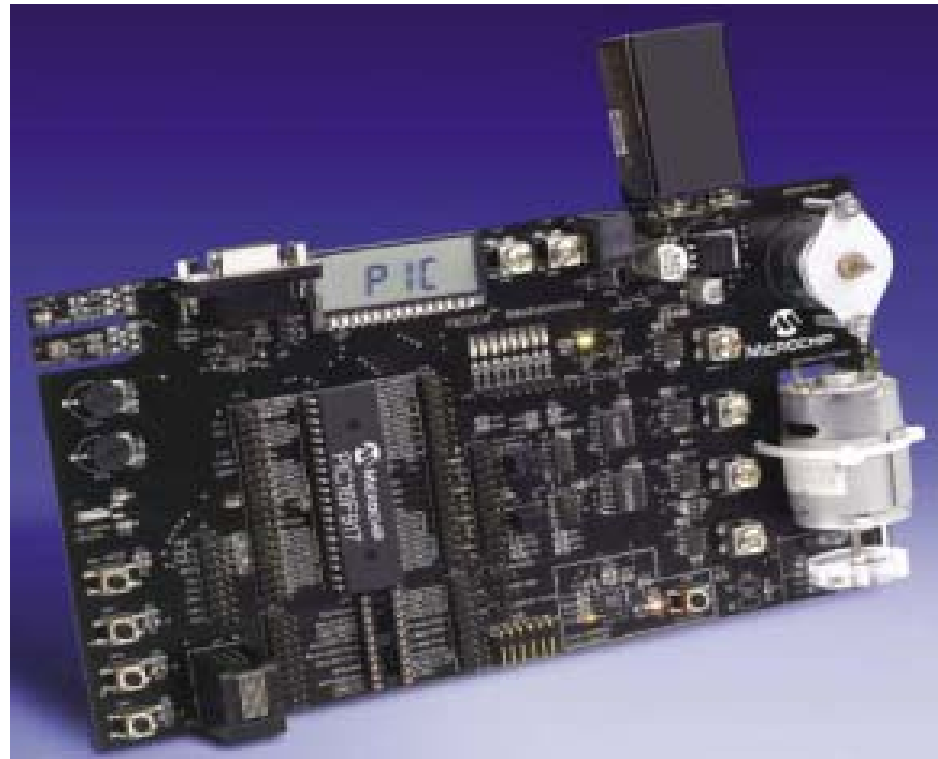
# Lab 4

- Use the Enhanced PWM mode of the ECCP to drive a motor
- Use a Full-Bridge PWM mode to drive the motor forward, brake and reverse



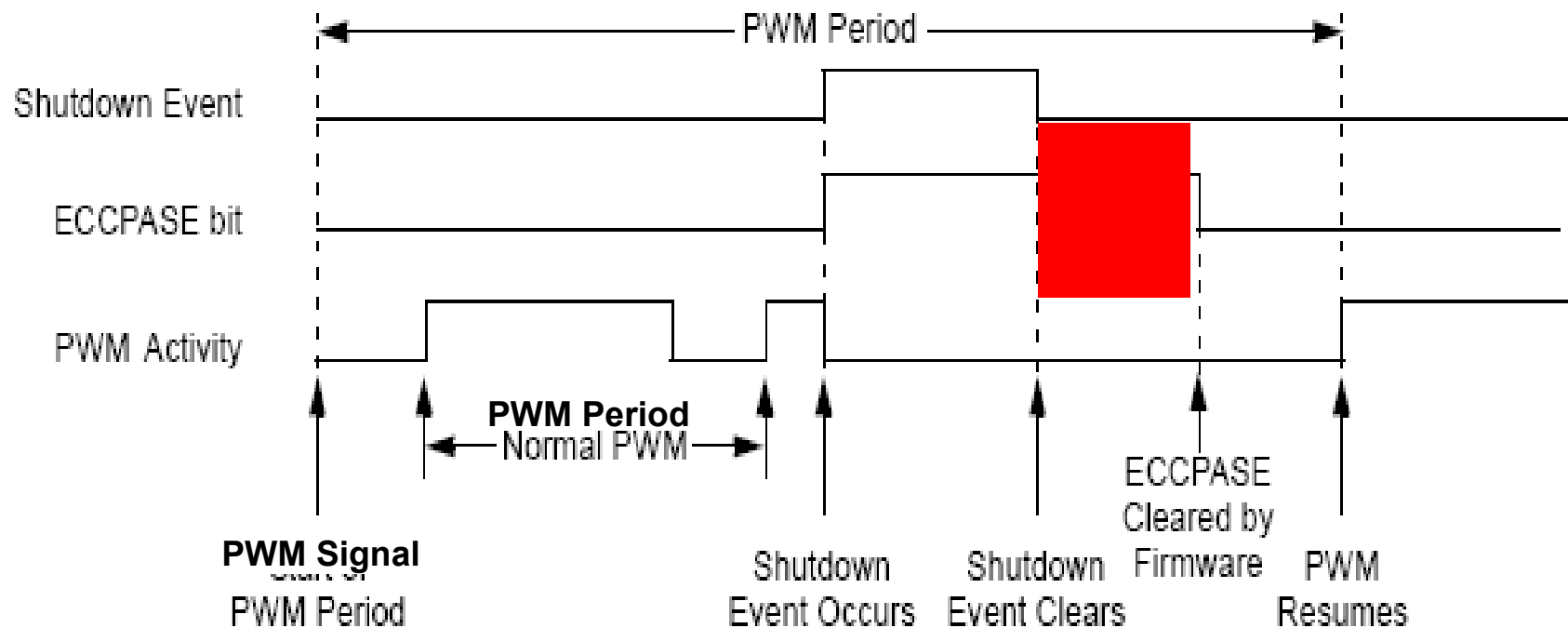
# Auto-Shutdown Mode

- What does it do?
  - It is a feature that will disable the PWM outputs when an external shutdown event occurs
    - ▶ Shutdown events: - A logic '0' on the INT pin


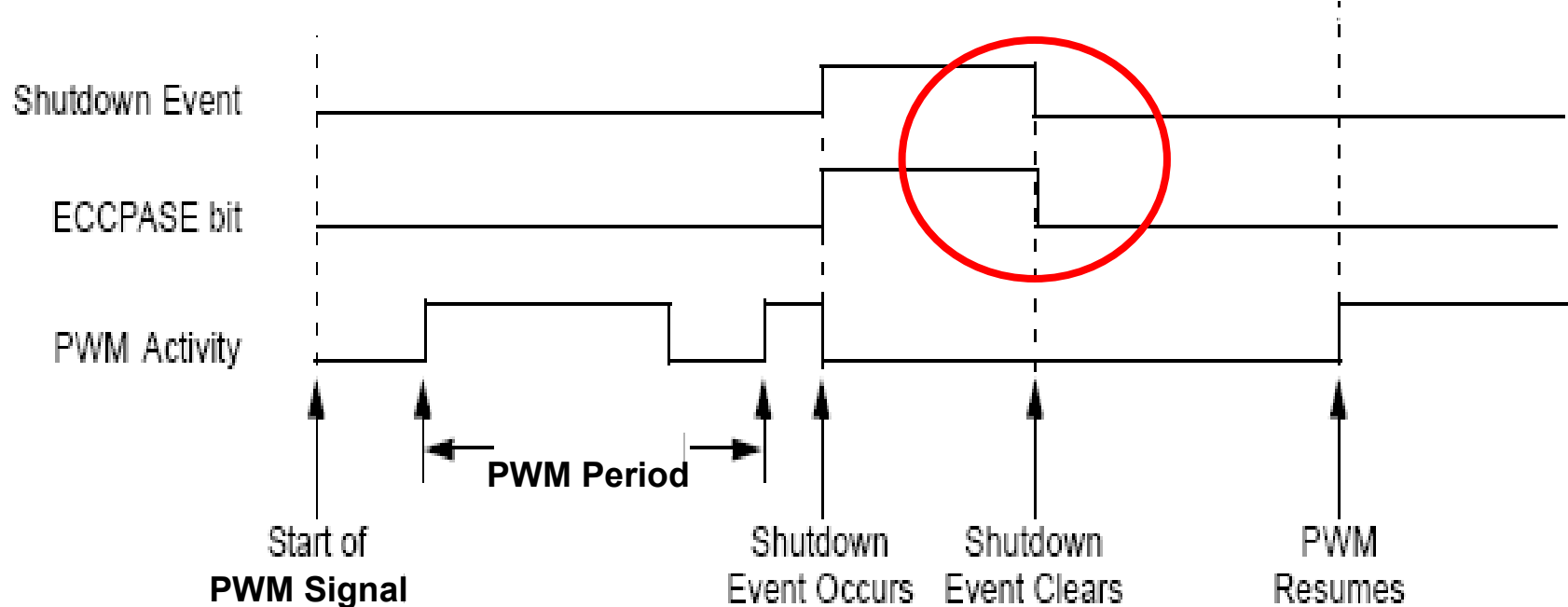
# Auto-Restart Mode

- What does it do?
  - The Auto-Restart can be configured to automatically restart the PWM signal once the Auto-Shutdown condition has been removed



# Current Sensing



# Current Sensing

- What can sensing the current flowing through a motor tell us?
  - Torque ( When you control current you control torque )
- How can current be sensed in a given application?

Current can be sensed by measuring:


  - 1). The voltage drop through a known resistor value
  - 2). The magnetic field strength of a known inductor value
- Where can current be sensed?

Current is generally sensed at one of two places:

  - 1). The supply side of the drive circuit ( High Side Current Sense )
  - 2). The sink side of the drive circuit ( Low Side Current Sense )

# Current Sensing

## High Side Resistive Circuit

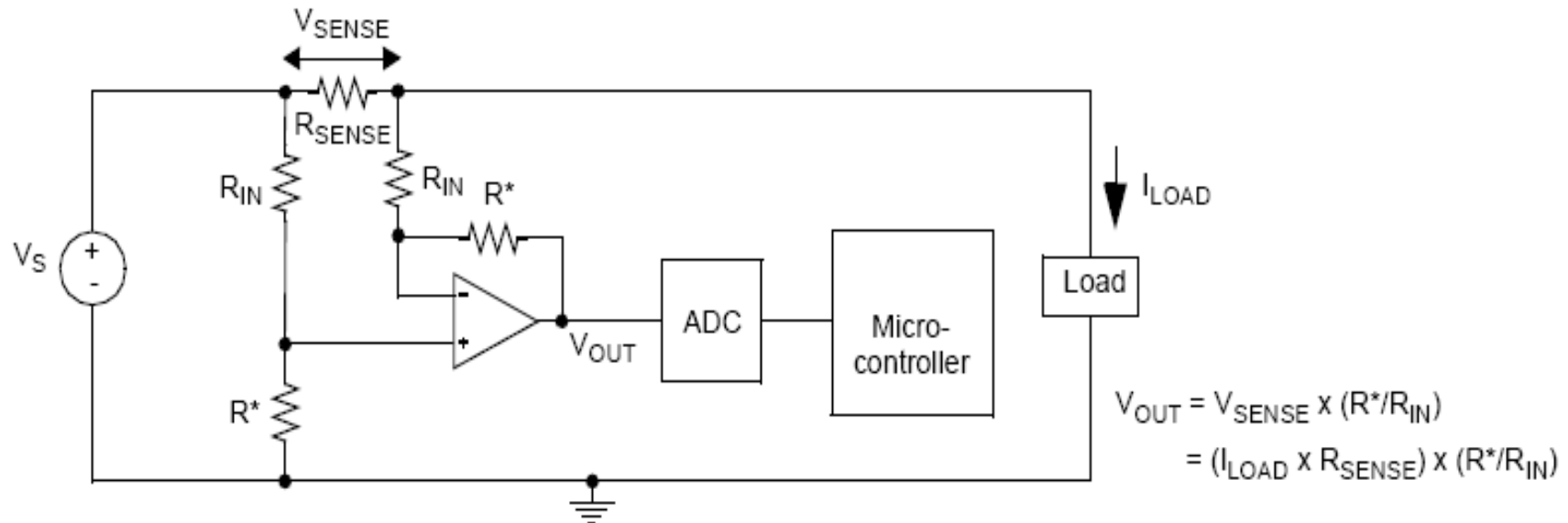

- As  $I_{Load}$   $\uparrow$  or  $\downarrow$ ,  $V_{Out}$  will  $\uparrow$  or  $\downarrow$
- If  $R_{Sense}$   $\uparrow$  or  $\downarrow$ ,  $I_{Load}$  and  $V_{Out}$  will act the same proportionally

# Current Sensing

## High Side Advantages:


- Can detect over current faults that can occur by short circuits
- Differential amplifier circuit will filter noise via the common-mode-rejection-ratio (CMRR) of the amplifier

## High Side Disadvantages:

- $V_{\text{SENSE}}$  voltage is approx. equal to the  $V_s$ , which may be beyond the max input voltage range of op-amp
- A differential amplifier's CMRR will be degraded by mismatches in amplifier resistors

# Current Sensing

## Low Side Resistive Circuit

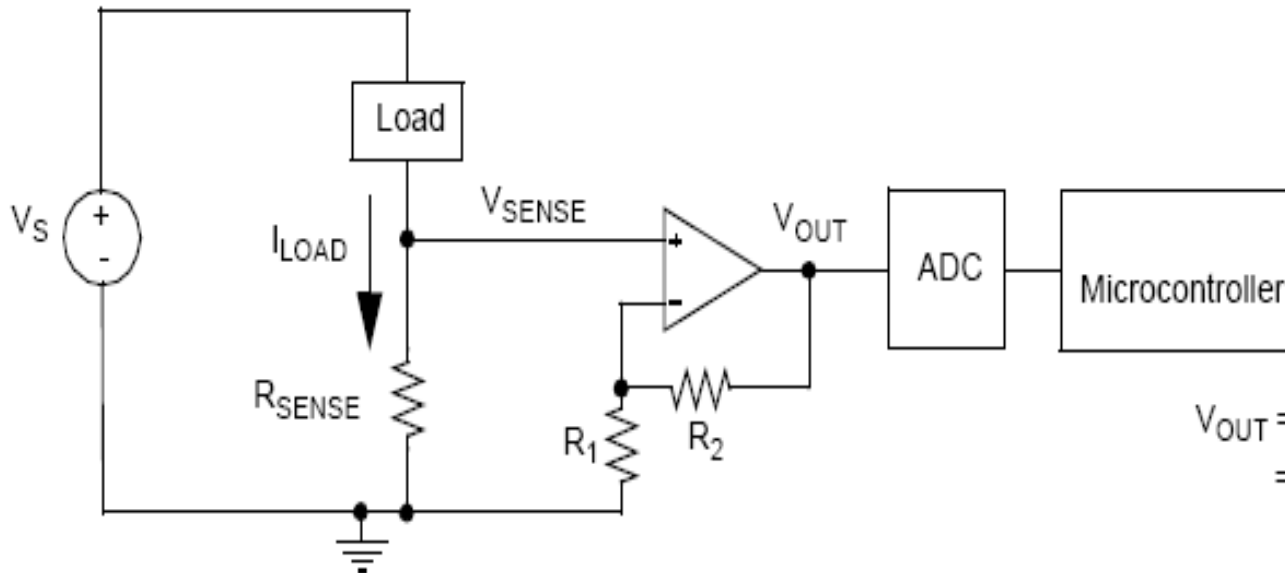

$$V_{OUT} = (V_{SENSE}) \times (1 + R_2/R_1)$$
$$= (I_{LOAD} \times R_{SENSE}) \times (1 + R_2/R_1)$$

- As  $I_{Load}$   $\uparrow$  or  $\downarrow$ ,  $V_{Out}$  will  $\uparrow$  or  $\downarrow$
- If  $R_{Sense}$   $\uparrow$  or  $\downarrow$ ,  $I_{Load}$  and  $V_{Out}$  will act the same proportionally

# Current Sensing

## Low Side Advantages:

- $V_{\text{SENSE}}$  is referenced to ground, thus a low voltage amplifier can be used
- A non-inverting amplifier can be used and the input impedance of the circuit will be equal to the large input impedance of the amplifier

## Low Side Disadvantage:


- Low-side current monitors are unable to detect a fault where the load is accidentally connected to ground via an alternative ground path

# Lab 5

Using Current Sensing to detect current loading on a brushed DC motor

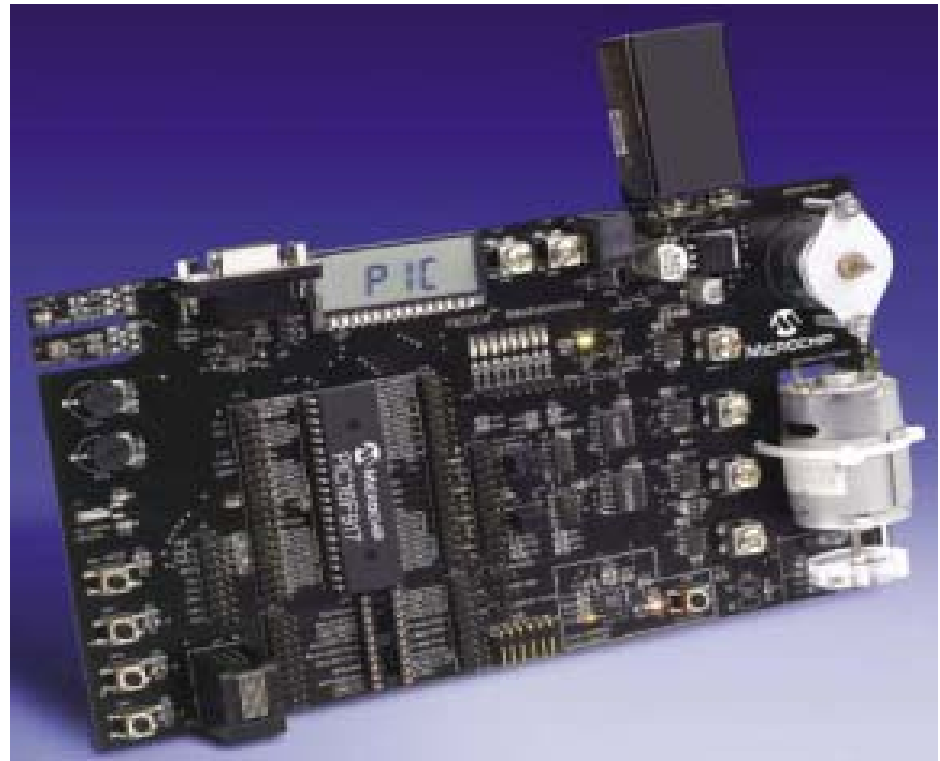
# Lab 5

- Use a Low-side Resistive current sensing circuit to detect a load on the motor
- Use Auto-Shutdown mode to shut the motor off at a given load
- Use Auto-Restart mode to restart the motor when the load is removed



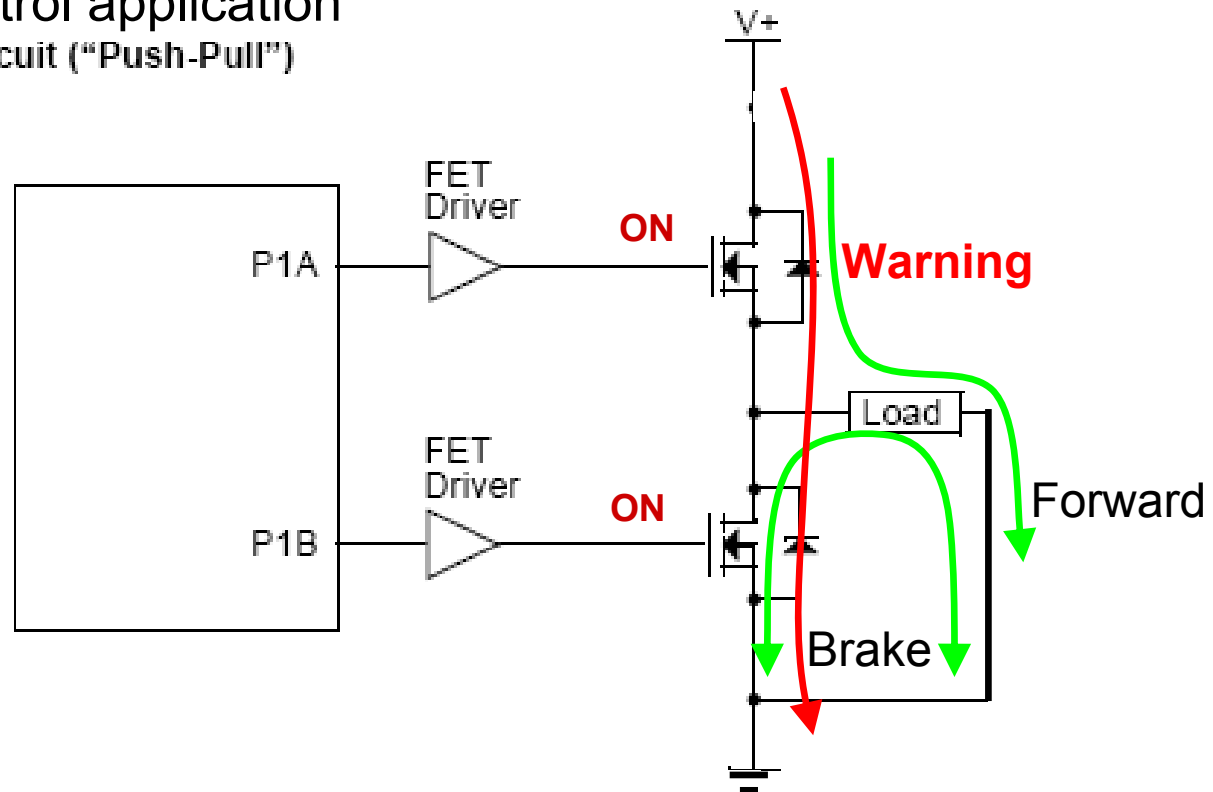
# Programmable Dead Band Delay

- Why do I need it?
    - To avoid Shoot-Through Current from shorting the bridge supply of your motor control application
- Standard Half-Bridge Circuit ("Push-Pull")





# Programmable Dead Band Delay

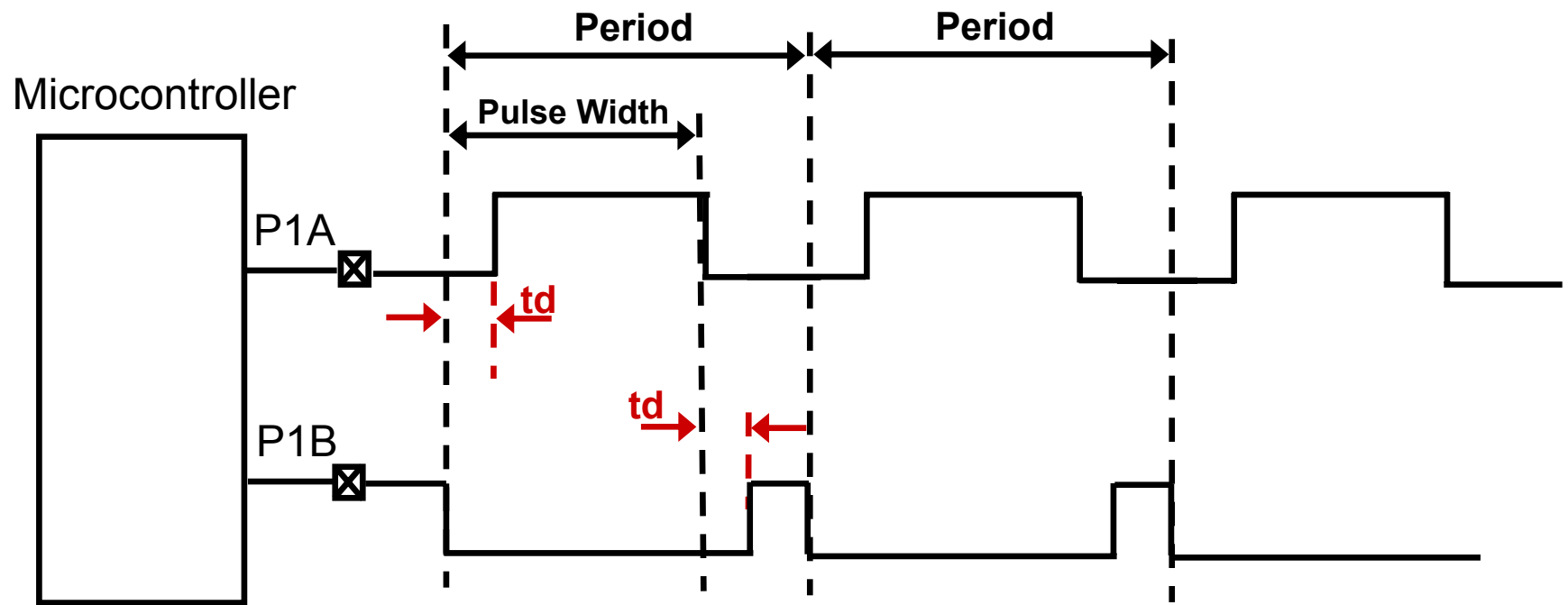


$t_d$  = Dead Band Delay

# Pulse Steering Mode

- What does it do?
  - Pulse Steering Mode allows any of the PWM output pins to carry a PWM signal ( Basically, it's a single PWM )
  - The same PWM signal can be put on one, two, three or four output pins at the same time


Microcontroller

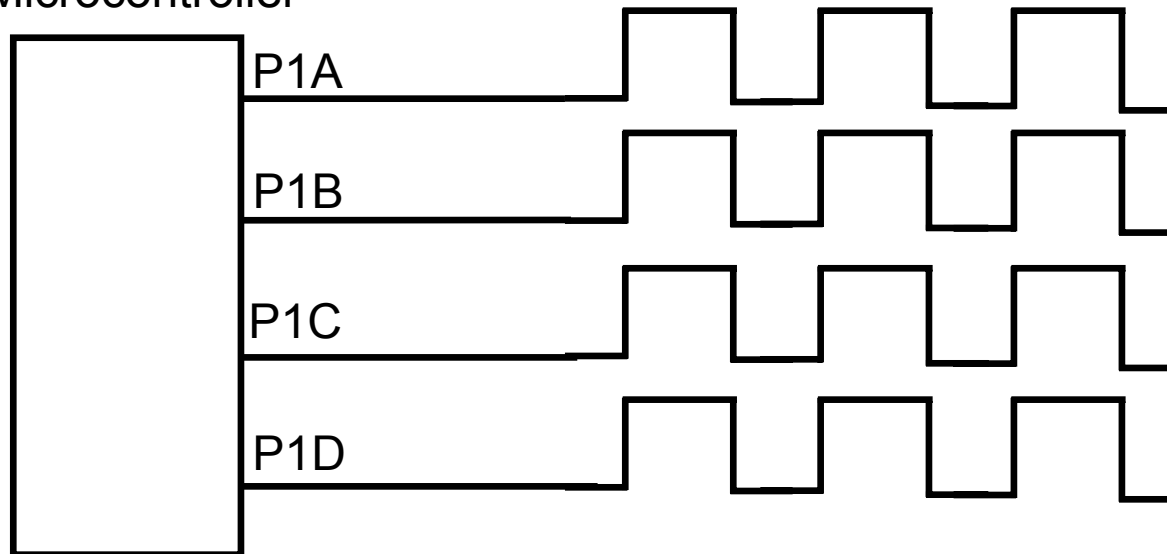

# Slot Car Demo

Brushed DC motor control of an electric  
Slot car and track

# Slot Car Demo

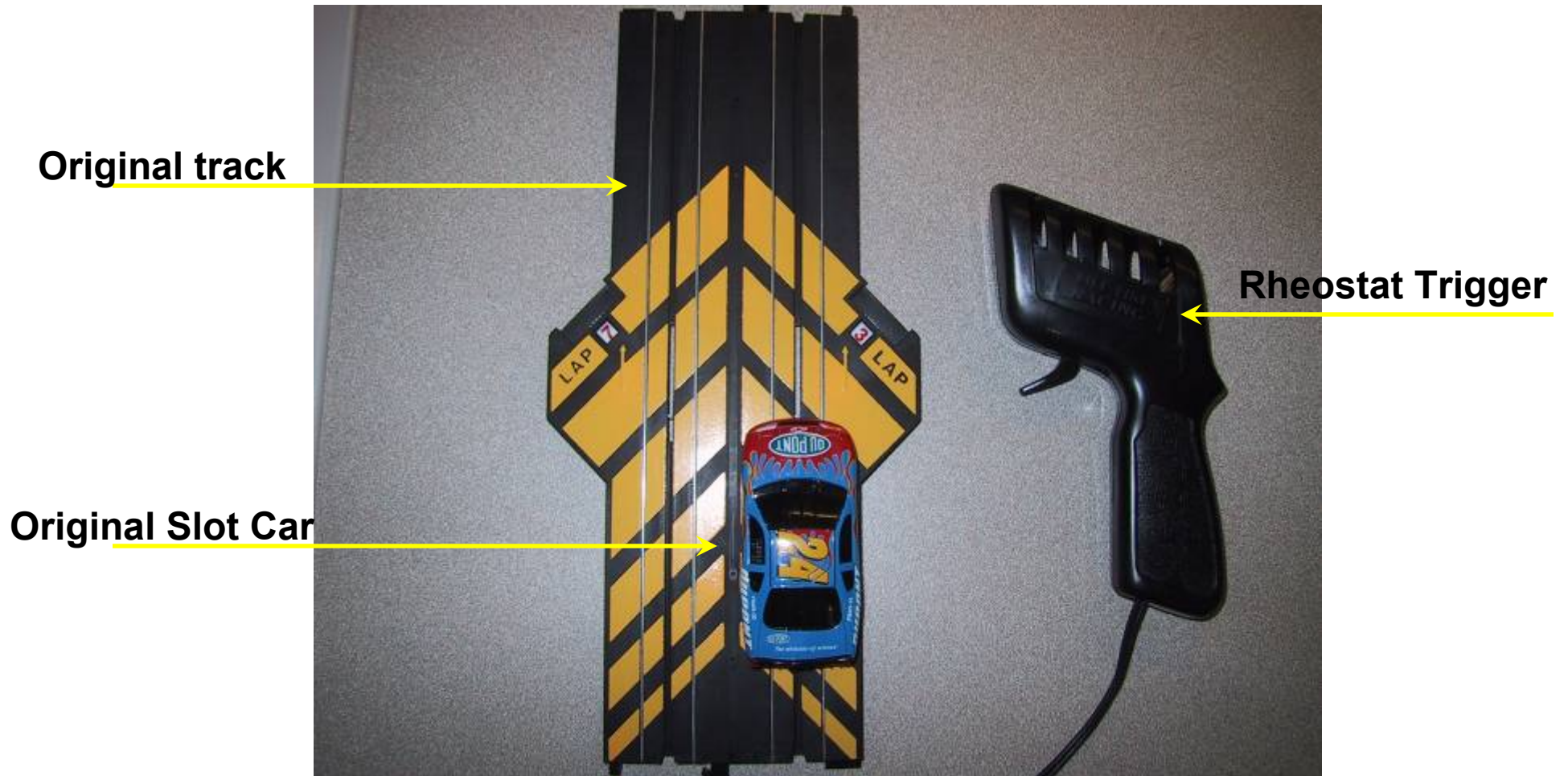

# Slot Car Demo

Original Car (Top)


Original Car  
(Bottom)


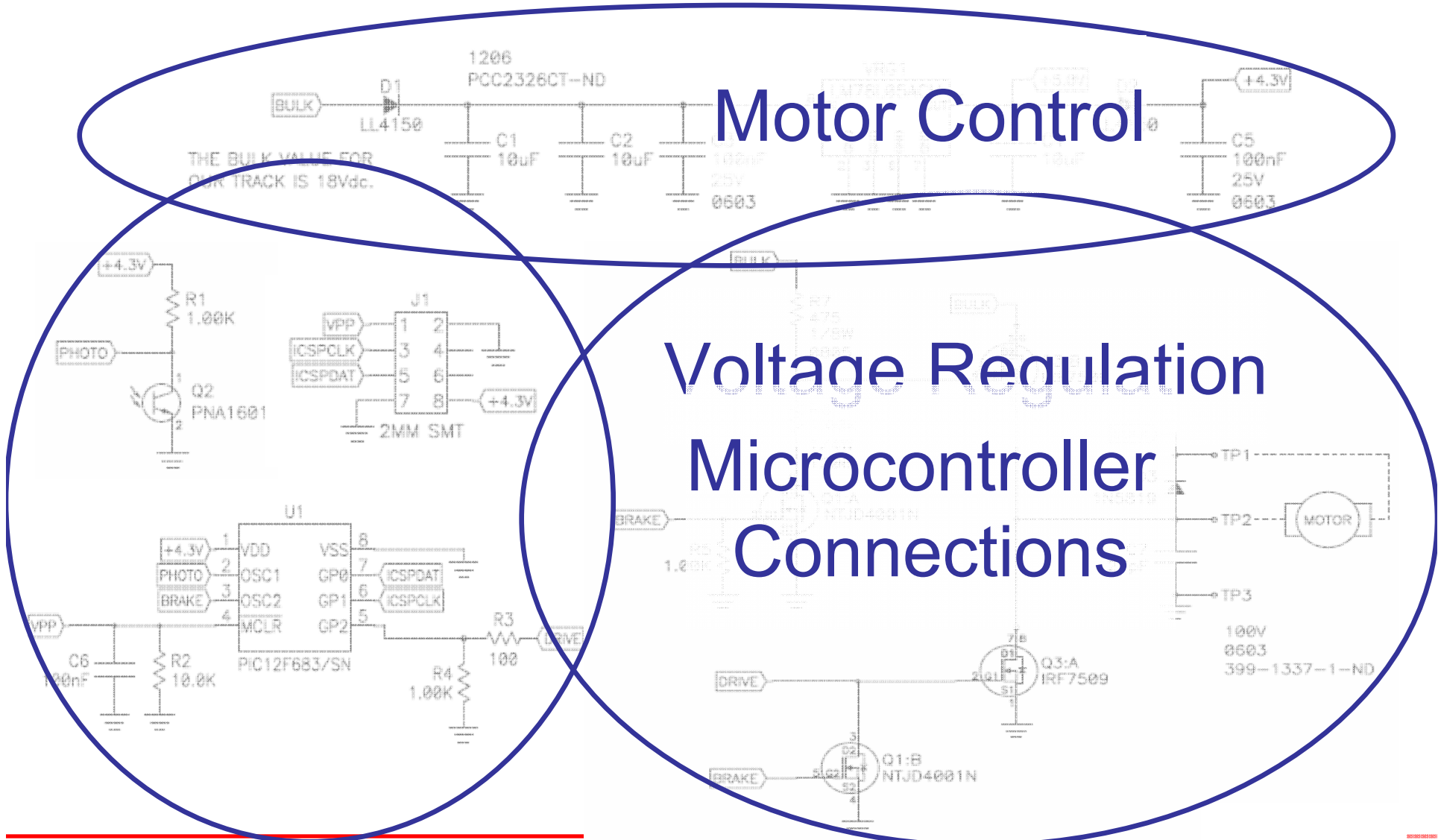
# Slot Car Demo

Motor Control


Voltage Regulation  
Microcontroller  
Connections



# Slot Car Demo

5V Voltage Regulator

MOSFETs

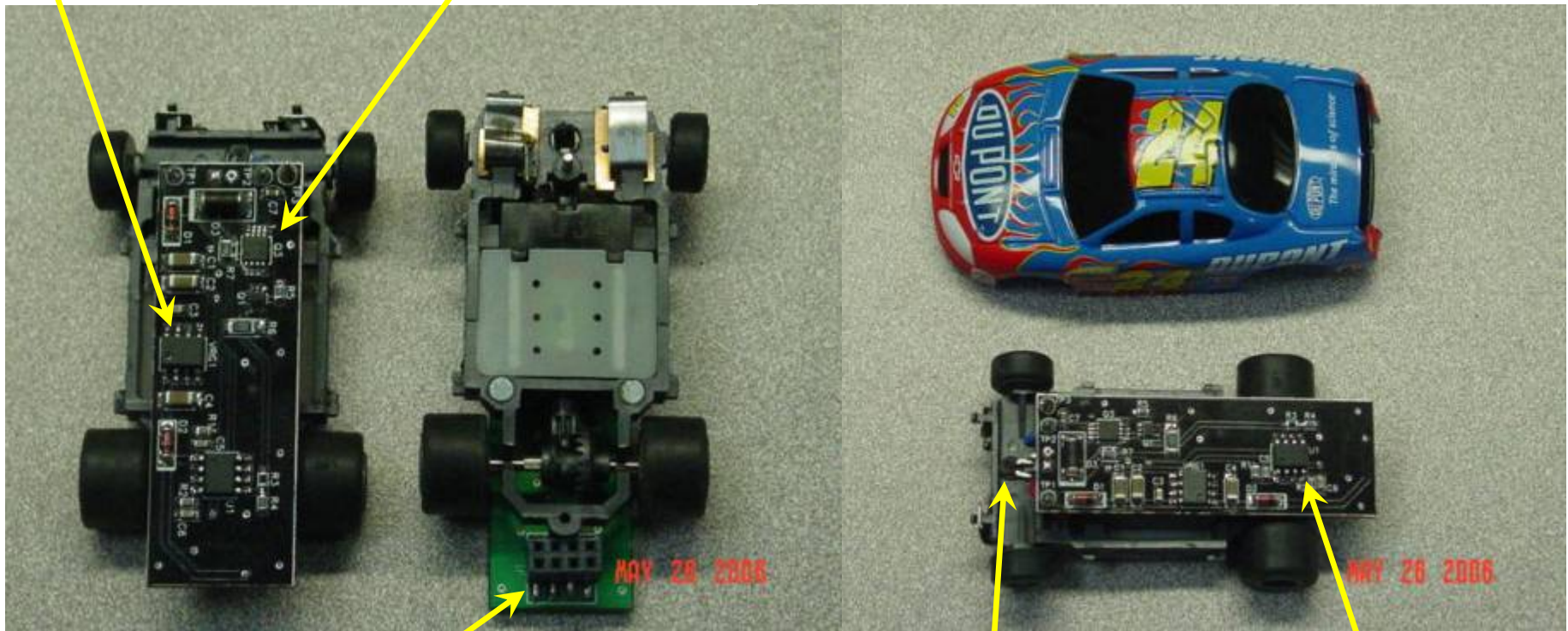

Programming  
Header

Phototransistor

PIC12F683

# Slot Car Demo



```

MPLAB IDE v7.31
File Edit View Project Debugger Programmer Tools Configure Window Help

Checksum: 0xa90d

DE Editor
new3.asm | Test_track_BRAKE.asm | TEST_TRACK_BRAKE.ASM | JM_slotcar_new4.asm | JMSLOTCAR_LAB1B.AS

;*****
;*****      PROGRAM: JM_SLOTCAR_LAB2PWM.ASM      *****
;*****      WRITTEN BY: JOHN MOUTON      *****
;*****      DATE: 5-8-06      *****
;*****      THIS PROGRAM IS AN EXAMPLE OF HARDWARE PWM      ****
;*****

LIST      P=12F683
#include <p12F683.inc>
_CONFIG  _MCLRE_OFF & _WDT_OFF & _INTRC_OSC_NOCLKOUT & _CP_OFF & _CP

      CBLOCK      0x20
      ENDC

      ORG      0x000      ; PROCESSOR RESET
      BCF      STATUS, RP0      ; SELECT BANK0
      GOTO     INIT_BANK0      ; GOTO THE START OF THE PRO
      ORG      0x004      ; INTERRUPT LOCATION
      RETFIE      ; RETURN FORM INTERRUPT


INIT_BANK0

      BCF      STATUS, RP0      ; CLEAR BIT F=0, THUS SELEC
      MOVLW   B'00000111'      ; 07H. SEE PAGE 47 OF DATAS
      MOVWF   CMCON0           ; SETTING REGISTER TO 7 WIL
                                   ; SO THE PWM MODE CAN BE US

MPLAB SIM      PIC12F683      pc:0      W:0      z dc c      bank
  
```




# Track Layout

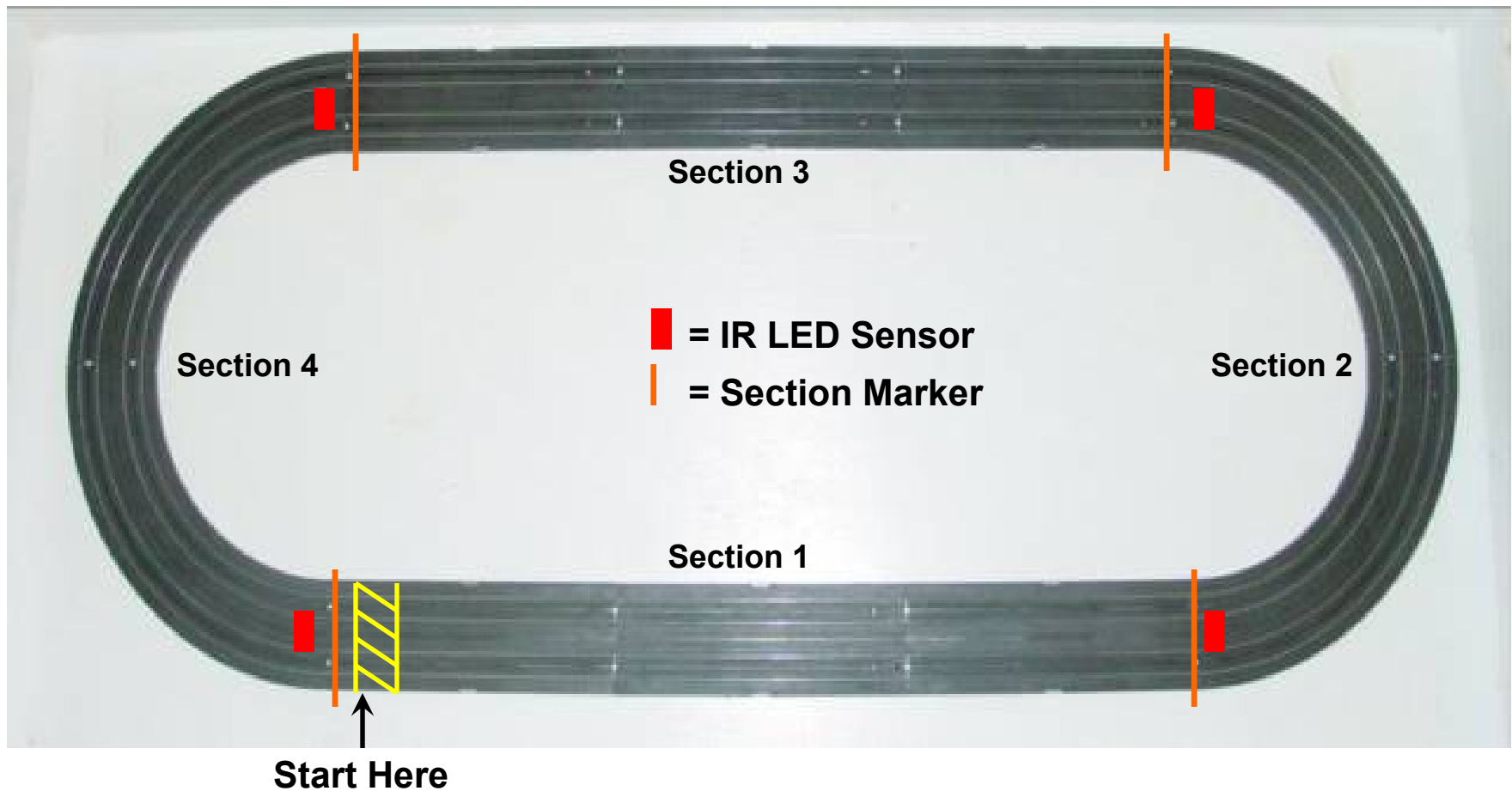


# Track Modification


Drilled Holes

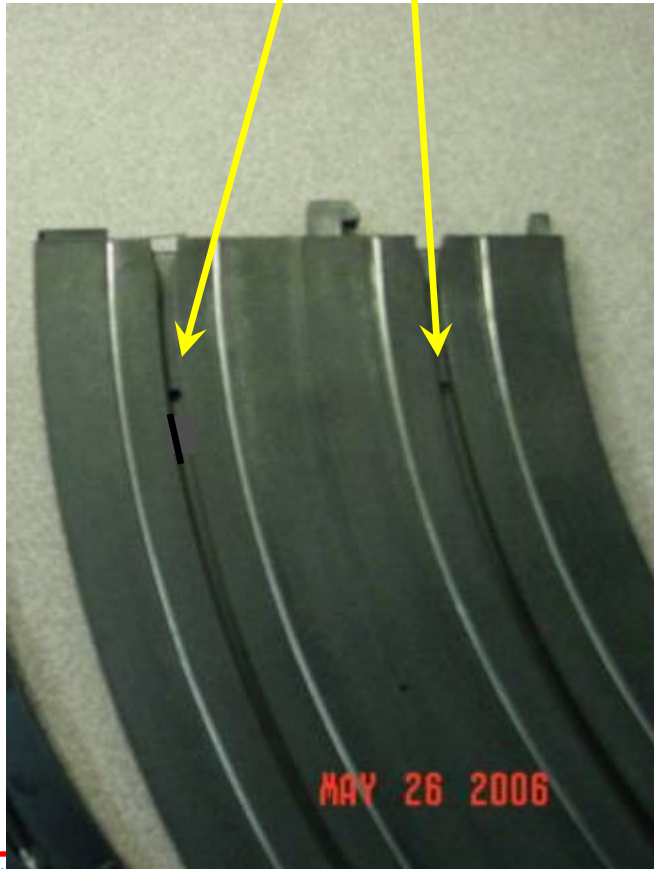

Infrared LEDs

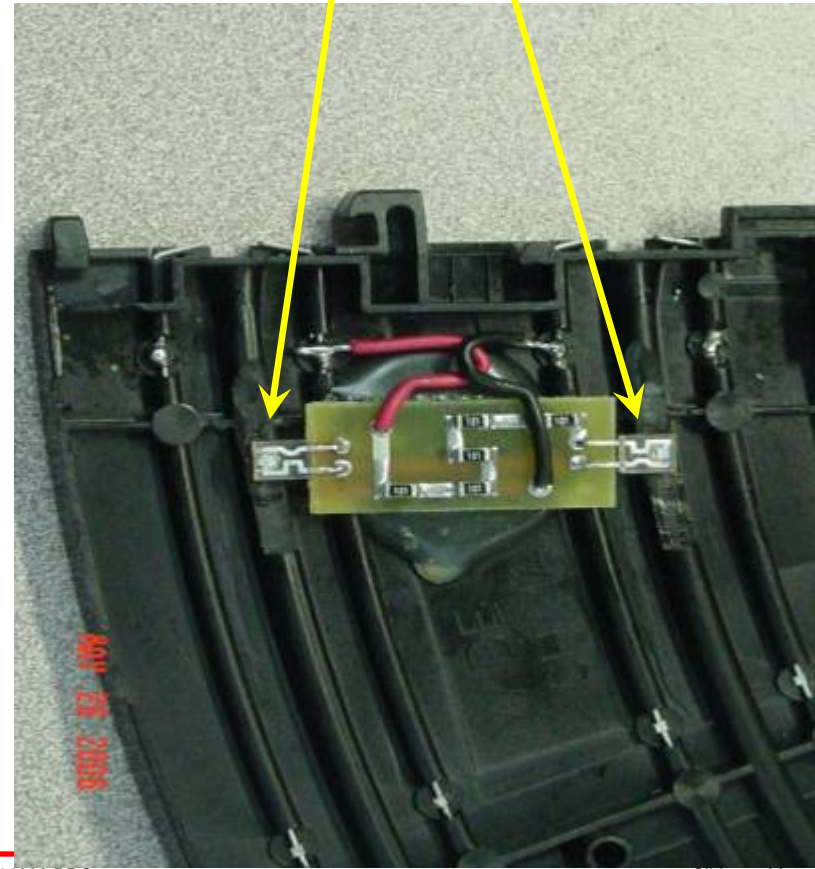

# Track Modifications

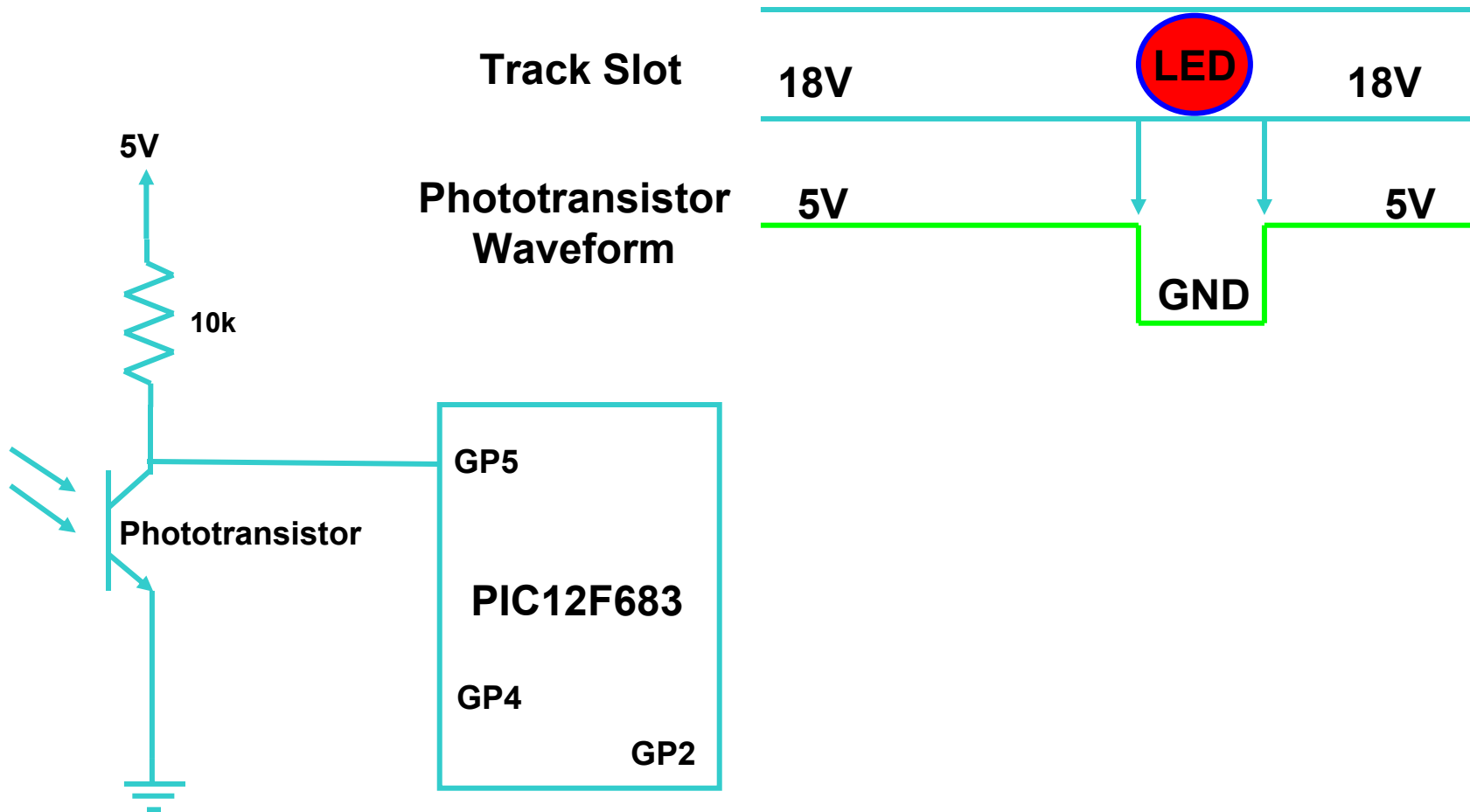

# Summary

- Basic brushed DC motor operation, 4 types, and 3 methods of driving them
- How to control speed using CCP and measure speed using Back EMF and Optical Encoder
- How to use ECCP ( Enhanced PWM ) with all of its modes

# Dev Tools Used

## Labs:

- **PICDEM™ Mechatronics Demo Board ( DM163029 )**
- **MPLAB® ICD 2 In-Circuit Debugger Kit ( DV164005 )**

## Slot Car Demo:

- **PICkit™ 1 Flash Starter Kit ( DV164101 )**

# Additional Reading

- AN847 – RC Model Aircraft Motor Control
- AN893 – Low-Cost Bidirectional Brushed DC Motor Control Using the PIC16F684
- AN894 – Motor Control Sensor Feedback Circuits
- AN898 – Determining MOSFET Driver Needs for Motor Drive Applications
- AN905 – Brushed DC Motor Fundamentals
- DS41233 – DC Motor Control Tips ‘n Tricks
- DS41214 – CCP and ECCP Tips ‘n Tricks

# Microchip's Advanced Parts Selector (MAPS)

The screenshot shows the Microchip website interface in Microsoft Internet Explorer. The address bar displays the URL: [http://www.microchip.com/stellent/idcplg?IdcService=SS\\_GET\\_PAGE&nodeId=64](http://www.microchip.com/stellent/idcplg?IdcService=SS_GET_PAGE&nodeId=64). The website header includes the Microchip logo, a navigation menu (Home, Products, Design, Sales, Sample, Buy Online, Corporate, What's New), and search options (Document Search, Site Search). Below the header, there are promotional banners for a Digital Power Contest, a 2 MHz 500 mA Switching Regulator, and the MASTERs Conference. A sidebar on the right lists features such as 'New 16-bit microcontroller & DSCs' and 'Microchip Advanced Parts Selector (MAPS)'. The main content area is divided into four columns: Products, Design, Support, and Buy. The 'Support' column contains a red-bordered box around the link 'Product Selection Tools'. A fifth column on the right, 'Applications', lists various design centers like Automotive, Connectivity, and Home Appliance.

# Microchip's Advanced Parts Selector (MAPS)

**Microchip Advanced Part Selector**

File Business Cards Global Part Search Updates Window Help

**Lookup - Microcontroller**

Classic View Express View

**Parameter Search** Match ALL (AND) Match ANY (OR)

Family -All-  8-Bit  16-Bit

From Thru

P.Memory (Kbytes) -All- -All- Program Memory

P.Memory (KWords) -All- -All-

Ram (Bytes) -All- -All- Sys. Mgmt Features

EEPROM (Bytes) -All- -All-

I/O Pins -All- -All-

Max CPU Speed -All- -All-

A/D Ch. -All- -All- Analog Peripherals

Comparator -All- -All-

UART Ch. -All- -All- Digital Comm. Features

SPI -All- -All-

I2C™ -All- -All-

CAN Ch. -All- -All- Connectivity

LCD Segments -All- -All-

Input Capture -All- -All- Capture/Compare PWM

PWM Ch. -All- -All-  CCP  ECCP  Standard PWM

8-Bit Timer -All- -All- App. Periph & Debug

16-Bit Timer -All- -All-

**Search Results** 82 MCHP parts found

PIC16F882  
 PIC16F883  
 PIC16F884  
 PIC16F886  
 PIC16F887

Reset Search  
 Side-By-Side  
 Express View

Specifications Dev Tools Technical Docs Budgetary Pricing

**PIC16F882** In Production

P.Memory (Kbytes) 3.5 flash  
 P.Memory (KWords) 2  
 Self-Write Flash Yes  
 RAM (Bytes) 128  
 EEPROM (Bytes) 128  
 I/O Pins 25  
 Max CPU Speed 20MHz, (5MIPS)  
 Internal OSC 8 MHz, 32 kHz  
 CodeGuard™ Security  
 System Mgmt Features PDR, WDT, nanoWatt

Analog Peripherals 2-Comparators w/SR-Latch; 1A/D, 11x10-bit @ 30ksps  
 Digital Comm. Peripherals 1-A/E/USART, 1-MSSP(SPI/I2C)  
 Connectivity

Capture/Compare PWM Peripherals 1-CCP, 1-ECCP  
 Digital Timers 2x8-Bit, 1x16-Bit

Application Peripherals

Debug/Development ICSP  
 Features  
 Device Package 28SP, 28SD, 28SS, 28ML

Other Features  
**Mid-Range 8-bit PICmicro® Microcontroller Family (14-bit Instruction Set)**  
 PIC16FXXX: 200 ns Instruction Execution, 35 Instructions, ICSP™ (except ROM), 25 mA source and sink per I/O

Analog  
 Memory  
 Microcontroller

Global Part Search

Have internet access? Select a part at the left, press one of the buttons below to buy, sample, or view current documentation for the PIC16F882

microchipDIRECT  
 sample.MICROCHIP  
 MICROCHIP

Can't find what you are looking for? Have a suggestion? Email us: mapshelp@microchip.com

Send Email

Specification and pricing information effective May 1, 2007

Start [Icons] Inbox - Microsoft... \\Overseer\picm... Sample Center O... Microchip Adva... Microsoft Office ... 1:58 PM



# Thank You!

# Trademarks

The Microchip name and logo, the Microchip logo, Accuron, dsPIC, KeeLoq, KeeLoq logo, microID, MPLAB, PIC, PICmicro, PICSTART, PRO MATE, rfPIC and SmartShunt are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

AmpLab, FilterLab, Linear Active Thermistor, Migratable Memory, MXDEV, MXLAB, SEEVAL, SmartSensor and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, Application Maestro, CodeGuard, dsPICDEM, dsPICDEM.net, dsPICworks, ECAN, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, Mindi, MiWi, MPASM, MPLAB Certified logo, MPLIB, MPLINK, PICkit, PICDEM, PICDEM.net, PICLAB, PICtail, PowerCal, PowerInfo, PowerMate, PowerTool, REAL ICE, rLAB, Select Mode, Smart Serial, SmartTel, Total Endurance, UNI/O, WiperLock and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A. All other trademarks mentioned herein are property of their respective companies.