



Figure 7 . Open Source BDM Schematic

2.2.1 USB interface Details

A 1.5 K Ω ($\pm 1\%$) pull-up resistor is provided on D-USB signal. A jumper is added to the pull-up resistor in order to assist in the ICP programming of the JB16, using techniques from AN2399.