

The World Leader in High Performance Signal Processing Solutions



差分放大器以及相关 设计软件的基础知识

Introduction to Differential Amplifiers

- ◆ **What is a Differential Amplifier?**
 - Op amp vs. differential amplifier
 - Discrete differential amplifier
 - Integrated differential amplifier
 - Advantages of differential amplifiers
- ◆ **Design Equations**
- ◆ **Design Example**
- ◆ **Demonstration of *NEW* Differential Amplifier Calculator**
- ◆ **Evaluation Boards**
- ◆ **Summary**


Differential Amplifiers

- ◆ **Are also know as:**
 - **Diff Amps**
 - **ADC Drivers**
 - **Fully Differential Amplifiers**




Differential Signals

What is a Differential Signal?

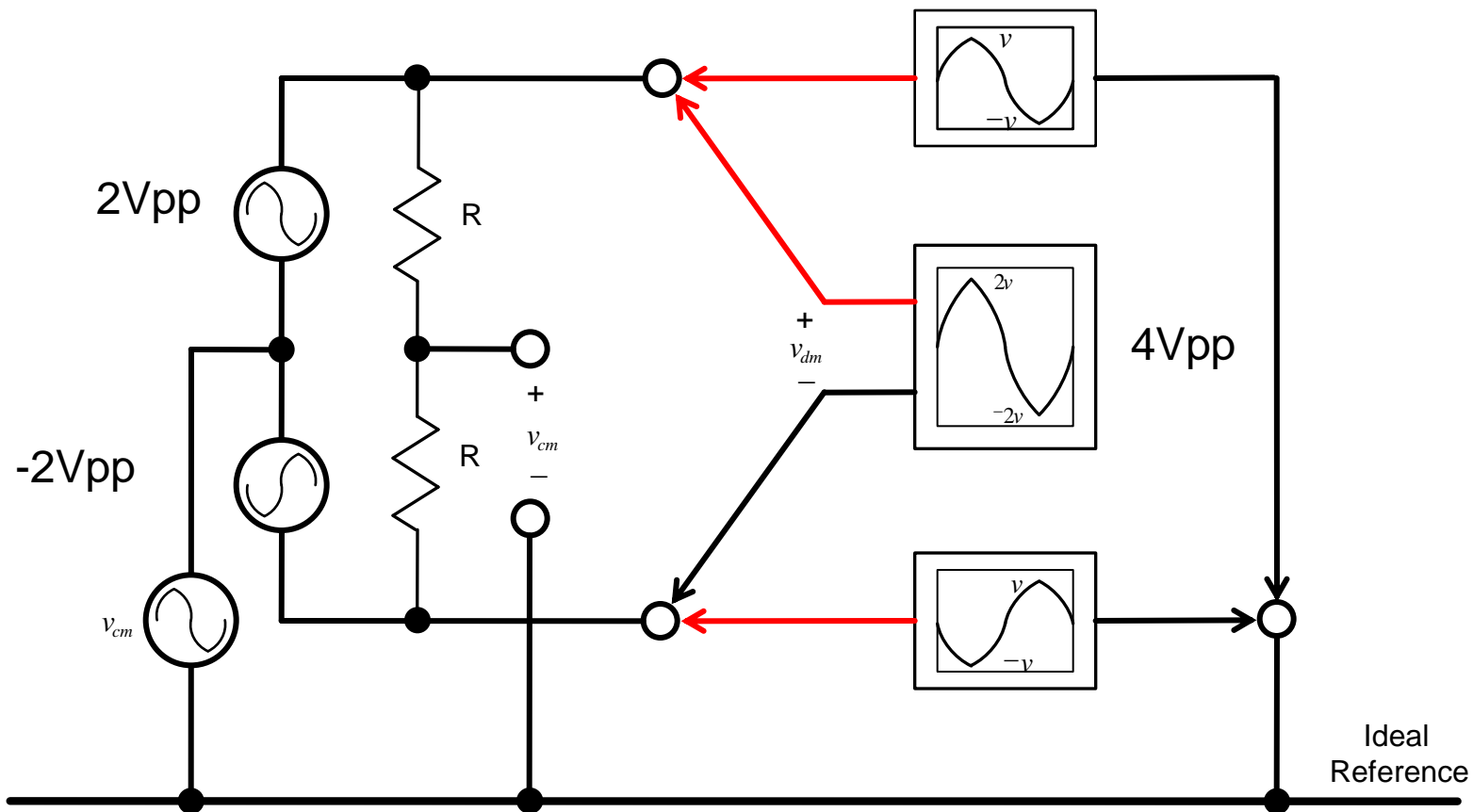

Key Points and Mathematical Definitions

- ◆ **Differential Voltage** is simply the potential *DIFFERENCE* between two conductors.
- ◆ **BALANCED** signaling uses two conductors that have signals of equal magnitude and opposite polarity with respect to a common reference.
- ◆ The terms **BALANCED** signaling and **DIFFERENTIAL** signaling are often used interchangeably.
- ◆ For any signal, balanced or otherwise, on two conductors, the signals can be defined as shown to the right with respect to a common reference, arbitrarily set = 0.



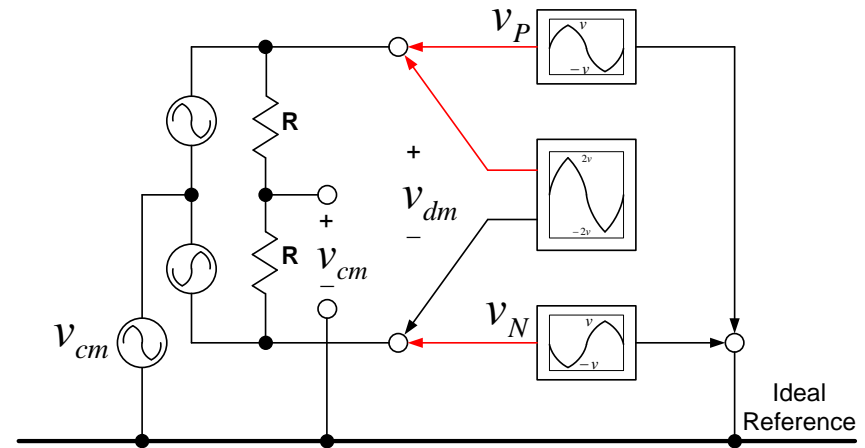


$$v_{dm} = v_P - v_N$$

$$v_{cm} = \frac{v_P + v_N}{2}$$

$$v_P = v_{cm} + \frac{v_{dm}}{2} \quad v_N = v_{cm} - \frac{v_{dm}}{2}$$

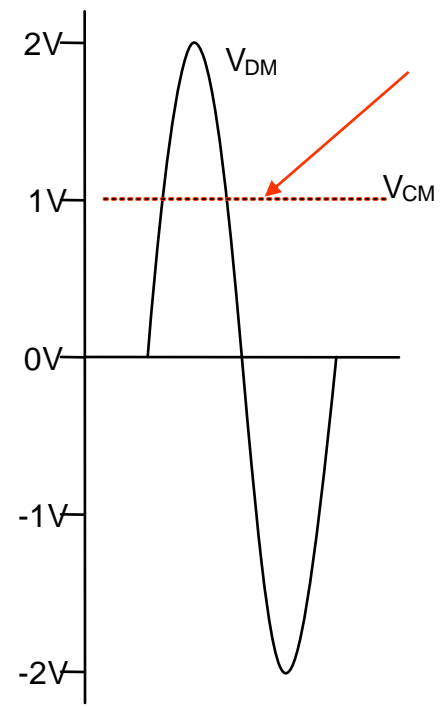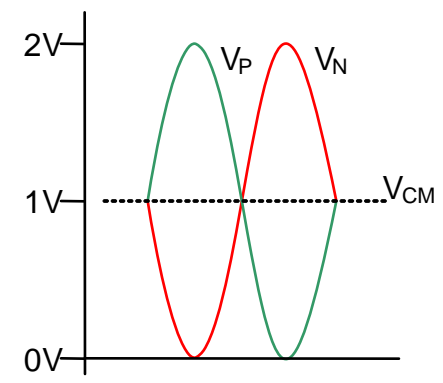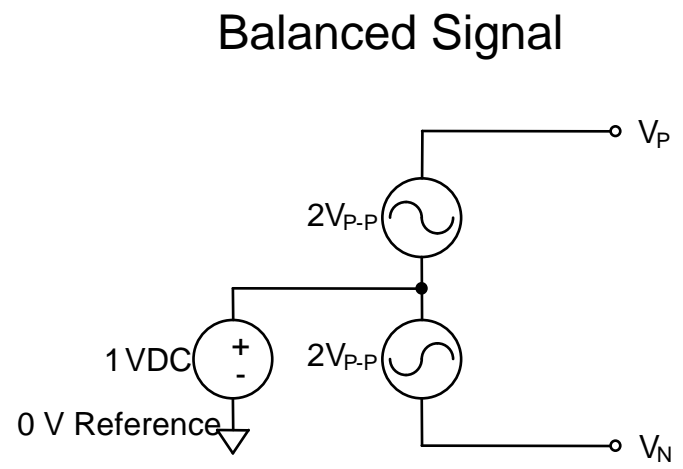Example of Differential and Common-Mode Signals




Essentially Constant
Common-Mode Voltage
Ensures Low EMI Radiation



$$v_{cm} = \frac{v_P + v_N}{2}$$

Example of Differential and Common-Mode Signals (cont'd)

Unbalanced Amplitude Signal

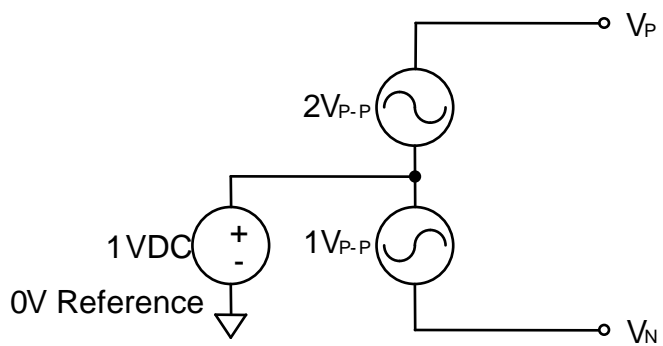

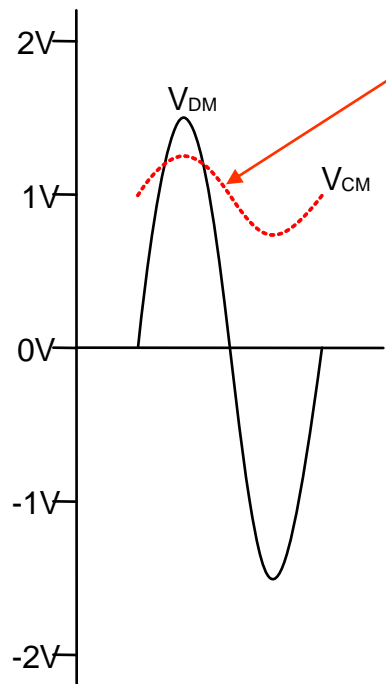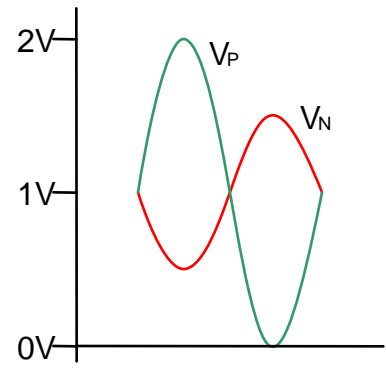A common-mode signal is also generated for phase errors between V_P and V_N .




Common-Mode Signal Causes EMI Radiation

$$v_{cm} = \frac{v_P + v_N}{2}$$


Comparison of Coupled Noise Behavior in Differential and Single-Ended Circuits (cont'd)

Noise Behavior In a Single-Ended Circuit

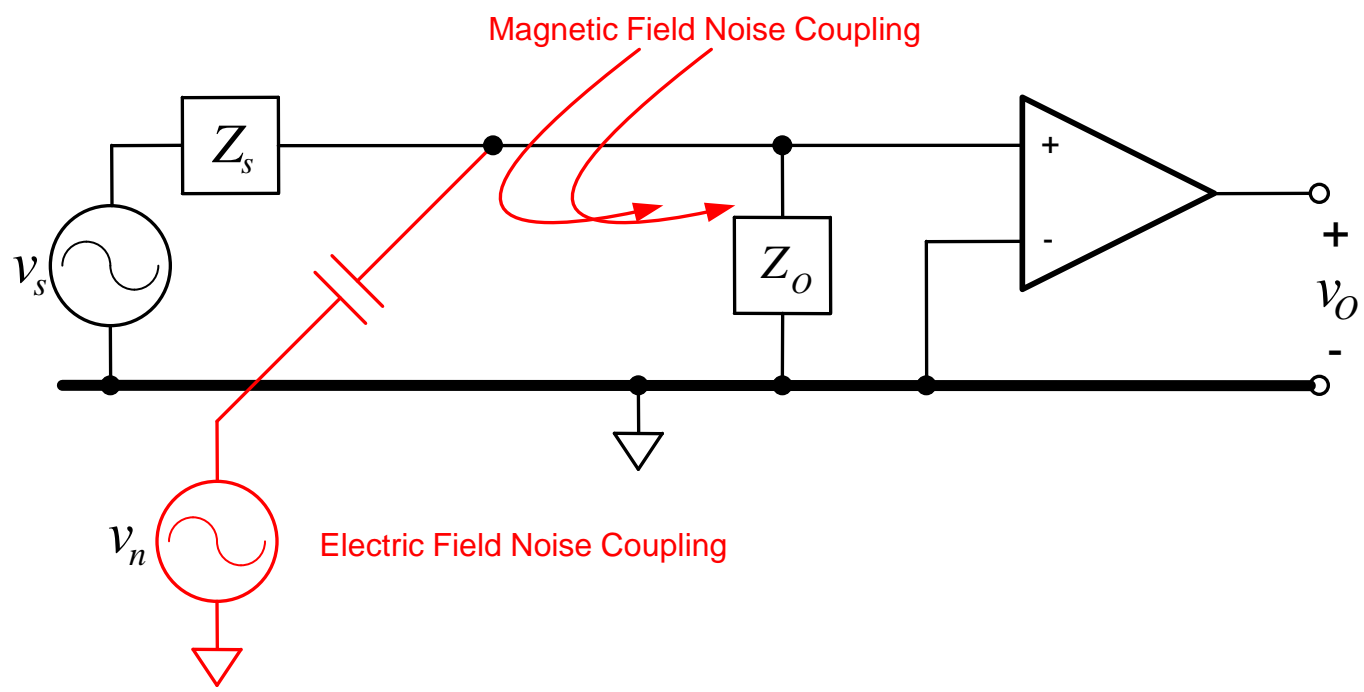


Comparison of Coupled Noise Behavior in Differential and Single-Ended Circuits (cont'd)

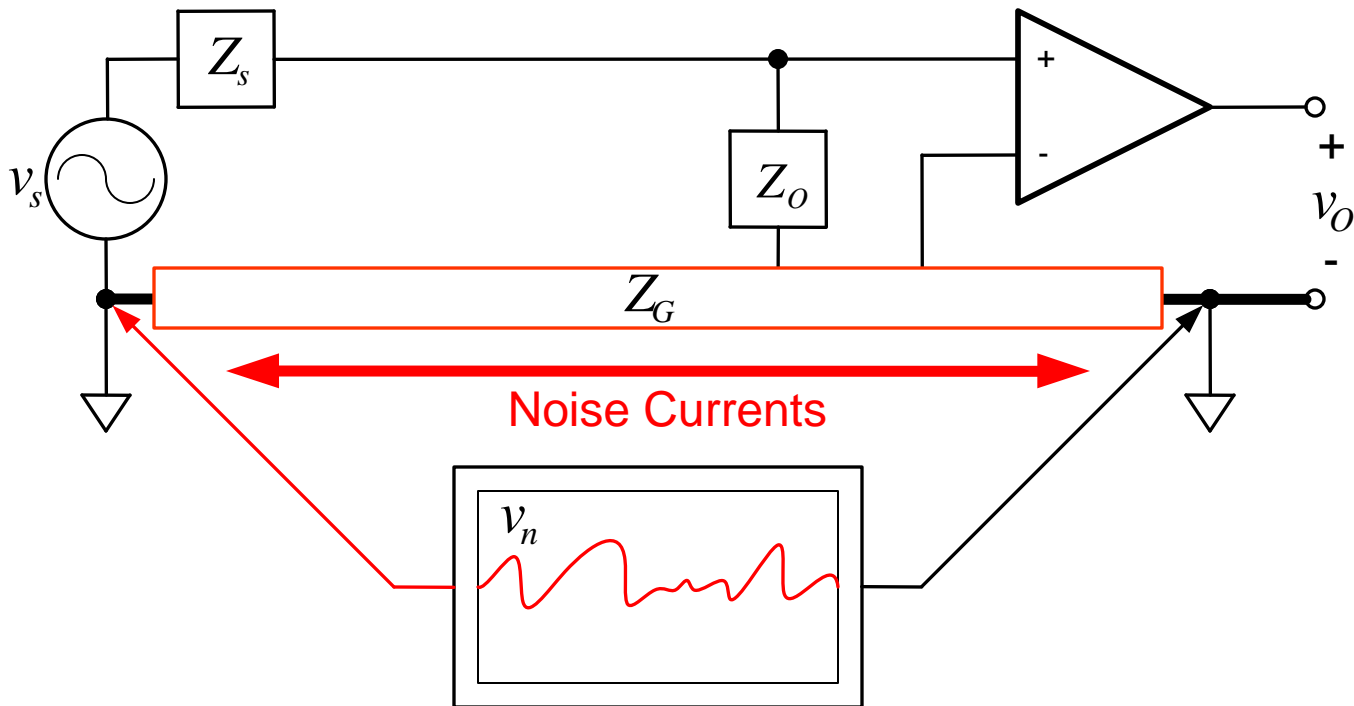Noise Behavior In a Single-Ended Circuit (cont'd)



Comparison of Coupled Noise Behavior in Differential and Single-Ended Circuits

Noise Behavior In a Differential Circuit

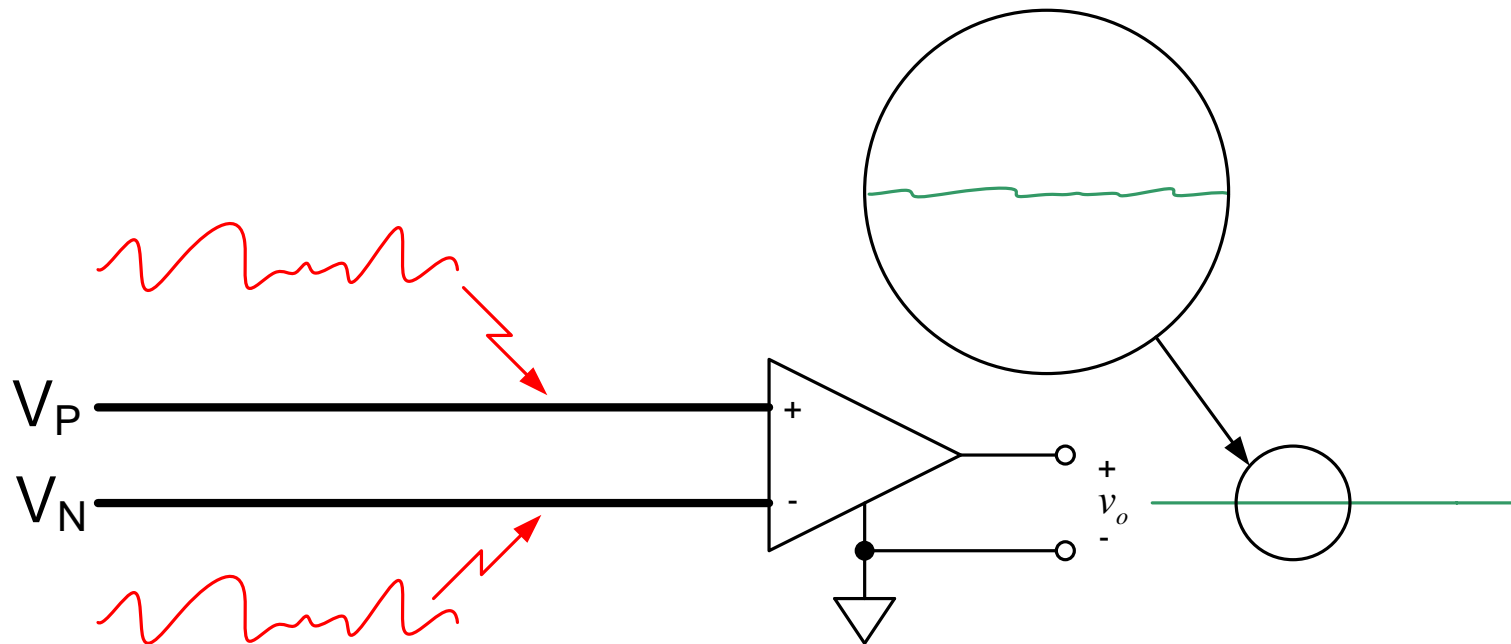


What is a Differential Amplifier?



Operational Amplifier vs. Differential Amplifier


Operational Amplifier

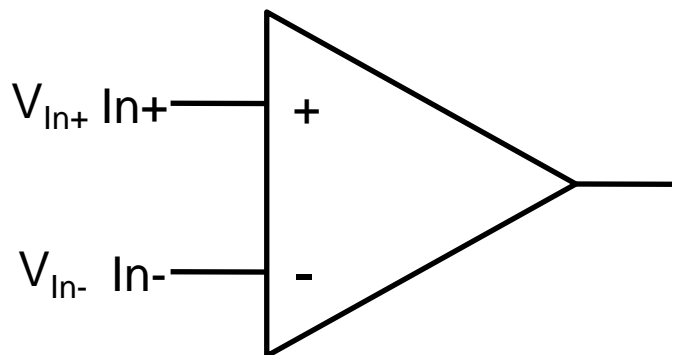- ◆ Differential input
 - Can be used single ended
- ◆ Single ended output
- ◆ Output common mode is set by signal
- ◆ Gain set by R_F & R_G





Differential Amplifier

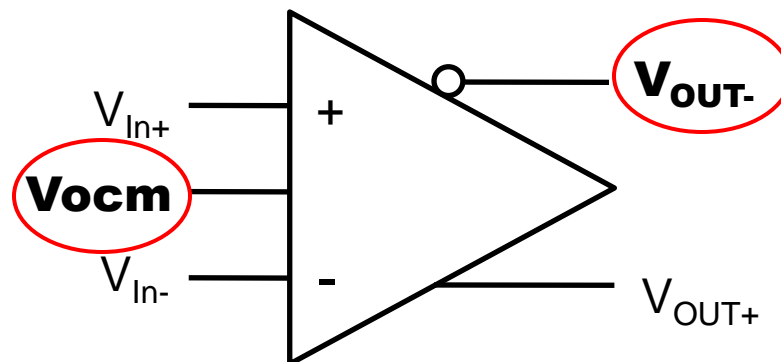
- ◆ Differential input
 - Can be used single ended
- ◆ Differential balanced output
- ◆ Output common mode set by V_{ocm} input pin
- ◆ Gain set by two pairs of R_F & R_G



Discrete Differential Amplifier

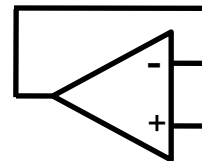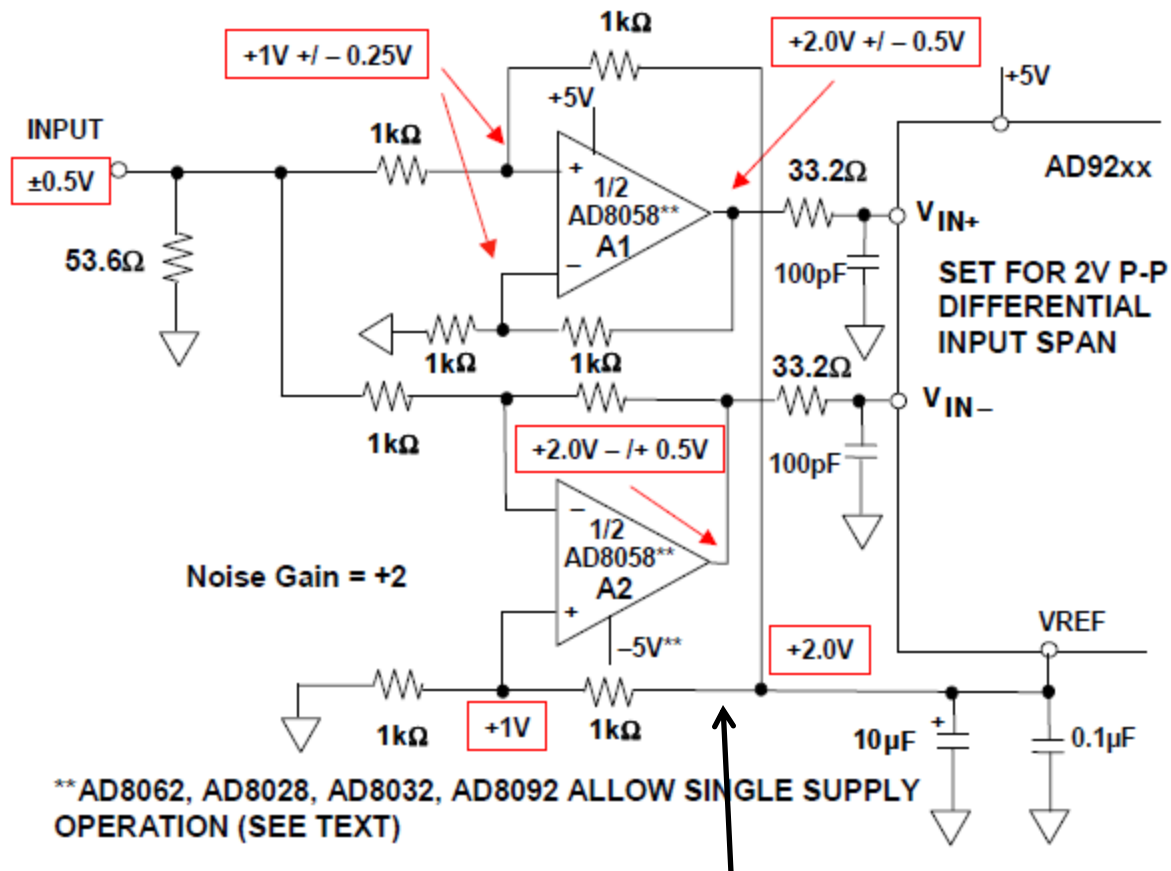


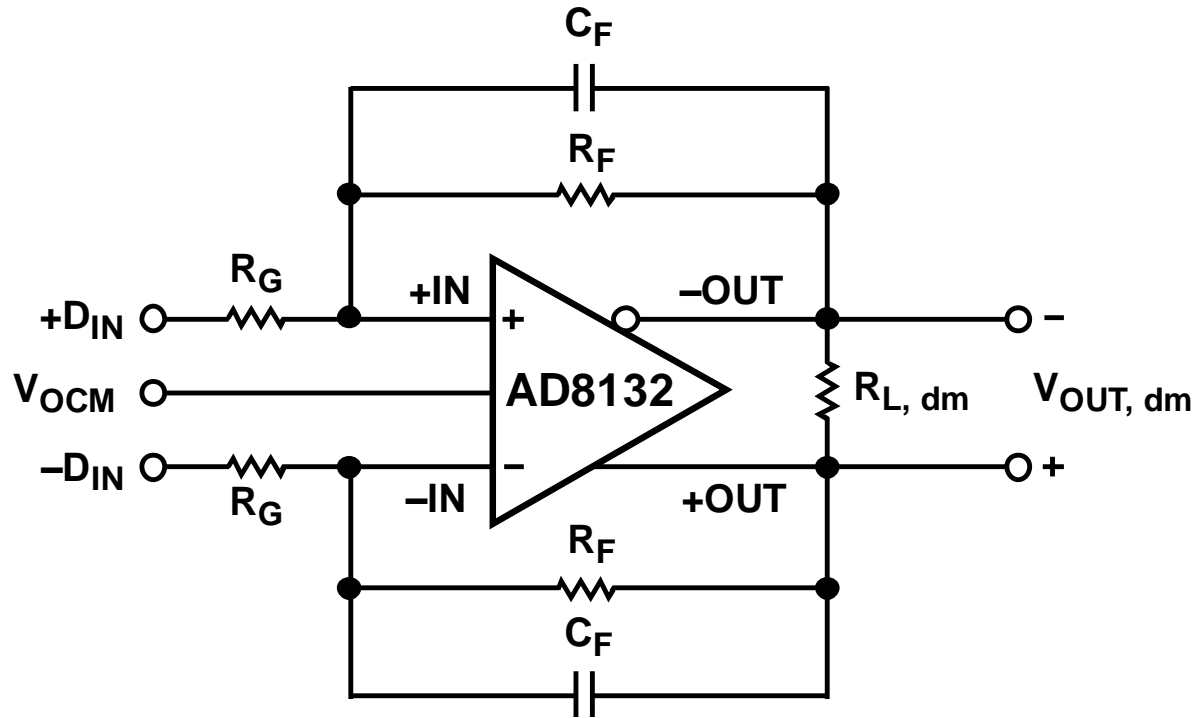Integrated Differential Amplifier Schematic



Integrated Differential Amplifier

Standard pinout vs. dedicated feedback

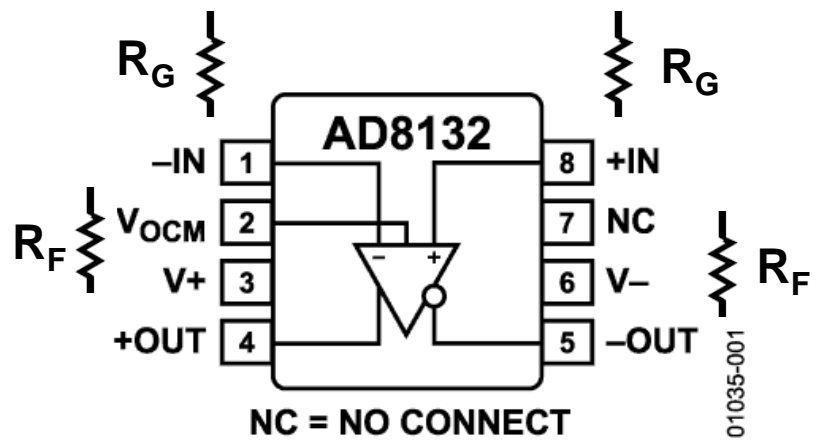

NC = NO CONNECT

Pin Configuration Diagram for AD8132

01035-001


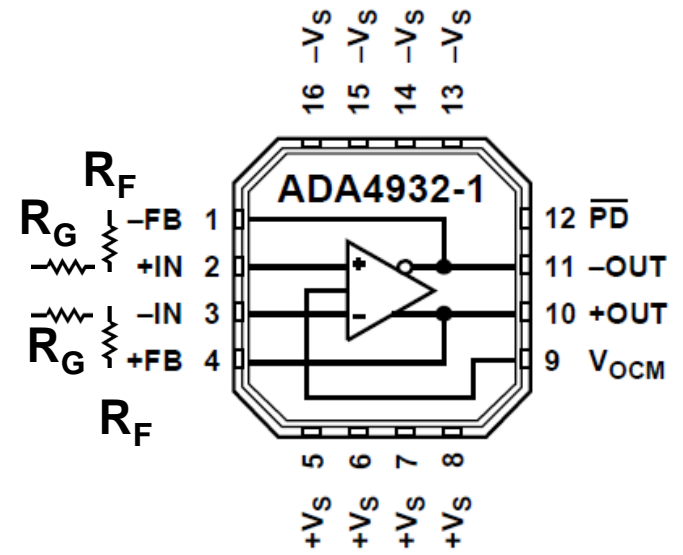


Figure 1. ADA4932-1

07752-001

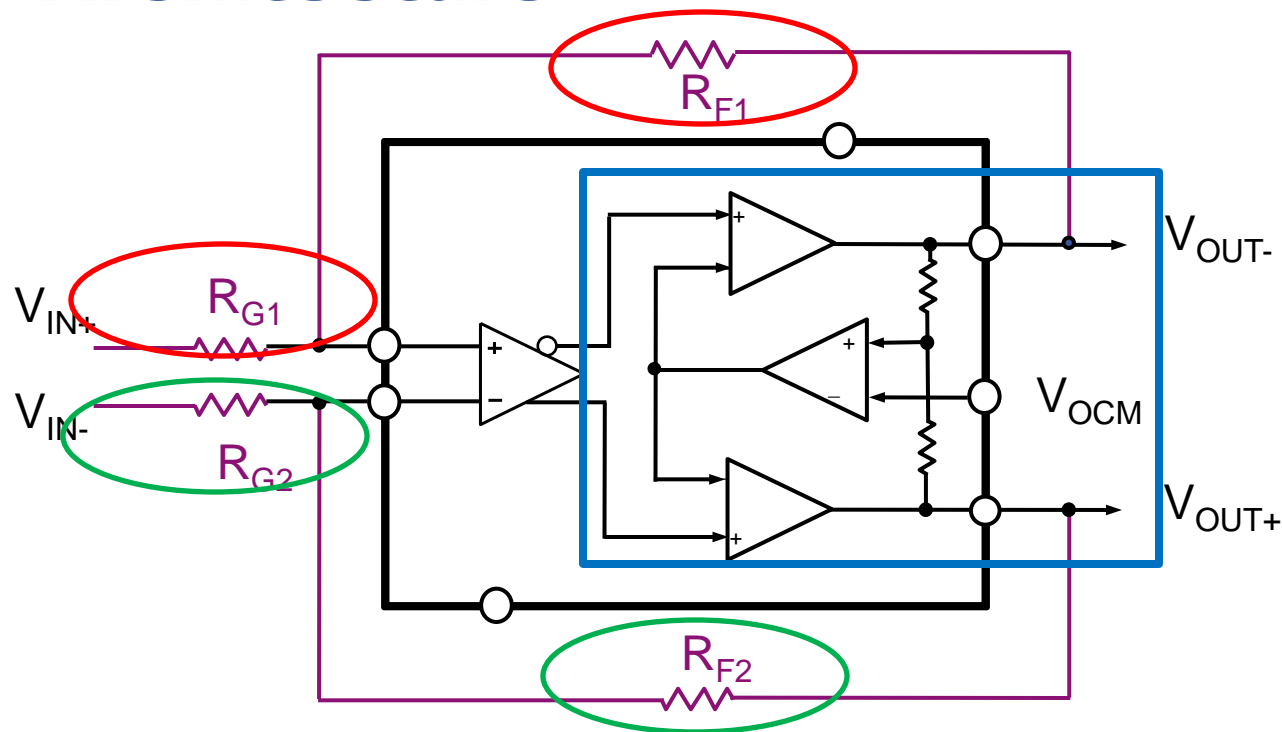AD813x/ADA493x Series Internal Architecture




- ◆ Differential Amplifier Uses Two Separate Feedback Loops
- ◆ Negative Feedback Forces Output CM Voltage to Equal V_{OCM}
- ◆ Output Balance Controlled By Internal Feedback Loop, Not R_F/R_G Ratios
- ◆ Internal Feedback Loop Allows Applications With Unequal R_F/R_G Ratios


Advantages of Differential Amplifiers

- ◆ Integration
- ◆ Output balance
- ◆ Independent output Vocm adjustment
- ◆ Reduced second harmonic distortion
- ◆ High common mode rejection
- ◆ **Wide output swing on single supply**

Op amp 1V headroom

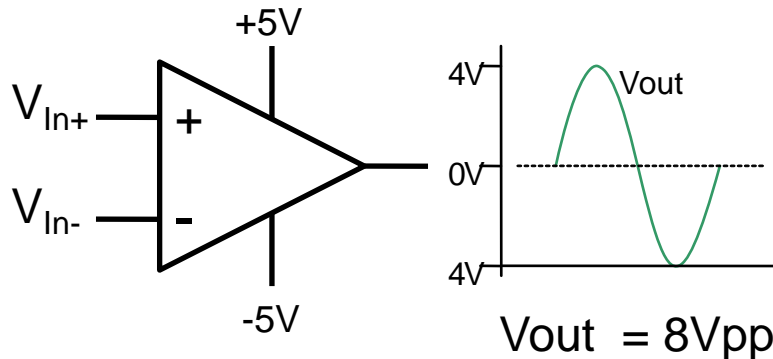


Diff amp 1V headroom

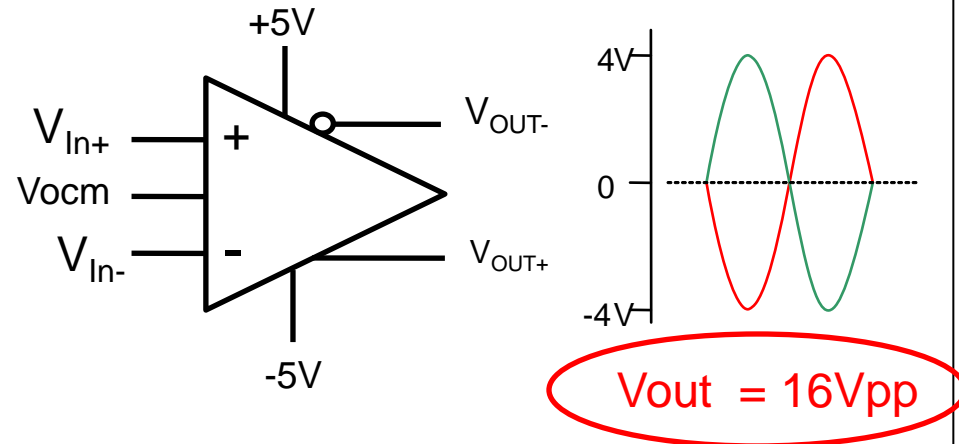



Applications

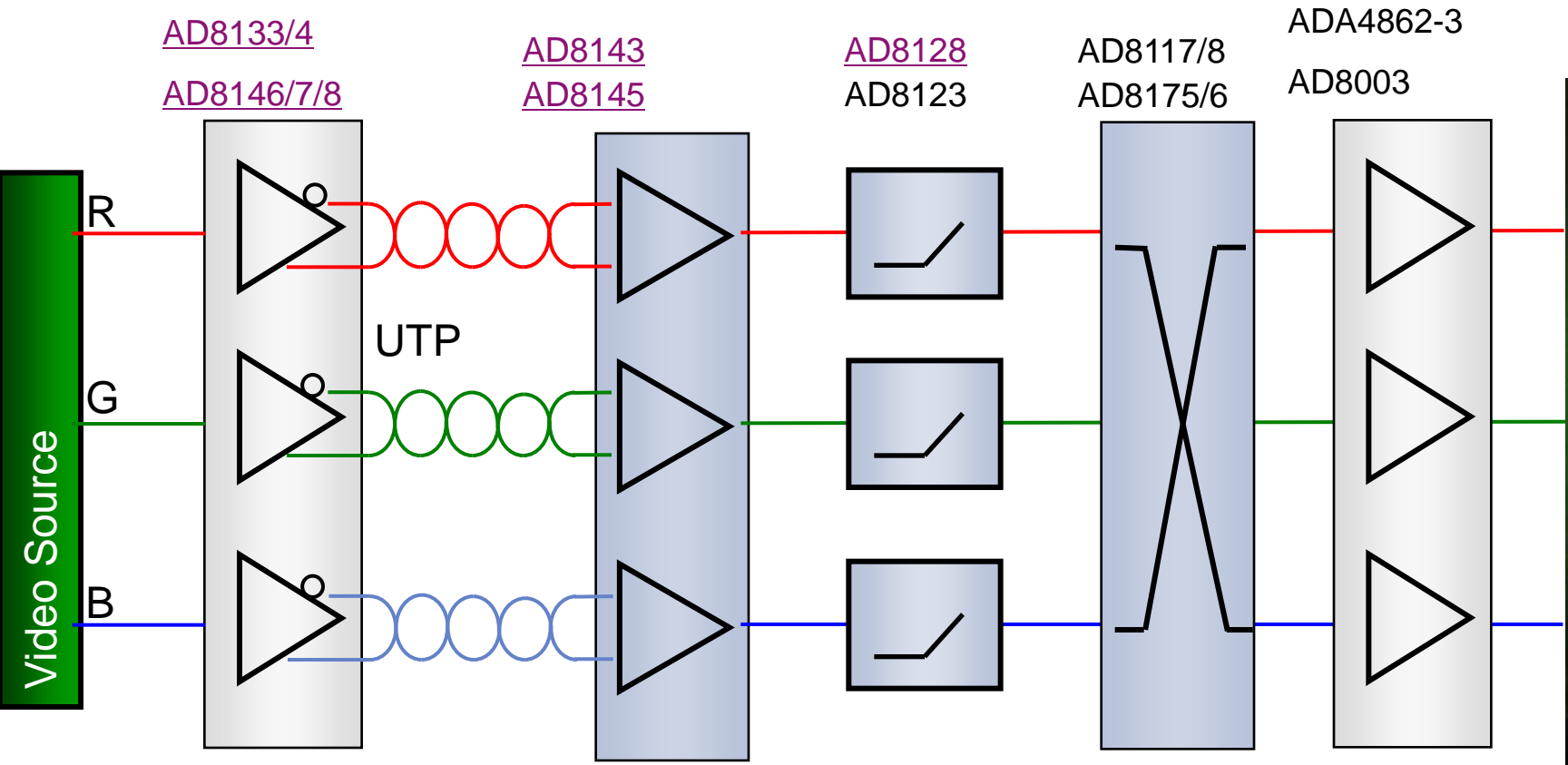ADI Complete Solution for Video over UTP Utilize X-points and High Speed Amps



DAC Output Buffer

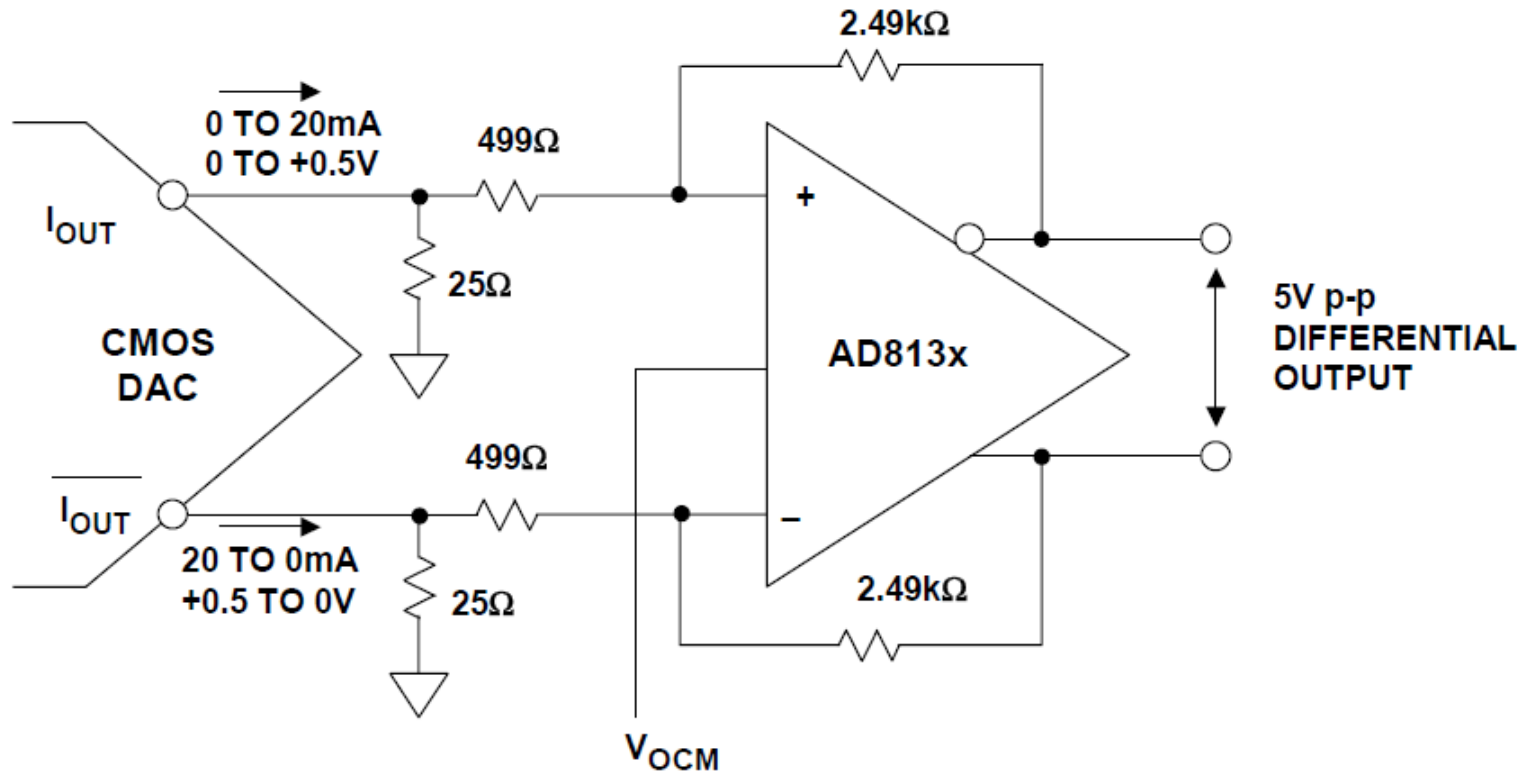


Figure 6.74: Buffering High Speed DACs Using AD813X Differential Amplifier

Differential Amplifier ADC Driver


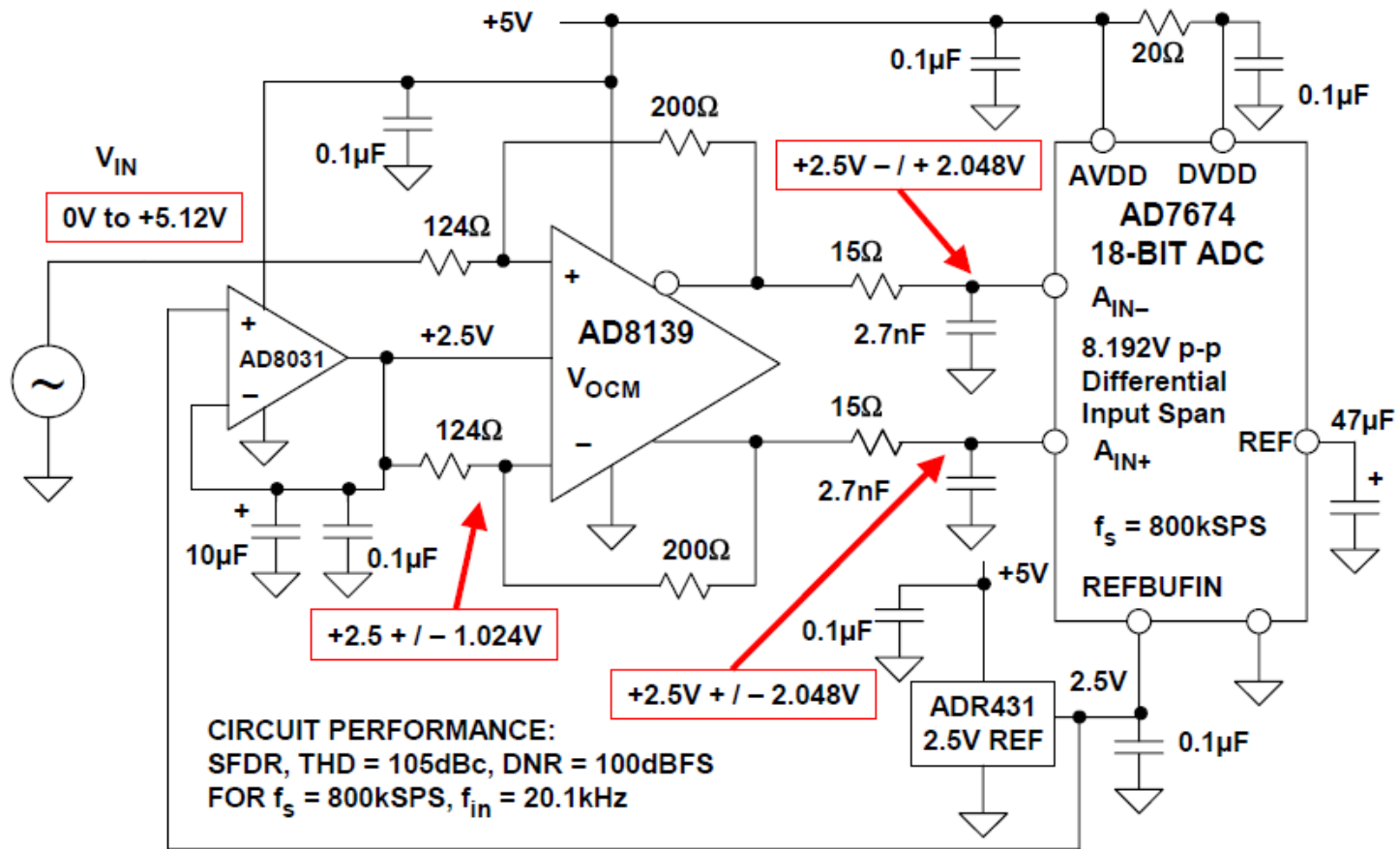


Figure 6.47: AD8139 Low Noise Differential Driver in a 18-bit ADC Application

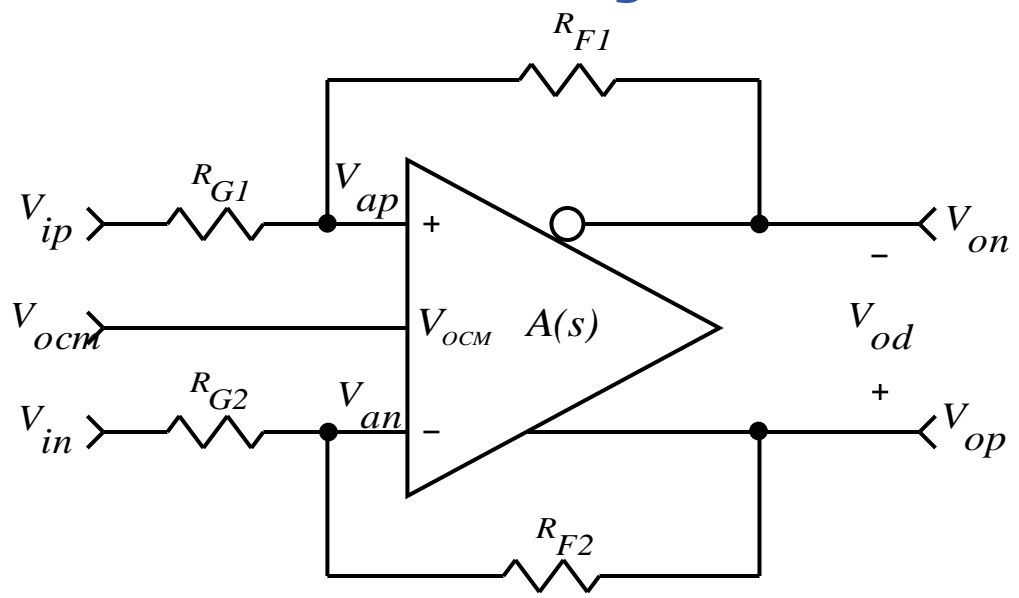

Differential Amplifier Design Equations

General Gain Analysis - Differential Drivers



$$\beta_1 \equiv \frac{R_{G1}}{R_{F1} + R_{G1}}$$

$$\beta_2 \equiv \frac{R_{G2}}{R_{F2} + R_{G2}}$$

$$V_{od} = A(s) (V_{ap} - V_{an})$$

$$V_{id} \equiv (V_{ip} - V_{in})$$

$$V_{od} = \left[\frac{2}{\beta_1 + \beta_2} \right] \left[\frac{V_{ocm} (\beta_1 - \beta_2) + V_{ip} (1 - \beta_1) - V_{in} (1 - \beta_2)}{1 + \frac{2}{A(s) (\beta_1 + \beta_2)}} \right]$$


General Case, $\beta_1 \neq \beta_2$

For $\beta_1 = \beta_2 \equiv \beta$:

$$\frac{V_{od}}{V_{id}} = \left[\frac{R_F}{R_G} \right] \left[\frac{1}{1 + \frac{1}{A(s)\beta}} \right] \rightarrow 0$$

$$\frac{V_{od}}{V_{id}} = \left[\frac{R_F}{R_G} \right]$$

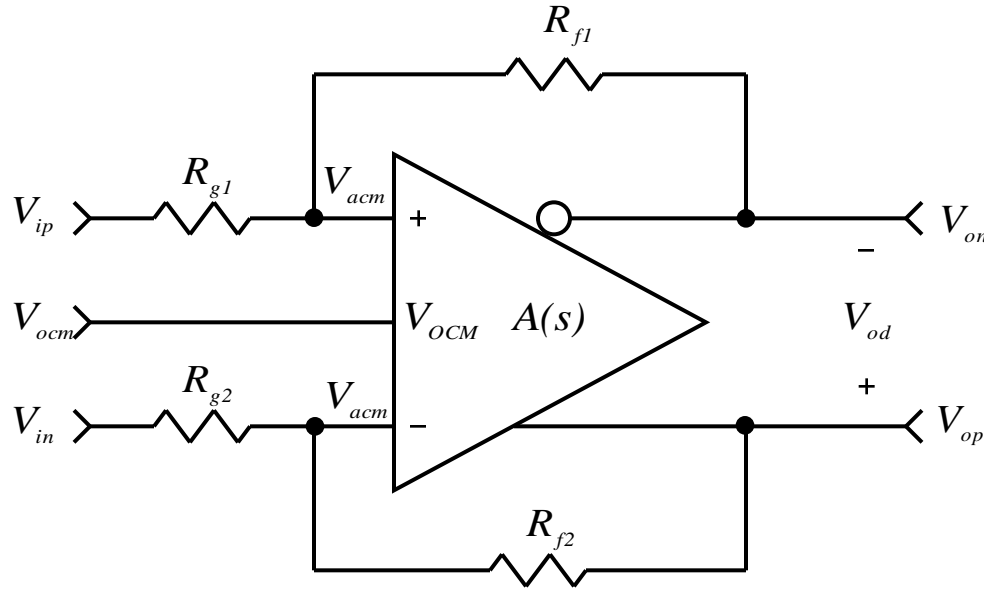General Common Mode Voltage Analysis – Differential Drivers



$$\beta_1 \equiv \frac{R_{g1}}{R_{f1} + R_{g1}}$$

$$\beta_2 \equiv \frac{R_{g2}}{R_{f2} + R_{g2}}$$

$$A(s) \rightarrow \infty$$

$$V_{acm} = \frac{2\beta_1\beta_2V_{ocm} + V_{ip}\beta_2(1-\beta_1) + V_{in}\beta_1(1-\beta_2)}{\beta_1 + \beta_2}$$

$$\beta_1 = \beta_2 \equiv \beta$$


$$V_{acm} = \beta V_{ocm} + (1-\beta)V_{icm}$$

or

$$V_{acm} = V_{icm} + \beta(V_{ocm} - V_{icm})$$


$$V_{icm} \equiv \frac{V_{ip} + V_{in}}{2}$$

Differential Input Impedance

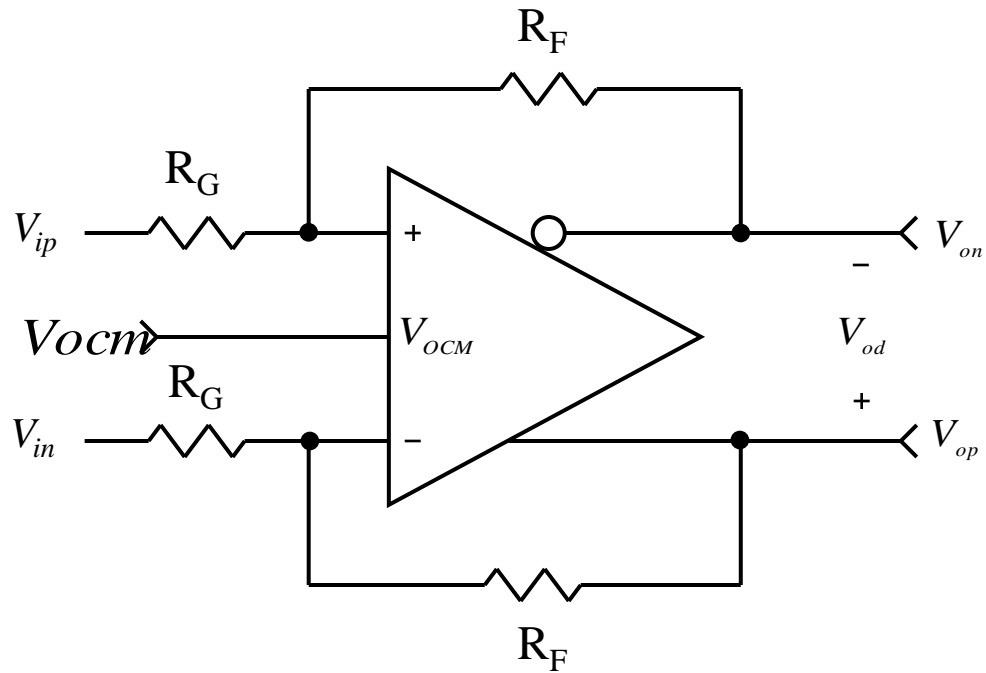

$$R_{IN,dm} = 2 \times R_G$$

Single Ended Input Impedance

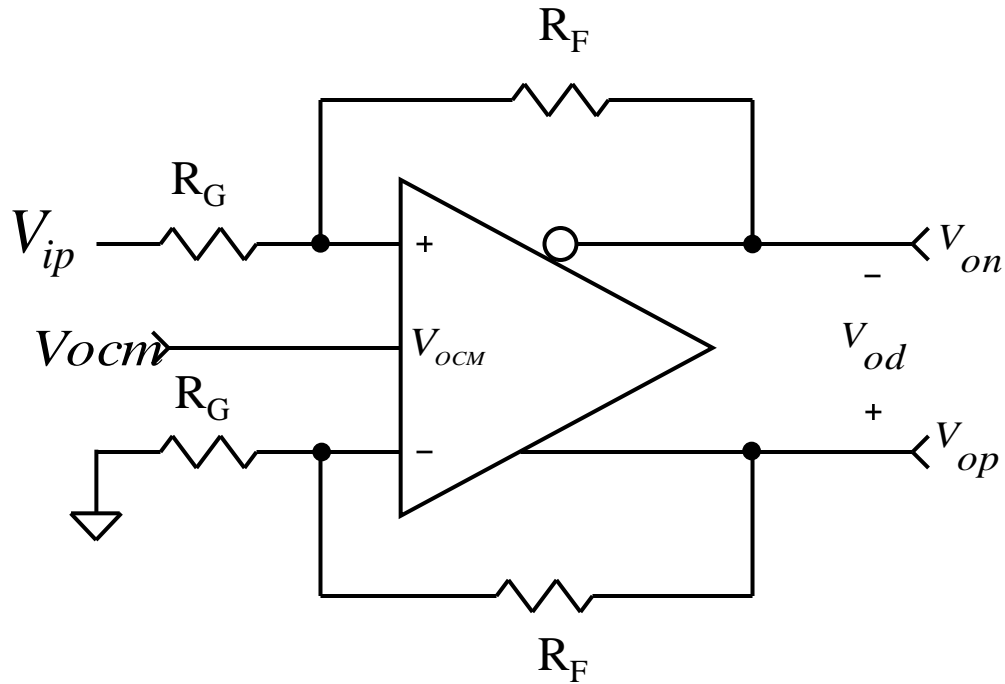



$$R_{IN} = \left\{ \frac{R_G}{1 - \frac{R_F}{2 * (R_G + R_F)}} \right\}$$




Single Ended to Differential Design Example

Terminate a Single-Ended Input and Calculate the Noise

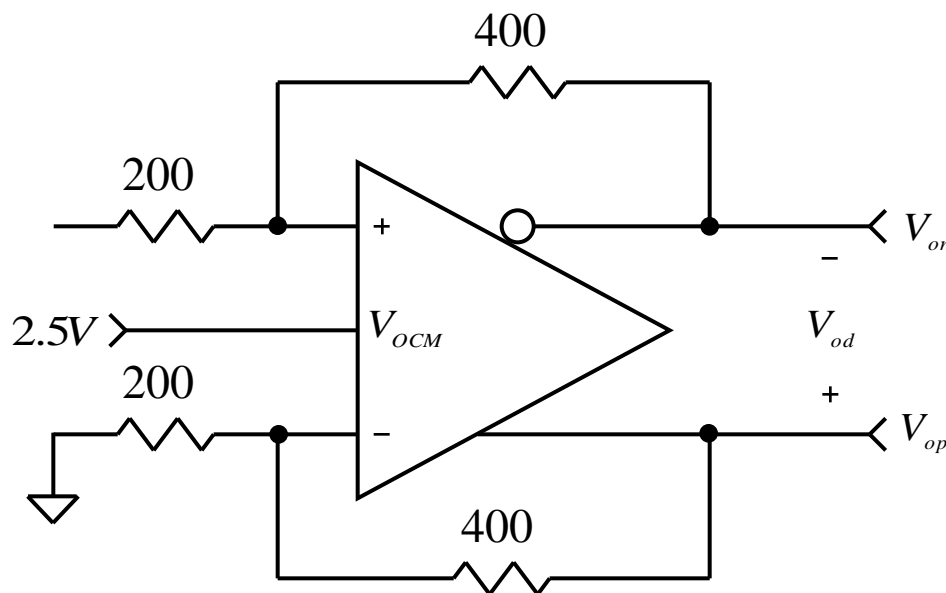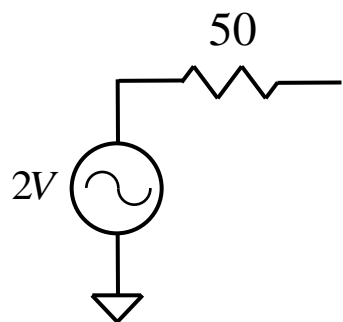Requirements: Differential Gain = 1, 50Ω Termination, Resistors ~200/400Ω




Single Ended Input Impedance

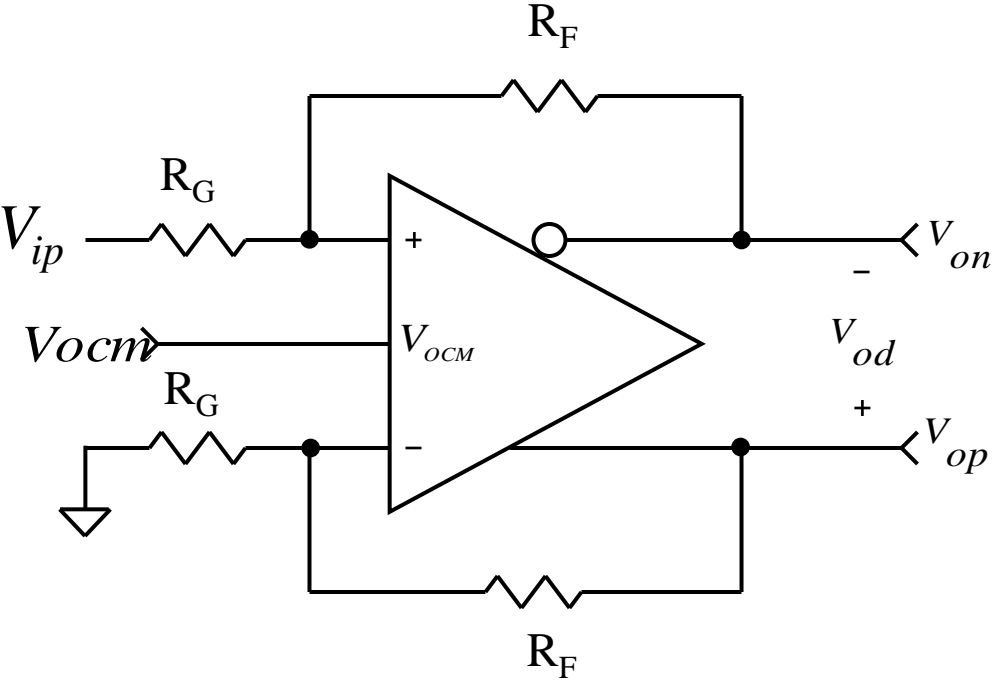

$$R_{IN} = \left\{ \frac{R_G}{1 - \frac{R_F}{2 * (R_G + R_F)}} \right\}$$


Terminating a Single-Ended Input

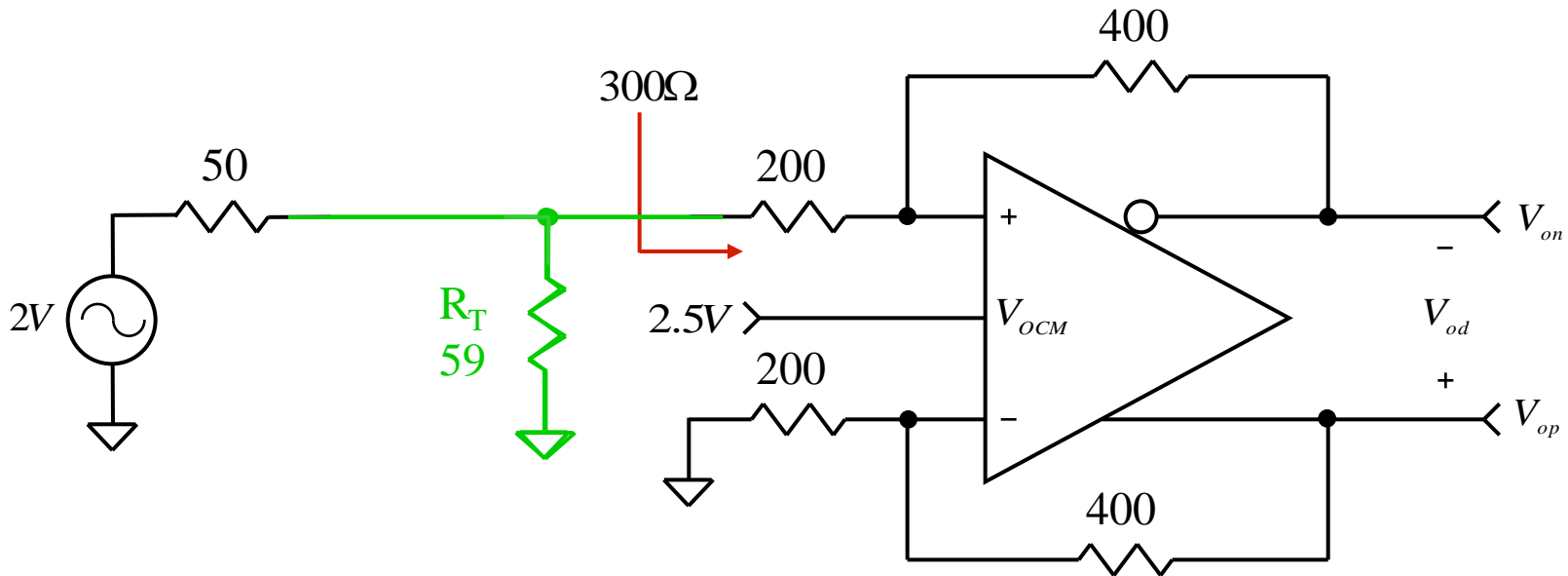Requirements: Differential Gain = 1, 50Ω Termination, Resistors ~200Ω




Terminating a Single-Ended Input

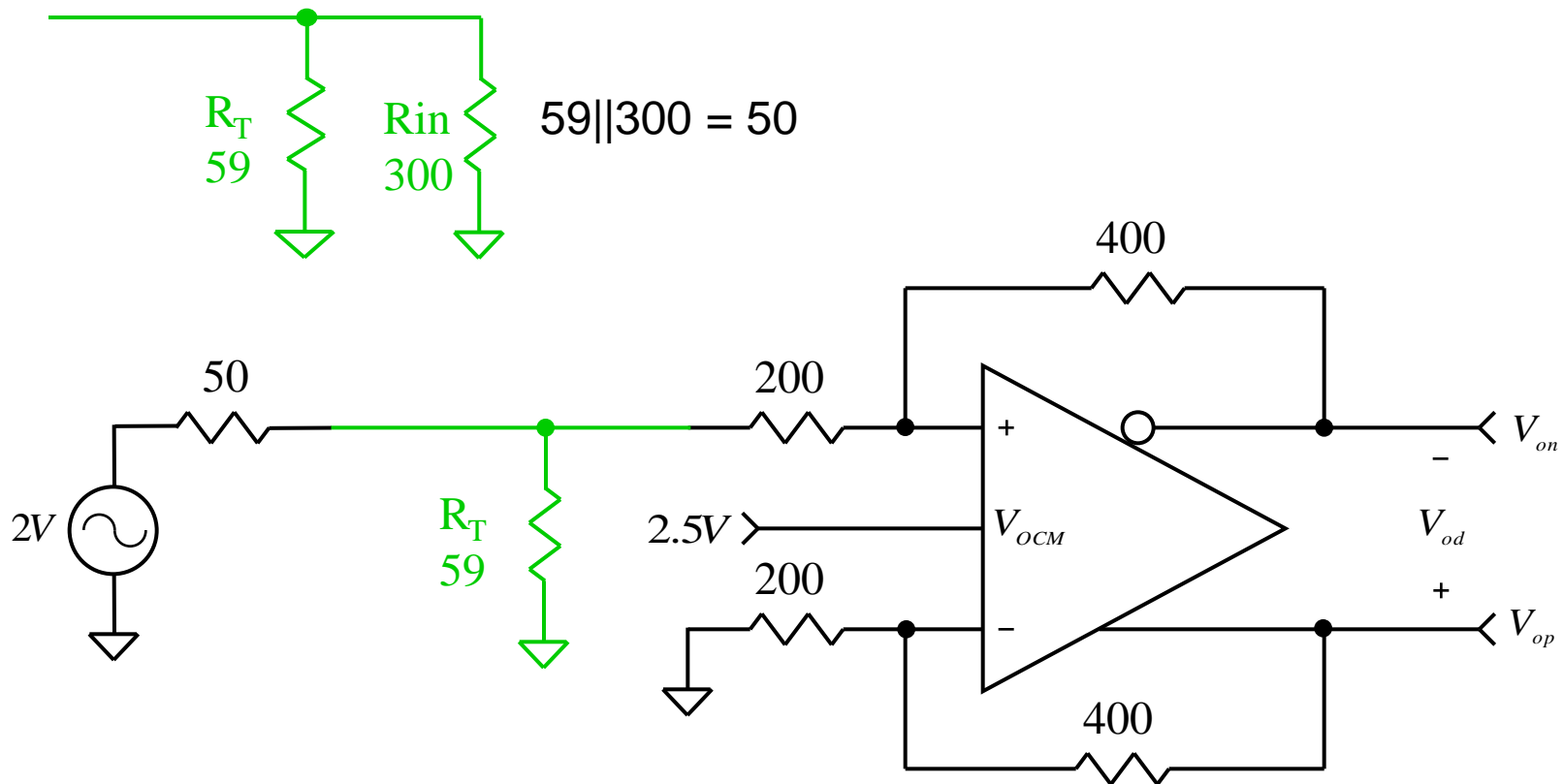Requirements: Differential Gain = 1, 50Ω Termination, Resistors ~200Ω




Terminating a Single-Ended Input

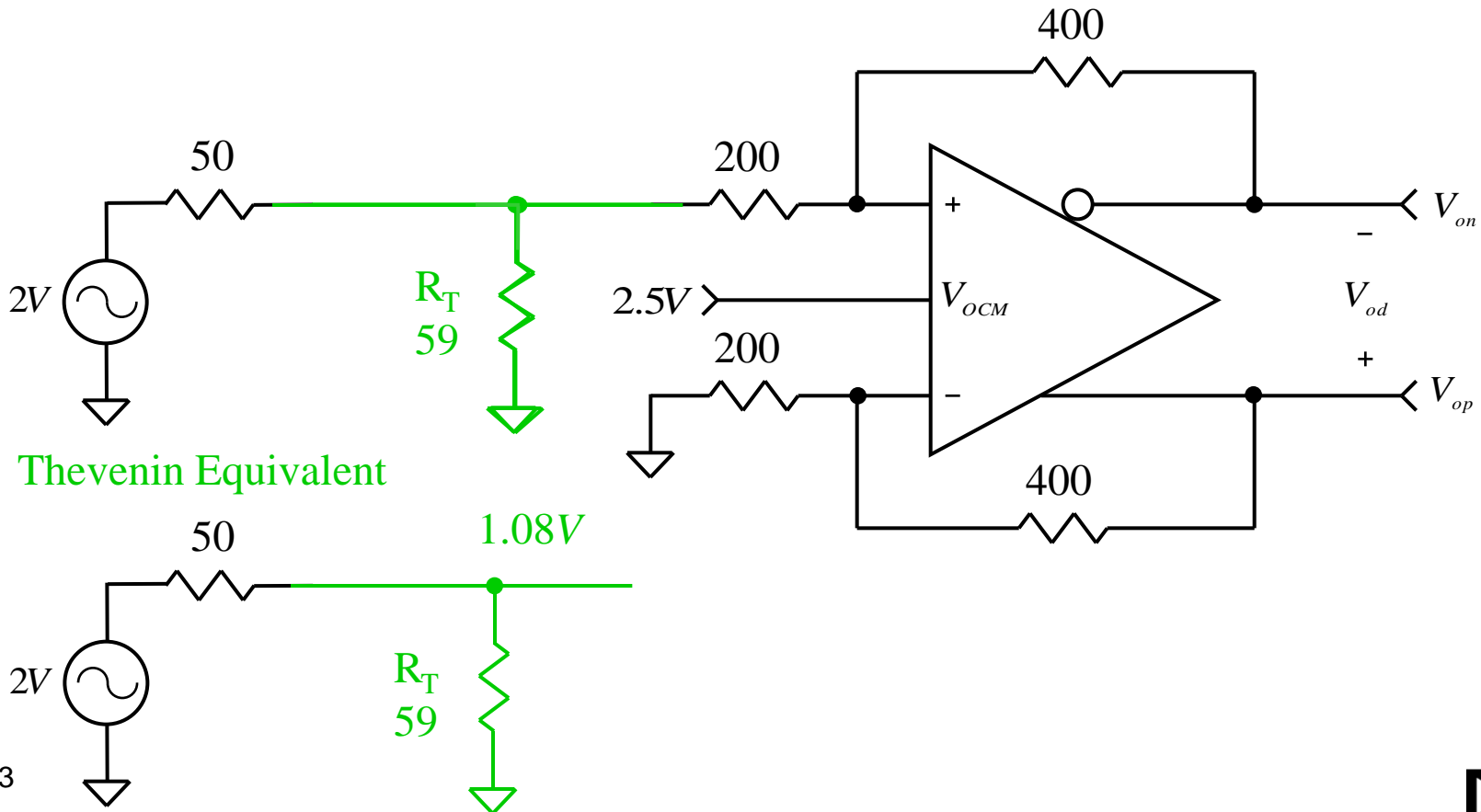Requirements: Differential Gain = 1, 50Ω Termination, Resistors ~200Ω



Terminating a Single-Ended Input

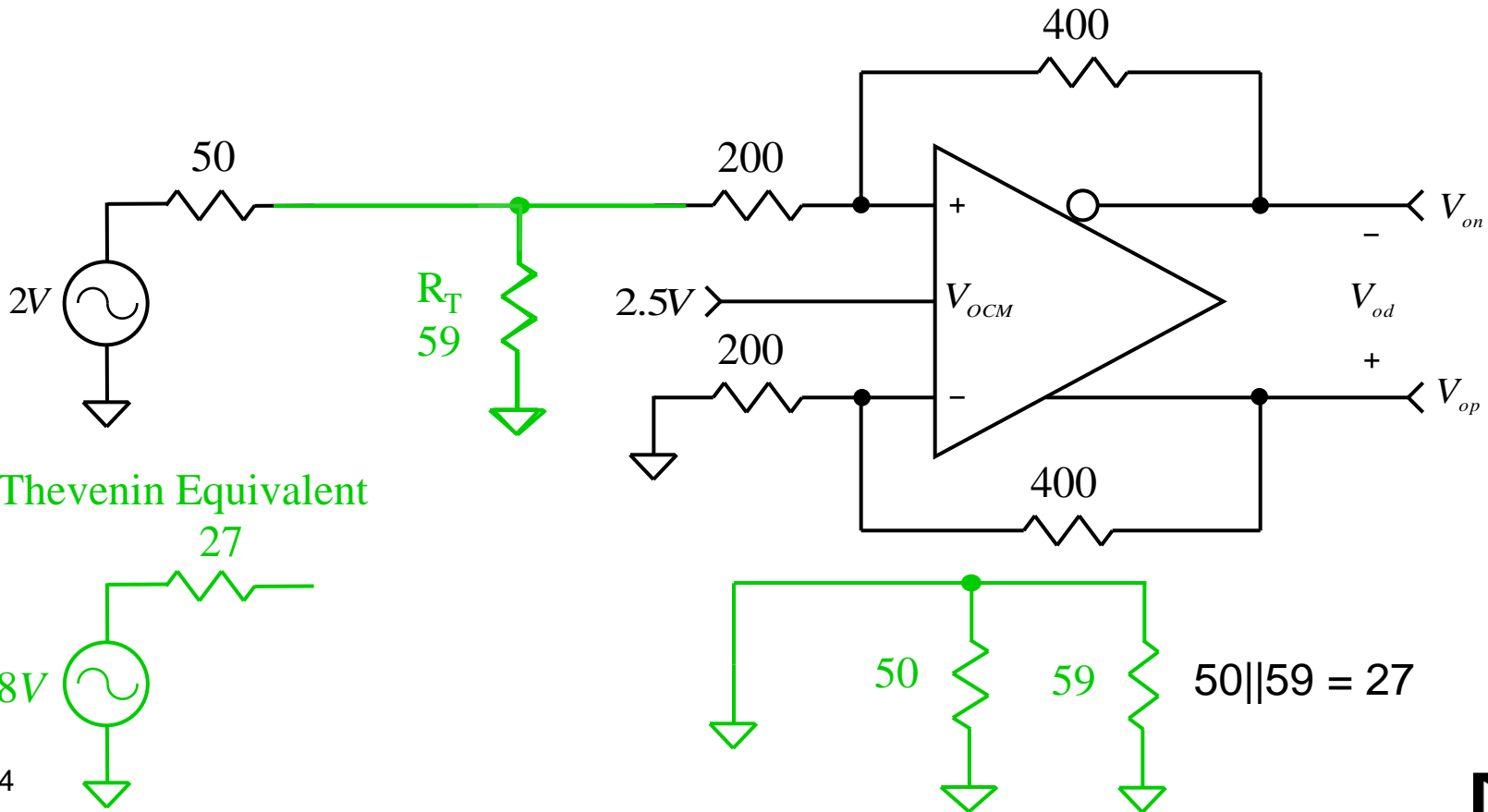Requirements: Differential Gain = 1, 50Ω Termination, Resistors ~200Ω




Terminating a Single-Ended Input

Requirements: Differential Gain = 1, 50Ω Termination, Resistors ~200Ω

$$\frac{V_{od}}{V_{id}} = \left[\frac{R_F}{R_G} \right]$$

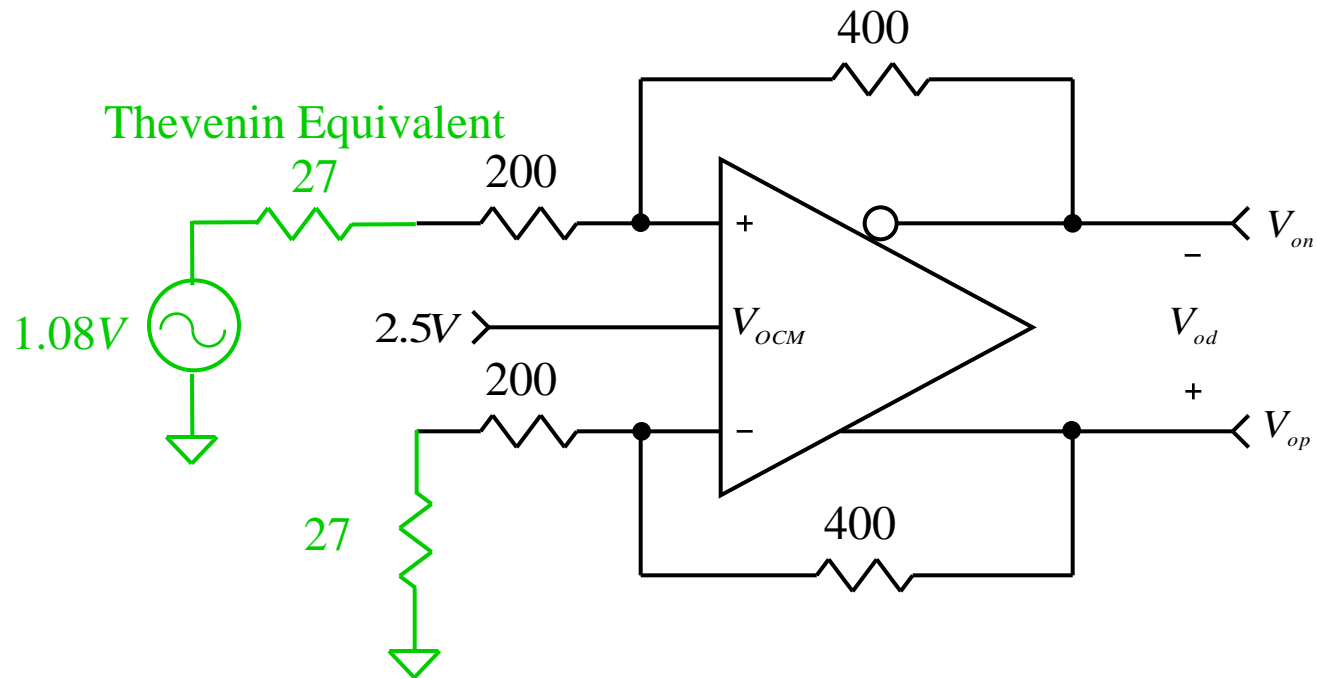
$$\frac{V_{od}}{V_{id}} = \left[\frac{400}{227} \right] = 1.76 * 1.08V = 1.9V$$



Terminating a Single-Ended Input


Requirements: Differential Gain = 1, 50Ω Termination, Resistors ~200Ω
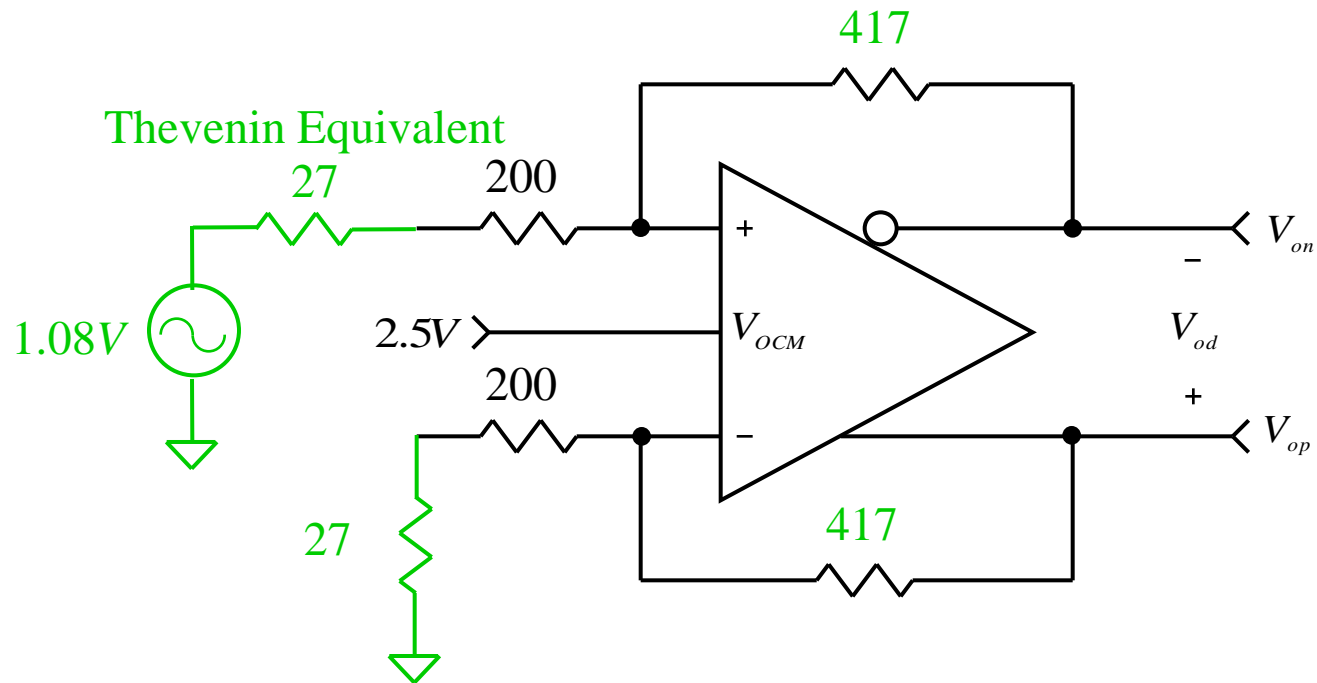
$$\frac{V_{od}}{V_{id}} = \left[\frac{R_F}{R_G} \right] = \frac{417}{227} = 1.84 * 1.08V = 1.99V$$




Terminating a Single-Ended Input

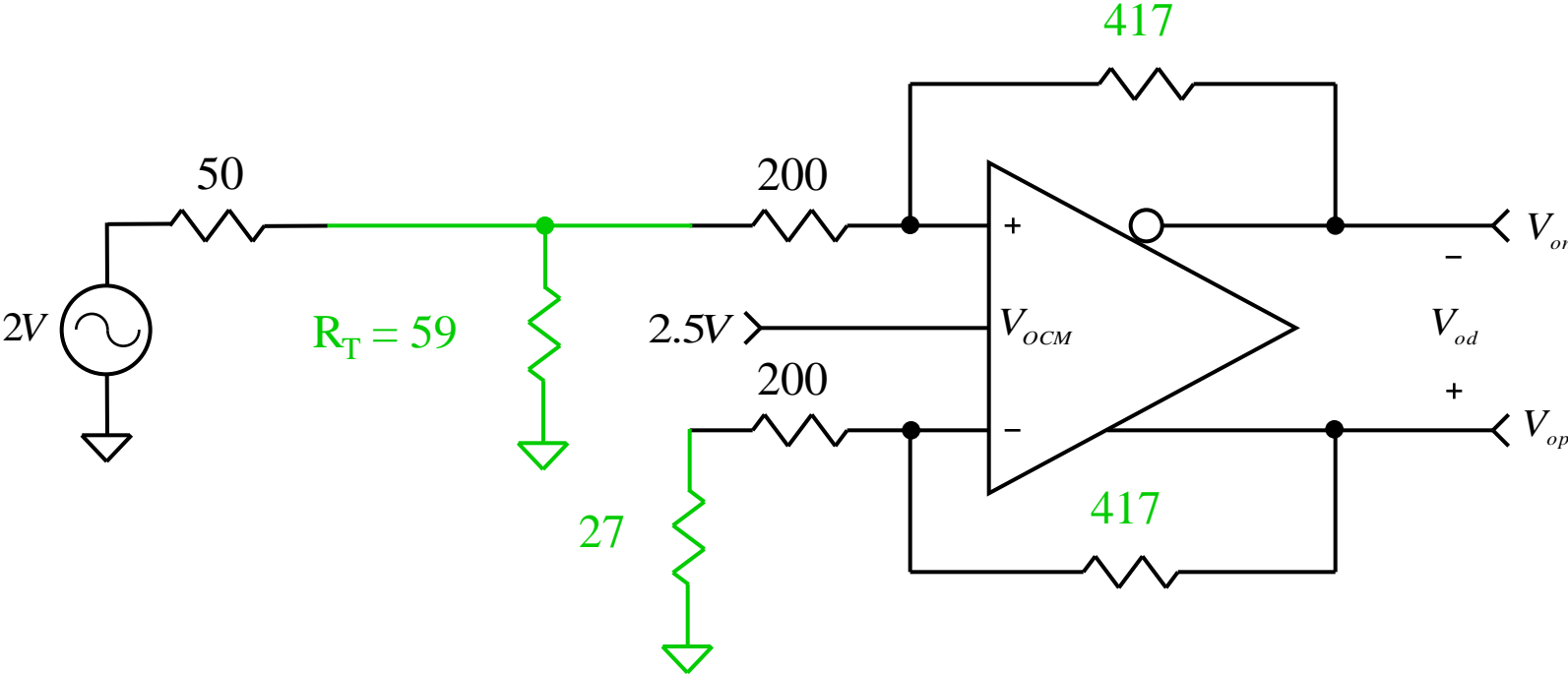Requirements: Differential Gain = 1, 50Ω Termination, Resistors ~200Ω



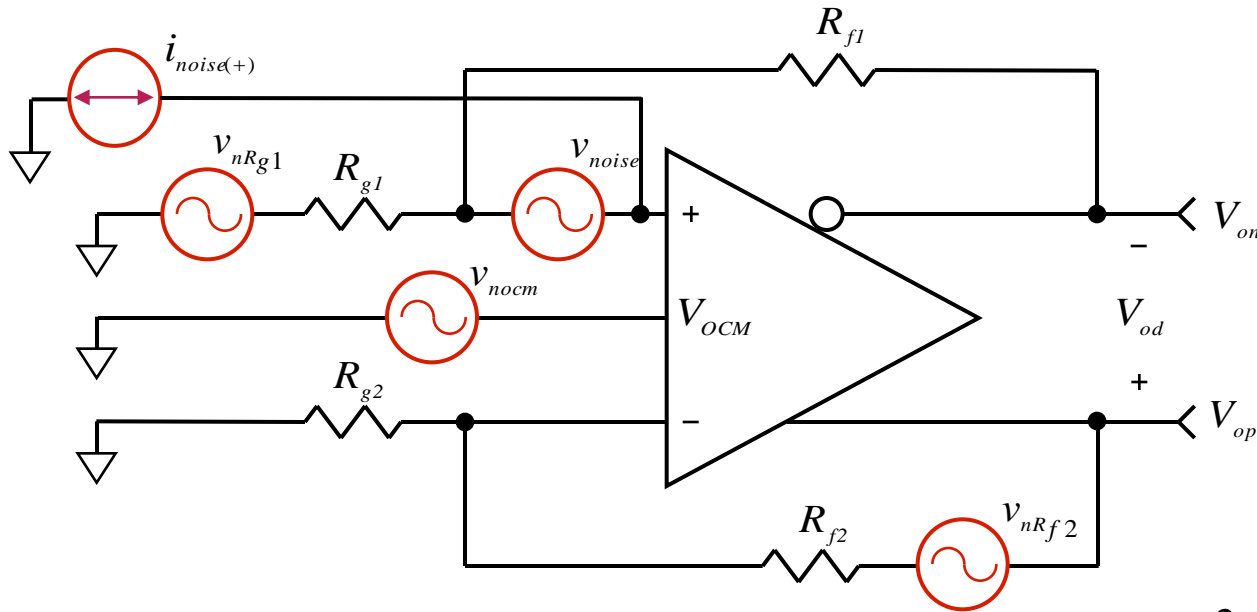General Differential Driver Noise Analysis



$$\beta_1 \equiv \frac{R_{g1}}{R_{f1} + R_{g1}}$$

$$\beta_2 \equiv \frac{R_{g2}}{R_{f2} + R_{g2}}$$

$$A(s) \rightarrow \infty$$

Differential output noise due to Input – Referred Voltage Noise = $\frac{2v_{noise}}{\beta_1 + \beta_2} = \frac{v_{noise}}{\beta}$ for $\beta_1 = \beta_2 \equiv \beta$

Differential output noise due to V_{OCM} Input – Referred Noise = $\frac{2v_{nocm}(\beta_1 - \beta_2)}{\beta_1 + \beta_2} = 0$ for $\beta_1 = \beta_2$

Differential output noise due to $i_{noise(+)}$ = $\frac{(2i_{noise(+)}R_{g1})(1 - \beta_1)}{\beta_1 + \beta_2} = i_{noise(+)}R_{f1}$ for $\beta_1 = \beta_2$; similar for $i_{noise(-)}$

Differential output noise due to R_{g1} = $\frac{(2\sqrt{4kTR_{g1}})(1 - \beta_1)}{\beta_1 + \beta_2} = \sqrt{4kTR_{g1}} \left(\frac{R_f}{R_g} \right)$ for $\beta_1 = \beta_2$; similar for R_{g2}

Differential output noise due to R_{f2} = $\frac{2\beta_2\sqrt{4kTR_{f2}}}{\beta_1 + \beta_2} = \sqrt{4kTR_{f2}}$ for $\beta_1 = \beta_2$; similar for R_{f1}



Single Ended to Differential Design Example Using **New Differential Amplifier Calculator**

Differential Amplifier Calculator

Differential Amplifier Calculator
ANALOG DEVICES
Version 1.0.1

Resistor Tolerance

None (3SF)

<1% (E192)

1% (E96)

2% (E48)

5% (E24)

Topology

Single Ended

Differential

Terminate

Output Load

None

Differential

GND Referred

V Referred

Vs pp: 2.000

Vs dc: 0.000

Vin+ 1.000Vpp
0.106Vdc

Vin- 0.042Vpp
0.105Vdc

VoutN -0.999Vpp
2.500Vdc

VoutP 0.999Vpp
2.500Vdc

Actual Gain: 0.999 Vout/Vs

Target Gain: 1.000 Vout/Vs

Power Analysis

$P_{TOTAL} = P_Q + P_{D+Vs} + P_{D-Vs}$

$P_{TOTAL} = 100 + 20 + 0 \text{ mW}$

$P_{TOTAL} = 120 \text{ mW}$

Peak currents: into +Vs = 25.5 mA
from -Vs = 20.0 mA

Differential Output Noise Analysis

Include termination resistors

Ambient Temperature: 25 °C

Max 3dB Bandwidth: 168 MHz

Differential Output Swing: 1.999 Vp-p

Differential Output Noise Components		Differential Output Noise	
Voltage Noise:	14.2 nV/√Hz	Differential Output Noise Density:	15.3 nV/√Hz
Current noise(-):	0.8 nV/√Hz	rms Differential Output Noise:	248.9 uV(rms)
Current noise(+):	0.8 nV/√Hz	SNR:	69
Gain Resistors:	4.6 nV/√Hz		
Feedback Resistors:	3.4 nV/√Hz		
Vocm Noise:	0.0 nV/√Hz		

Output Noise Mean Square Contribution

- 85% Diff V Noise
- <1% I noise(-)
- <1% I noise(+)
- 9% Both Rg & RT
- 5% Both Rf
- <1% Vocm

Instructions

CTRL Z: To Turn Input Tracking ON

CTRL X: To Turn Auto Offset ON

Differential Amplifier Calculator

Differential Amplifier Calculator

Resistor Tolerance

- None (3SF)
- <1% (E192)
- 1% (E96)
- 2% (E48)
- 5% (E24)

Topology

- Single Ended
- Differential

Terminate

Output Load

- None
- Differential
- GND Referred
- V Referred

ANALOG DEVICES

Version 1.0.1

Instructions

$P_{TOTAL} = P_o + P_{D+Vs} + P_{D-Vs}$
 $P_{TOTAL} = 100 + 20 + 0 \text{ mW}$
 $P_{TOTAL} = 120 \text{ mW}$

Peak currents: into +Vs = 25.5 mA
 from -Vs = 20.0 mA

Differential Output Noise Analysis

Include termination resistors

Max 3dB Bandwidth: 168 MHz

Ambient Temperature: 25 °C

Differential Output Swing: 1.999 Vp-p

Differential Output Noise Components		Differential Output Noise	
Voltage Noise:	14.2 nV/√Hz	Differential Output Noise Density:	15.3 nV/√Hz
Current noise(-):	0.8 nV/√Hz	rms Differential Output Noise:	248.9 uV(rms)
Current noise(+):	0.8 nV/√Hz	SNR:	69
Gain Resistors:	4.6 nV/√Hz		
Feedback Resistors:	3.4 nV/√Hz		
Vocm Noise:	0.0 nV/√Hz		

Output Noise Mean Square Contribution

- 85% Diff V Noise
- <1% I noise(-)
- <1% I noise(+)
- 9% Both Rg & RT
- 5% Both Rf
- <1% Vocm

Differential Amplifier Calculator

Differential Amplifier Calculator
ANALOG DEVICES
Version 1.0.1

Resistor Tolerance

None (3SF)

<1% (E192)

1% (E96)

2% (E48)

5% (E24)

Topology

Single Ended

Differential

Terminate

Output Load

None

Differential

GND Referred

V Referred

Rs

50

Vin+

Rg

200

Rf

417

+Vs

5.00

Amplifier Data

Part #	Supply Range		Input Range				Output Range		Speed		Input Noise			
	(+Vs)-(-Vs)		Vp,Vn	Vocm	Vp,Vn	Vocm	VoutP, VoutN	-3 dB BW	Slew Rate	V	Vocm	I		
	Max	Min	(+Vs)	-	(-Vs)	+	(+Vs) - (-Vs) +	MHz	V/us	nV/√Hz	μA/√Hz			
AD8132	11	2.7	12	2	1.4	0.3	1.4	1.4	1.4	360	1200	8	12	1.8
AD8137	12	2.7	3.2	1	1	1	1	0.5	0.5	75	375	8.25	18	1
AD8138	11	2.8	20	1.6	1.2	0.3	1.2	1.1	1.1	320	1150	5	17	2
AD8139	12	4.5	24.5	1	1.2	1	1.2	0.2	0.2	410	800	2.25	3.5	2.1
ADA4927	11	4.5	20	1.5	1.5	1.5	1.5	1.2	1.2	2300	5000	1.4	15	14
ADA4932	11	3	9.6	1.8	1.2	0.2	1.2	1.2	1.2	560	2800	3.6	9.6	1
ADA4937	5.25	3	39.5	2	1.2	0.3	1.2	0.9	0.9	1900	6000	2.2	7.5	4
ADA4938	11	4.5	37	1.6	1.3	0.3	1.3	1.2	1.2	1000	4700	2.6	7.5	4.8
ADA4939	5.25	3	36.5	1.1	1.3	1.1	1.5	0.9	0.9	1400	6800	2.3	7.5	6
TestPart	12	2.5	1	0.1	0.1	0.1	0.1	0.1	0.1	10000	10000	1	1	1

Instructions

CTRL Z: To Turn Input Tracking ON

CTRL X: To Turn Auto Offset ON

Differential Output Noise Analysis

Include termination resistors

Ambient Temperature: 25 °C

Max 3dB Bandwidth: 487 MHz

Differential Output Swing: 0.999 Vp-p

Differential Output Noise Components		Differential Output Noise	
Voltage Noise:	7.4 nV/√Hz	Differential Output Noise Density:	9.7 nV/√Hz
Current noise(-):	2.0 nV/√Hz	rms Differential Output Noise:	269.3 uV(rms)
Current noise(+):	2.0 nV/√Hz	SNR:	62
Gain Resistors:	4.6 nV/√Hz		
Feedback Resistors:	3.4 nV/√Hz		
Vocm Noise:	0.0 nV/√Hz		

Output Noise Mean Square Contribution

- 57% Diff V Noise
- 4% I noise(-)
- 4% I noise(+)
- 22% Both Rg & RT
- 12% Both Rf
- <1% Vocm

Power Calculations:

$P_{TOTAL} = P_0 + P_{D+Vs} + P_{D-Vs}$

$P_{TOTAL} = 370 + 20 + 0 \text{ mW}$

$P_{TOTAL} = 390 \text{ mW}$

Peak currents: into +Vs = 41.7 mA, from -Vs = 37.0 mA

Differential Amplifier Calculator

Differential Amplifier Calculator
Beta V8.0
International Edition

Version 1. 1. 0

Resistor Tolerance

None (3SF)

<1% (E192)

1% (E96)

2% (E48)

5% (E24)

Topology

Single Ended

Differential

Terminate

Output Load

None

Differential

GND Referred

V Referred

Actual Gain: 2.006 V_{out}/V_s

Target Gain: 2.000 V_{out}/V_s

RLN = 25.0 Ω

RLP = 25.0 Ω

$P_{TOTAL} = P_Q + P_{D+Vs} + P_{D-Vs}$

$P_{TOTAL} = 185 + 516 + 0 \text{ mW}$

$P_{TOTAL} = 701 \text{ mW}$

Peak currents: into +Vs = 159.6 mA
from -Vs = 37.0 mA

Differential Output Noise Analysis

Include termination resistors

Ambient Temperature: 25 $^{\circ}\text{C}$

Max 3dB Bandwidth: 227 MHz

Differential Output Swing: 2.106 Vp-p

Differential Output Noise Components		Differential Output Noise	
Voltage Noise:	11.8 $\text{nV}/\sqrt{\text{Hz}}$	Differential Output Noise Density:	16.6 $\text{nV}/\sqrt{\text{Hz}}$
Current noise(-):	4.0 $\text{nV}/\sqrt{\text{Hz}}$	rms Differential Output Noise:	313.0 $\mu\text{V}(\text{rms})$
Current noise(+):	4.0 $\text{nV}/\sqrt{\text{Hz}}$	SNR:	68
Gain Resistors:	9.0 $\text{nV}/\sqrt{\text{Hz}}$		
Feedback Resistors:	4.8 $\text{nV}/\sqrt{\text{Hz}}$		
Vocm Noise:	0.0 $\text{nV}/\sqrt{\text{Hz}}$		

Output Noise Mean Square Contribution

50%	Diff V Noise
6%	I noise(-)
6%	I noise(+)
29%	Both Rg & RT
8%	Both Rf
<1%	Vocm

Instructions

CTRL Z: To Turn Input Tracking ON

CTRL X: To Turn Auto Offset OFF



New Differential Amplifier Calculator (cont)

Instructions:

Data Entry:

Scrolling:

Scroll left to decrease, right to increase the text box value in 100mV steps for source and supply voltages, by 0.1 for gain, by 1 ohm for the source resistance and by a resistance step for Rg.

Direct Entry into text boxes:

Click at the desired entry point in a white textbox. The textbox turns green and the text to the right of the entry point is highlighted. Alter the value by typing over the highlighted portion.

Automatic Calculations:

Calculations are immediate as the values in the input boxes are entered or as the values are scrolled. No ENTER function.

Resistor Tolerance Choices:

None: Linear progression with a resolution of 1000 steps/decade (3SF).

<1% to 5%: EIA Standard Log progression
24 steps for 5% to 192 steps for <1% resistors per decade.

Rg Adjustment:

Enter the resistor value into the Rg text box when linear resistors are selected. Use the letter "k" for values ≥ 1000 ohms.

Scroll to change Rg in one step increments when a tolerance is selected.

Use the **ALT UP** and **ALT DOWN** keys as an alternate method to change Rg in one step increments in all modes.

Topology Choices:

Single ended: One ac signal source on the non-inverting side of the amplifier and two independent dc sources, one on each input side of the amplifier.

Differential: Two independent ac signal sources, each with its dc source.

CTRL X locks/unlocks the ac source and source offset on the inverting side to those on the non-inverting side.

CTRL Z activates/deactivates the **AUTO OFFSET** function. When activated, the dc source voltages and Vocm are adjusted automatically to maintain maximum dynamic range at the amplifier inputs and outputs.

Gain Adjustment:

Click on the Gain textbox and type in the desired gain into the "Target Gain" box. The "Actual Gain" will depend on the Tolerance setting and will be as close to the Target Gain as allowed by the available resistor values in the selected tolerance.

Use the **UP** and **DOWN** keys as an alternate method to change the gain in 0.1 steps from a minimum value of 0.1 to a maximum value of 20.

Gain is restricted in terminated mode to a minimum value that does not cause Rin to go below Rs.

Keyboard shortcuts:

SHIFT UP/DOWN: Source signal at non-inverting input side in 10mV increments.

CTRL UP/DOWN: Source signal at non-inverting input side in 1mV increments

SHIFT ALT UP/DOWN: Source dc offset at non-inverting input side in 10mV increments.

CTRL ALT UP/DOWN: Source dc offset at non-inverting input side in 1mV increments.

SHIFT CTRL UP/DOWN: Vocm in 10mV increments.

Plots:

While the mouse is inside a plot area, click the LEFT mouse button to zoom in vertically 2X, 5X, 10X, 20X and 100X. Click the RIGHT mouse button to zoom out vertically down to 1X. Each plot zooms independently.

Text Box Color Coding:

White Text boxes: User accessible.
Gray Text Boxes: Not accessible
Green Text Box: Currently being adjusted.
Pink Text Boxes: Warning
Red Text Box: Wrong or incomplete entry.

Warnings:

Warnings related to current conditions are shown on the top center of the form.

Warnings specific to the selected amplifier are shown in the center of the form.

Warnings related to undesirable conditions remain ON until conditions are corrected.

Warnings are shown in pink.

HIDE

ADI DiffAmpCalc™

Differential Amplifier Calculator
ANALOG DEVICES
Version 1.0.1

Resistor Tolerance

None (3SF)

<1% (E192)

1% (E96)

2% (E48)

5% (E24)

Topology

Single Ended

Differential

Terminate

Output Load

None

Differential

GND Referred

V Referred

Instructions

CTRL Z: To Turn Input Tracking ON

CTRL X: To Turn Auto Offset ON

Differential Output Noise Analysis

Include termination resistors

Ambient Temperature: 25 °C

Max 3dB Bandwidth: 168 MHz

Differential Output Swing: 1.999 Vp-p

Differential Output Noise Density: 15.3 nV/√Hz

rms Differential Output Noise: 248.9 uV(rms)

SNR: 69

Output Noise Mean Square Contribution

85% Diff V Noise

<1% I noise(-)

<1% I noise(+)

9% Both Rg & RT

5% Both Rf

<1% Vocm

Actual Gain: 0.999 Vout/Vs
Target Gain: 1.000 Vout/Vs

Power Calculations:
 $P_{TOTAL} = P_O + P_{D+Vs} + P_{D-Vs}$
 $P_{TOTAL} = 100 + 20 + 0 \text{ mW}$
 $P_{TOTAL} = 120 \text{ mW}$
Peak currents: into +Vs = 25.5 mA
from -Vs = 20.0 mA

Differential Amplifier Calculator

- ◆ **Downloadable**
- ◆ **Easy to use**
- ◆ **Fast and intuitive**
- ◆ **Various configurations**
- ◆ **Calculate: Gain, noise, power dissipation, input common mode range, output swing and more**
- ◆ **Test part**
- ◆ **What if scenarios**

FREE Universal Evaluation Boards

KEY BENEFITS

- ◆ Boards are blank, maximizing design flexibility
 - Amplifiers must be ordered separately
- ◆ Optimized for high speed amplifiers
- ◆ User defined circuit configurations
- ◆ EVAL-ADOPAMP-1CPEZ and -1REZ feature INV and NINV configurations on the same board
- ◆ SMA connectors for easy interface to test equipment or other circuits
- ◆ RoHS Compliant
- ◆ Available on ADI web site!
 - Free to customers
 - Order from ADI web site www.analog.com

Note:

Z Indicates lead free

Order Number	Description
EVAL-ADOPAMP-1CPZ	Single CSP
EVAL-ADOPAMP-1KSZ	Single SC70
EVAL-ADOPAMP-1RINZ	Single SO AD8099
EVAL-ADOPAMP-1RNIZ	Single SO AD8099
EVAL-ADOPAMP-1CPZ	LFCSP AD8099
EVAL-ADOPAMP-1CPNZ	LFCSP AD8099
EVAL-ADOPAMP-1CPEZ	LFCSP INV and NINV
EVAL-ADOPAMP-1REZ	SOIC INV and NINV
EVAL-ADOPAMP-1RZ	Single SO
EVAL-ADOPAMP-1RTZ	Single SOT23
EVAL-ADOPAMP-2RZ	Dual SO
EVAL-ADOPAMP-2RJZ	Dual SOT23
EVAL-ADOPAMP-2RM	Dual μ SO
EVAL-ADOPAMP- 3CPZ	LFCSP
EVAL-ADOPAMP- 3RUZ	Triple TSSOP
EVAL-ADOPAMP-4RUZ	Quad TSSOP
EVAL-ADDIFFAMP-1RZ	Single SO
EVAL-ADDIFFAMP-1RMZ	Single MSOP (μ SOIC)
EVAL-ADDIFAMP-1CPZ	Single LFCSP (ADA4937/38-1)
EVAL-ADDIFFAMP-CPZ	Single LFCSP
EVAL-ADDIFAMP-2CPZ	Dual LFCSP (ADA4937/38-2)
EVAL-ADDIFFRX-1RZ	Single SO
EVAL-ADDIFFRX-1RM	Single MSOP (μ SOIC)

Support Collateral High-Speed Amplifiers

◆ Selection Guides

- “High-Speed Amplifiers” Order code: ST06702-2-10/09(L)

◆ Design Tutorials

- <http://www.analog.com/static/imported-files/tutorials/MT-0XX.pdf>
- [MT-032: Ideal Voltage Feedback](#)
- [MT-033: Voltage Feedback Op Amp Gain and Bandwidth](#)
- [MT-049: Op Amp Total Output Noise Calculations for Single-Pole System](#)
- [MT-056: High Speed Voltage Feedback Op Amps](#)
- [MT-060: Choosing Between Voltage Feedback and Current Feedback Op Amps](#)

◆ Circuits From The Lab

- <http://www.analog.com/en/verifiedcircuits/index.html>

◆ Sites of Interest

- Differential Amplifiers: www.analog.com/diffamp
- Active Filter Evaluation Boards: www.analog.com/active-fltr
- Solutions Bulletins: www.analog.com/bulletins

Summary of Differential Amplifiers

- ◆ **Integration**
- ◆ **Output balance**
- ◆ **Independent output Vocm adjustment**
- ◆ **Reduced second harmonic distortion**
- ◆ **Wide output swing on single supply**
- ◆ **High common mode rejection**
- ◆ **Differential Amplifier Calculator**
 - **Simplifies design time**
 - **Lowers risk**
 - **What if scenario's**
- ◆ **Evaluation Boards**



谢谢！

ADI中国地区技术支持热线：4006 100 006

ADI中国地区技术支持信箱：china.support@analog.com

ADI样片申请网址：<http://www.analog.com/zh/sample>

MAKEADIFFERENCE