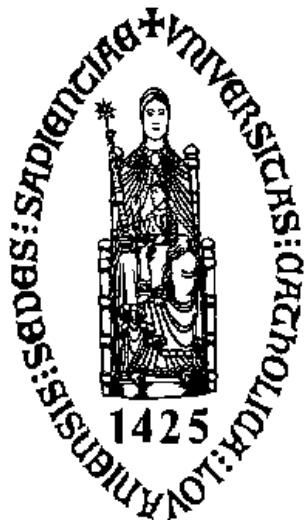

Amplifiers, Source followers & Cascodes



Willy Sansen

**KULeuven, ESAT-MICAS
Leuven, Belgium**

willy.sansen@esat.kuleuven.be



Operational amplifier


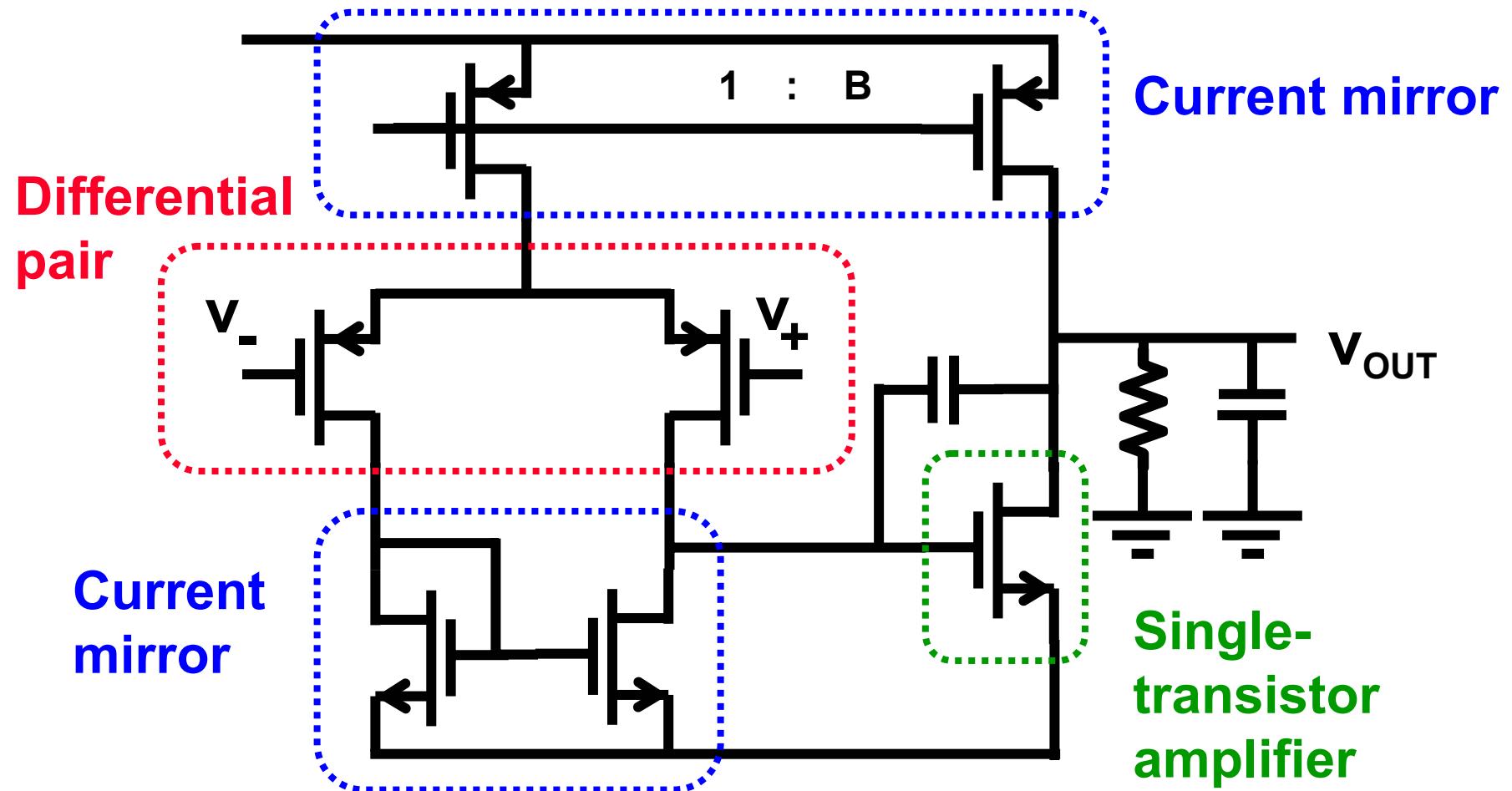


Table of contents

- Single-transistor amplifiers**
- Source followers**
- Cascodes**

Single-transistor amplifier - 1

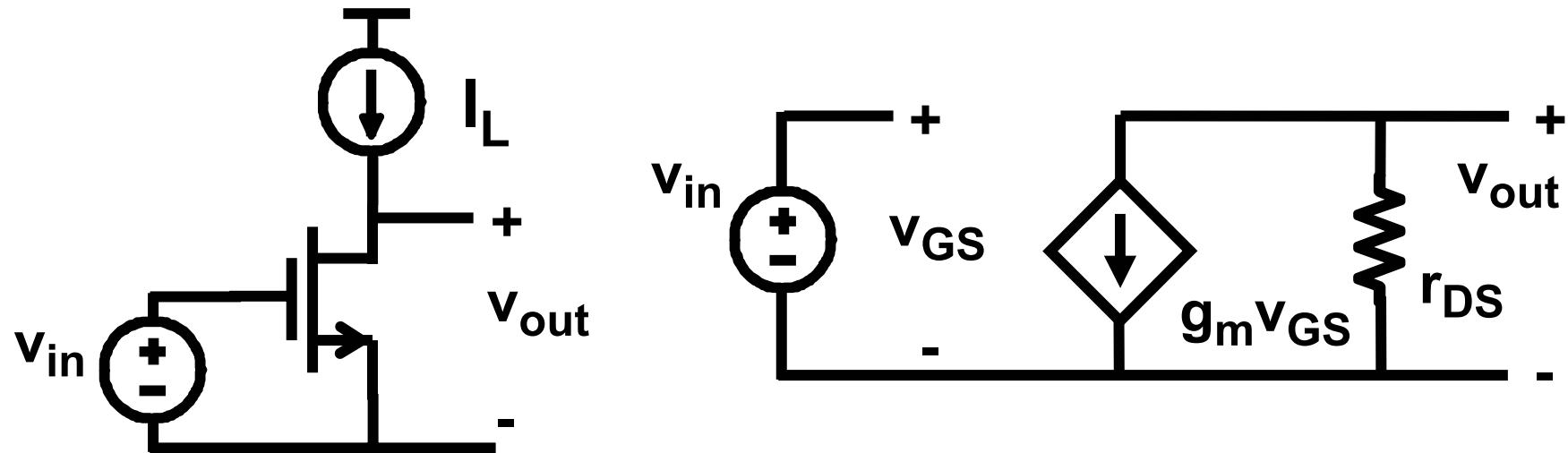

$$A_v = g_m r_{DS} = \frac{2 I_{DS}}{V_{GS} - V_T} \frac{V_E L}{I_{DS}} = \frac{2 V_E L}{V_{GS} - V_T}$$

$$A_v \approx 100 \quad \text{if } V_E L \approx 10 \text{ V and } V_{GS} - V_T \approx 0.2 \text{ V}$$

Single-transistor amplifier - 2

High gain ?

Low $V_{GS} - V_T$ and large L !!!



MOST or bipolar amplifier ?

MOST $A_v = \frac{V_E L}{(V_{GS} - V_T)/2}$

Bipolar $A_v = \frac{V_E}{kT/q}$

$A_v \approx 100$ if $V_E L \approx 10 \text{ V}$ and $V_{GS} - V_T \approx 0.2 \text{ V}$


3 vs 2 stages for 10^6

$A_v \approx 1000$ if $V_E \approx 26 \text{ V}$ since $kT/q = 26 \text{ mV}$





Gain, Bandwidth and Gain-bandwidth

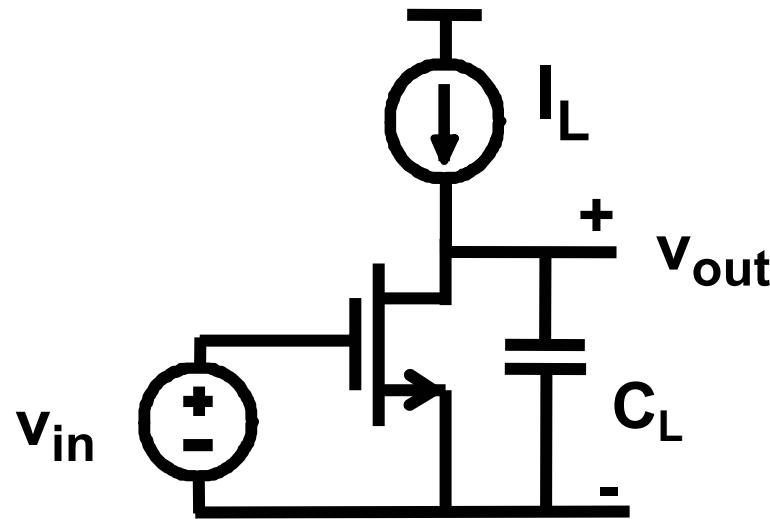


$$A_{v0} = g_m r_{DS}$$

$$BW = \frac{1}{2\pi r_{DS} C_L}$$

$$GBW = \frac{g_m}{2\pi C_L}$$

For all single-stage
Operational amplifiers

Gain A_v , BW and GBW

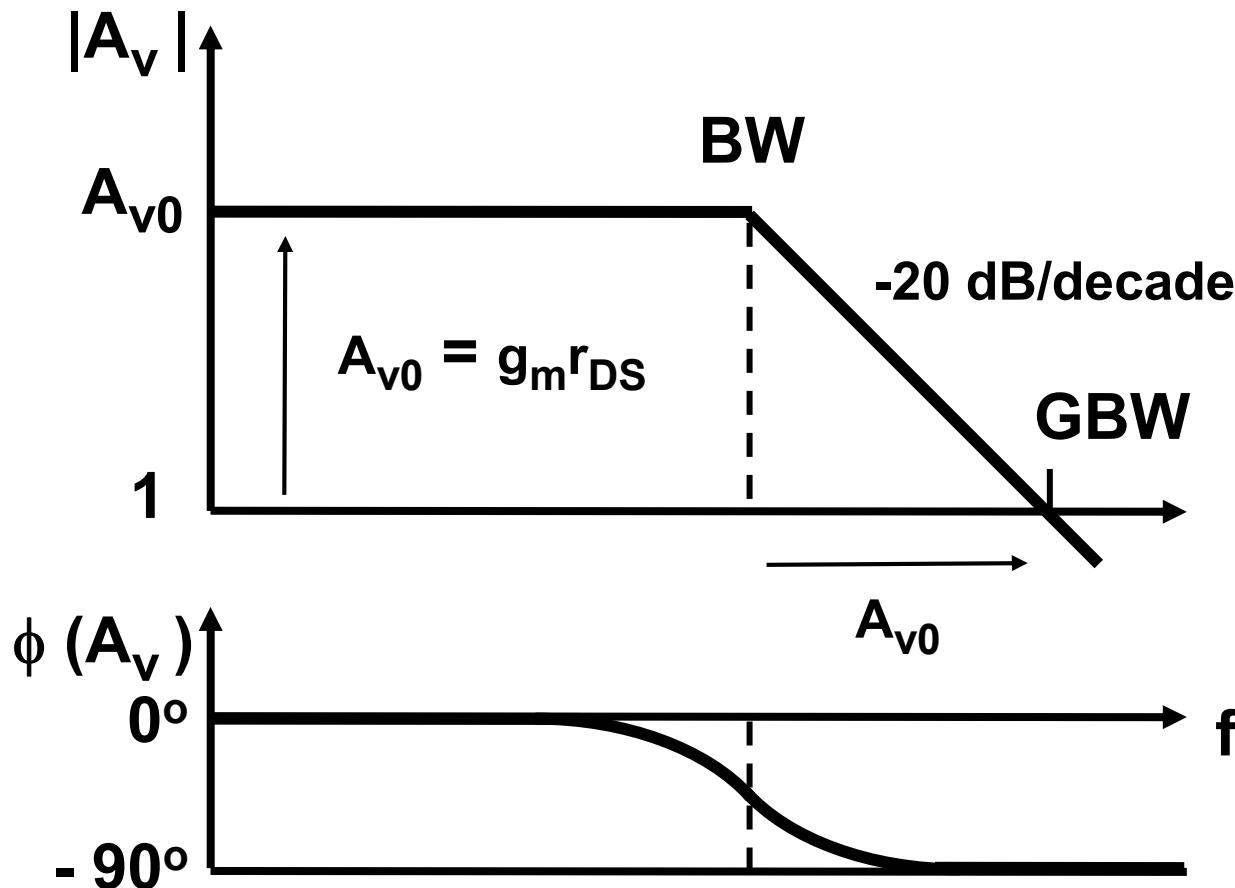

$$\text{GBW} = \frac{g_m}{2\pi C_L}$$

$$\phi(A_v) = -45^\circ \text{ at BW}$$

Single-transistor amplifier : Exercise

GBW = 100 MHz for $C_L = 3 \text{ pF}$


Techno.: $K'_n \approx 50 \mu\text{A/V}^2$

$L_{\min} = 0.5 \mu\text{m}$

$I_{DS} ? \quad L ? \quad W ?$

$\frac{\text{GBW}.C_L}{I_{DS}} ?$

Gain, Bandwidth and Gain-bandwidth

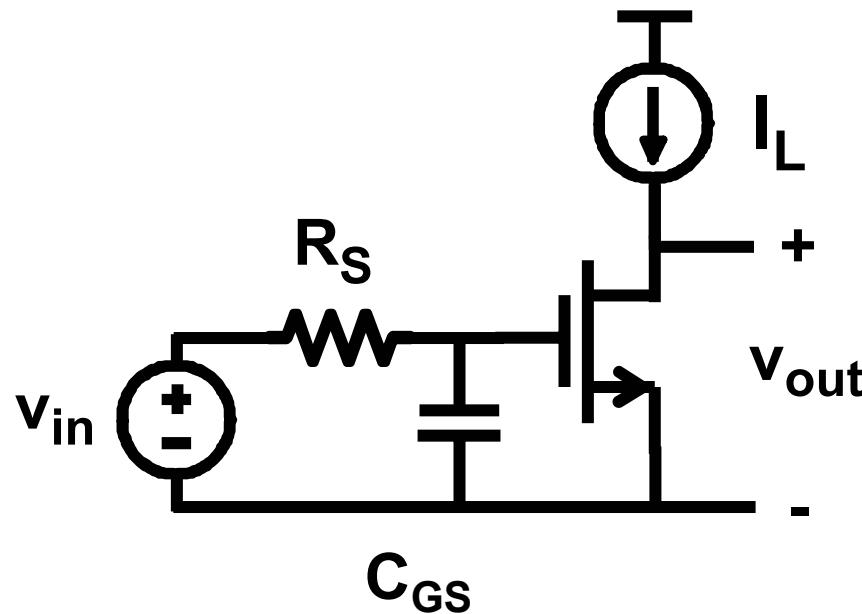


$$A_{v0} = g_m r_{DS}$$

$$BW = \frac{1}{2\pi R_S C_{GS}}$$

$$GBW = \frac{g_m}{2\pi C_{GS}} \frac{r_{DS}}{R_S} = f_T \frac{r_{DS}}{R_S} \sim \frac{1}{WC_{ox}} \frac{1}{V_{GS}-V_T}$$

$W ? \quad L ? \quad V_{GS}-V_T ?$

Gain, Bandwidth and Gain-bandwidth


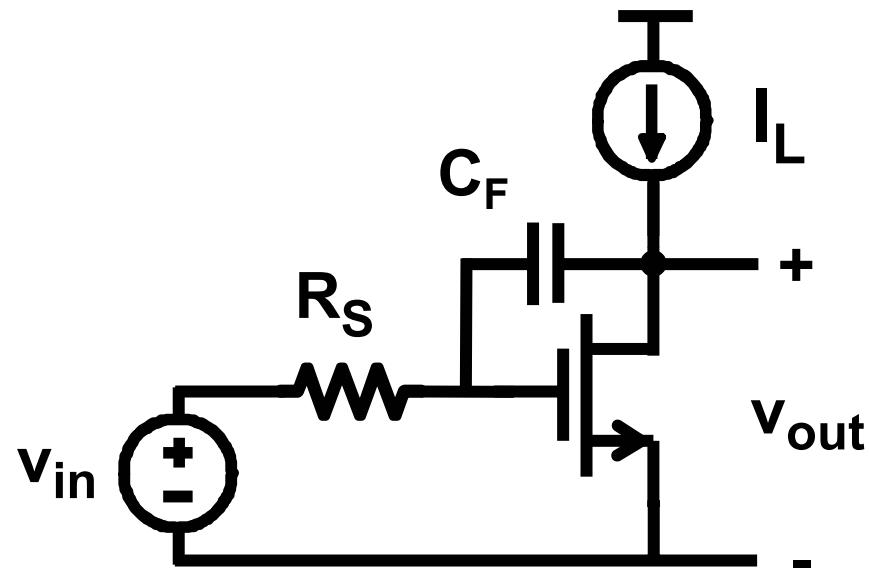


$$A_{v0} = g_m r_{DS}$$

$$BW = \frac{1}{2\pi R_S A_{v0} C_F}$$

$$GBW = \frac{1}{2\pi R_S C_F}$$

Miller effect

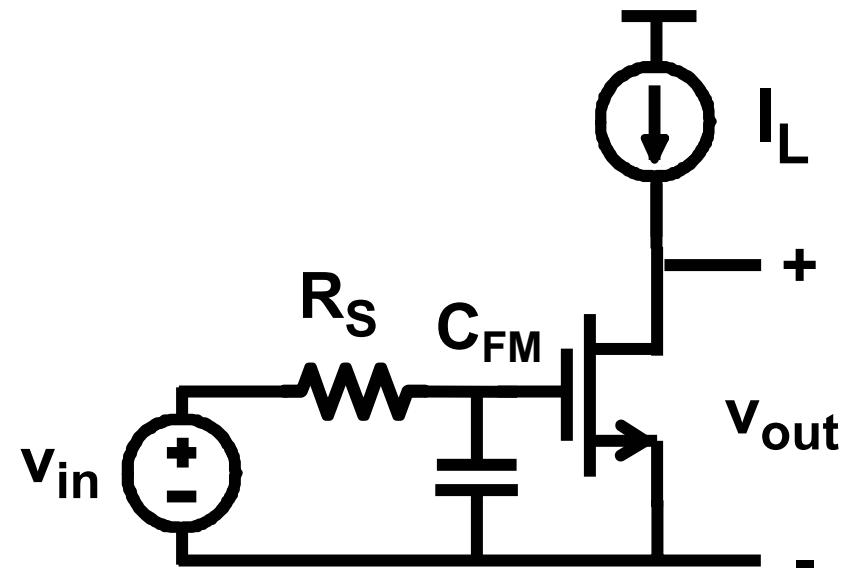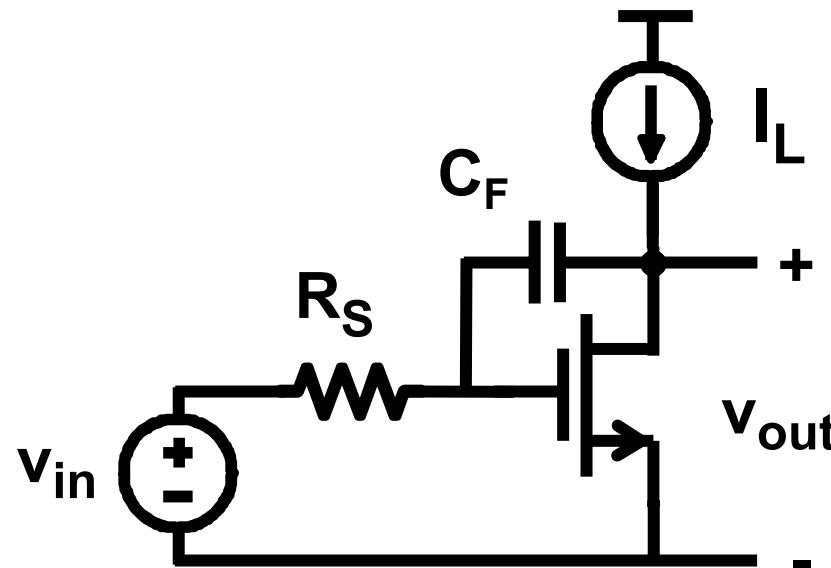


$$A_{v0} = g_m r_{DS}$$


$$C_{FM} = (1 + A_{v0}) C_F$$

Miller, Dependence of the input impedance of a three-electrode vacuum tube upon the load in the plate circuit, Scient. Papers Bur. Standards, 1920, 367-385.

Miller capacitance feedback effects

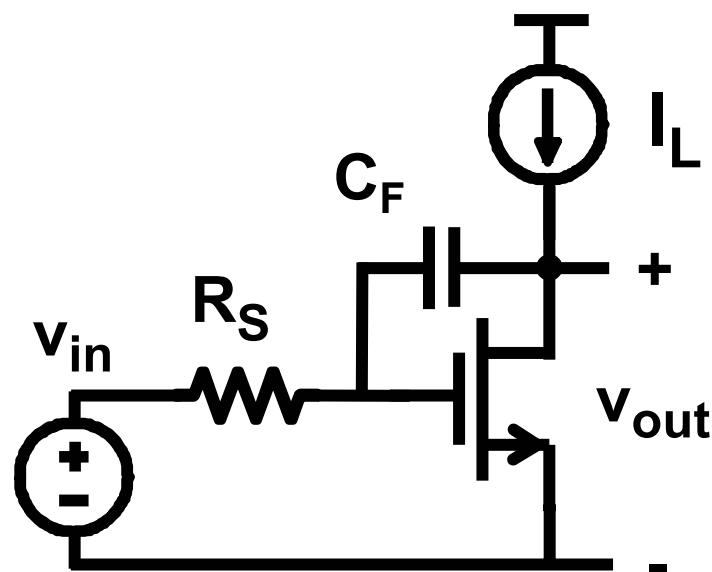


$$f_z = \frac{g_m}{2\pi C_F}$$

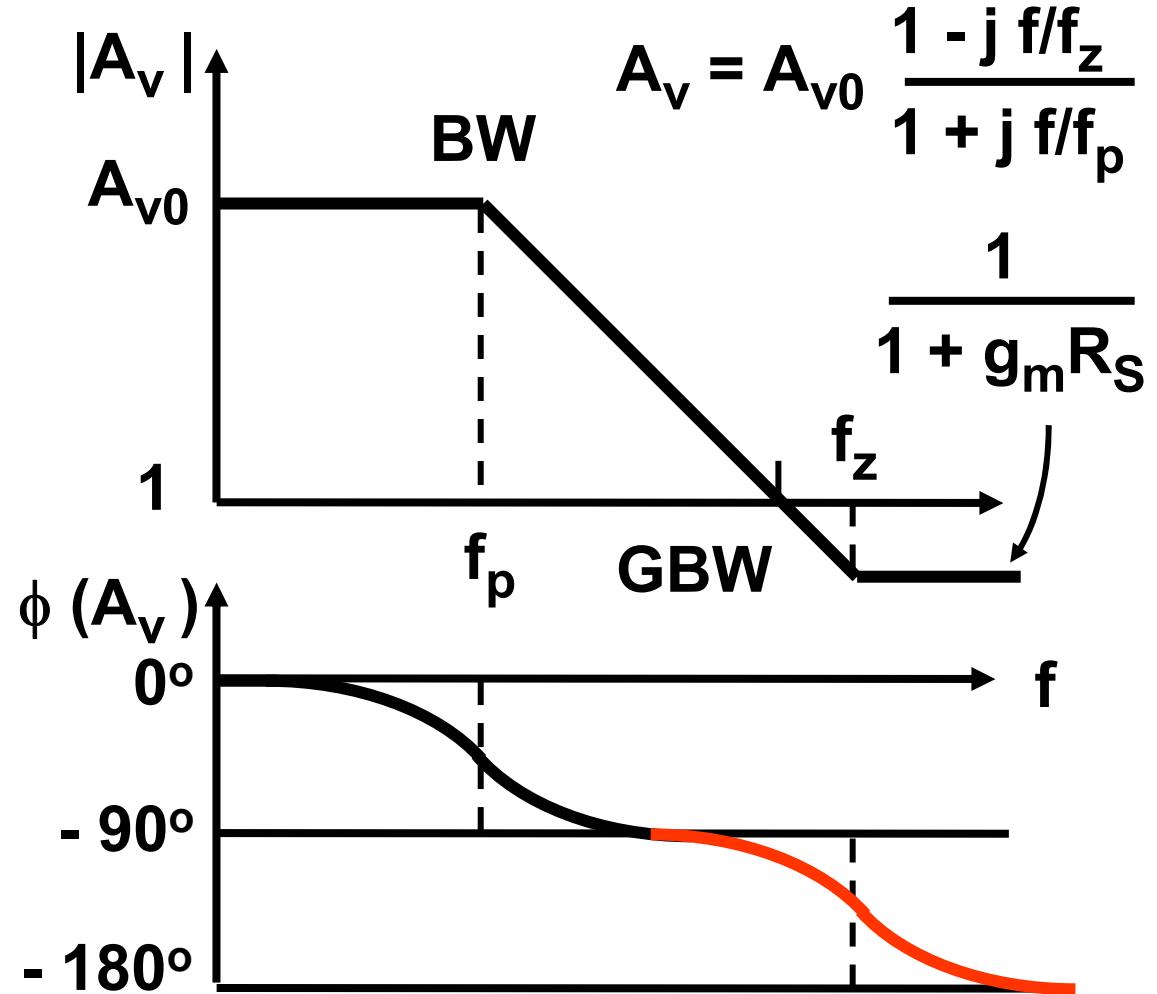

For phase, a positive zero
is like a negative pole !!!

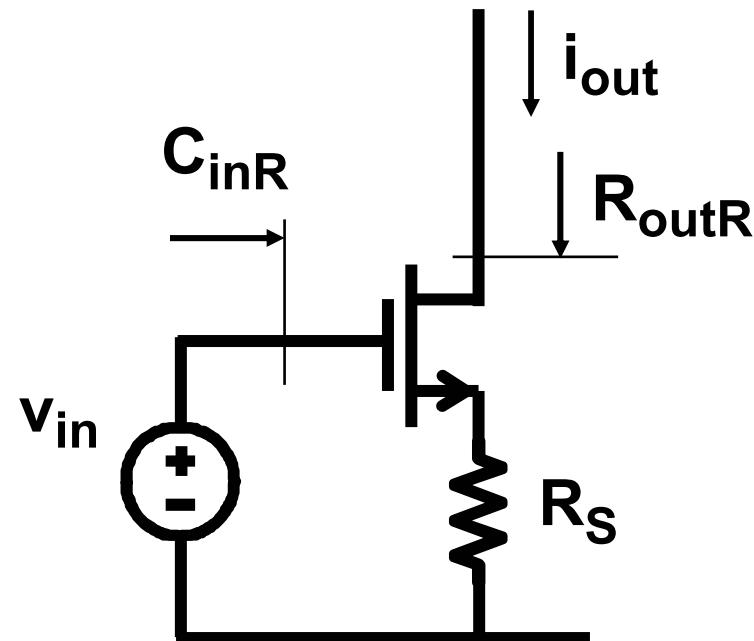Amplifier with local R- (series) feedback



$$g_{mR} = \frac{g_m}{1 + g_m R_s} \sim \frac{1}{R_s}$$


$$\begin{aligned} R_{outR} &= r_{DS} (1 + g_m R_s) \\ &\approx (g_m r_{DS}) R_s \end{aligned}$$

$$C_{inR} = \frac{C_{GS}}{1 + g_m R_s}$$

But R_s gives extra noise !



Amplifier with local L- feedback

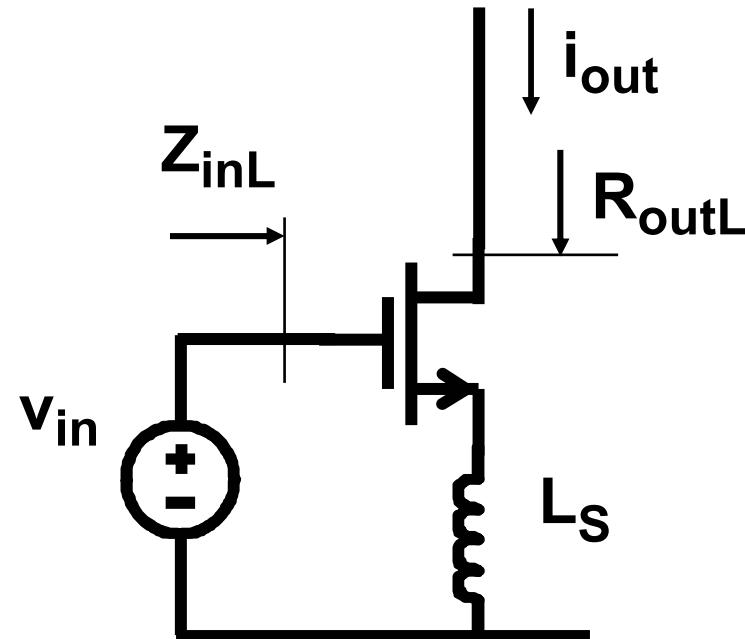

$$g_{mL} = \frac{g_m}{1 + g_m L_s s}$$


$$R_{outL} = r_{DS} (1 + g_m L_s s)$$

$$Z_{inL} = g_m \frac{L_s}{C_{GS}} + \frac{1 + L_s C_{GS} s^2}{s C_{GS}}$$

No extra noise !

$$Z_{inL} = L_s \omega_T + L_s s + \frac{1}{s C_{GS}}$$

Amplifier with local MOST-R- Feedback

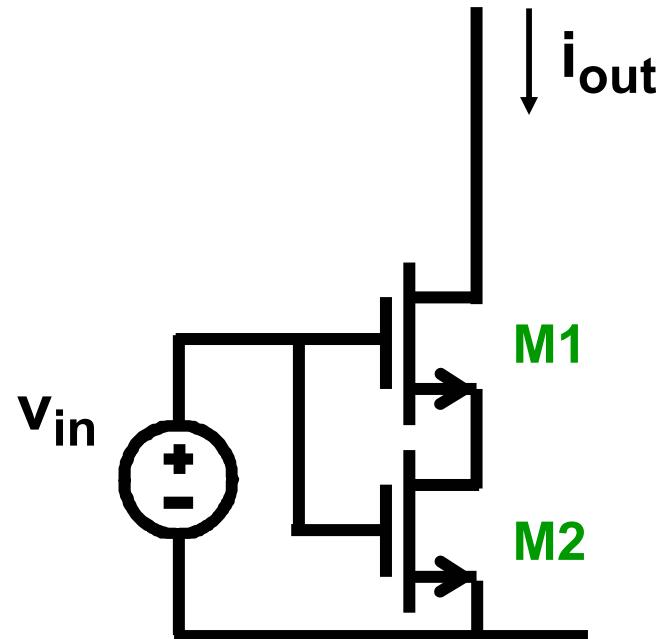


$$V_{DS2} = V_{GS2} - V_{GS1} \approx 0.2 \text{ V}$$

$$r_{DS2} = \frac{1}{K_P W_2 / L_2 (V_{GS2} - V_T)}$$


$$R_{outR} = r_{DS1} (1 + g_m r_{DS2})$$

$$C_{inR} = \frac{C_{GS1} + C_{GS2}}{1 + g_m r_{DS2}}$$



Diode-connected MOST : parallel Feedback

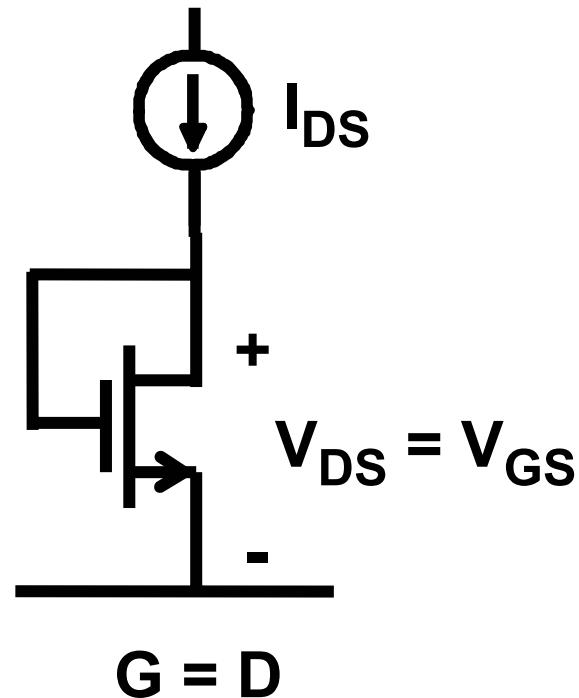
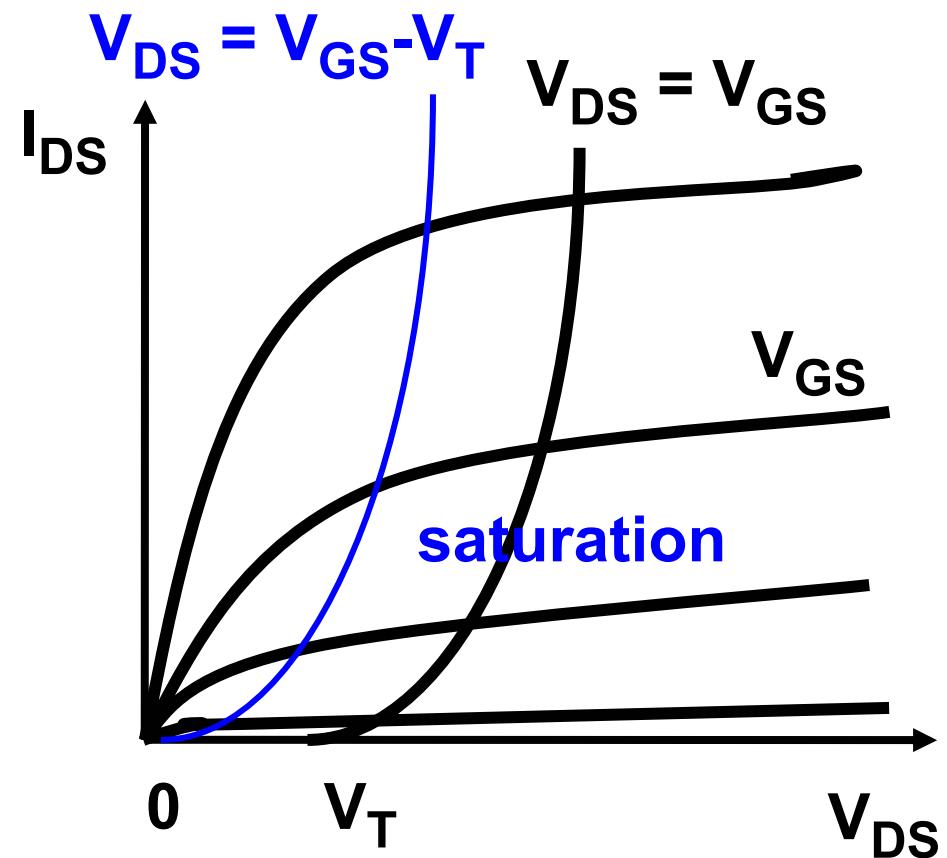
$$I_{DS} = K_n \frac{W}{L} (V_{DS} - V_T)^2$$





Diode-connected MOST: small-signal

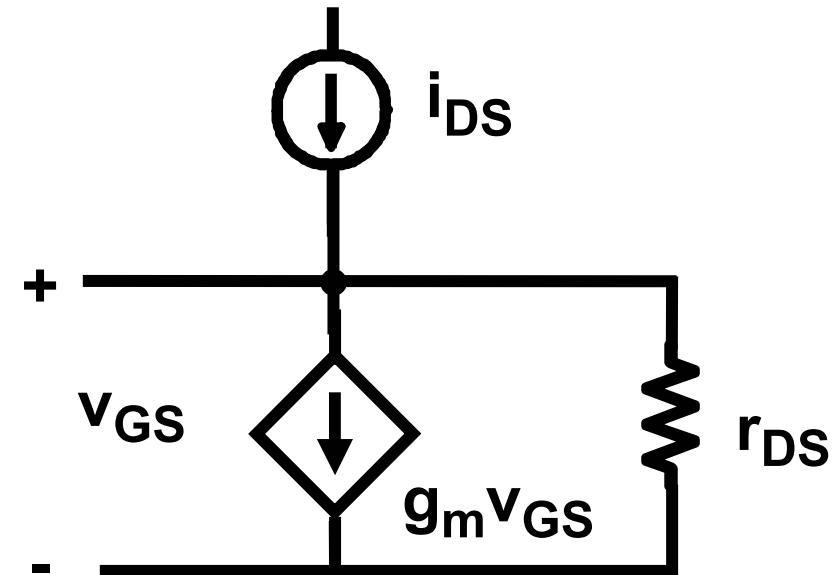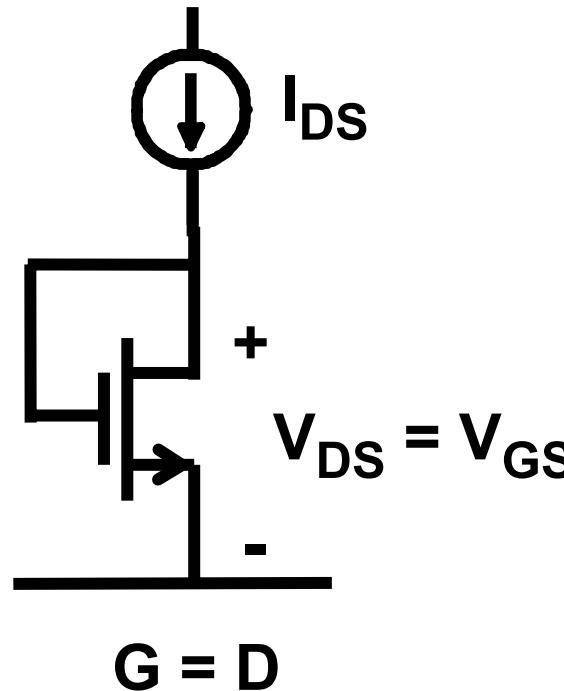


$$r_{ds} = 1/g_m \parallel r_{DS} \approx 1/g_m$$

Diode-connected MOST at high frequencies

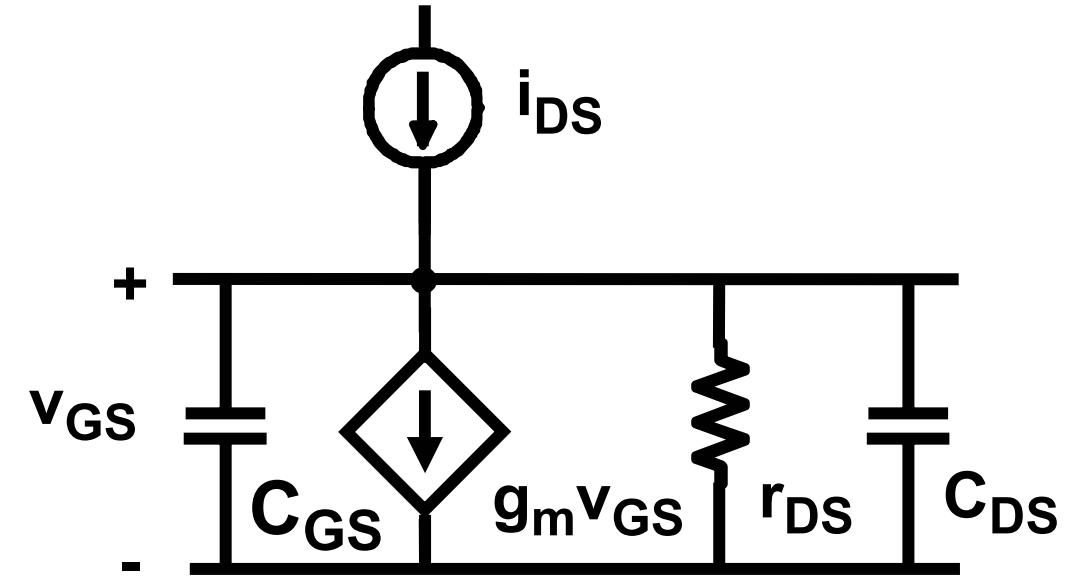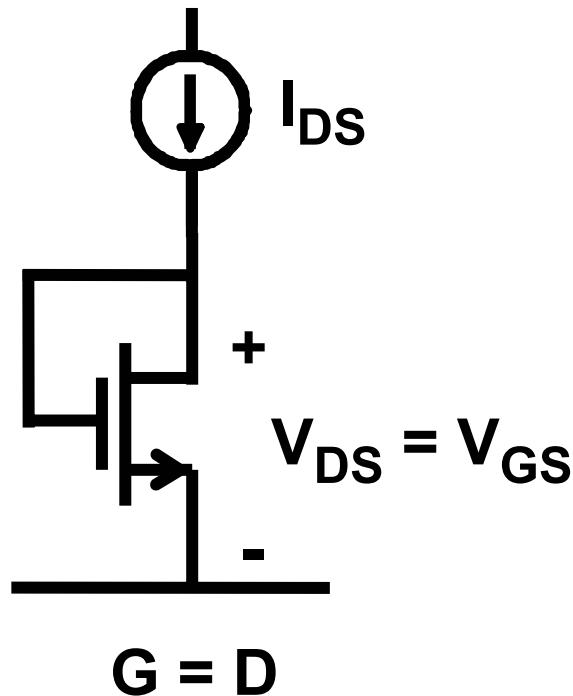

$$BW = \frac{g_m}{2\pi (C_{GS} + C_{DS})} \approx \frac{f_T}{2}$$

Wideband amplifier

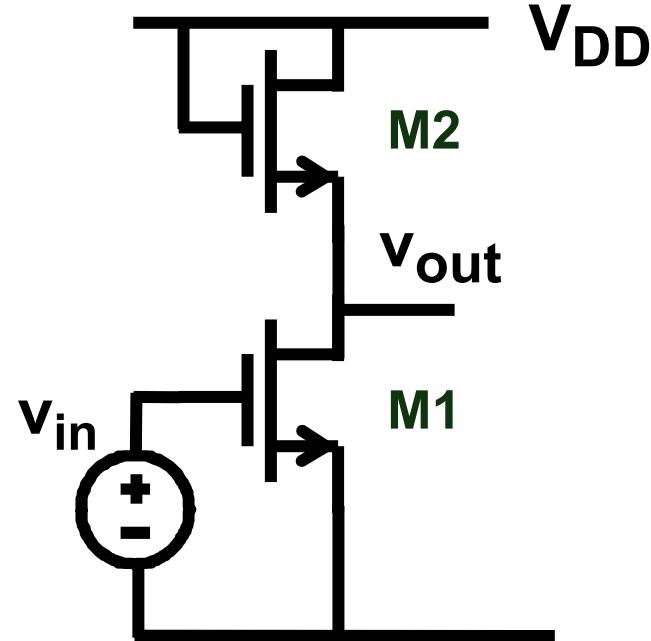


$$V_{OUT} = V_{DD} - V_{GS2}(V_{OUT})$$

$$A_{v0} = \frac{g_{m1}}{g_{m2}} = \sqrt{\frac{(W/L)_1}{(W/L)_2}} = \frac{V_{GS2} - V_T}{V_{GS1} - V_T}$$

$$R_{OUT} = 1/g_{m2}$$

Linear wideband amplifier

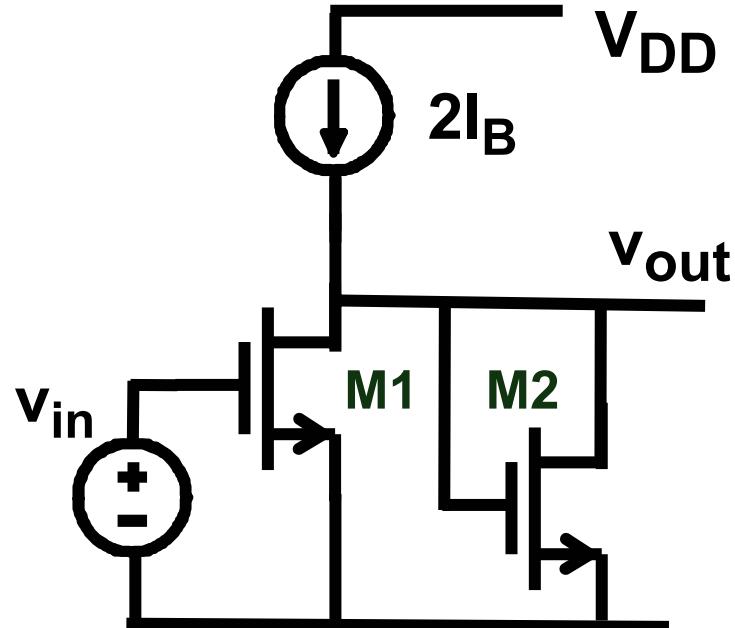

$$V_{OUT} = V_{GS2}$$

$$A_{v0} = \frac{g_{m1}}{g_{m2}} = \sqrt{\frac{(W/L)_1}{(W/L)_2}} = \frac{V_{GS2} - V_T}{V_{GS1} - V_T}$$

$$R_{OUT} = 1/g_{m2}$$

Current mirror with only nMOSes


Same V_{OUTDC} as V_{INDC}

No body bias effect

Good PSRR

Double power consumption

Wideband amplifiers

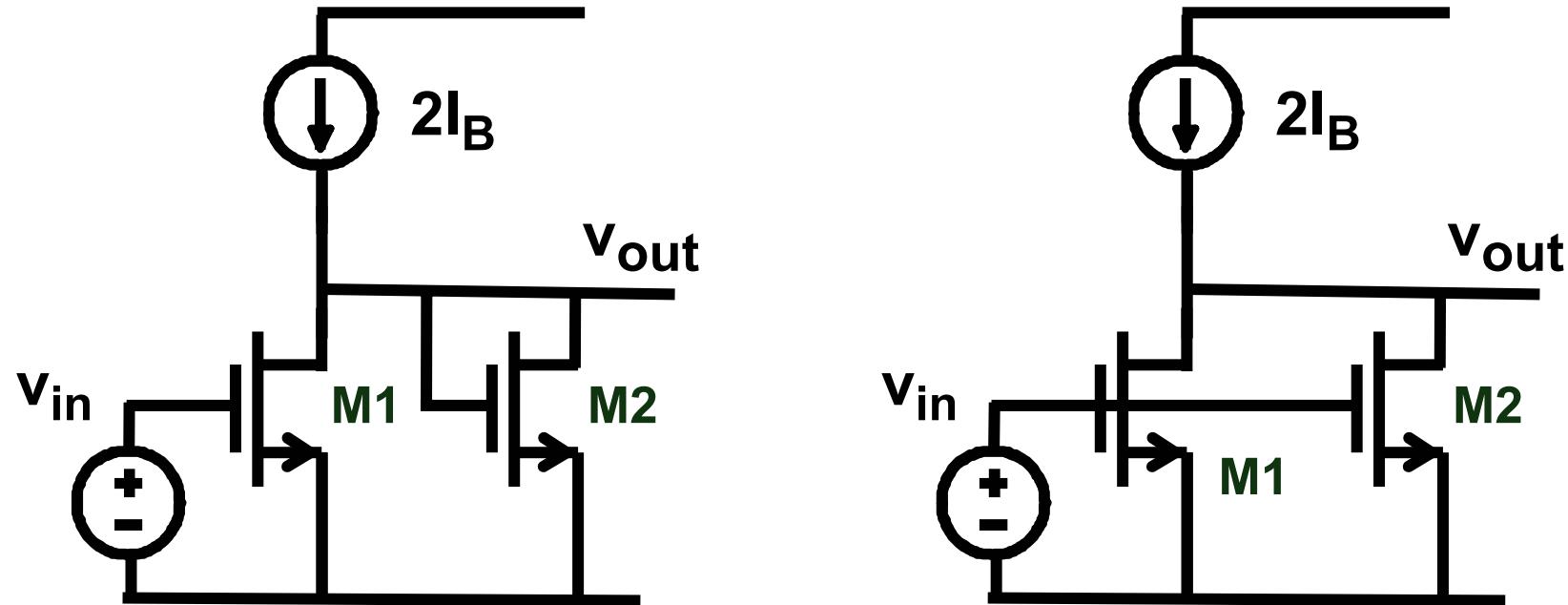


$$A_{v0} = \frac{g_{m1}}{g_{m2}} = \sqrt{\frac{(W/L)_1}{(W/L)_2}} = \frac{V_{GS2} - V_T}{V_{GS1} - V_T}$$

$$R_{out} = 1/g_{m2}$$

$$A_{v0} = g_m R_{out}$$


$$R_{out} = r_{DS1} // r_{DS2}$$

Class A versus class AB amplifier

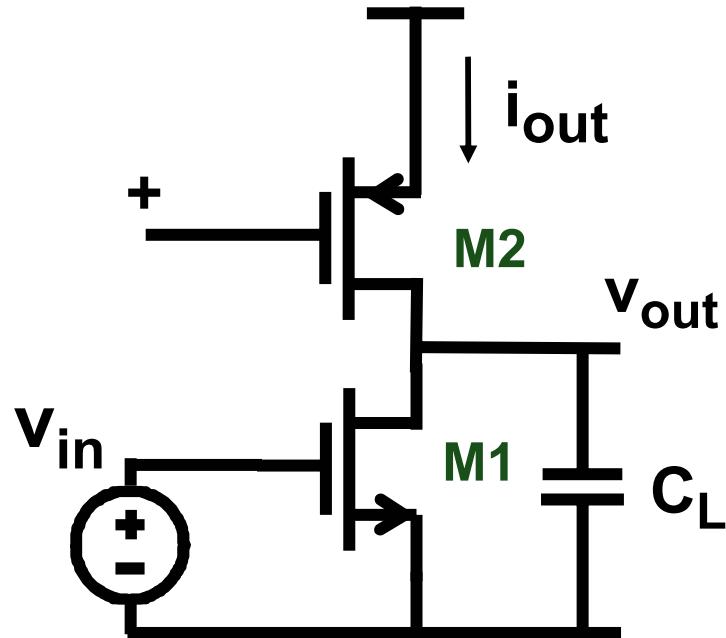

$$v_{out} = A_v v_{in}$$


Class A stage

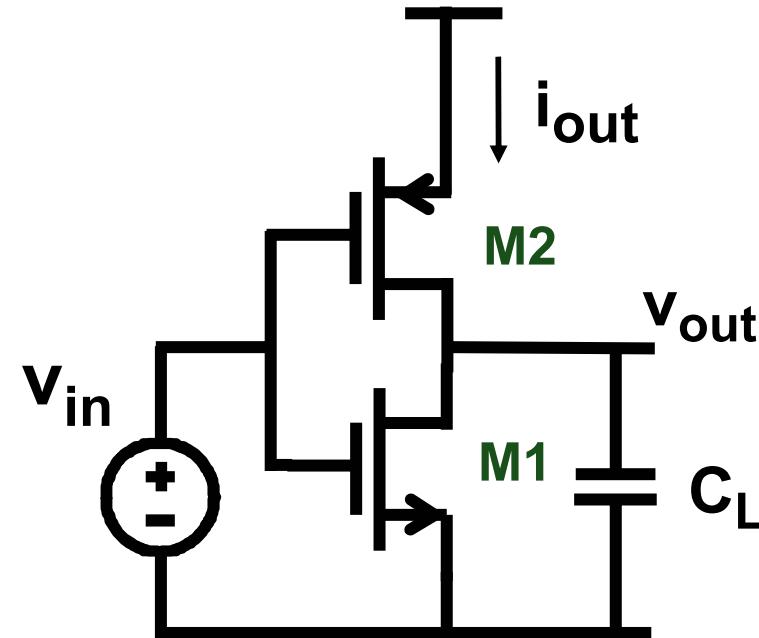


$$v_{out} = A_v v_{in}$$

Class AB stage

CMOS inverter-amplifier


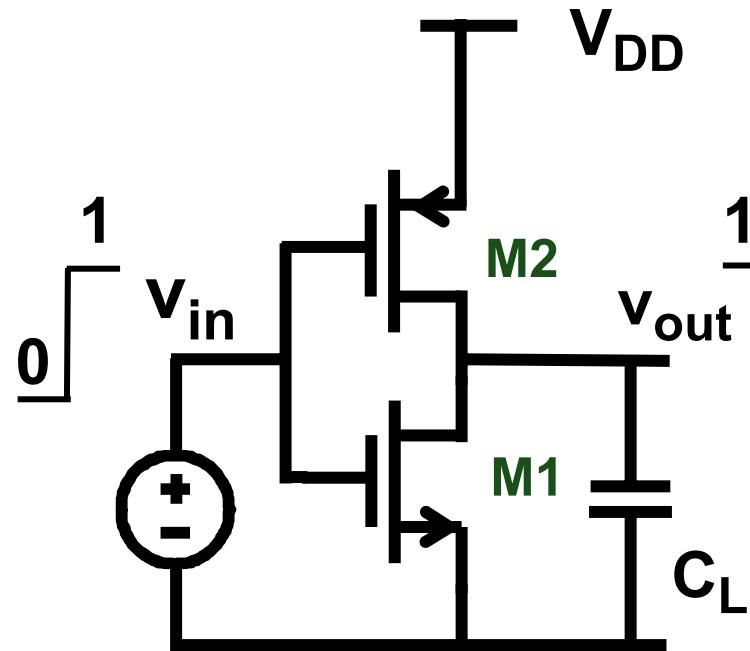


Digital inverter

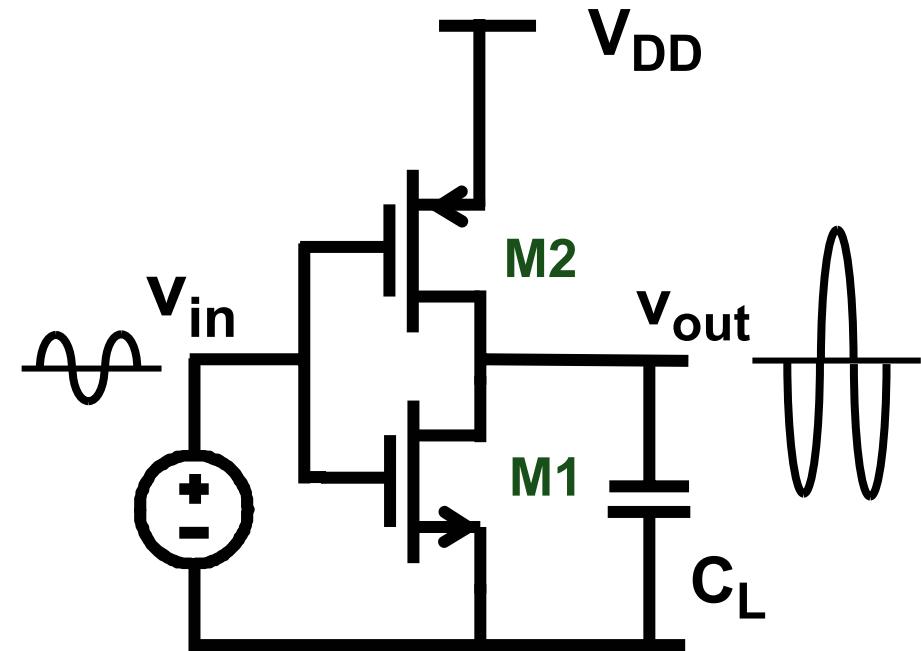

Analog amplifier

Operating points nMOST & pMOST

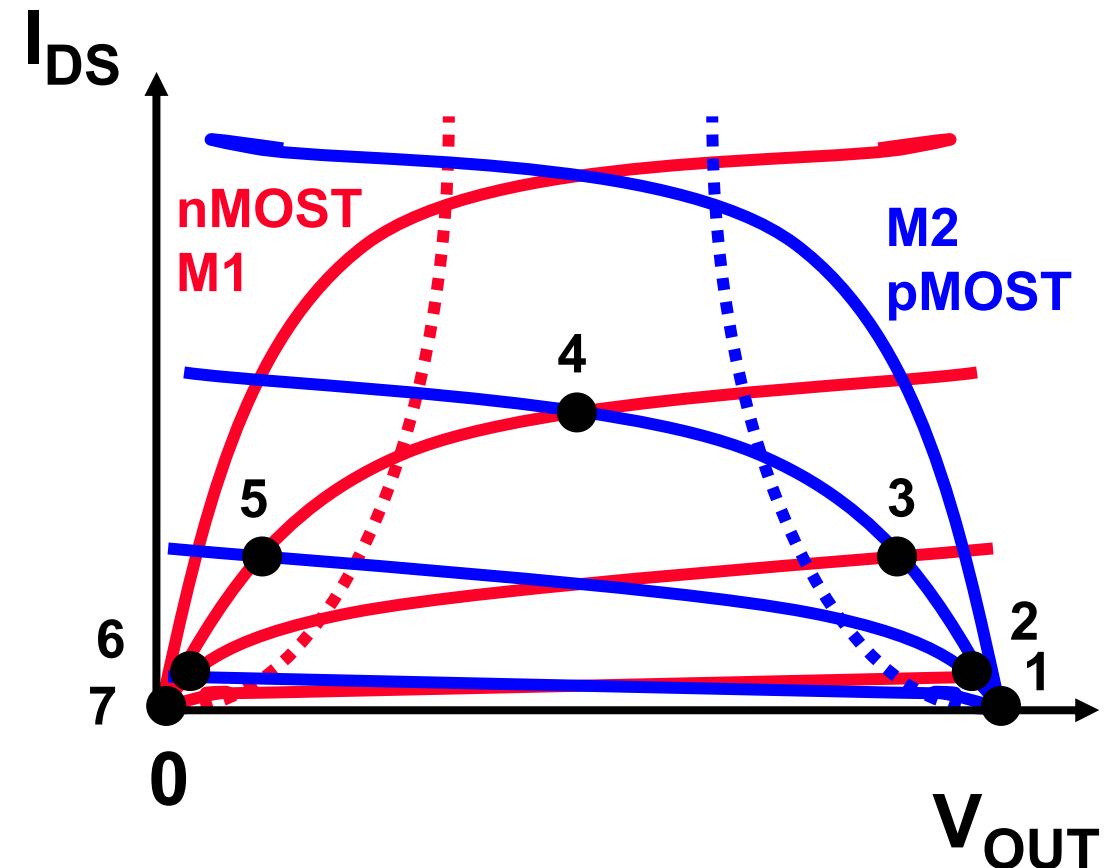
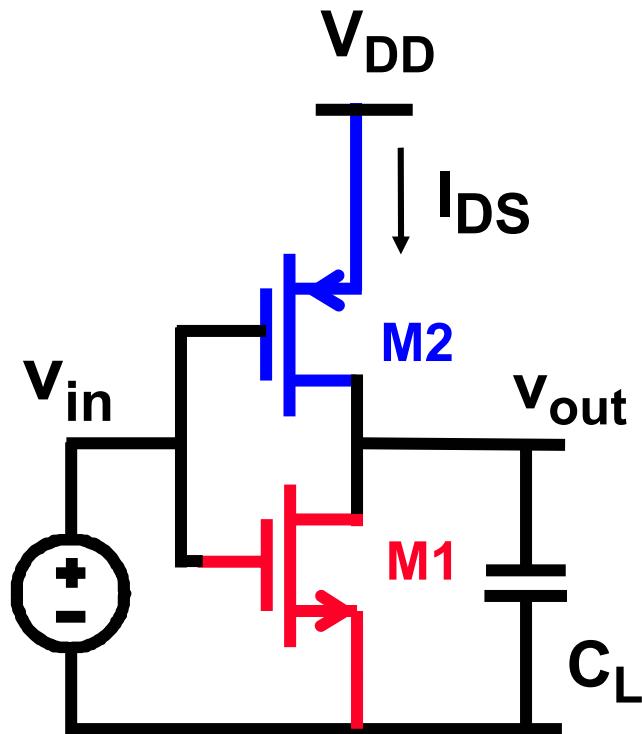


$$\begin{aligned}V_{DD} &= V_{DSn} + V_{DSP} \\&= V_{GSn} + V_{GSp}\end{aligned}$$


$$\begin{aligned}V_{DSn} &= V_{OUT} \\V_{GSn} &= V_{IN}\end{aligned}$$

$$\begin{aligned}V_{DSP} &= V_{DD} - V_{OUT} \\V_{GSp} &= V_{DD} - V_{IN}\end{aligned}$$

Transfer characteristic

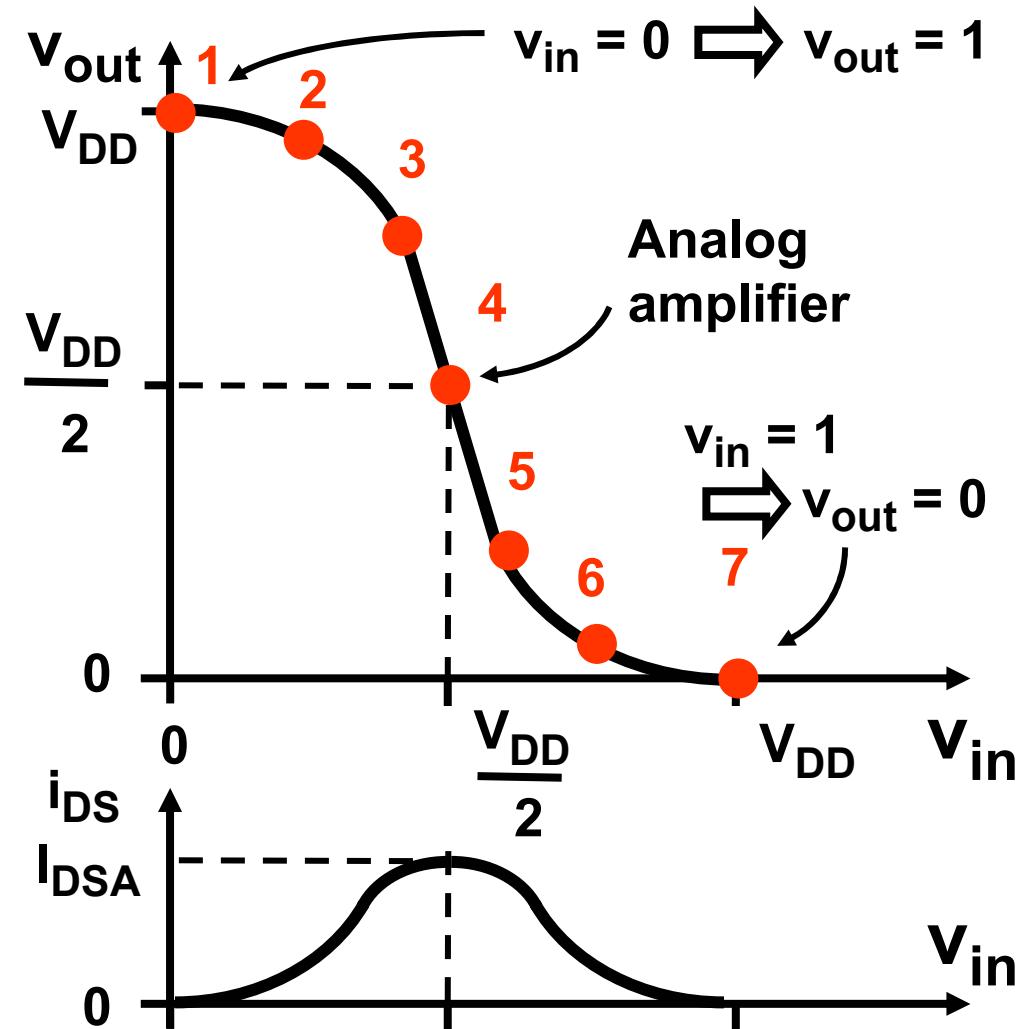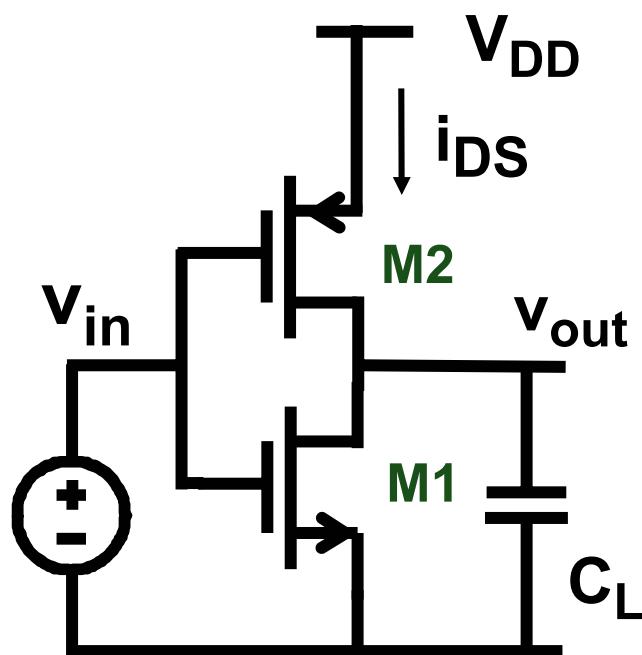

Analog amplifier : DC

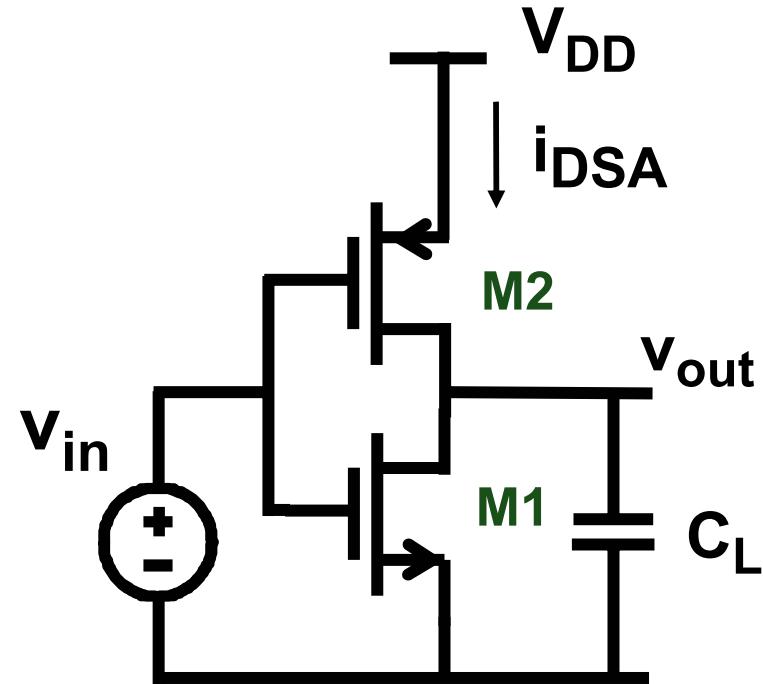

$$v_{in} = \frac{V_{DD}}{2} \rightarrow v_{out} = \frac{V_{DD}}{2}$$


$$I_{DSn} = K'_n \frac{W_n}{L_n} (V_{in} - V_T)^2$$

$$I_{DSP} = K'_p \frac{W_p}{L_p} (V_{DD} - V_{in} - V_T)^2$$

$$\rightarrow K'_n \frac{W_n}{L_n} = K'_p \frac{W_p}{L_p}$$


$$I_{DS} = K'_n \frac{W_n}{L_n} \left(\frac{V_{DD}}{2} - V_T \right)^2$$

Analog amplifier : AC model

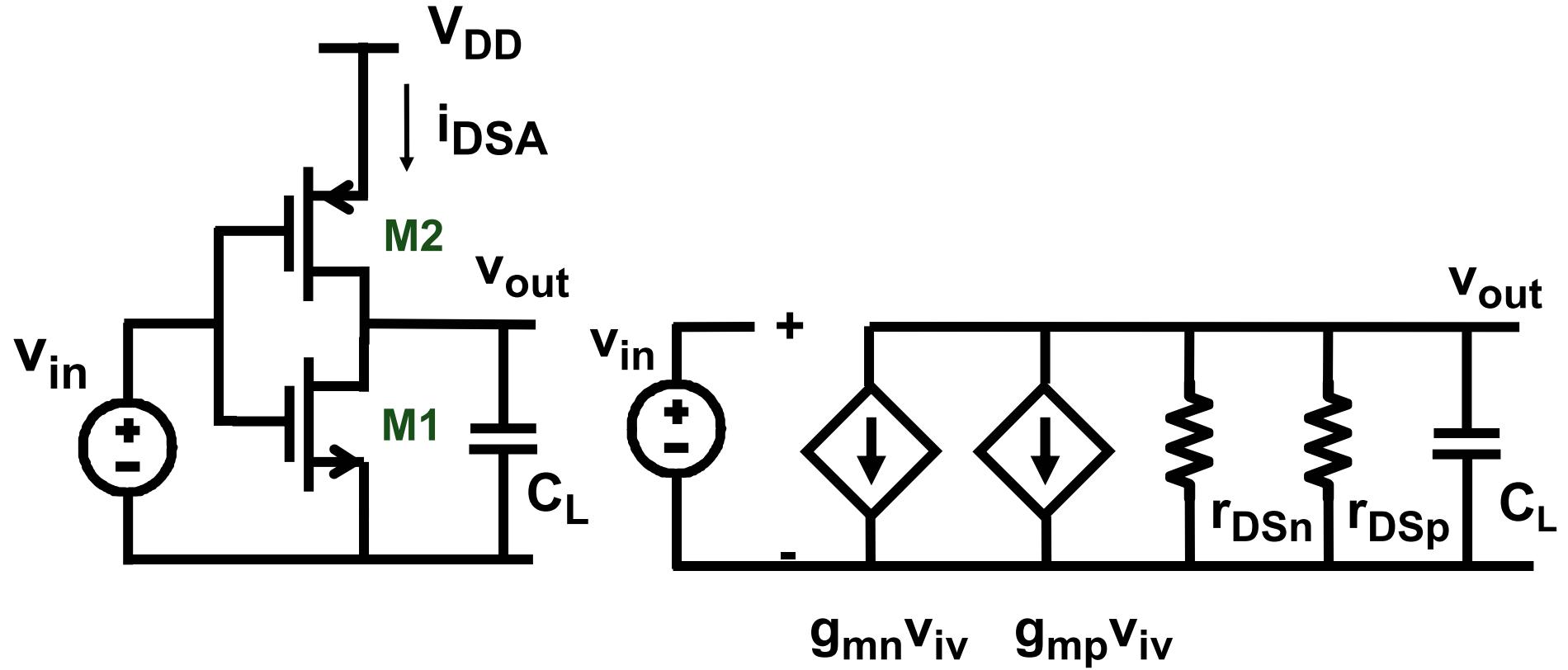

For the same I_{DS} en V_{GS}-V_T: g_{mn} = g_{mp} = g_m

Analog amplifier: AC gain A_v

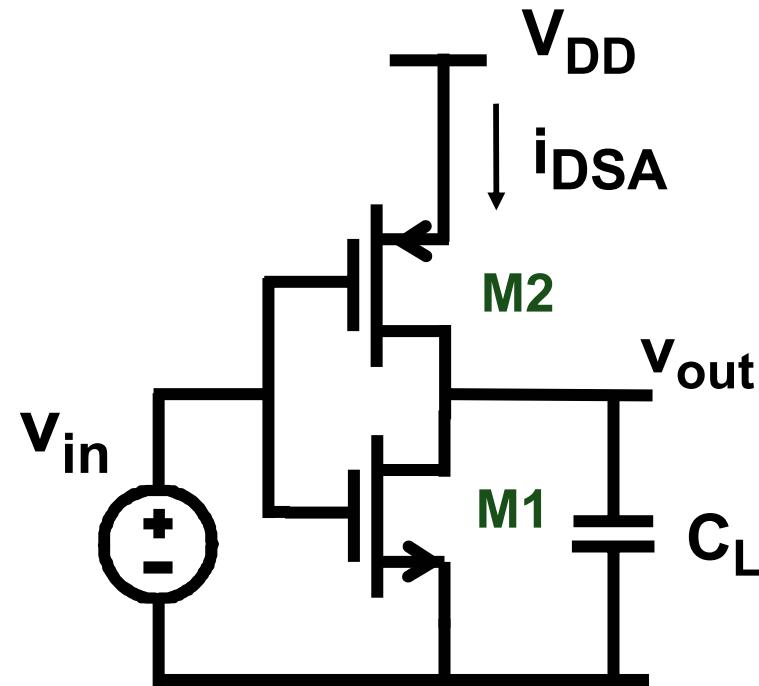


If $V_{En}L_n = V_{Ep}L_p = V_E$

$$g_{DSn} = g_{DSP} = g_{DS}$$

$$(g_{DS} = 1/r_{DS})$$

$$A_{v0} = - \frac{2g_m}{2g_{DS}} = - \frac{2V_E}{\frac{V_{DD}}{2} - V_T}$$

Analog amplifier : BW & GBW

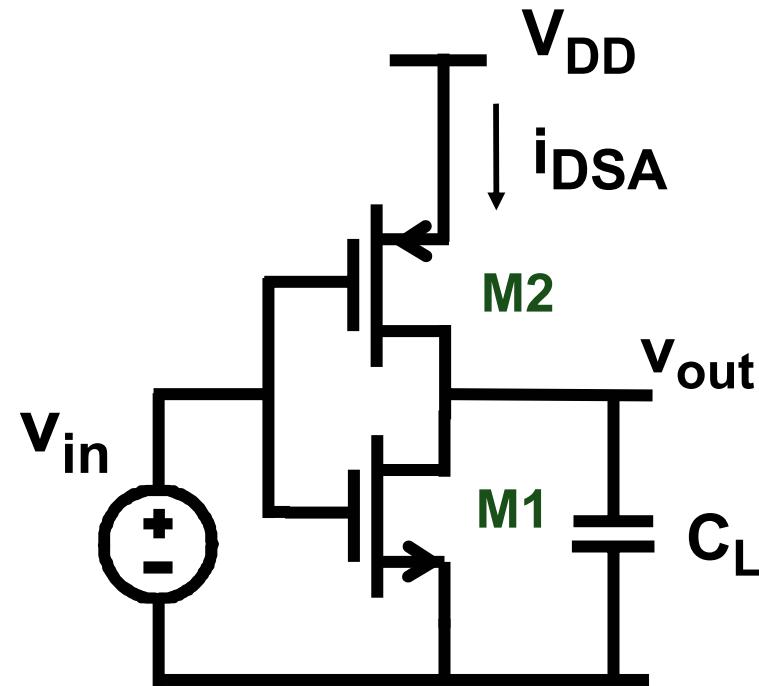


$$A_{v0} = 2g_m R_{out}$$

$$R_{out} = \frac{r_{DS}}{2}$$

$$BW = \frac{1}{2\pi R_{out} C_L}$$

$$GBW = \frac{2g_m}{2\pi C_L}$$

Analog amplifier: poles due to CGS

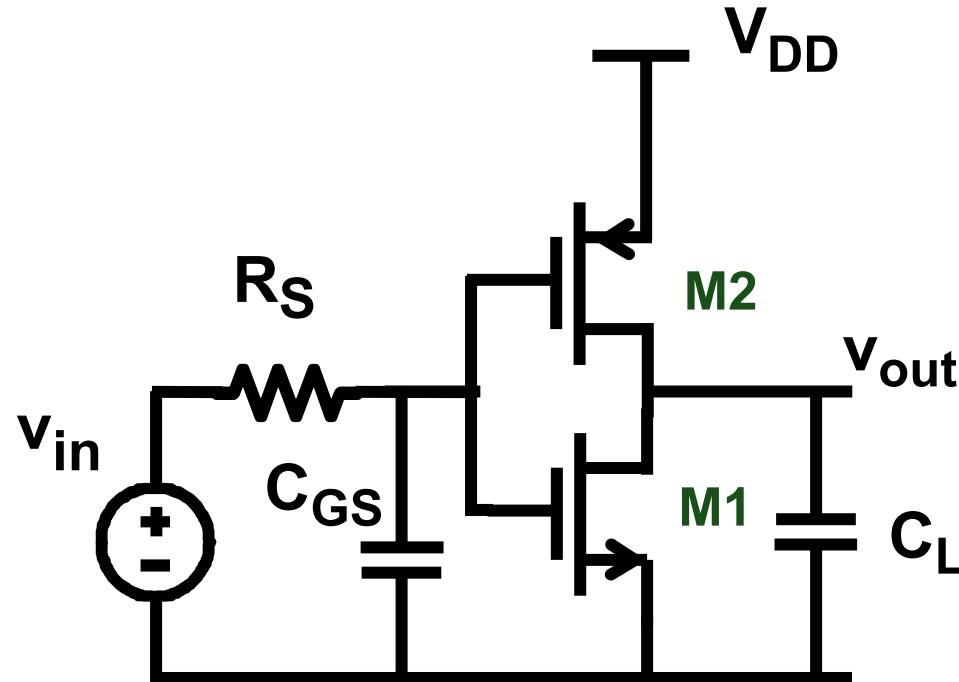

$$A_{v0} = 2g_m R_{out}$$


$$GBW = \frac{2g_m}{2\pi C_L}$$

$$C_{GST} = C_{GS1} + C_{GS2}$$


But if $R_S C_{GST} > r_{DS} C_L$:

$$GBW = f_T \frac{r_{DS}}{R_S}$$

Analog amplifier: poles due to CDG

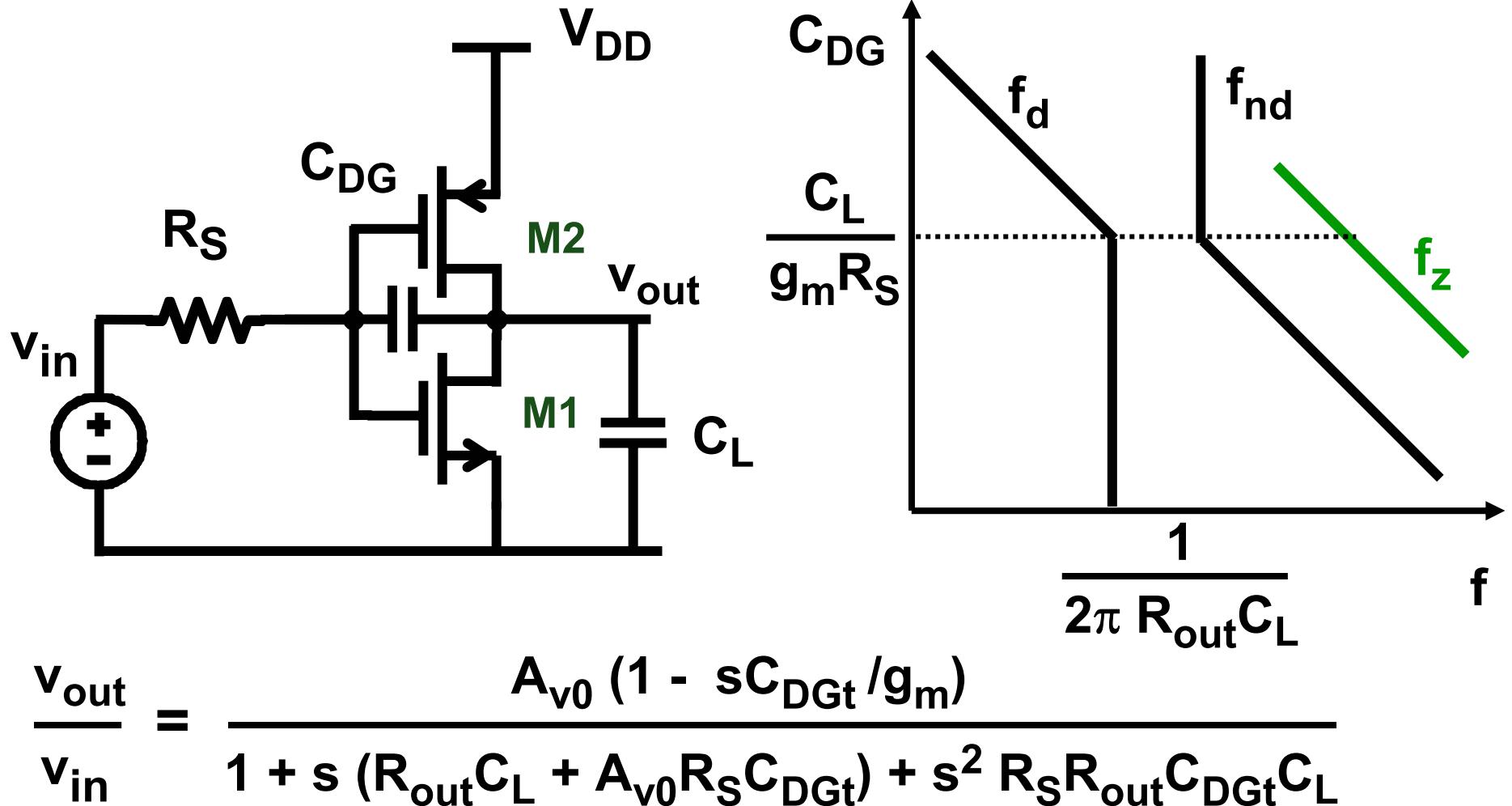

Analog amplifier: other poles

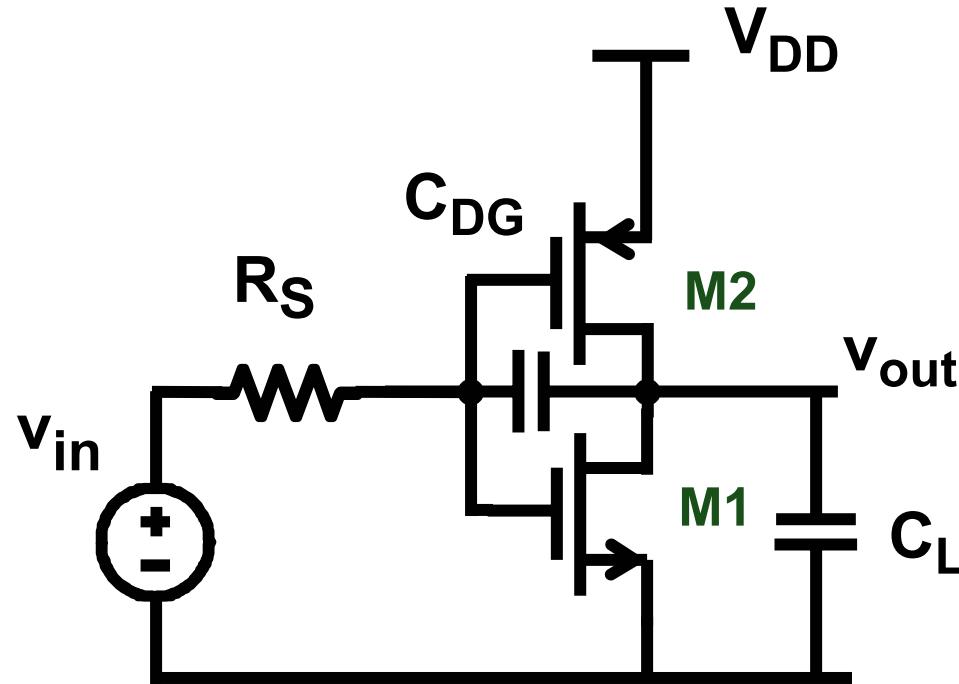

$$A_{v0} = 2g_m R_{out}$$



$$GBW = \frac{2g_m}{2\pi C_L}$$

$$C_{DGt} = C_{DG1} + C_{DG2}$$

But if $R_S C_{DGt} > \frac{1}{2\pi GBW}$:

$$GBW = \frac{1}{2\pi R_S C_{DGt}}$$

Class AB operation

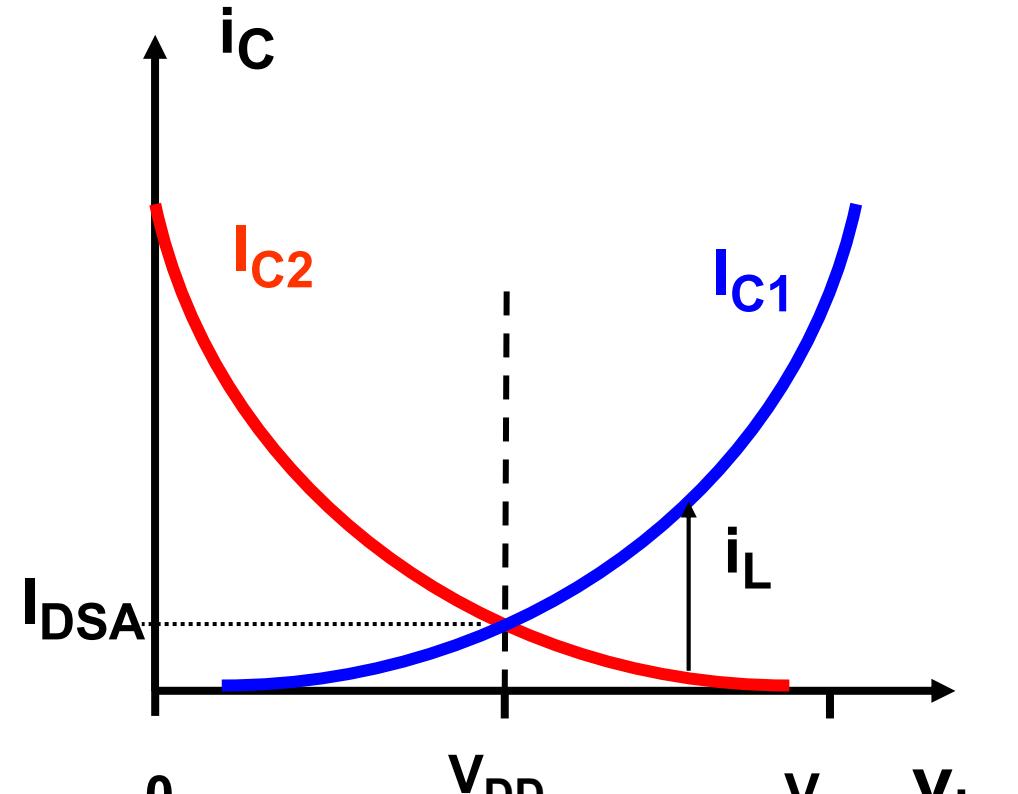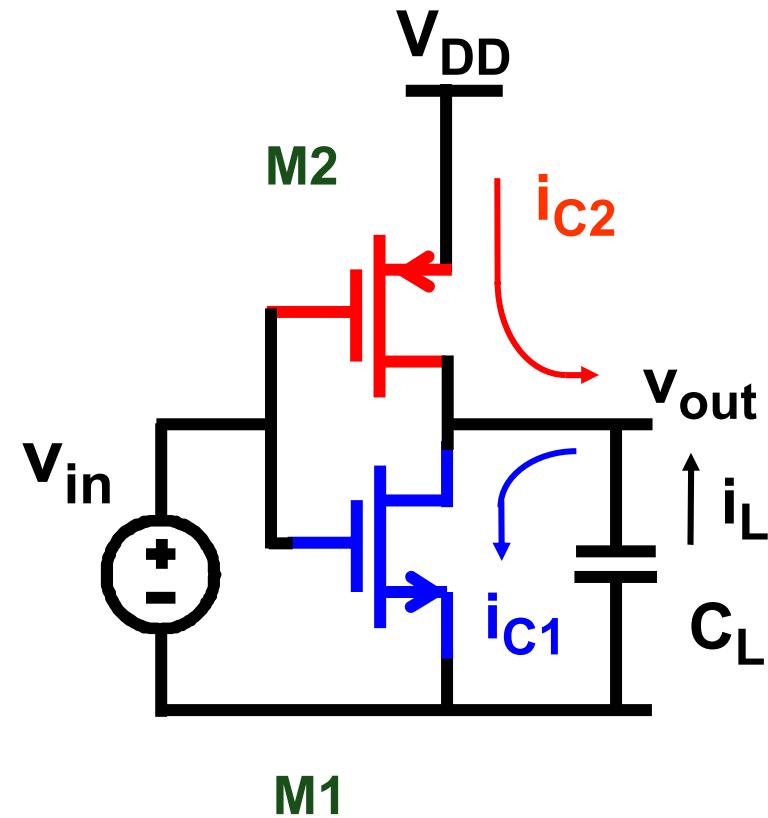


$$i_L = i_{C2} - i_{C1}$$

Table of contents


- Single-transistor amplifiers
- Source followers
- Cascodes

Single-transistor stages


Common source

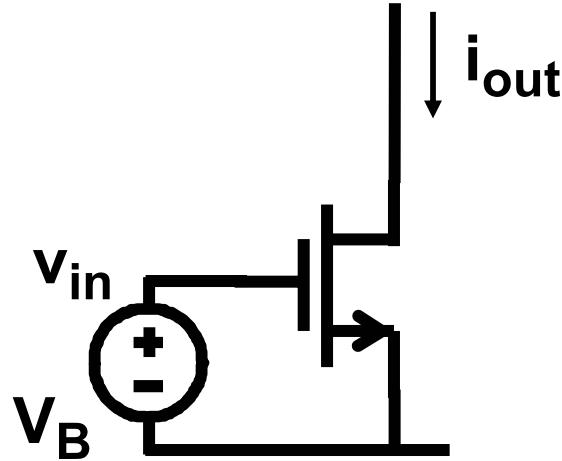

Common drain

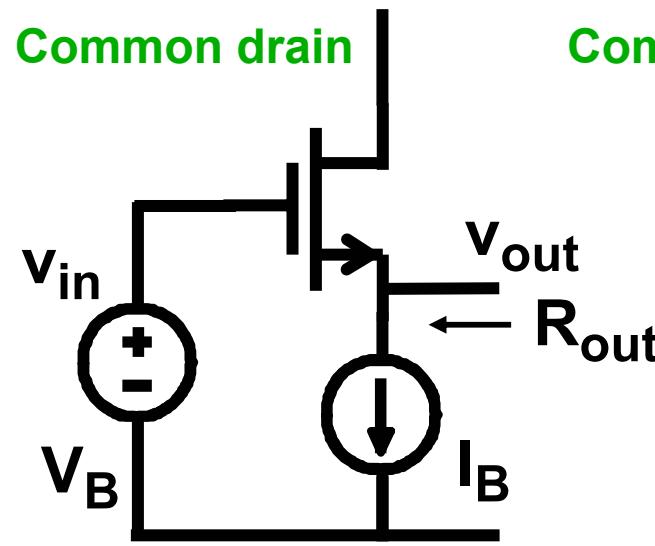

Common gate

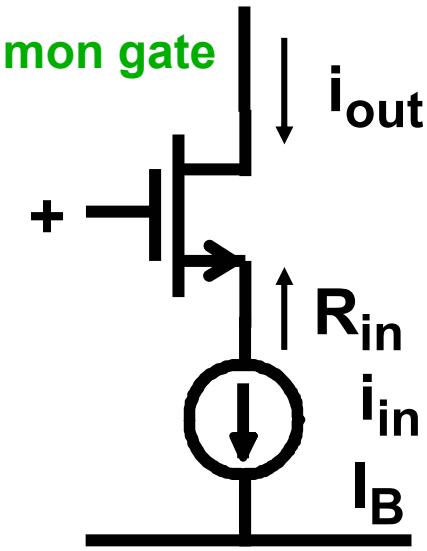

$$i_{out} = g_m v_{in}$$

$$v_{out} = v_{in}$$

$$i_{out} = i_{in}$$

$$R_{out} \approx 1/g_m$$


$$R_{in} \approx 1/g_m$$

Amplifier

Source follower
Voltage buffer

Cascode
Current buffer

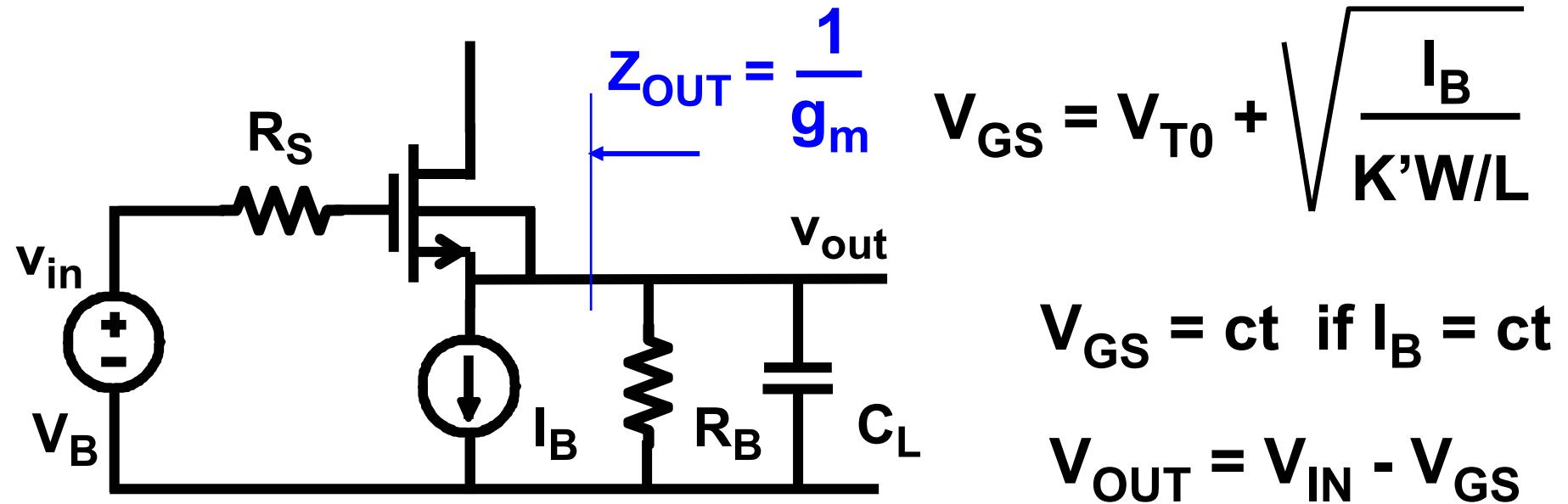
Source follower with $V_{BS} = 0$ (p-well)



$$\Delta V_{OUT} = \Delta V_{IN}$$

$A_v = 1$


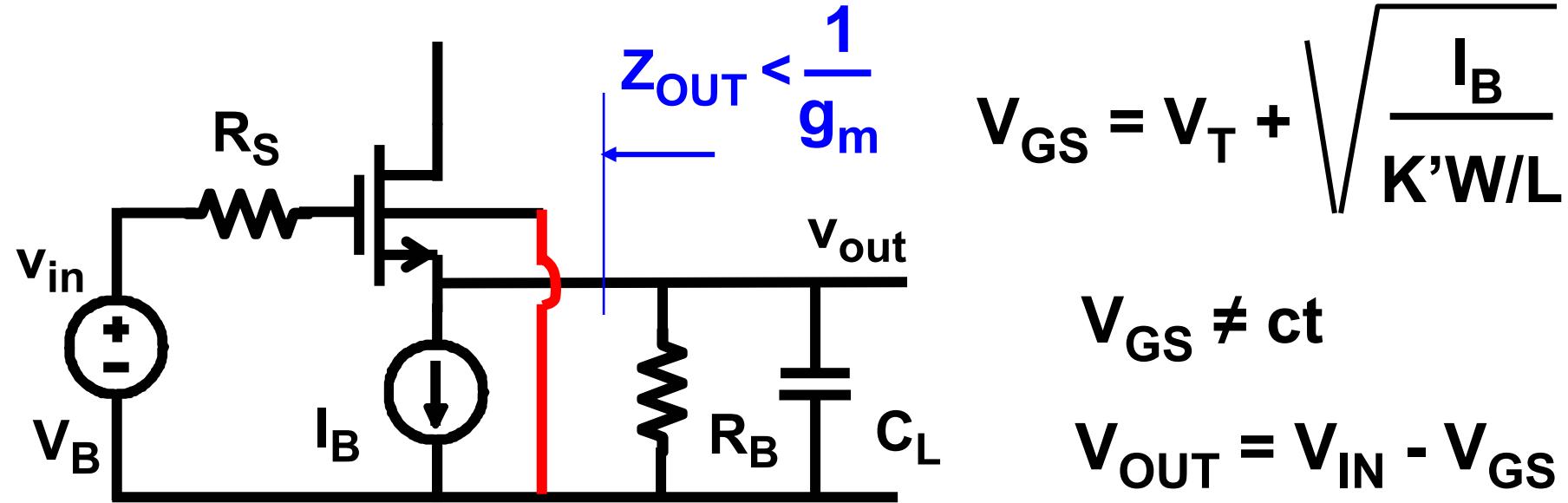
Source follower with $V_{BS} \neq 0$ (n-well)





$$V_T = V_{T0} + \gamma [\sqrt{|2\Phi_F| + V_{OUT}} - \sqrt{|2\Phi_F|}]$$

$$A_v = \frac{1}{n}$$

Source follower non-linearity

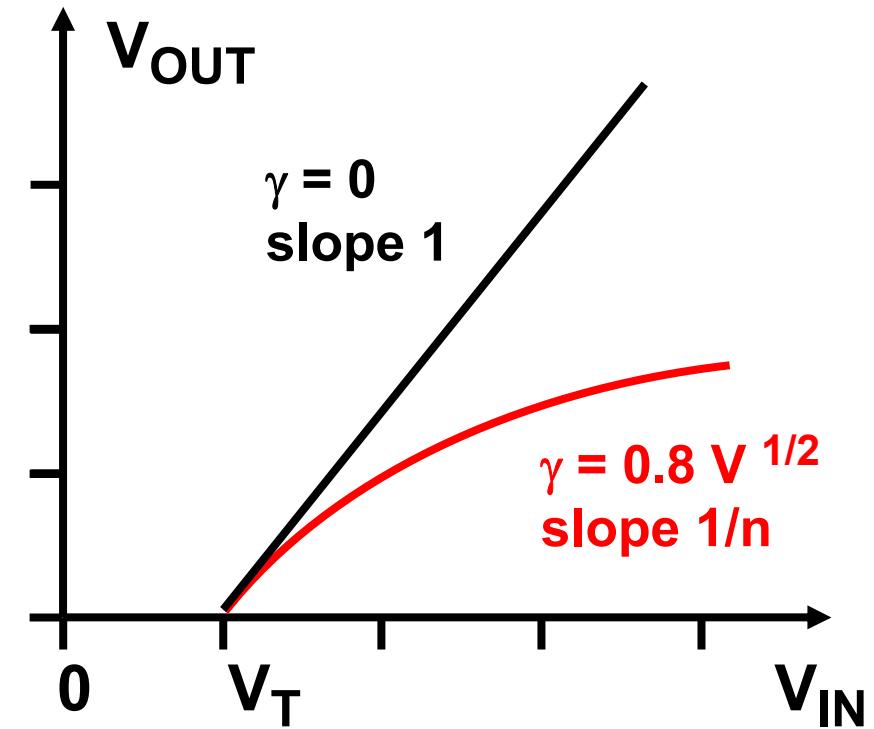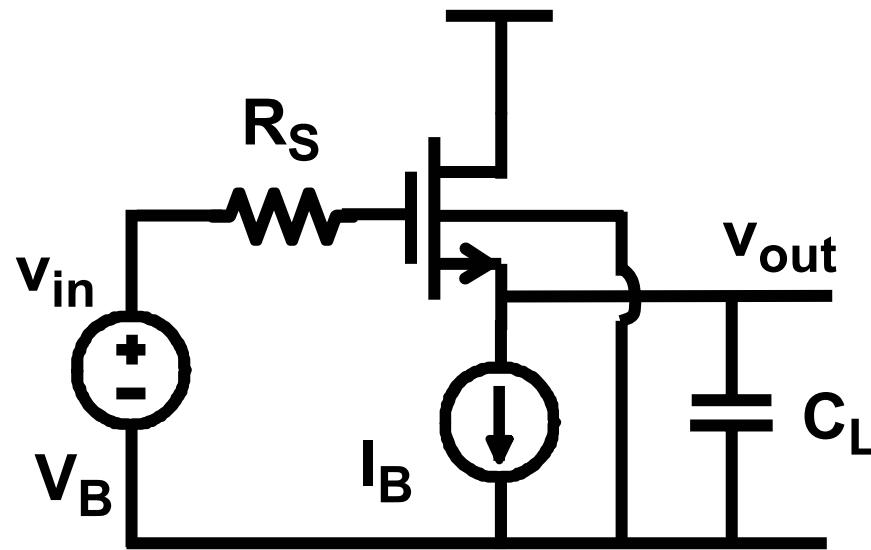

Emitter follower

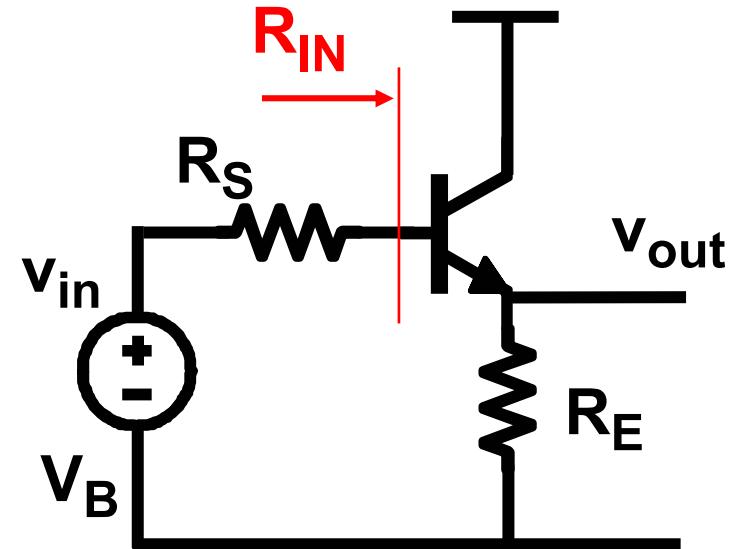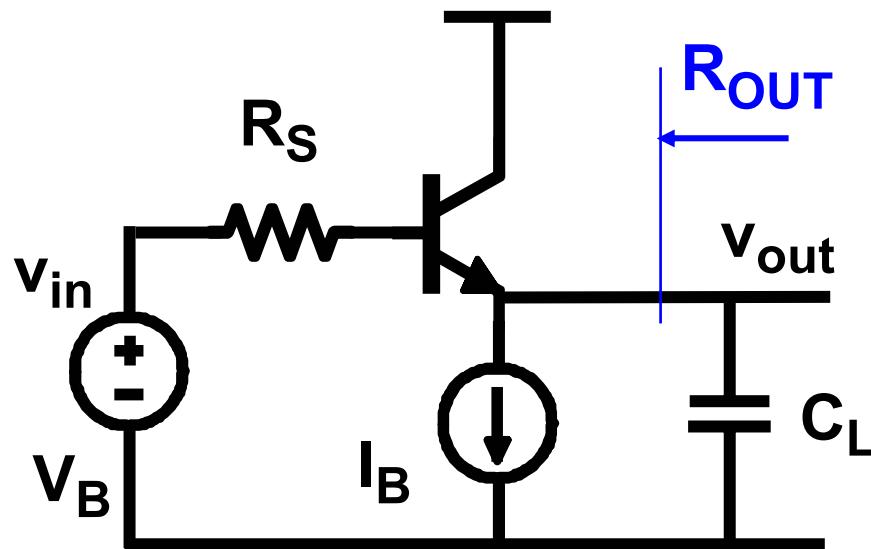


$$A_v = 1$$

$$R_{OUT} = \frac{1}{g_m} + \frac{R_s + r_B}{\beta + 1}$$

$$R_{IN} = r_\pi + r_B + (\beta + 1)R_E$$

Limited isolation !

Source follower with C_L load

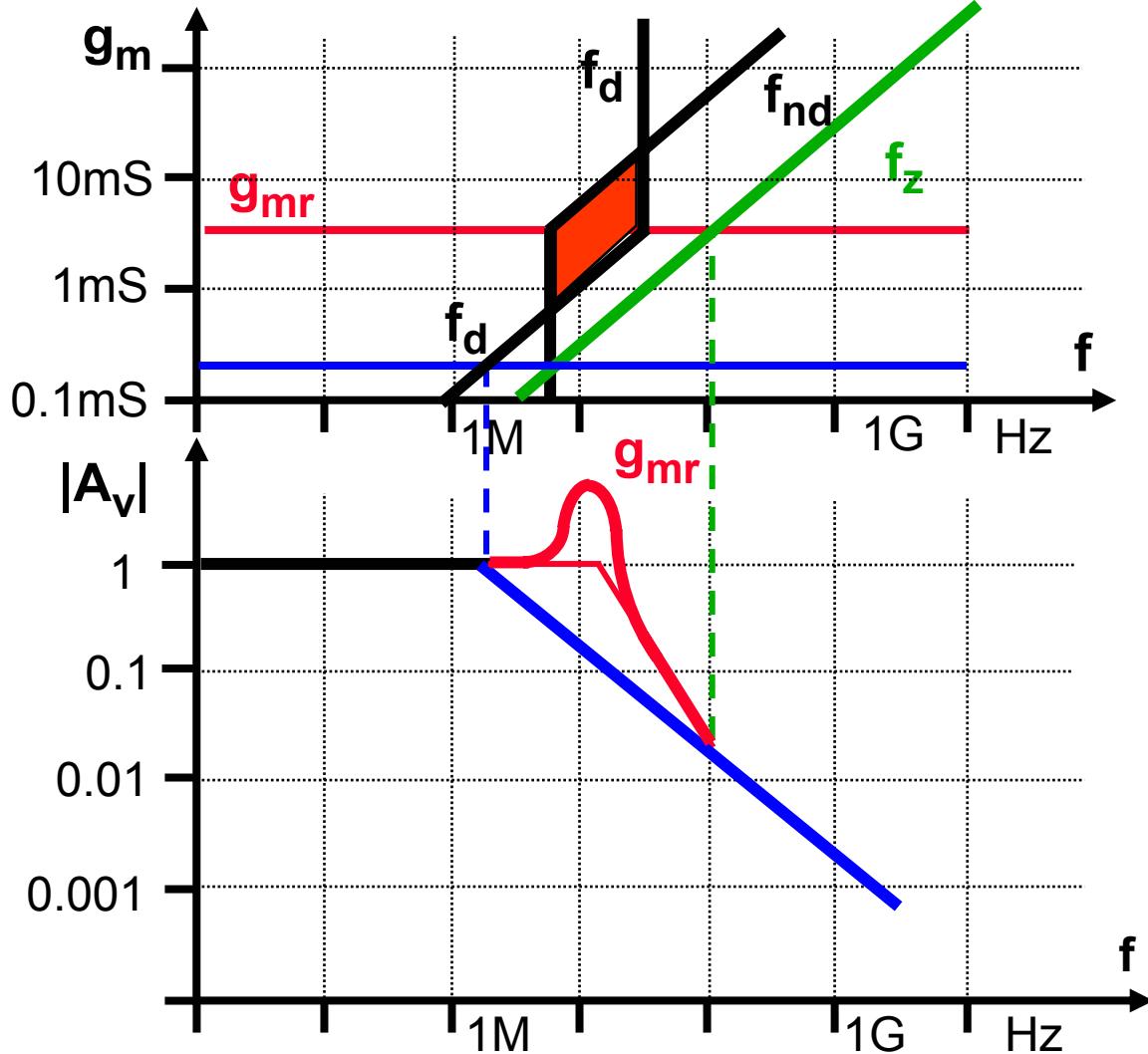

$$A_v = \frac{(1 + s C_{GS} / g_m)}{1 + s B + s^2 C^2 R_S / g_m}$$


$$B = R_S C_{DG} + \frac{C'_{DS}}{g_m}$$

$$+ \frac{C_{GS}}{g_m} \left(1 + \frac{R_S}{r_{DS}} \right)$$

$$C^2 = C'_{DS} C_{DG} + \\ C'_{DS} C_{GS} + C_{DG} C_{GS}$$

$$C'_{DS} = C_L + C_{DS}$$

Source follower with C_L load

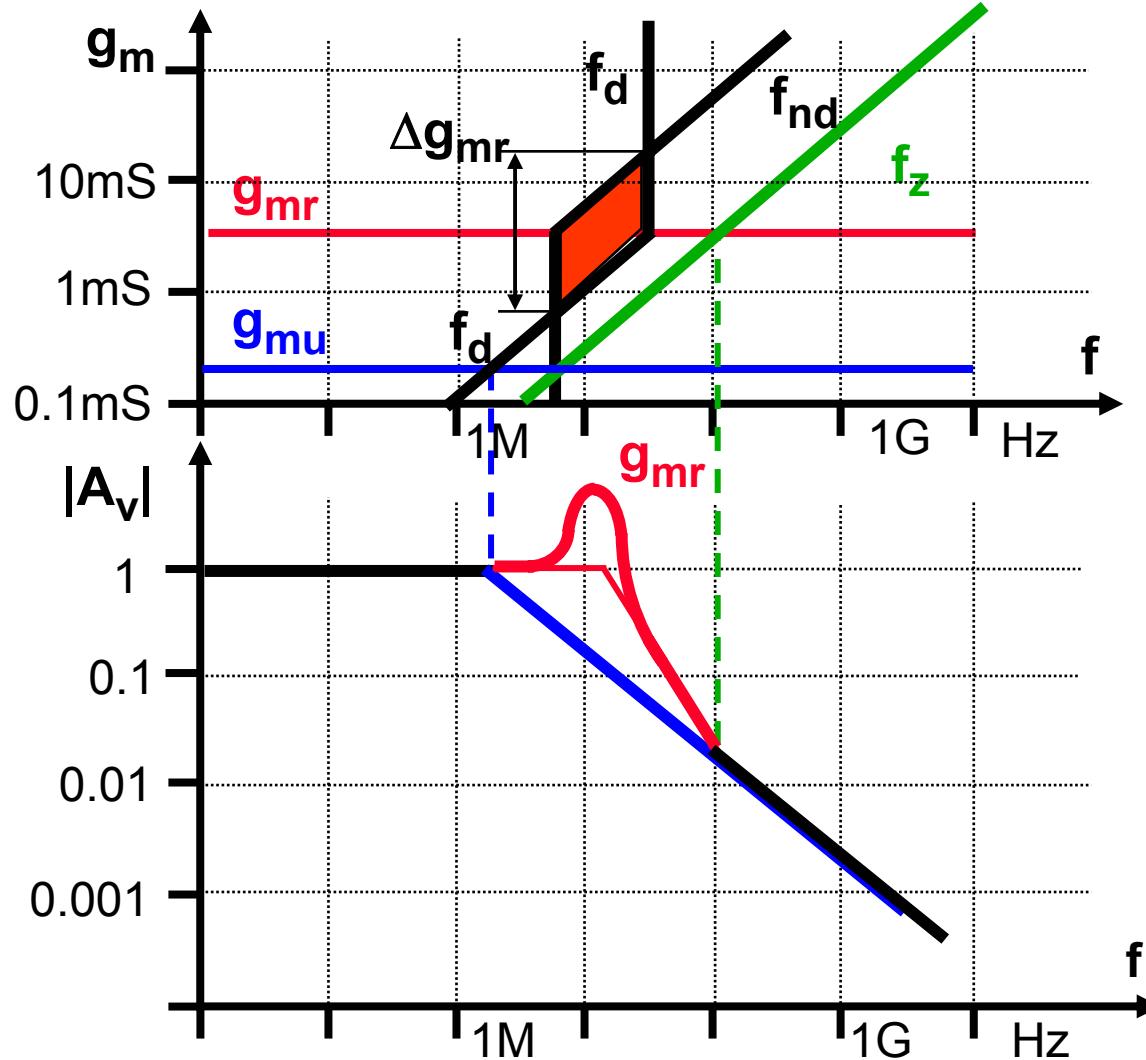


$$g_{mr} = \frac{1}{R_s} \frac{C_L + C_{DS} + C_{GS}}{C_{DG}}$$

$$\Delta g_{mr} = \frac{C_{DGt}}{C_{DG}}$$

$$C_{DGt} = \frac{C'_{DS} C_{GS}}{C'_{DS} + C_{GS}}$$

$$g_{mu} = \frac{1}{R_s}$$

Source follower : Output impedance

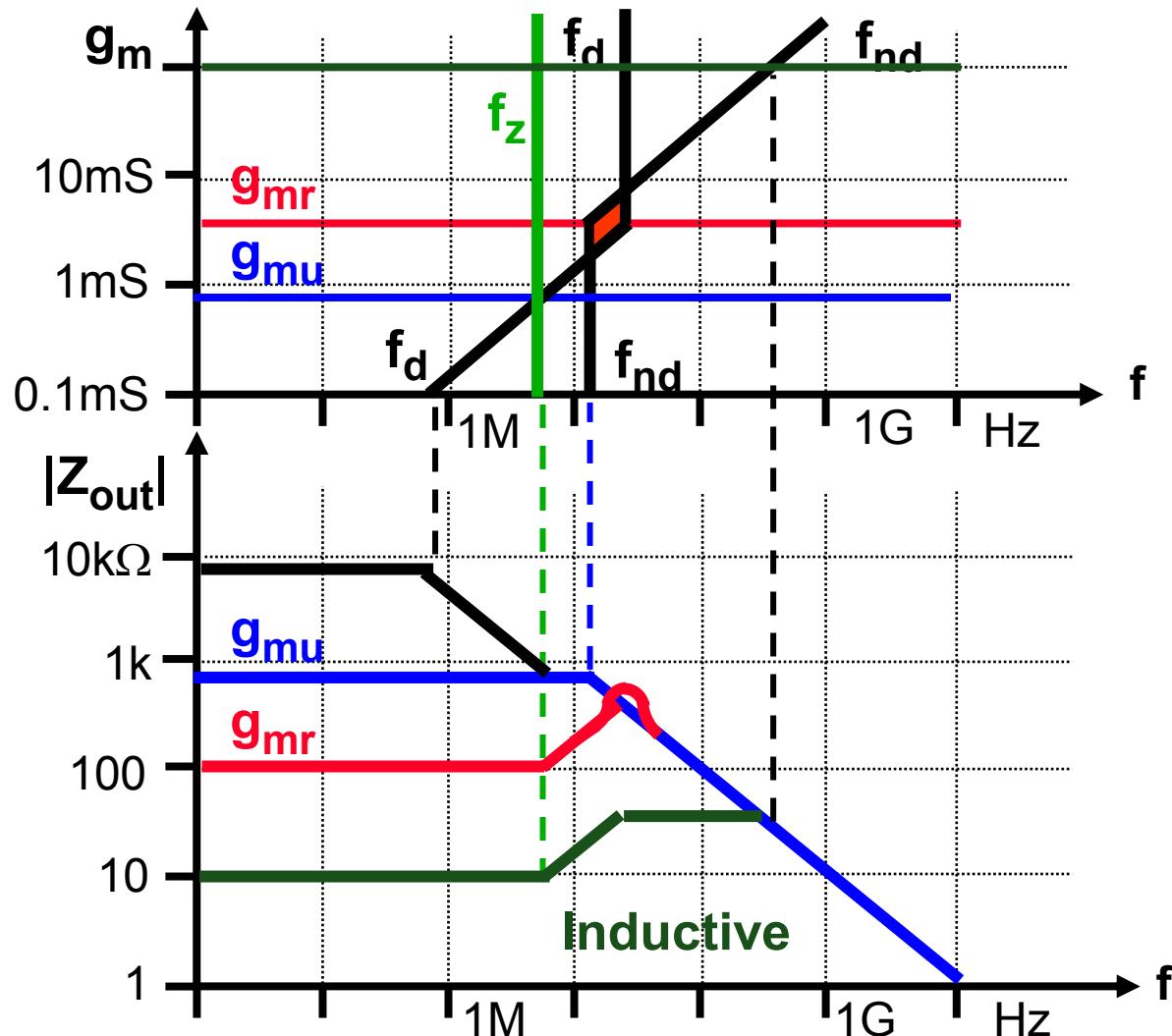


$$g_{mr} = \frac{1}{R_S} \frac{C_{GS} + C_{DS}}{C_{DG}}$$

$$g_{mu} \approx \frac{1}{R_S} \frac{C_{GS} + C_{DS}}{C_{GS} + C_{DG}}$$

$$f_z = \frac{1}{2\pi R_S C_{GS}}$$

$$f_{d,higm} = \frac{1}{2\pi R_S C_{DG}}$$

Emitter follower : Output impedance

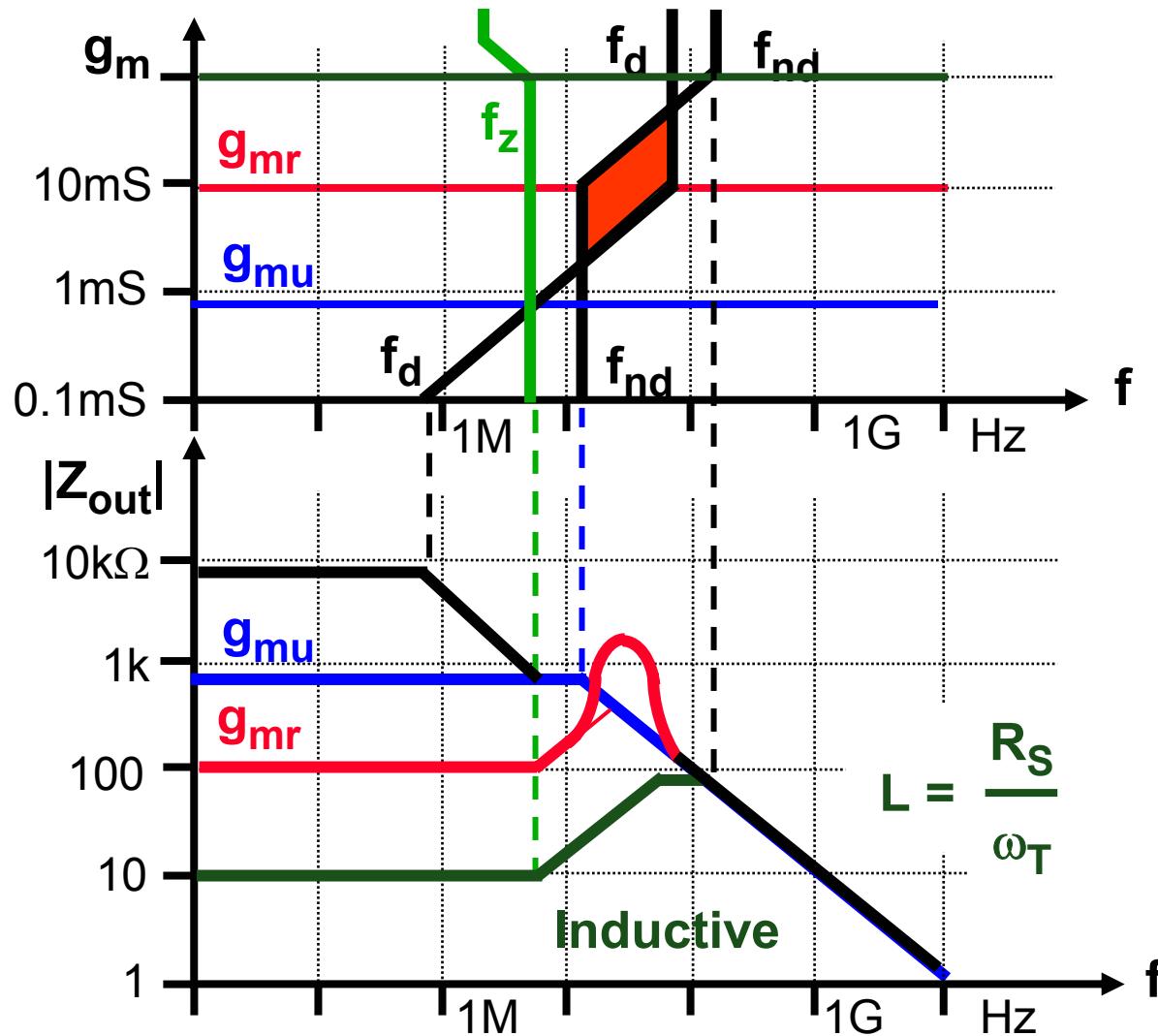


$$g_{mr} = \frac{1}{R_S} \frac{C_\pi + C_{CE}}{C_\pi + C_\mu}$$


$$g_{mu} \approx \frac{1}{R_S} \frac{C_{jE} + C_{CE}}{C_{jE} + C_\mu}$$

$$f_z = \frac{1}{2\pi R_S / r_\pi (C_\pi + C_\mu)}$$

Source follower as active L

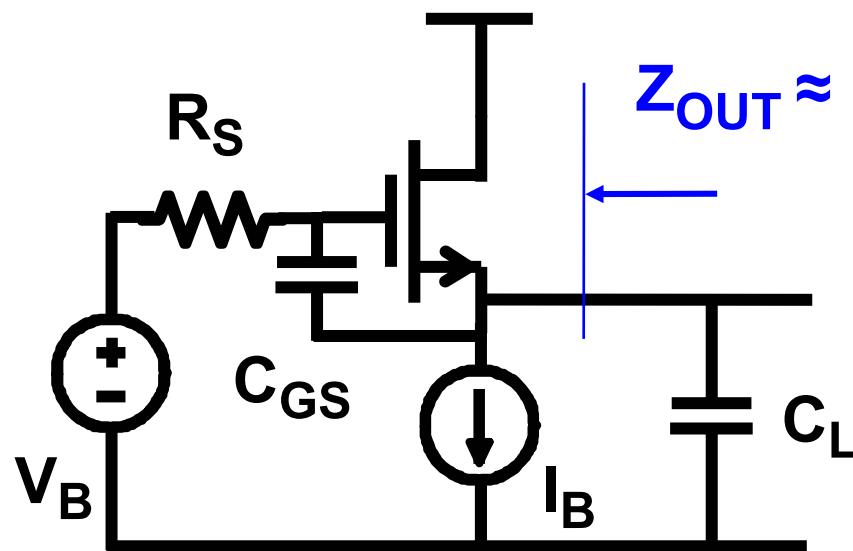


$$Z_{OUT} \approx \frac{1}{g_m}$$

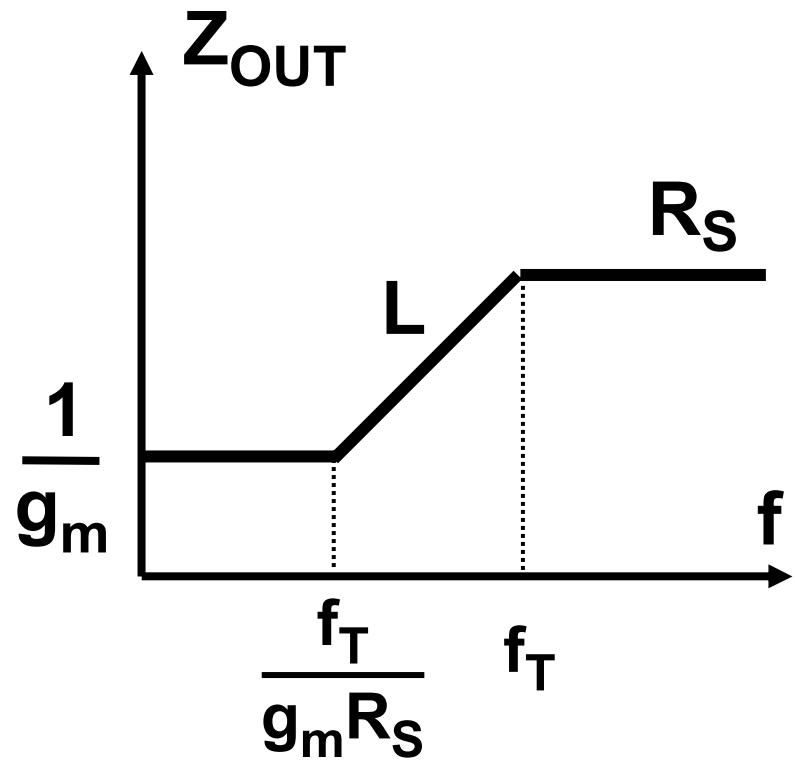

$$Z_{OUT} \approx \frac{1}{g_m} (1 + R_S C_{GS} s)$$

$$L \approx \frac{R_S}{2\pi f_T} \quad \text{up to } f_T = \frac{g_m}{2\pi C_{GS}}$$

Source follower as active L

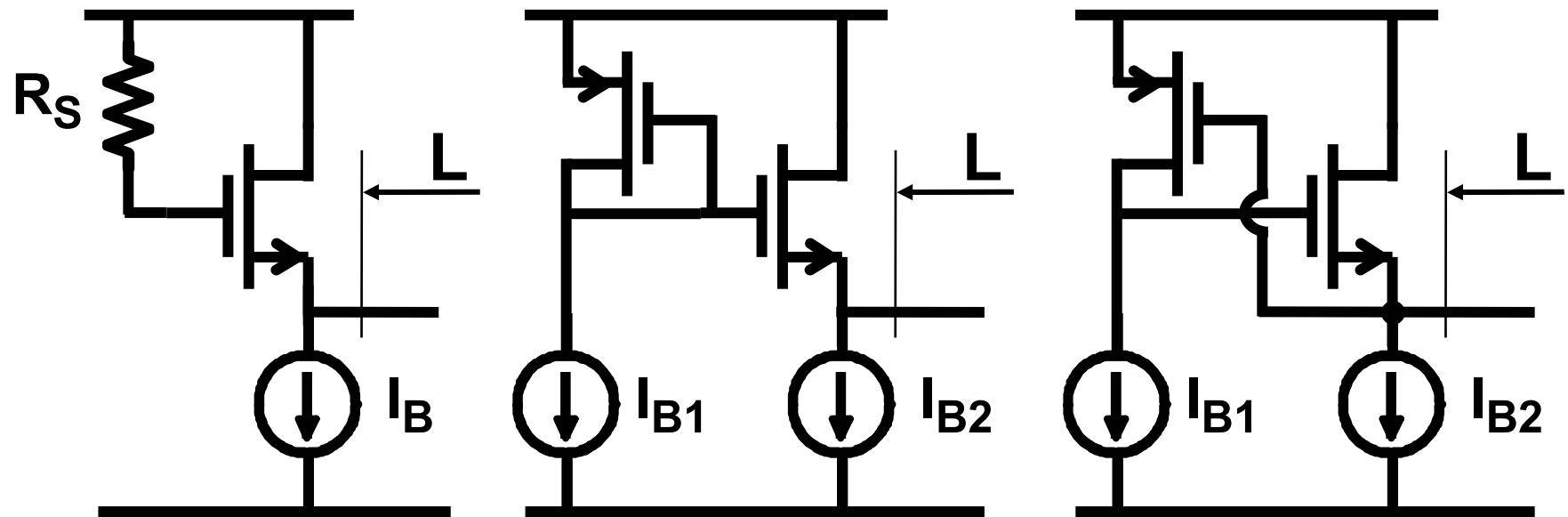

$$L \approx \frac{R_S}{2\pi f_T}$$

$$L \approx \frac{1/g_{mp}}{2\pi f_{Tn}}$$



$$L \approx \frac{1/g_{mp}}{2\pi f_{Tn}}$$

$$V_{DSn} = V_{GSn}$$

$$V_{DSn} = V_{GSn} + V_{GSp}$$

$$V_{DSn} = V_{GSp}$$

Floating inductor with parallel C

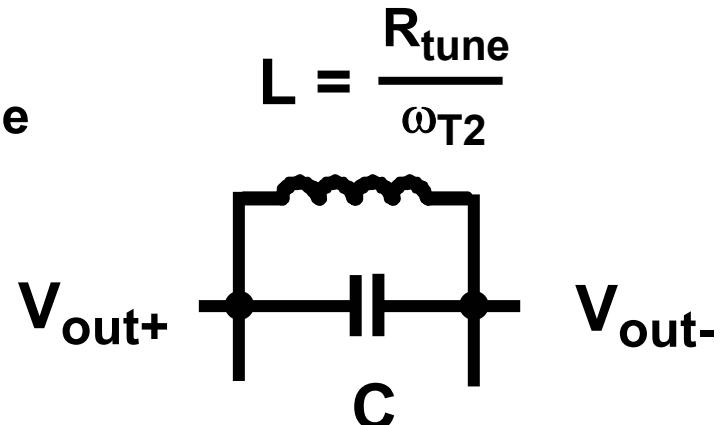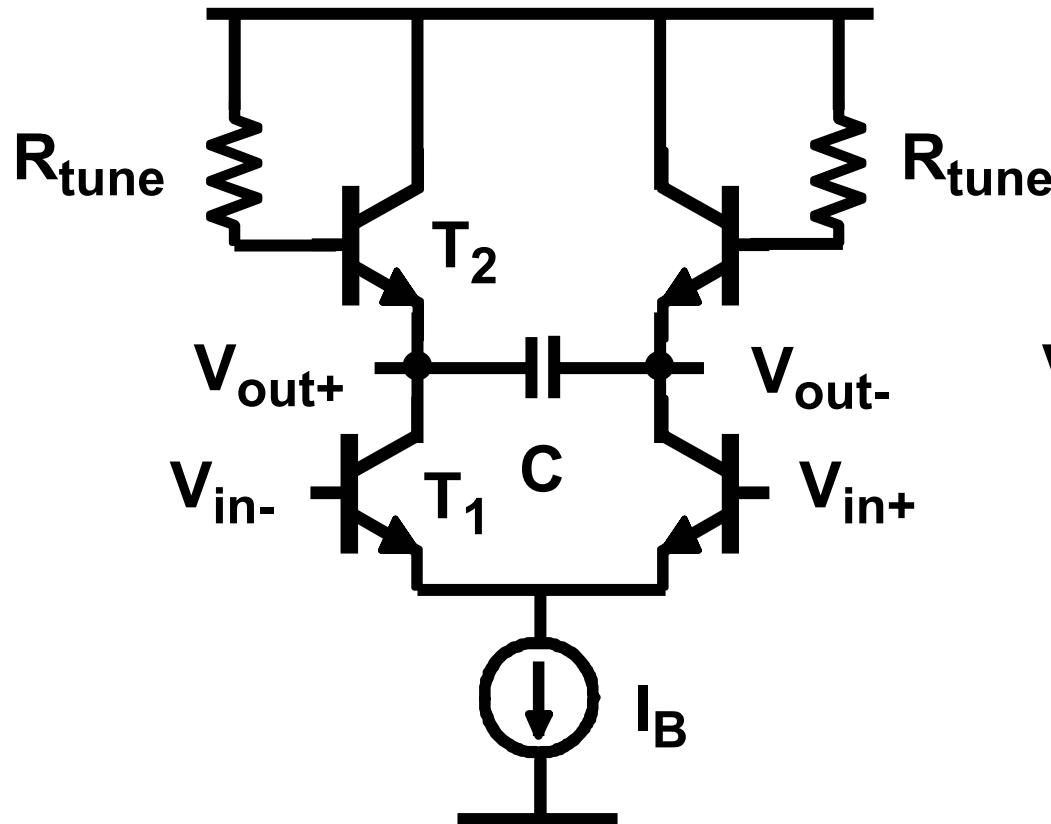

$$A_v = \frac{g_{m1}}{g_{m2}}$$


with HF peaking !

Table of contents


- Single-transistor amplifiers
- Source followers
- Cascodes

Single-transistor stages


Common source

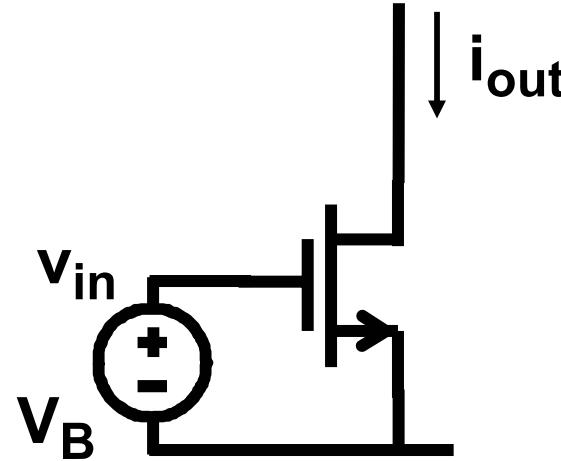

Common drain

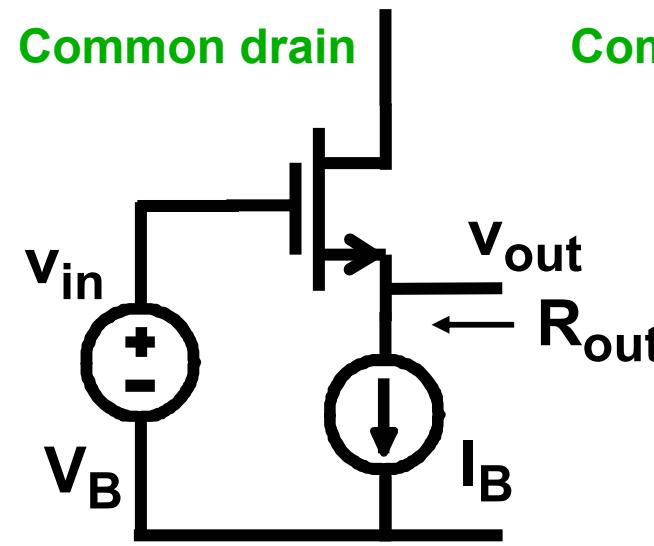

Common gate

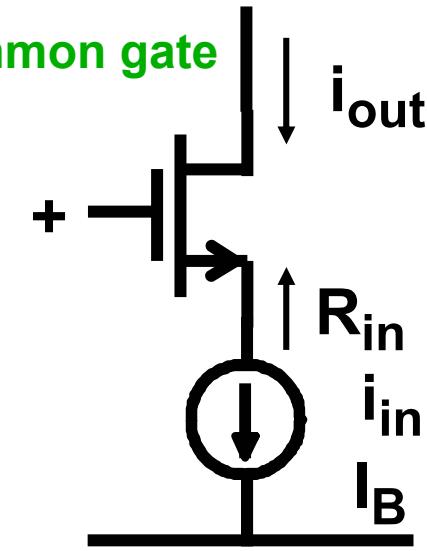

$$i_{out} = g_m v_{in}$$

$$v_{out} = v_{in}$$

$$i_{out} = i_{in}$$

$$R_{out} \approx 1/g_m$$



$$R_{in} \approx 1/g_m$$

Amplifier

Source follower
Voltage buffer

Cascode
Current buffer



Cascode with resistive load

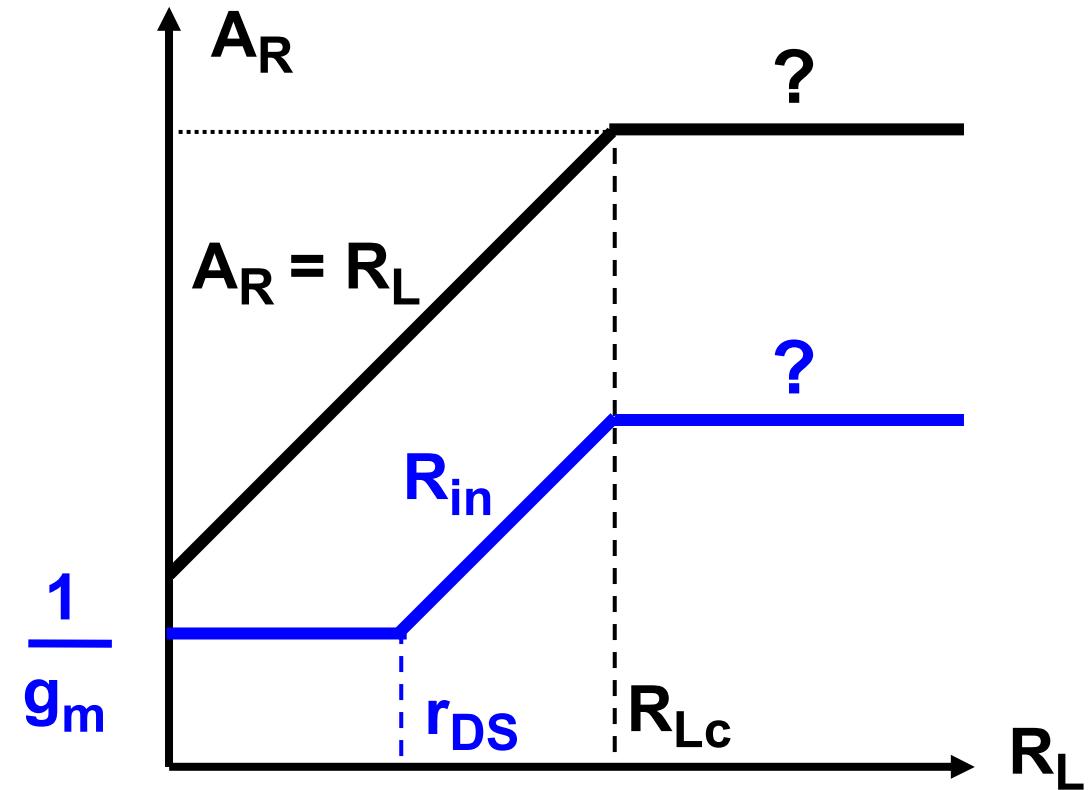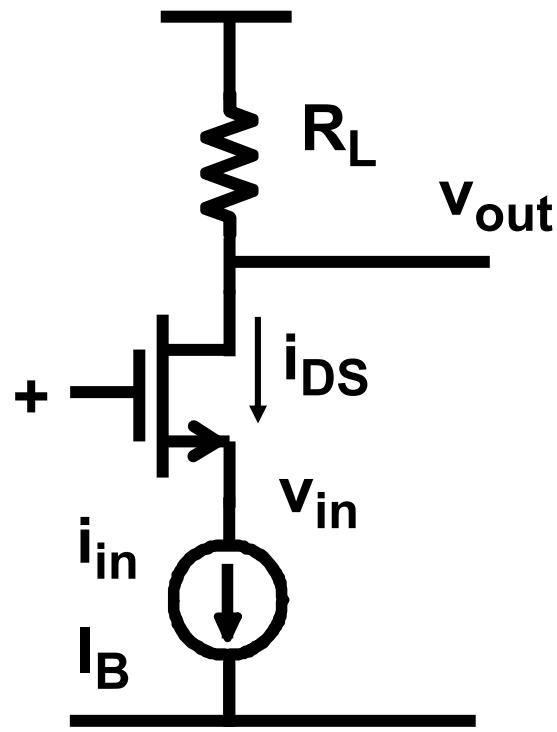

$$A_R = \frac{v_{out}}{i_{in}}$$

$$R_{in} = \frac{v_{in}}{i_{in}}$$



Cascode with resistive load

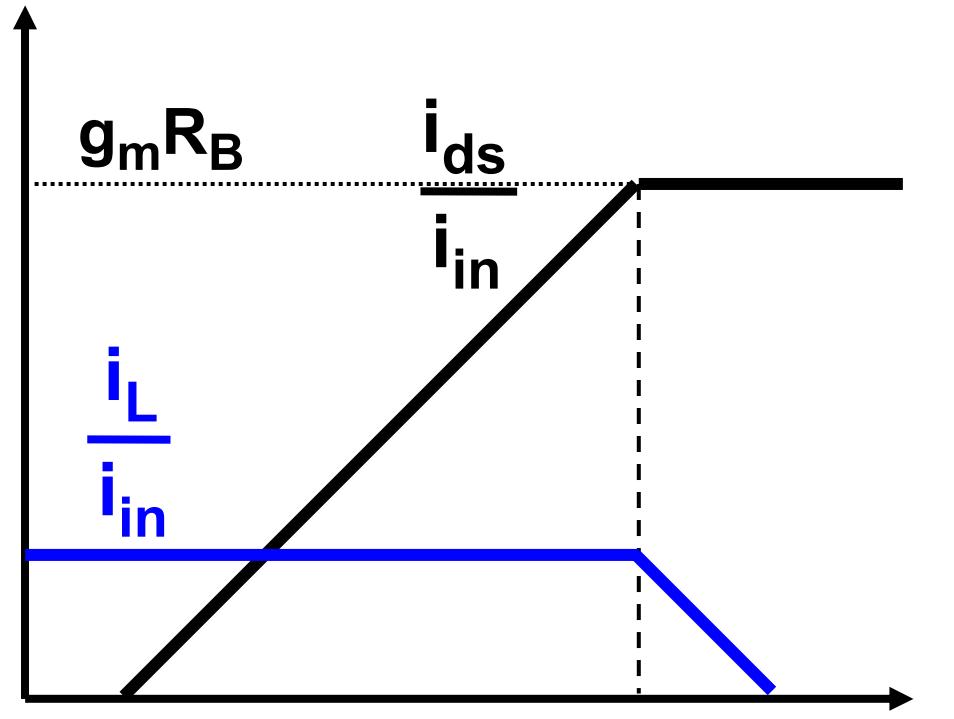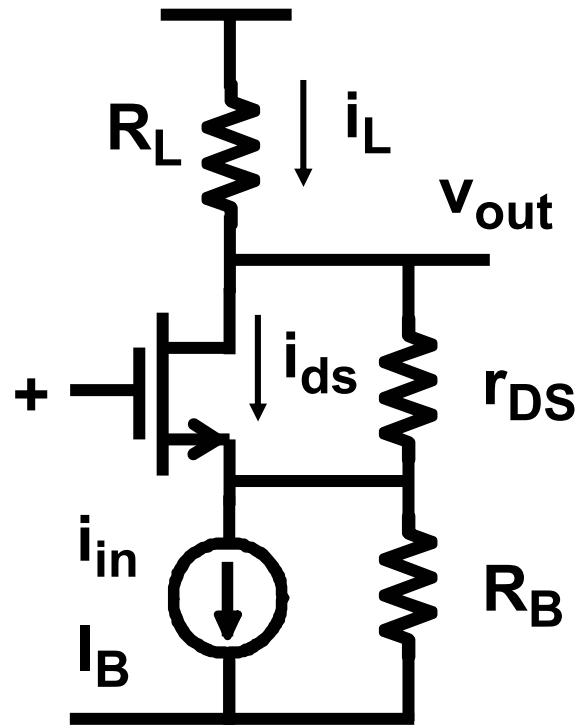

$$R_{Lc} = g_m r_{DS} R_B$$

R_{Lc} R_L

Cascode with active load

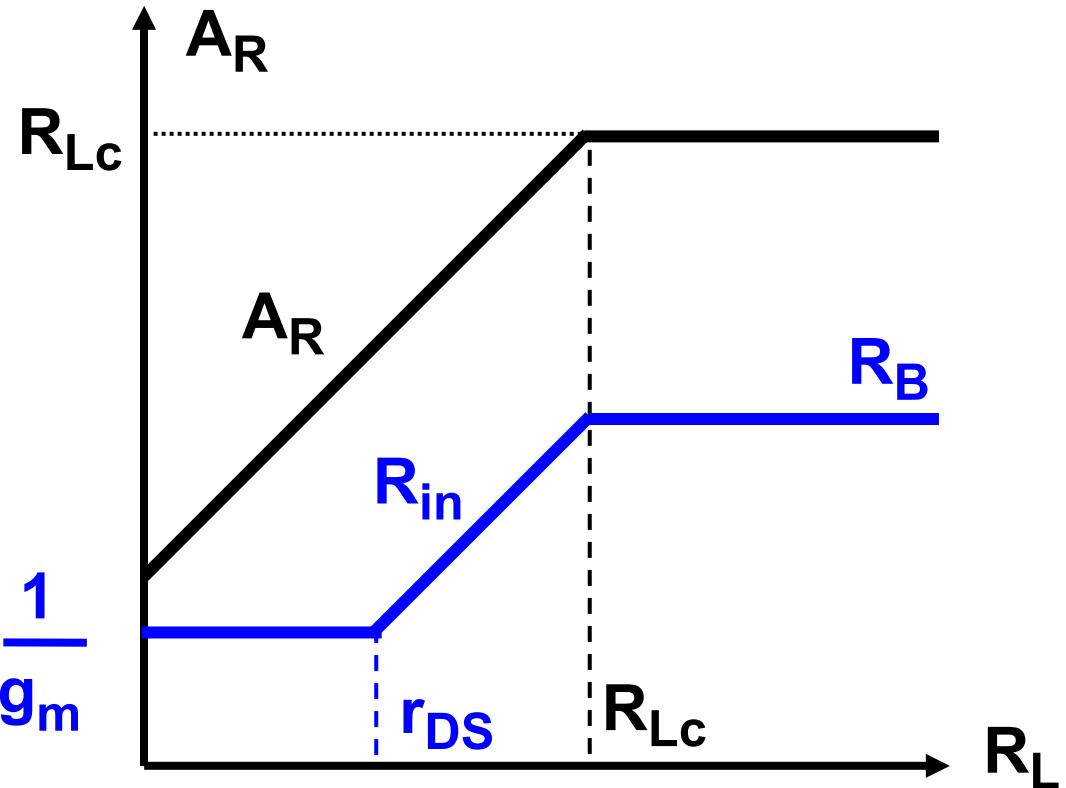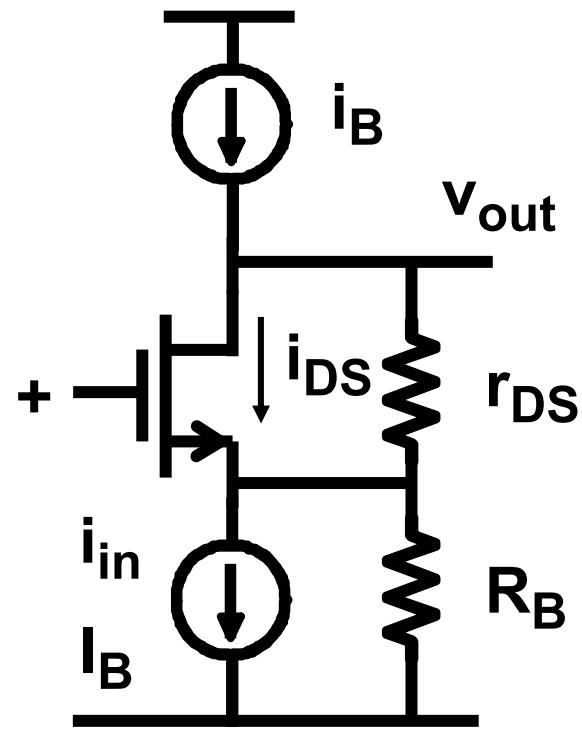


$$A_R = \frac{v_{out}}{i_{in}}$$

$$R_{in} = \frac{v_{in}}{i_{in}}$$


$$R_{Lc} = g_m r_{DS} R_B \approx 100 R_B$$

Cascode versus single-transistor

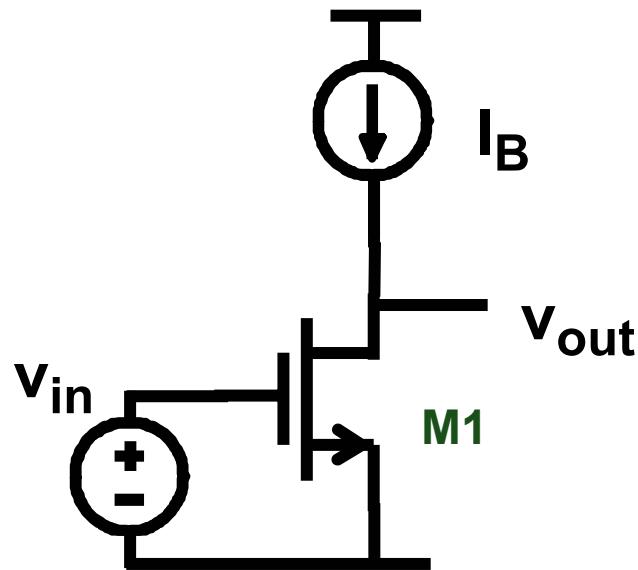

$$A_v = (g_m r_{DS})_1$$


$$R_{out} = r_{DS1}$$

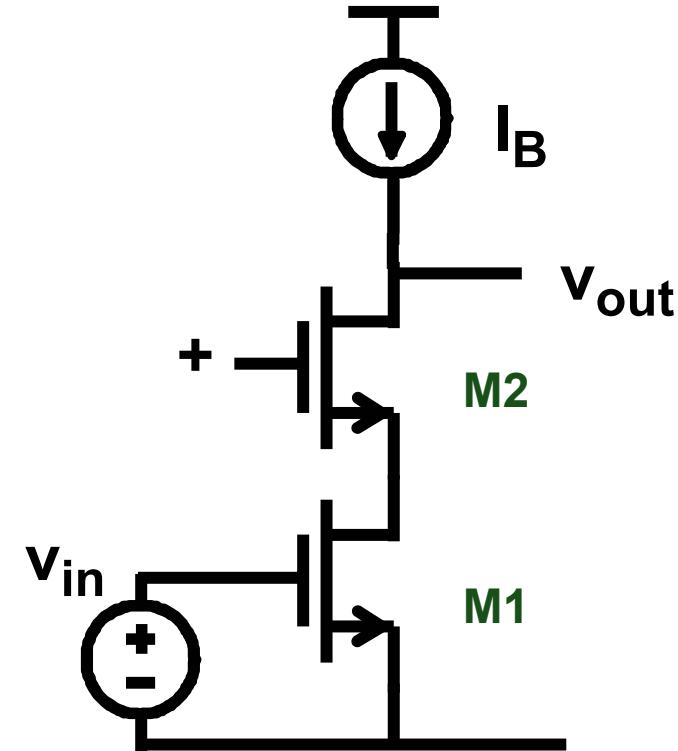


$$A_v = (g_m r_{DS})_1 (g_m r_{DS})_2$$

$$R_{out} = r_{DS1} (g_m r_{DS})_2$$

Cascode versus single-transistor


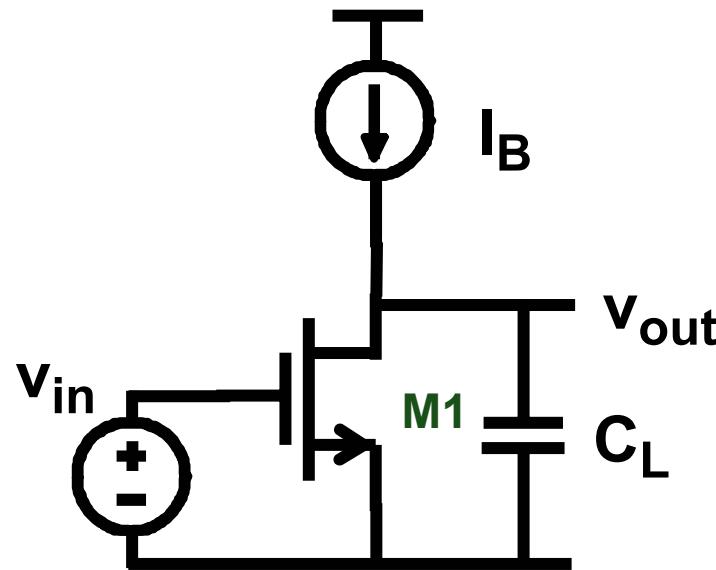


$$BW = \frac{1}{2\pi R_{out} C_L}$$

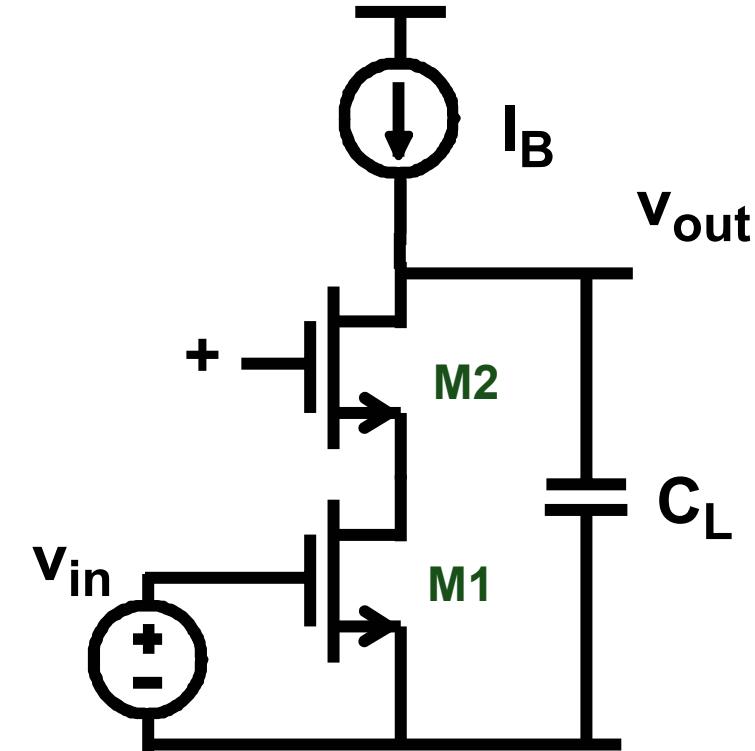

$$GBW = \frac{g_{m1}}{2\pi C_L} \quad \text{for both !}$$



Cascode versus single-transistor

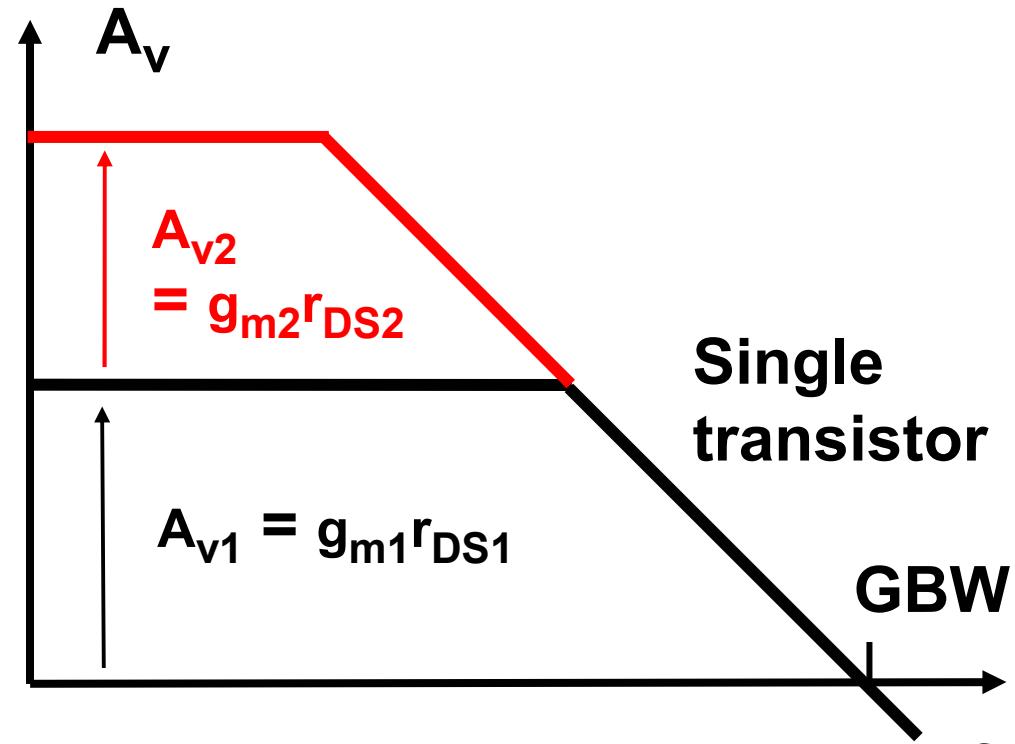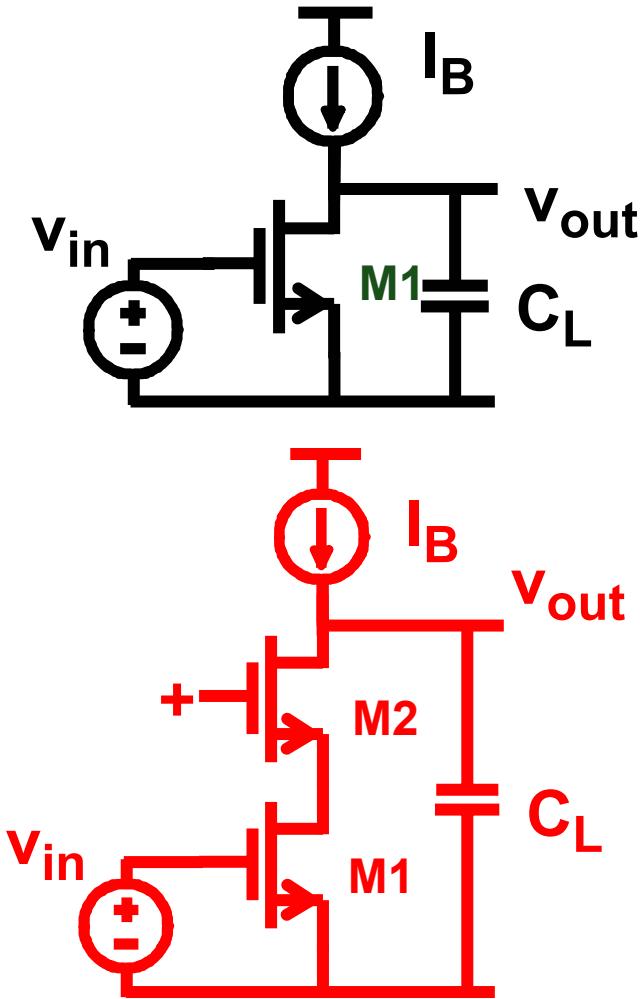

Cascode :
High gain
At low freq.

$$GBW = \frac{g_m}{2\pi C_L}$$



Miller effect in cascode ?

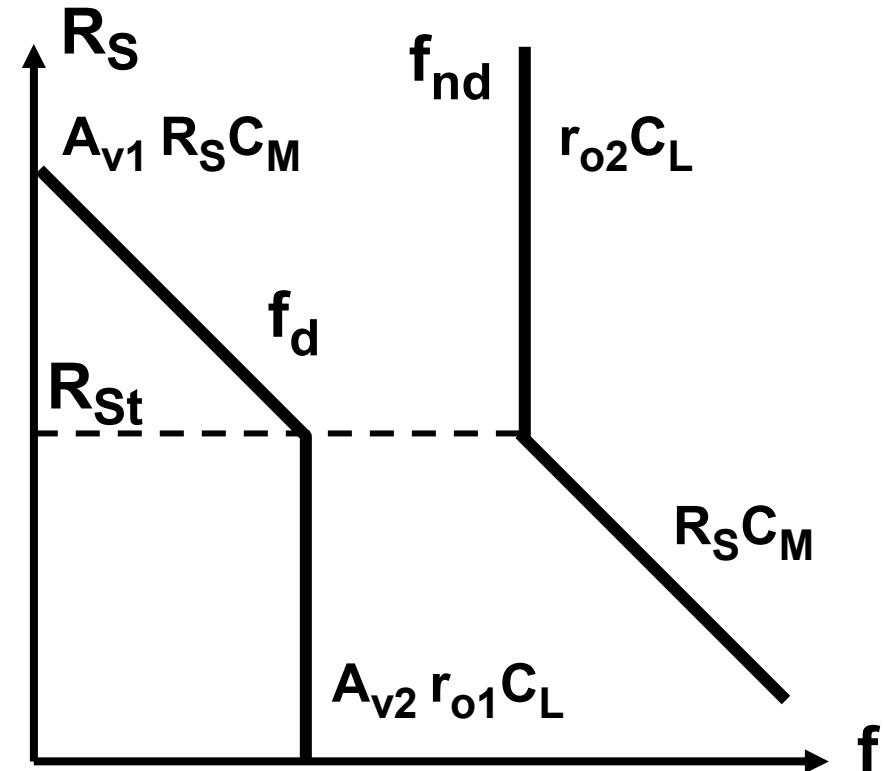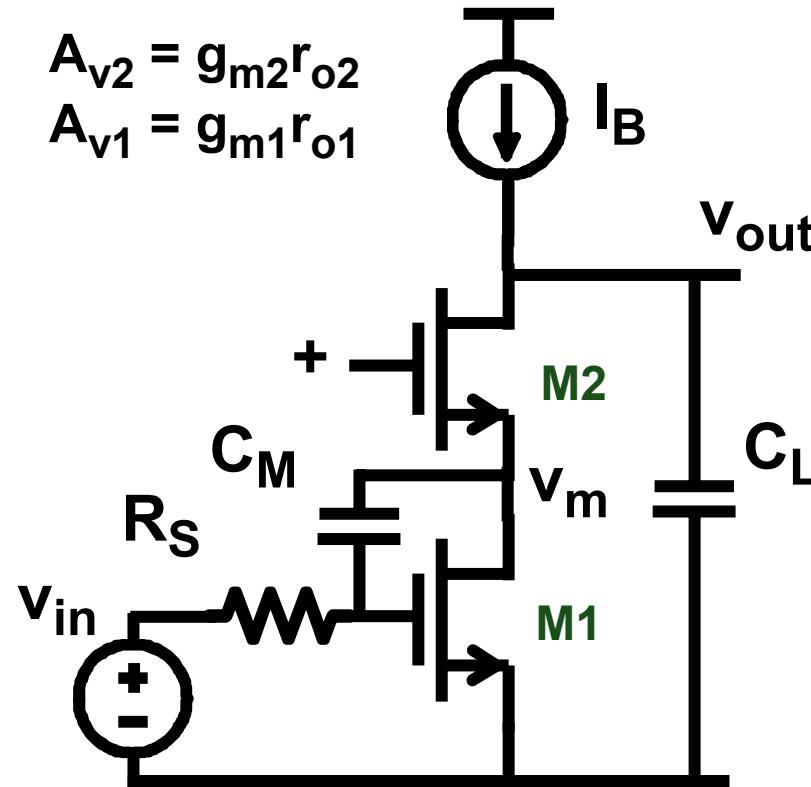

$$GBW = \frac{g_{m1}}{2\pi C_L}$$

No Miller if $R_s < R_{st} = r_{o2} \frac{C_L}{C_M} \frac{g_{m2}}{g_{m1}}$

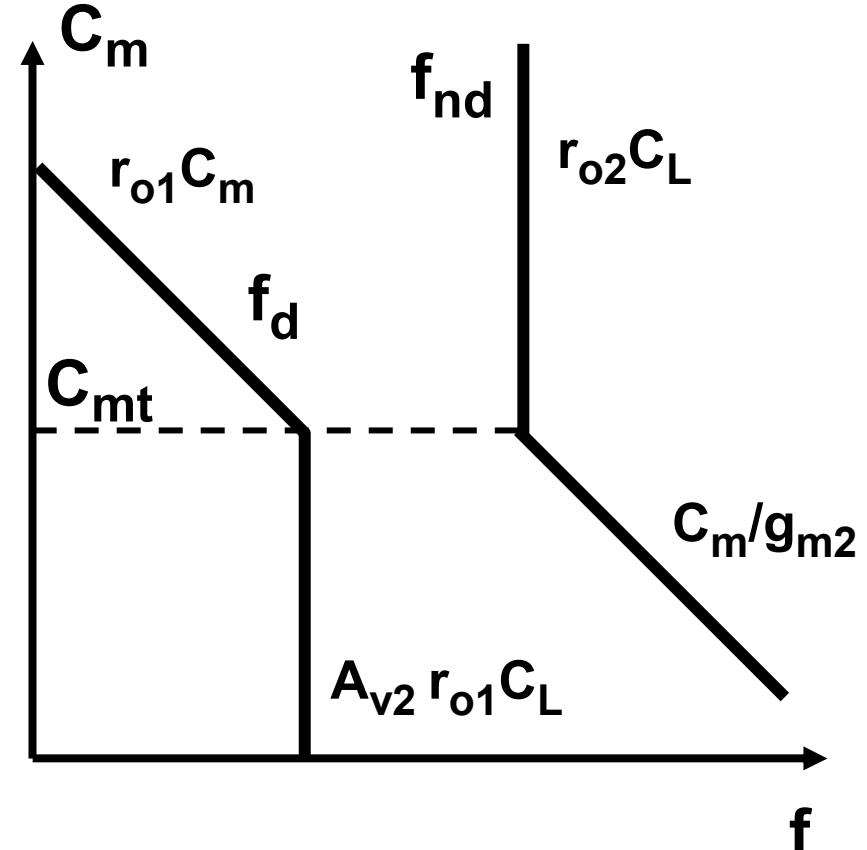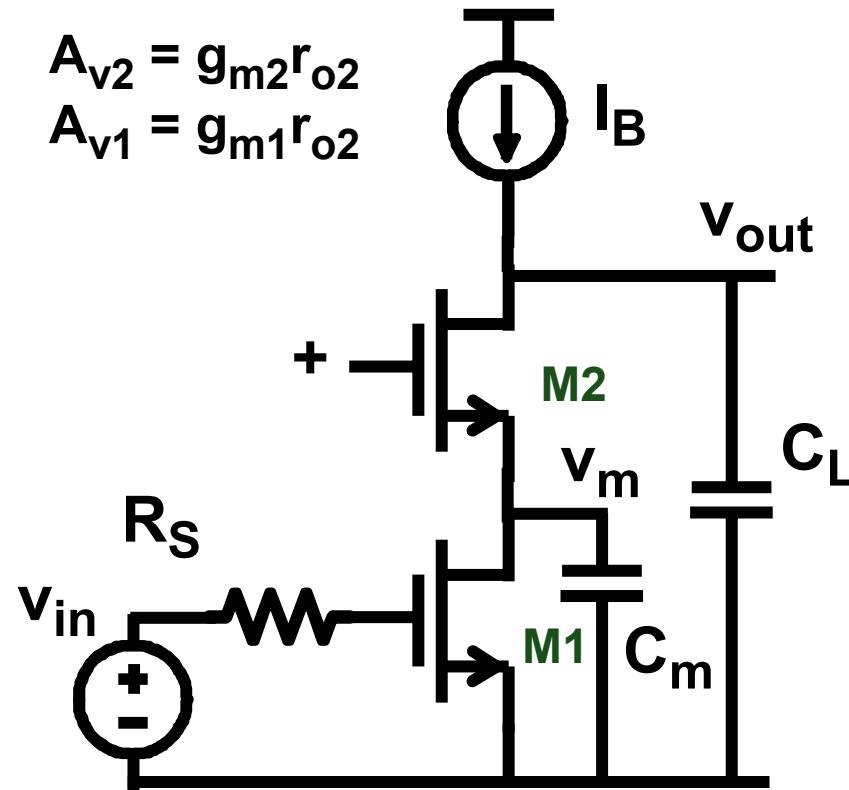
Cascode with capacitance C_m at middle point



$$GBW = \frac{g_{m1}}{2\pi C_L}$$

$$C_{mt} = g_{m2}r_{o2} C_L = A_{v2} C_L$$

Telescopic Cascode

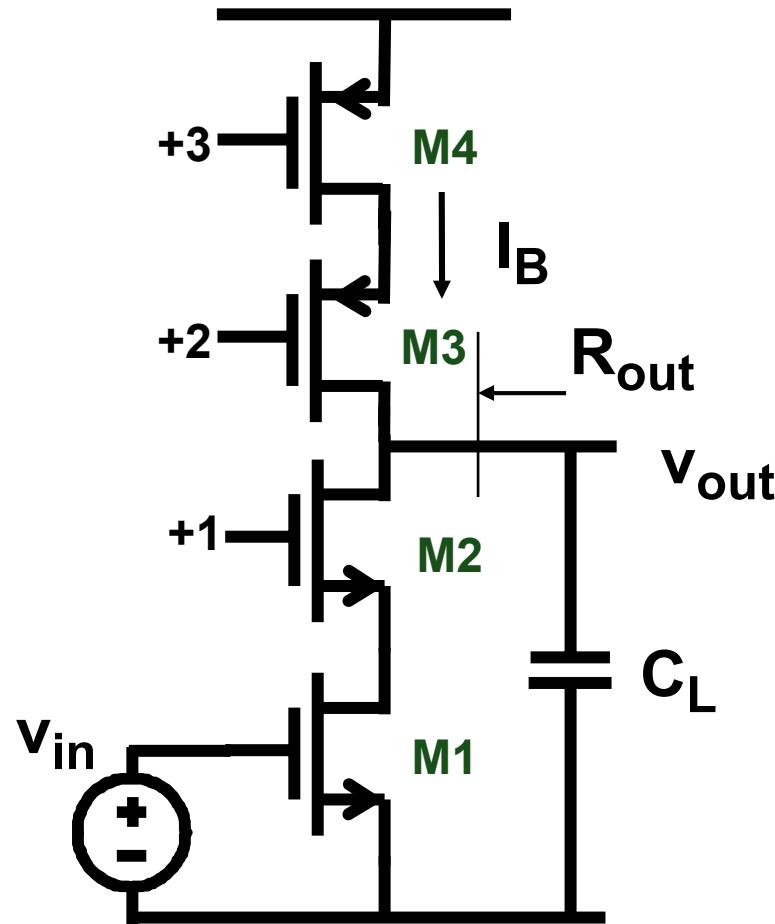


$$A_v = g_{m1} R_{out}$$

$$R_{out} = \frac{1}{2} r_{DS1} g_{m2} r_{DS2}$$

$$BW = \frac{1}{2\pi R_{out} C_L}$$

$$GBW = \frac{g_{m1}}{2\pi C_L}$$

Folded Cascode

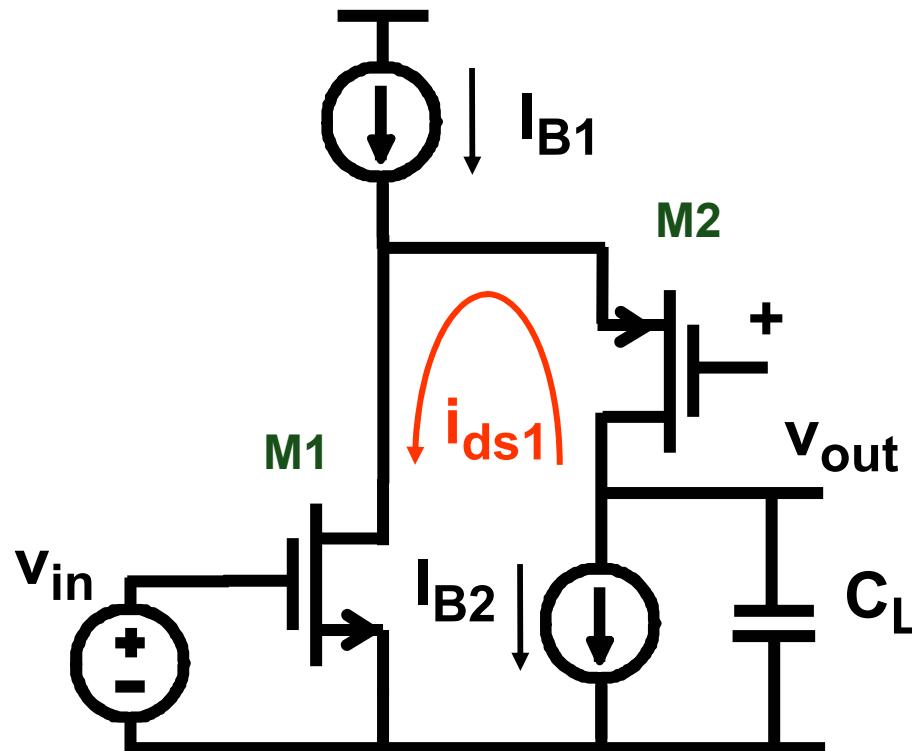

$$I_{DS1} = I_{B1} - I_{B2} \approx I_{B1} / 2$$


$$A_v = g_{m1} R_{out}$$

$$R_{out} = r_{DS1} g_{m2} r_{DS2}$$

$$BW = \frac{1}{2\pi R_{out} C_L}$$

$$GBW = \frac{g_{m1}}{2\pi C_L}$$


Cascode versus cascade

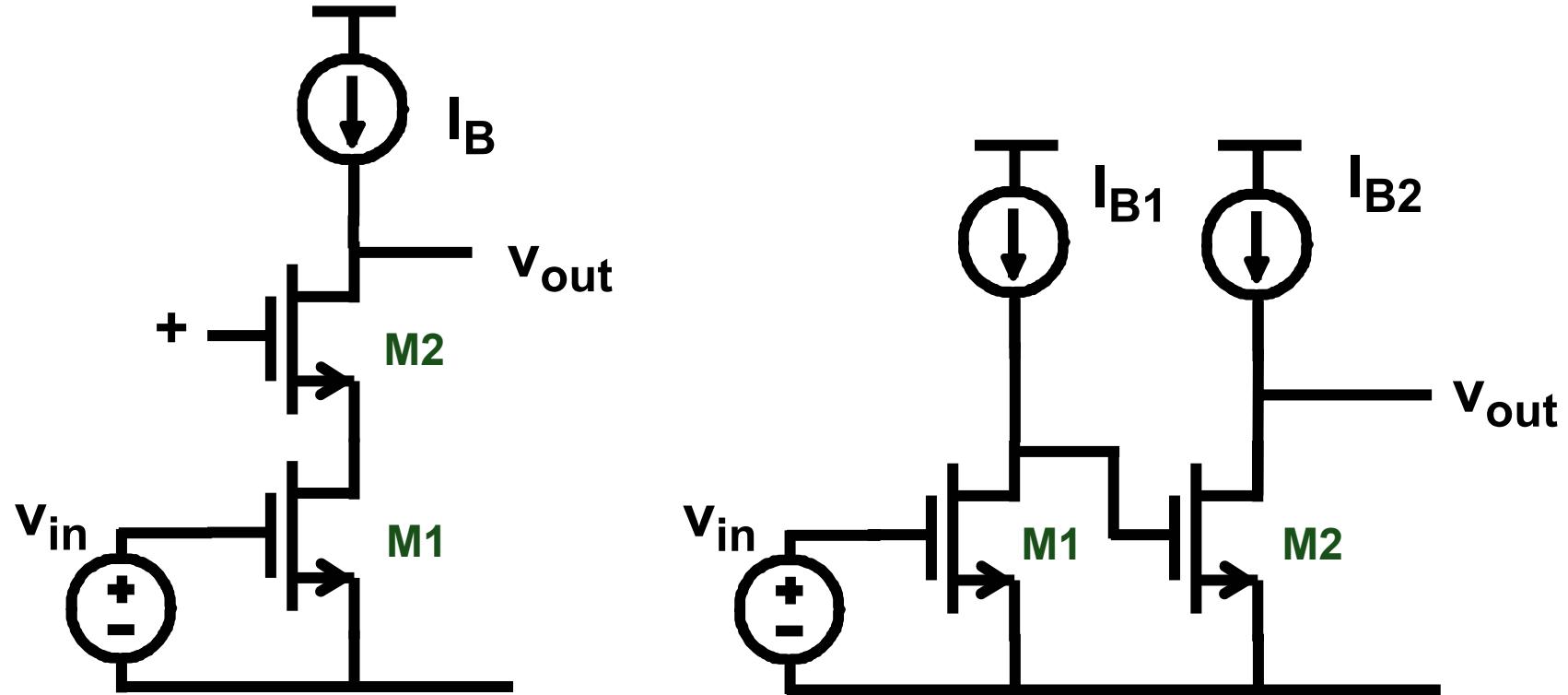


$$A_v = (g_m r_{DS})_1 (g_m r_{DS})_2$$

$$A_v = (g_m r_{DS})_1 (g_m r_{DS})_2$$

Cascode versus cascade

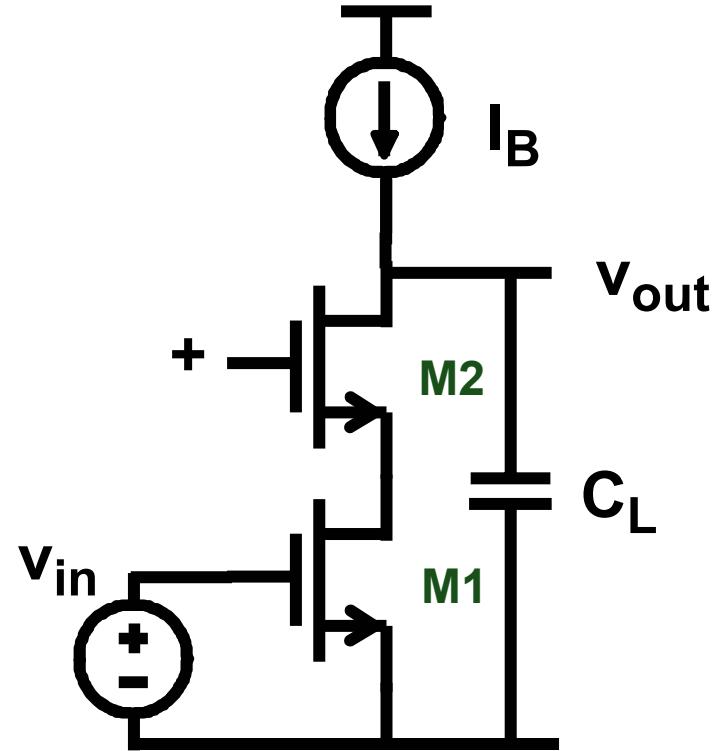

Two-stage Miller amplifier


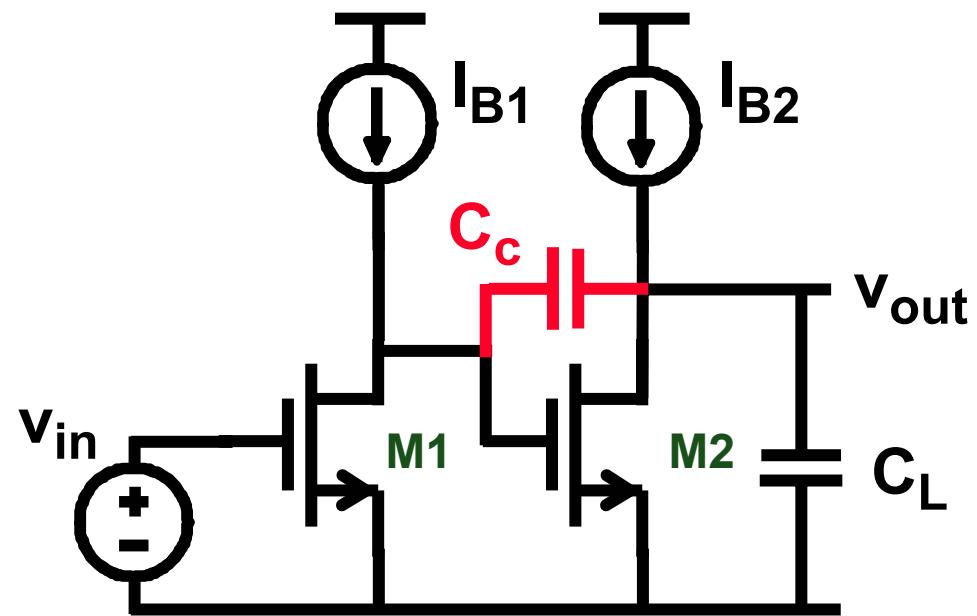


$$GBW = \frac{g_{m1}}{2\pi C_L}$$

$$GBW = \frac{g_{m1}}{2\pi C_c}$$





Regulated cascode or gain boosting

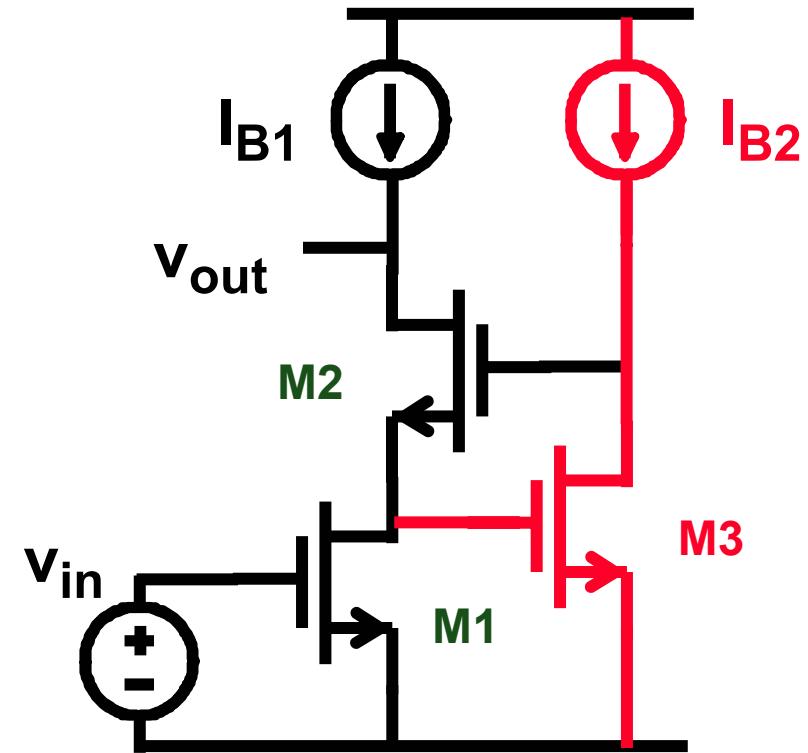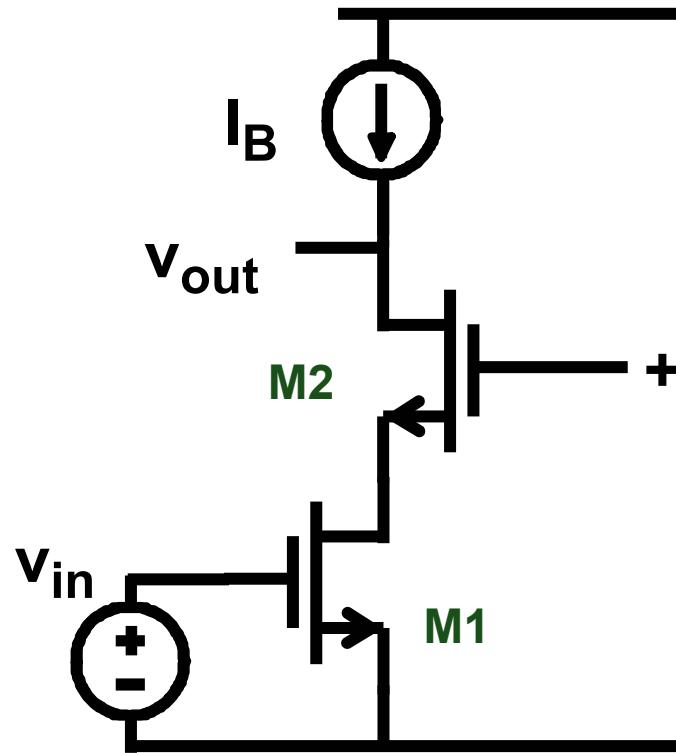


$$A_v = (g_m r_{DS})_1 (g_m r_{DS})_2 \quad A_v = (g_m r_{DS})_1 (g_m r_{DS})_2 (g_m r_{DS})_3$$

Hosticka, JSSC Dec.79, pp. 1111-1114; Sackinger, JSSC Febr.90, pp. 289-298;
Bult JSSC Dec.90, pp. 1379-1384

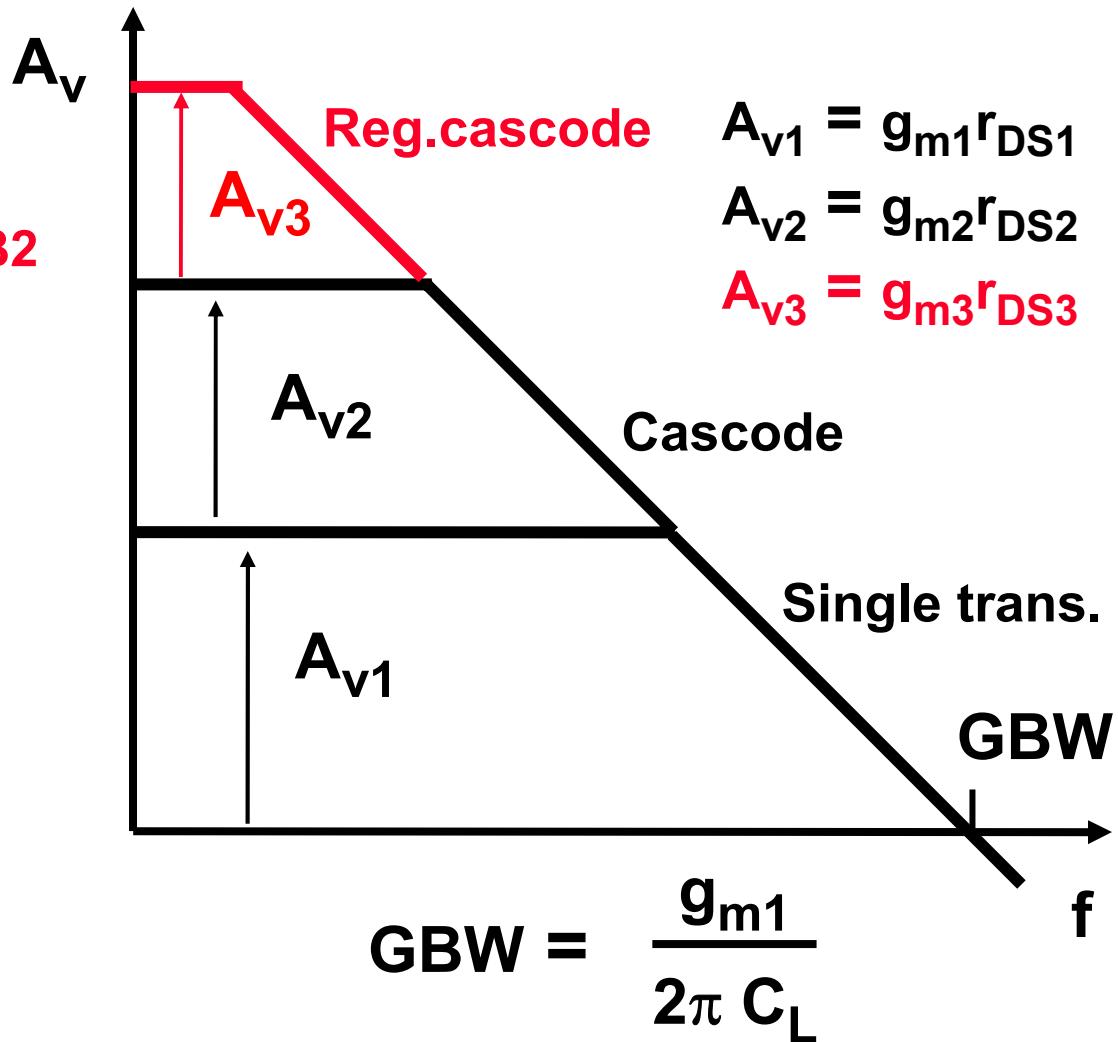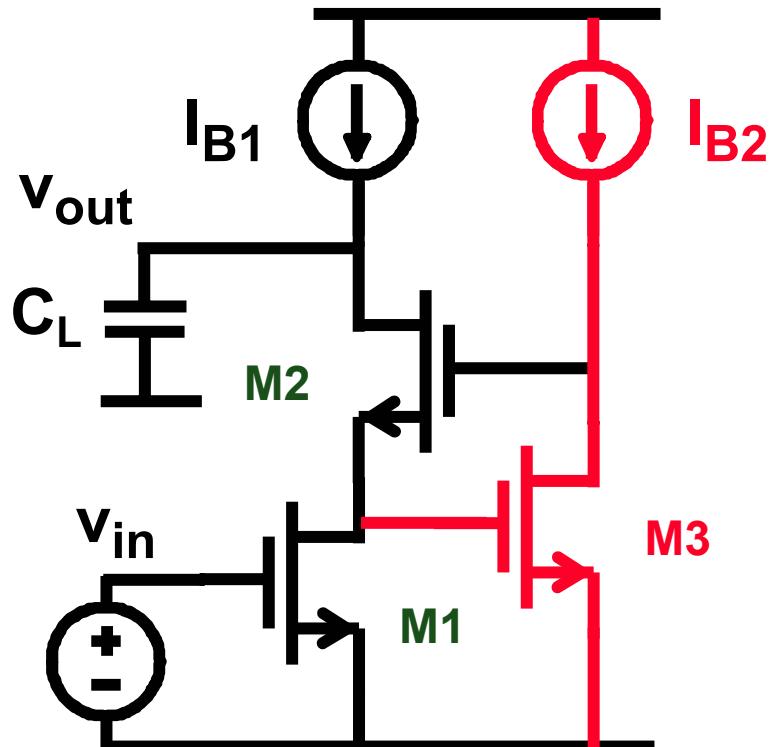
Regulated cascode, Cascode & single-transistor



Gain boosting


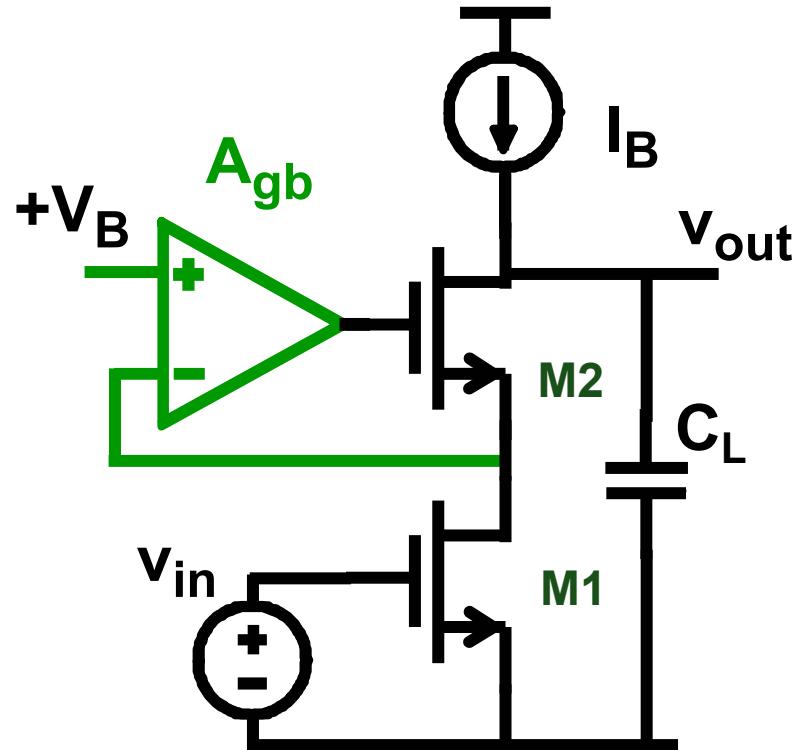

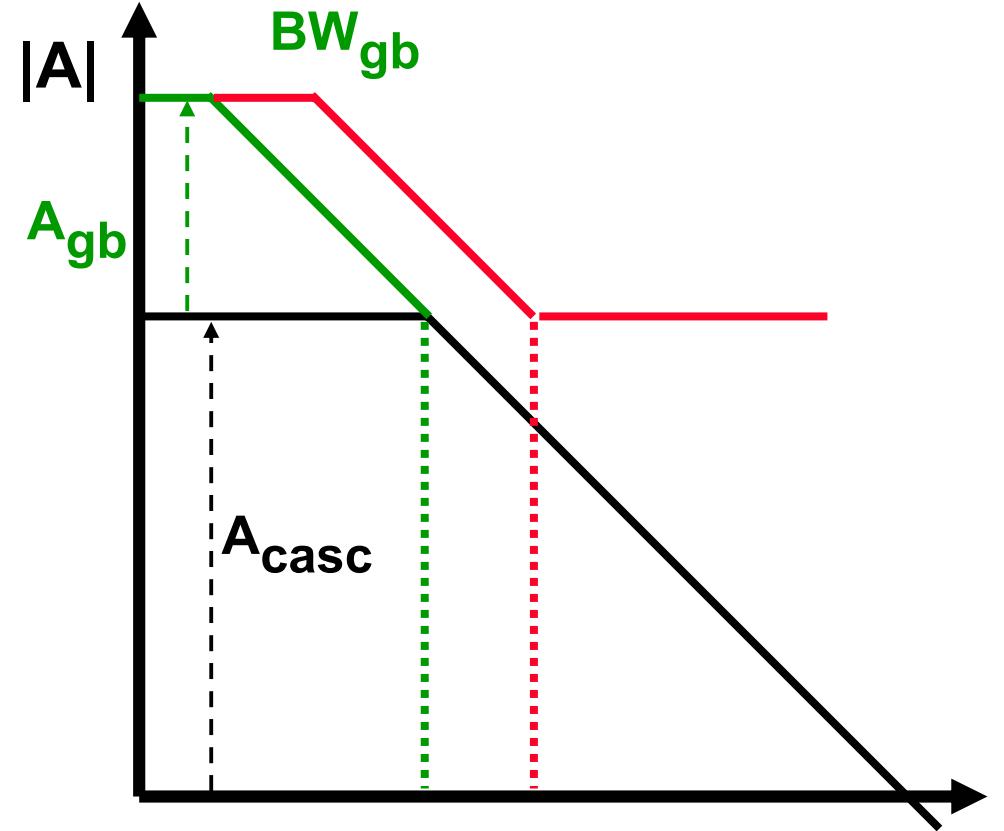
$$A_v = A_{gb} (g_m r_{DS})_1 (g_m r_{DS})_2$$



$$\frac{g_{m1}}{2\pi C_L}$$

Pole-zero doublet and settling time

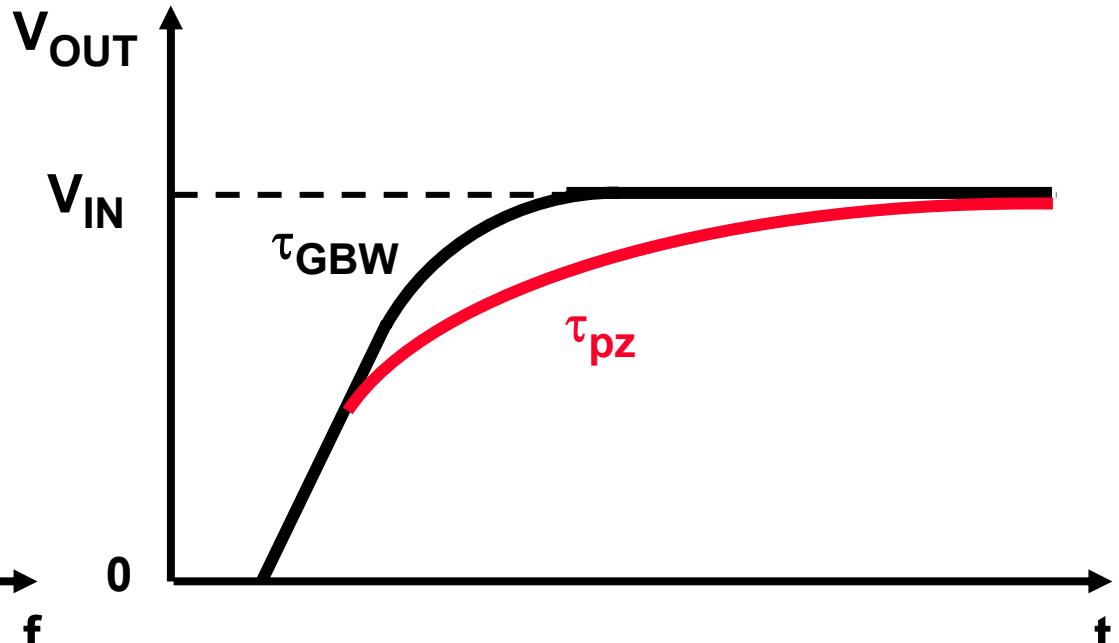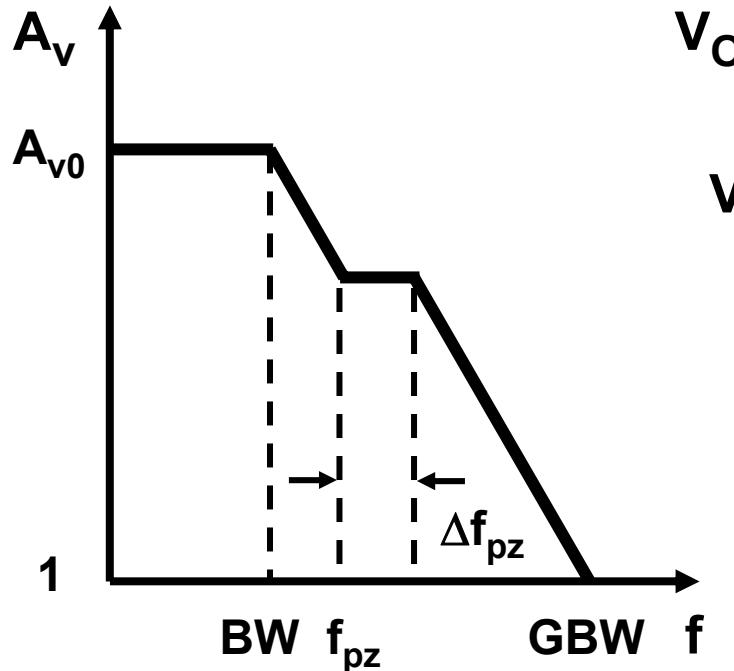


$$V_{\text{OUT}} = V_{\text{IN}} \left[1 - \exp \left(-\frac{t}{\tau_{\text{GBW}}} \right) - \frac{\Delta f_{\text{pz}}}{\text{GBW}} \exp \left(-\frac{t}{\tau_{\text{pz}}} \right) \right]$$

$$f_{\text{pz}} = \frac{1}{2\pi \tau_{\text{pz}}}$$

$$\text{GBW} = \frac{1}{2\pi \tau_{\text{GBW}}}$$


Kamath, et al, JSSC Dec.74, pp. 347-352

Single-transistor stages

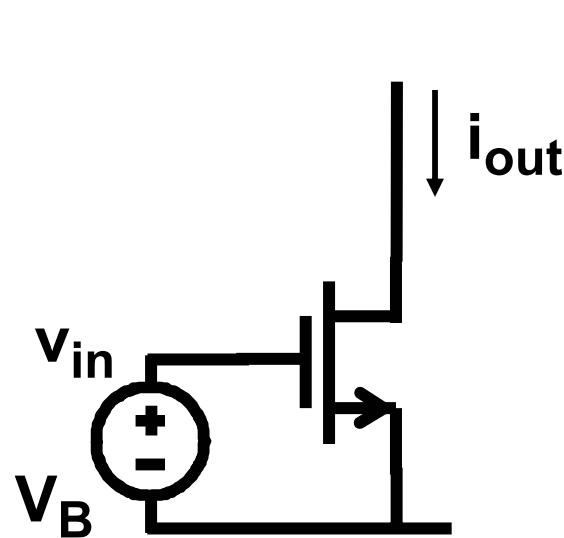

$$i_{out} = g_m v_{in}$$


Amplifier

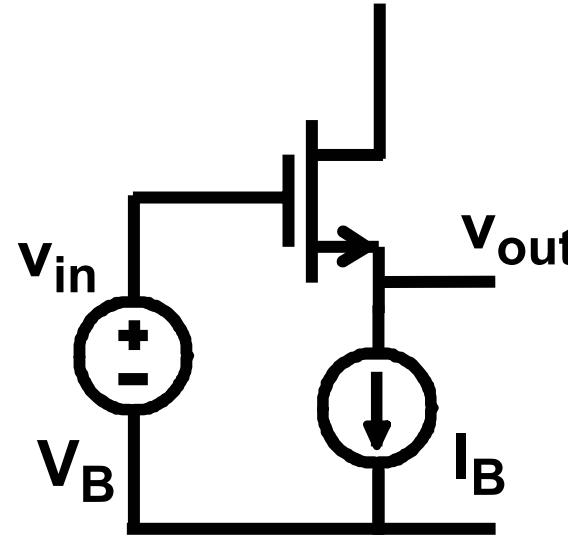

$$v_{out} = v_{in}$$

$$Z_{out} \approx 1/g_m$$

Source follower


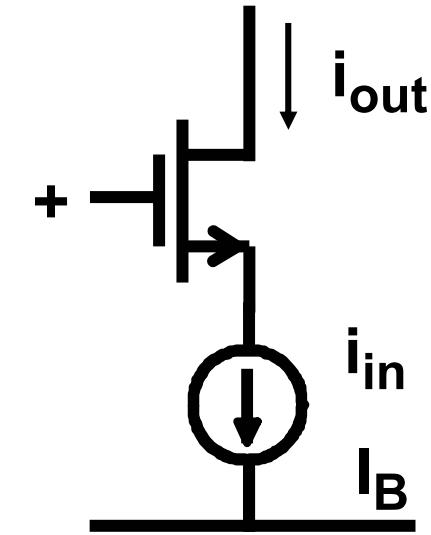


$$i_{out} = i_{in}$$


$$Z_{in} \approx 1/g_m$$

Cascode

MOST amplifier & follower

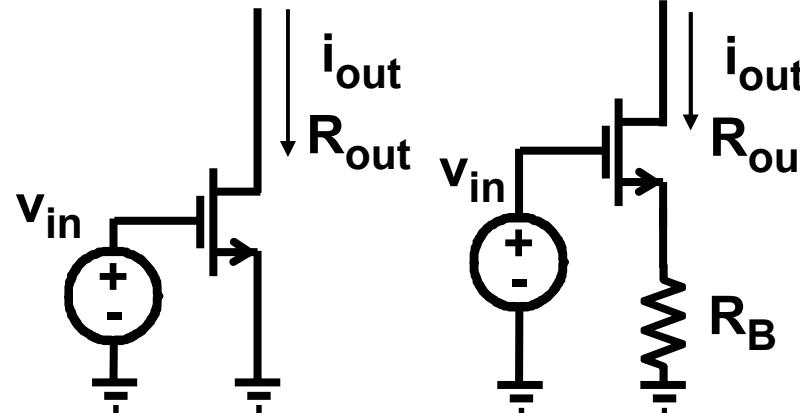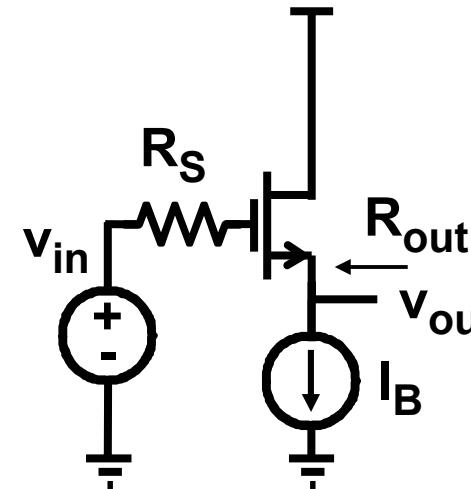	$R_B > 1/g_m$		$R_B > 1/g_m$
A_G	g_m	$1/R_B$	A_V
R_{in}	∞	∞	∞
R_{out}	r_o	$g_m R_B r_o$	$1/g_m$

Bipolar transistor ($\beta \gg 1$)

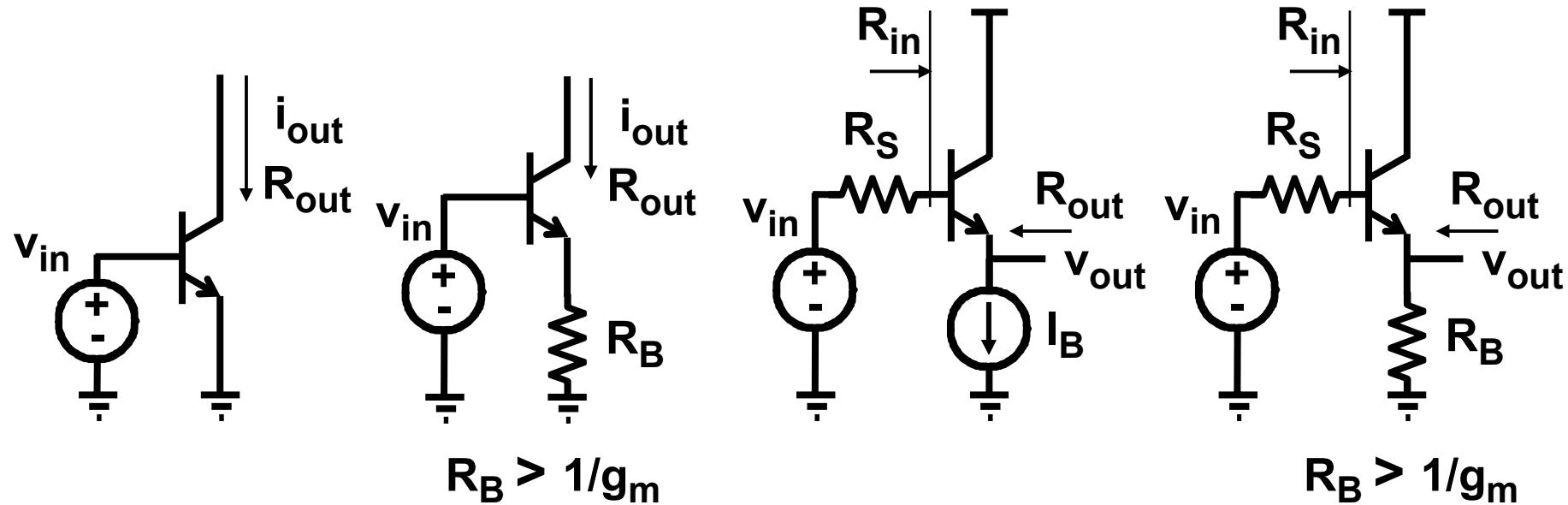

A_G

g_m

$1/R_B$

A_V

1

1

R_{in}

$r_B + r_\pi$

$r_B + r_\pi + \beta R_B$

$r_B + r_\pi + \beta r_o$

$r_B + r_\pi + \beta R_B$


R_{out}

r_o


$g_m R_B r_o$

$1/g_m + R_S/\beta$



In- & output resistances MOST cascode

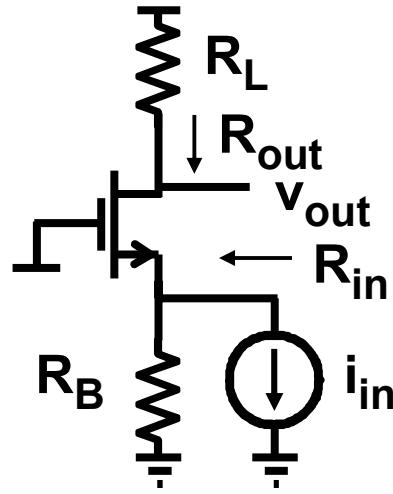

$$R_B > 1/g_m$$

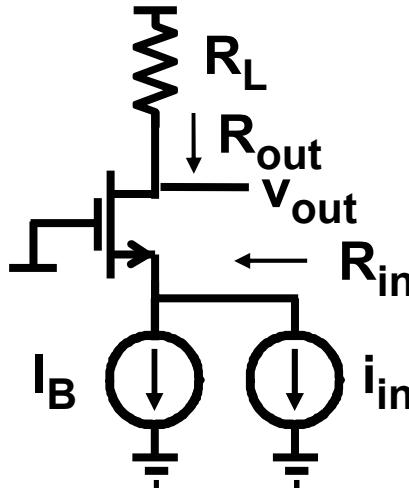

$$R_B > 1/g_m$$

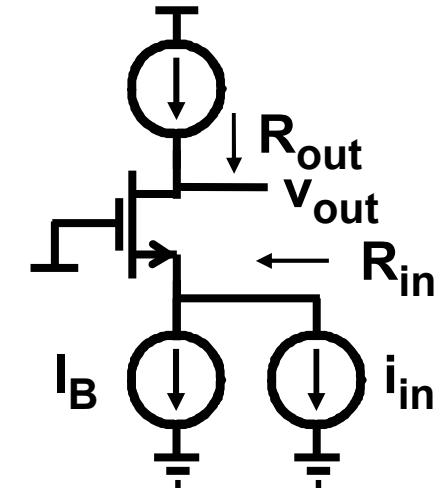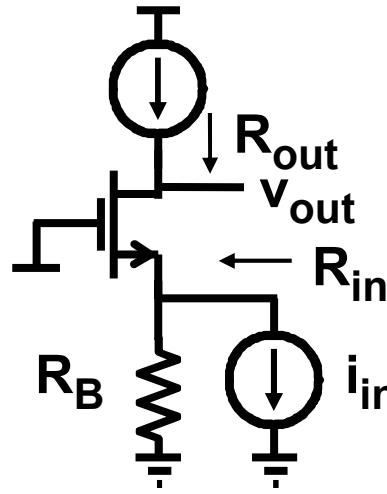

A_R

R_L

R_L

g_mr_oR_B

-

R_{in}

1/g_m

1/g_m

R_B

∞

R_{out}


g_mr_oR_B

∞


g_mr_oR_B

∞


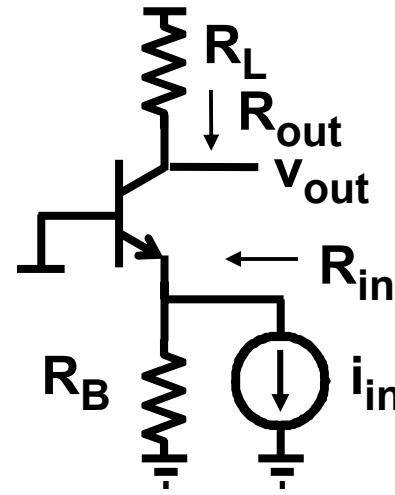
In- & output resistances Bipolar trans. cascode



$$R_B > 1/g_m$$

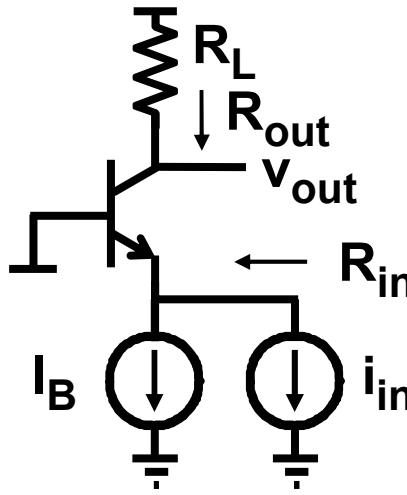

$$R_B > 1/g_m$$

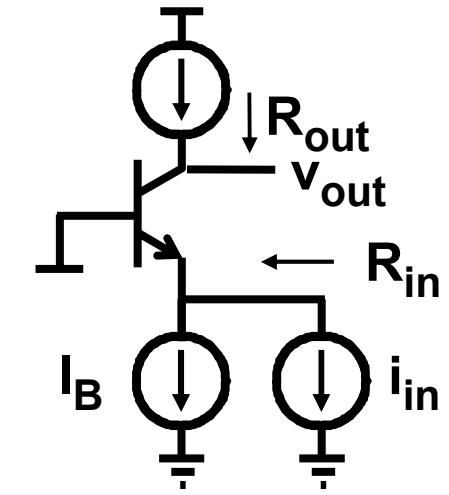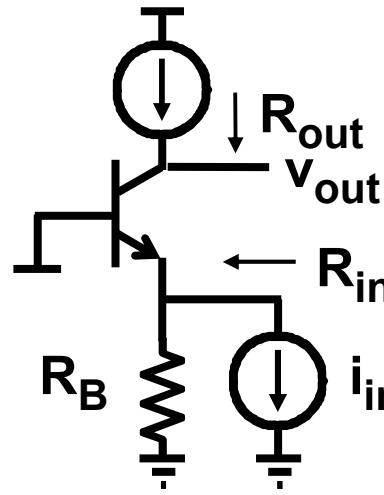

A_R

R_L

R_L

$g_m r_o R_B$

-

R_{in}

$1/g_m$

$1/g_m$

$R_B // (r_B + r_\pi)$

$r_B + r_\pi$

R_{out}


$g_m r_o R_B$

$\approx \beta r_o$

$g_m r_o (R_B // (r_B + r_\pi))$


$\approx \beta r_o$

Calculation of AR for a MOST cascode

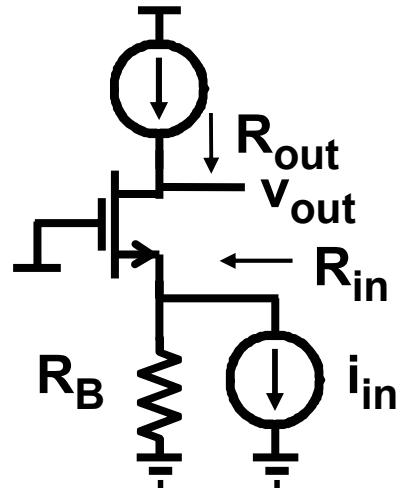

$$R_B > 1/g_m$$

$$A_R = g_m r_o R_B$$

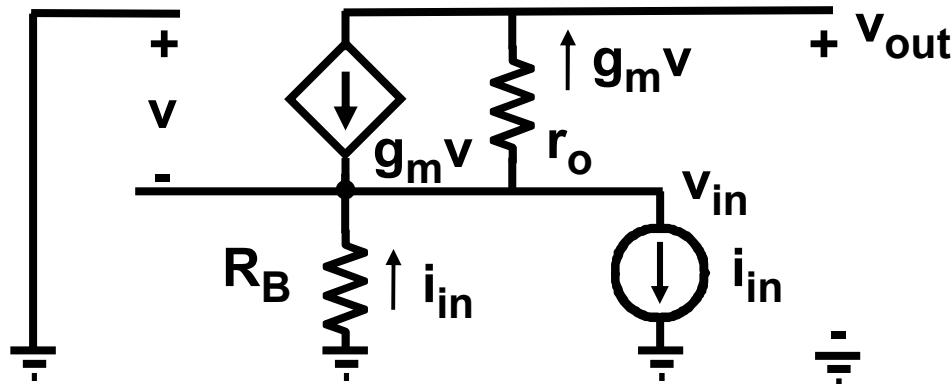

$$v = -v_{in}$$

$$v_{out} = v_{in} - g_m v r_o$$

$$v_{in} = -R_B v_{in}$$

yields $v_{out} = -R_B i_{in} (1 + g_m r_o)$

and $g_m r_o \gg 1$

Table of contents

- Single-transistor amplifiers**
- Source followers**
- Cascodes**