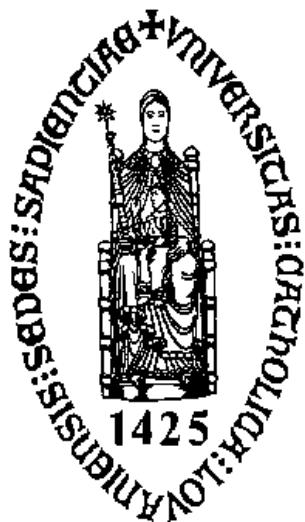


---

---

# Differential Voltage & Current amplifiers




**Willy Sansen**

**KULeuven, ESAT-MICAS  
Leuven, Belgium**

**willy.sansen@esat.kuleuven.be**




# Two-transistor circuits

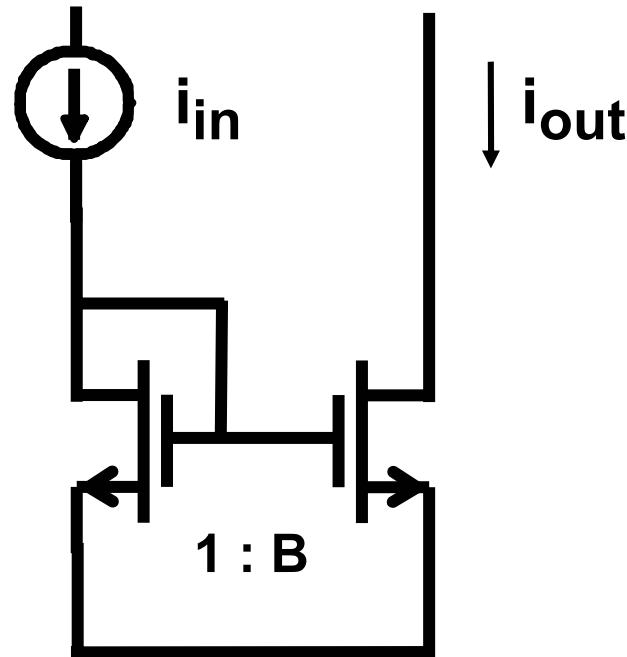

$$i_{out} = B i_{in}$$

Current mirror/amp.

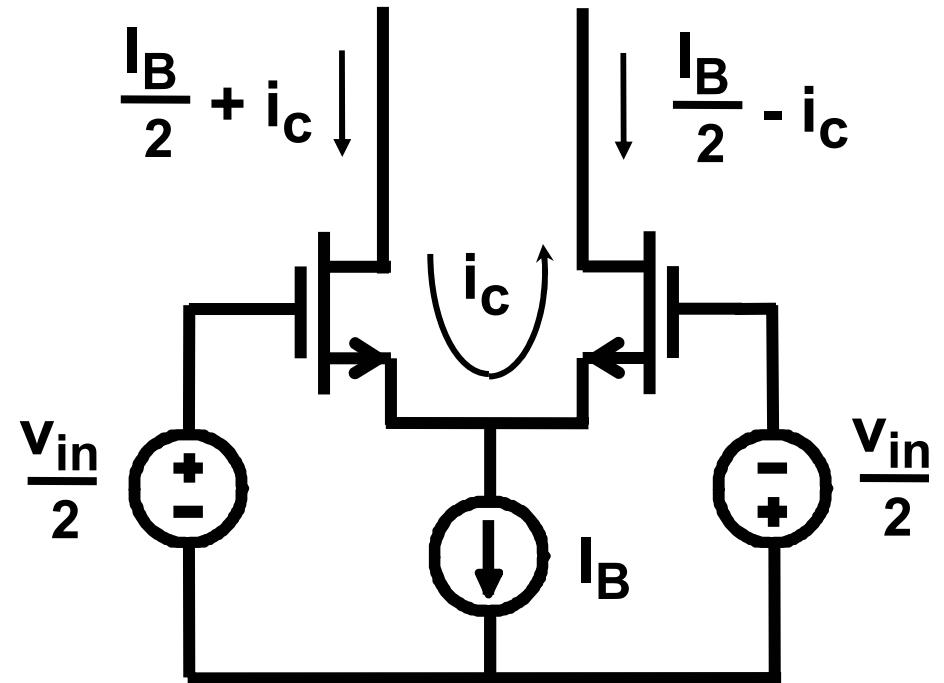

$$i_c = g_m \frac{v_{in}}{2}$$

Differential Voltage amp.


---

# Table of contents


---

- Current mirrors
- Differential pairs
- Differential voltage and current amps


# Diode-connected MOST

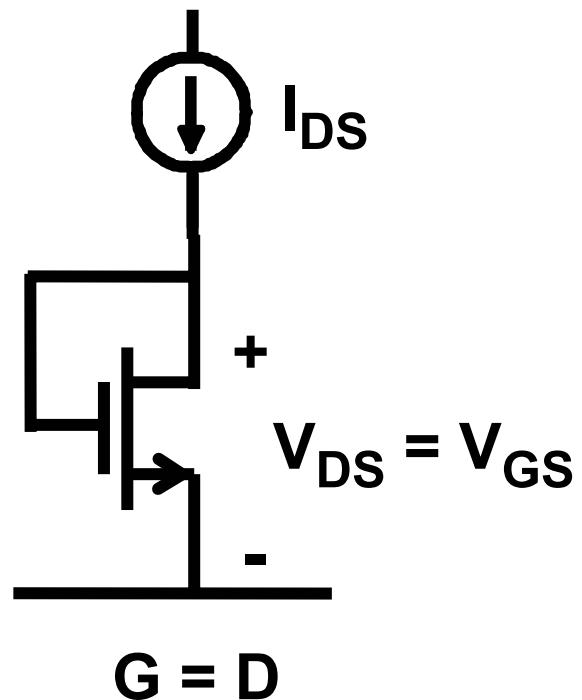
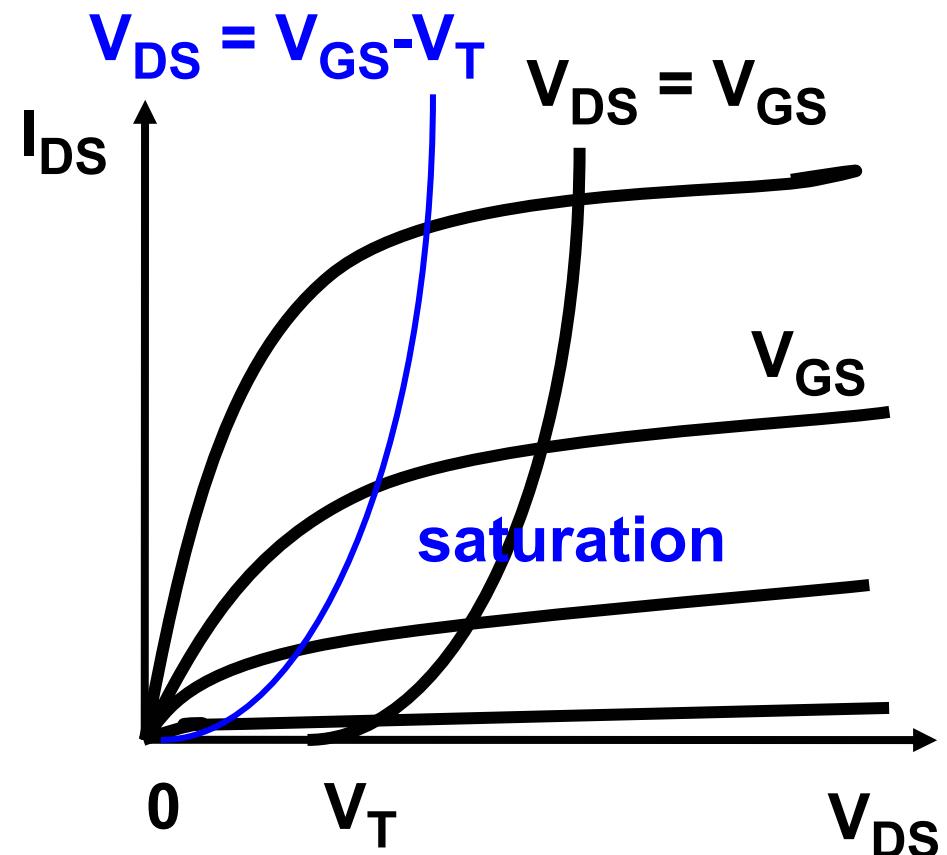
$$I_{DS} = K'_n \frac{W}{L} (V_{DS} - V_T)^2$$
$$g_m = dI_{DS} / dV_{DS}$$




# Current mirror

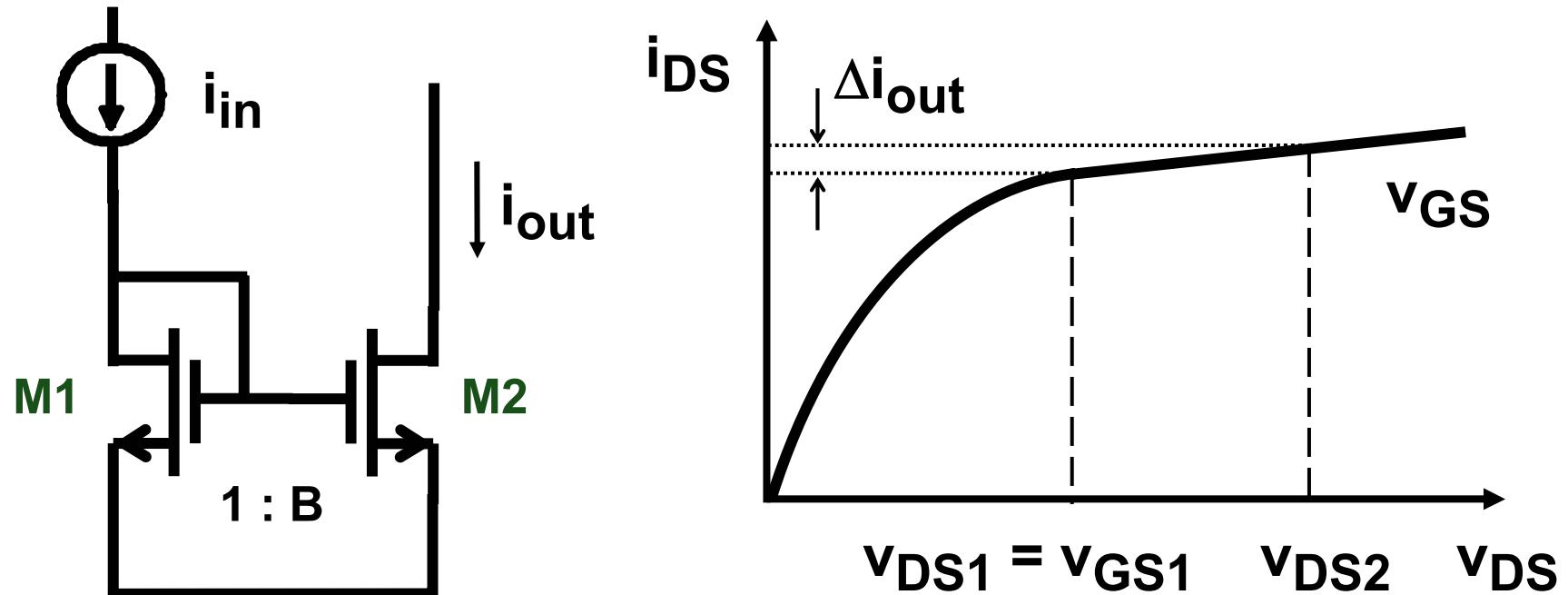



$$i_{out} = B i_{in}$$

$$\frac{\Delta i_{out}}{i_{out}} = \frac{v_{DS2} - v_{DS1}}{V_{EL2}}$$

# Improved current mirrors

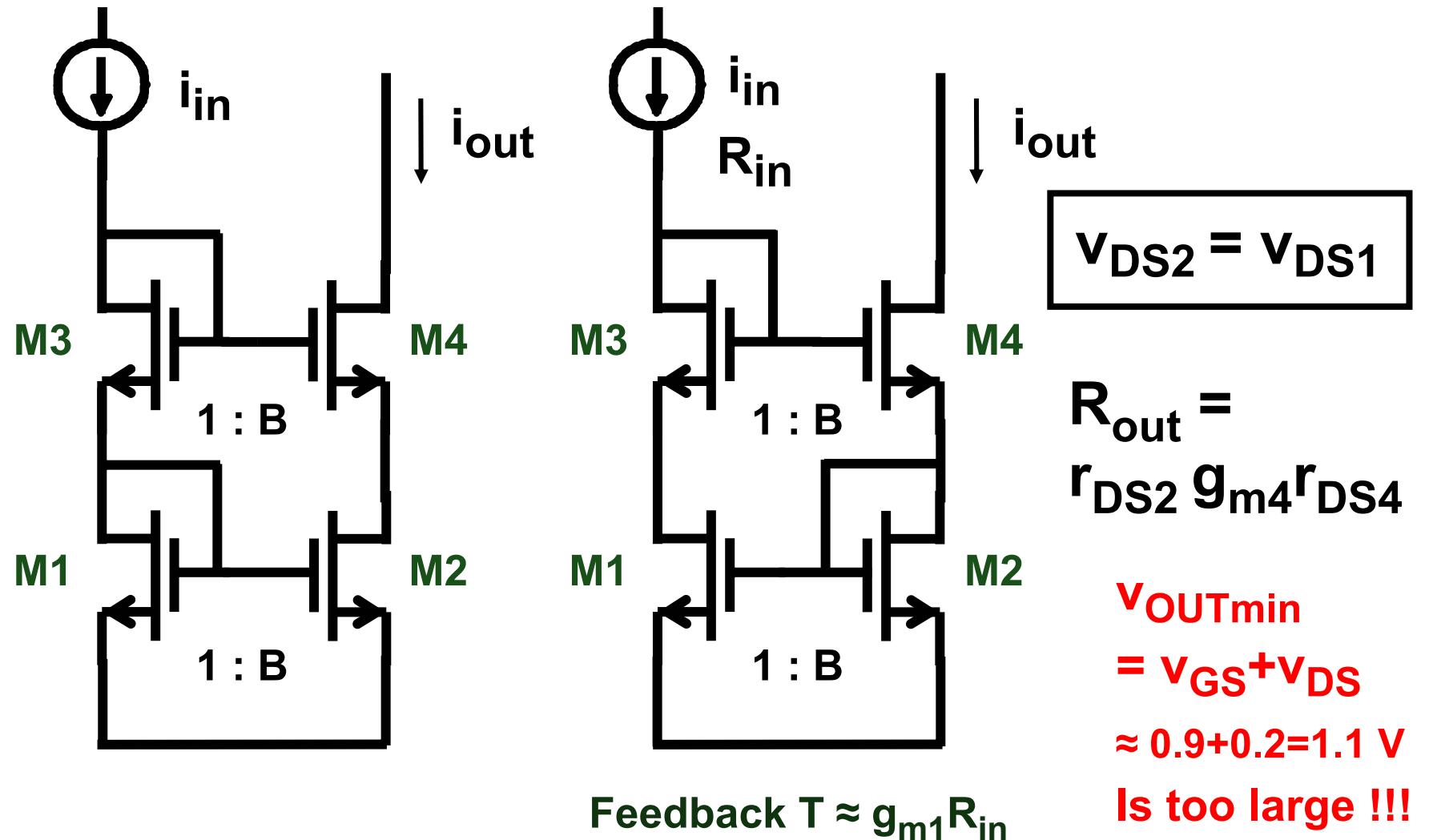

# Low-voltage current mirror

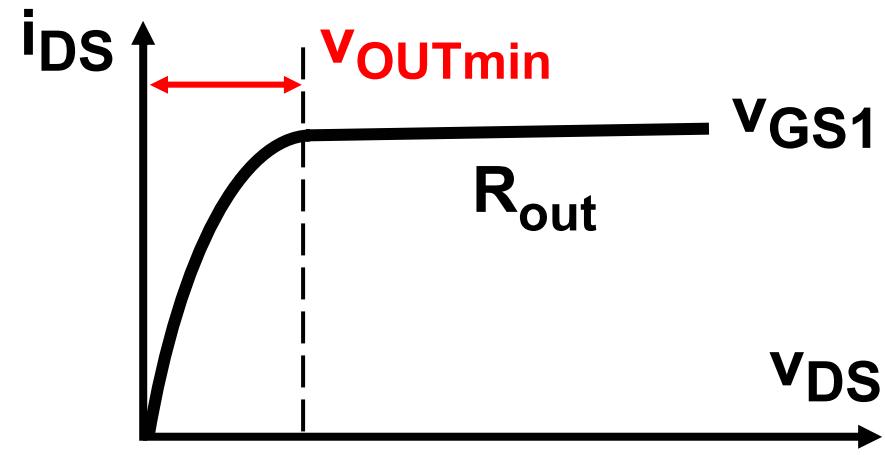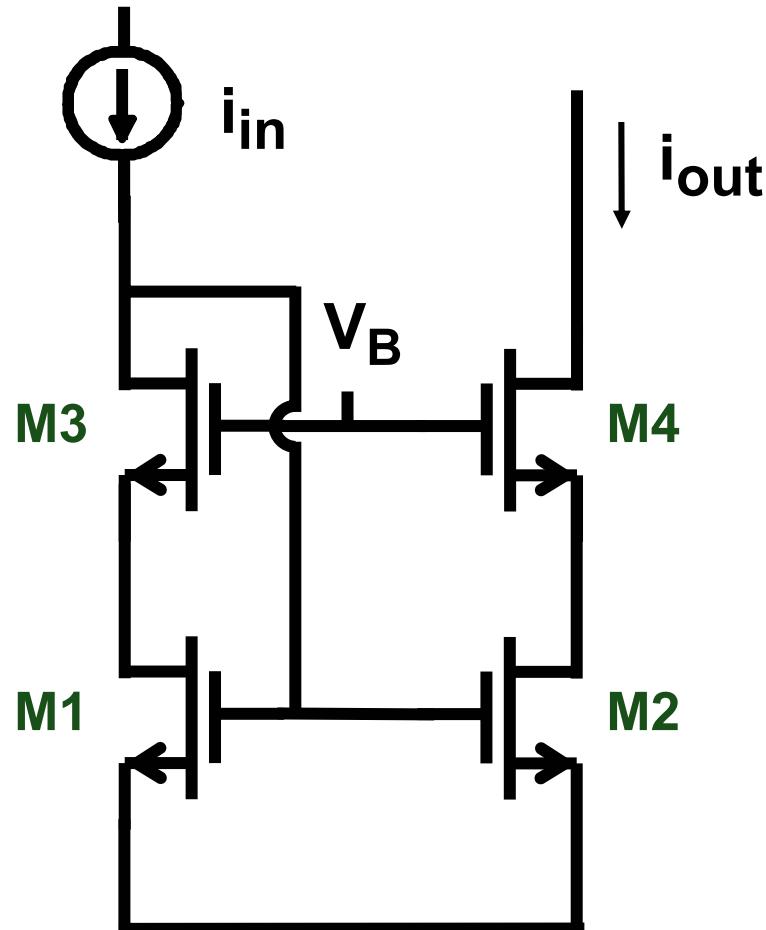


$$V_{DS2} = V_{DS1}$$

$$R_{out} = r_{DS2} g_{m4} r_{DS4}$$


$$V_{OUTmin} = V_{DS2} + V_{DS4}$$

**≈ 0.2 + 0.2 = 0.4 V is low !**

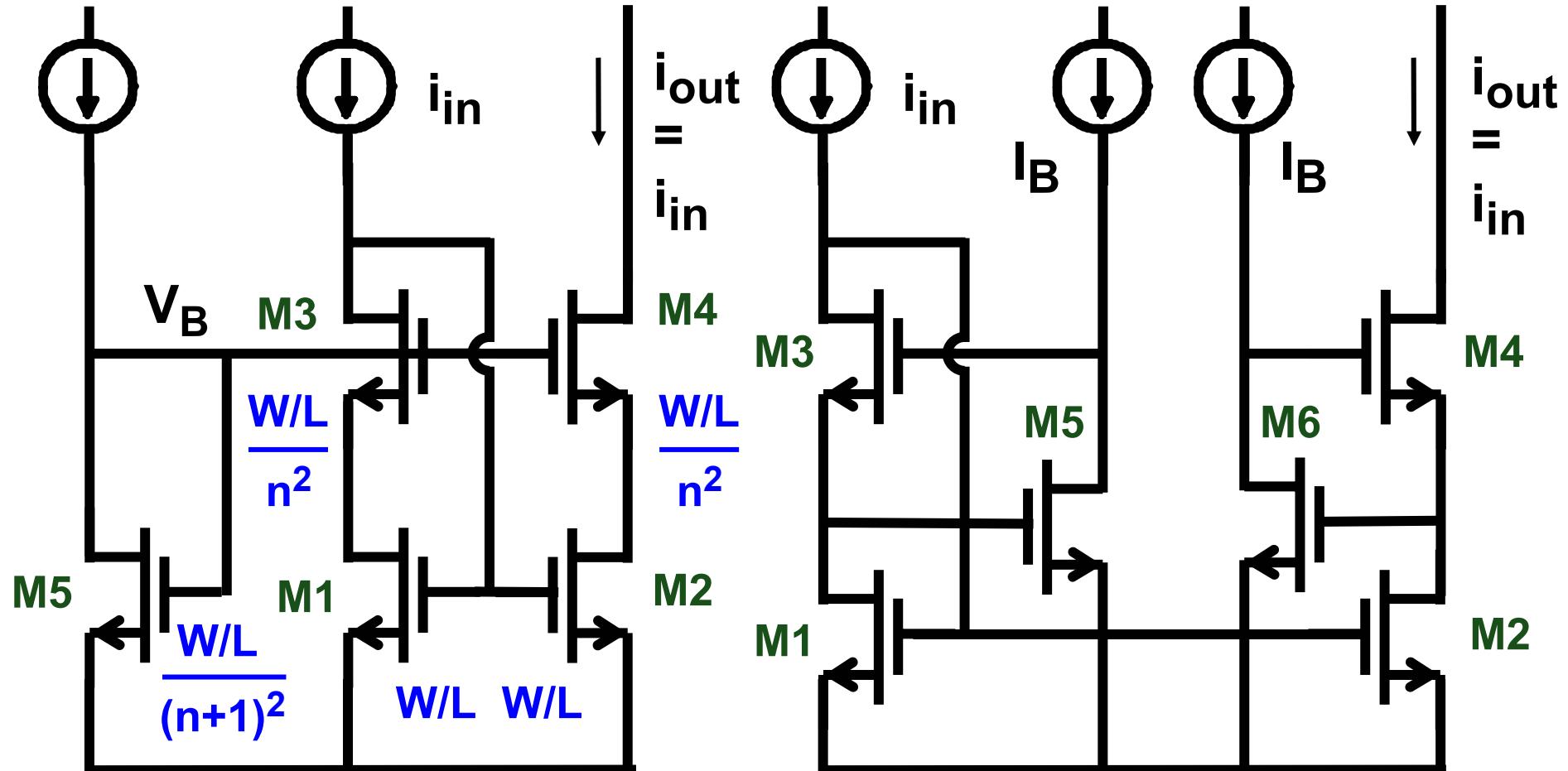
# Examples of low-voltage current mirrors






# Low-voltage diode-connected MOST

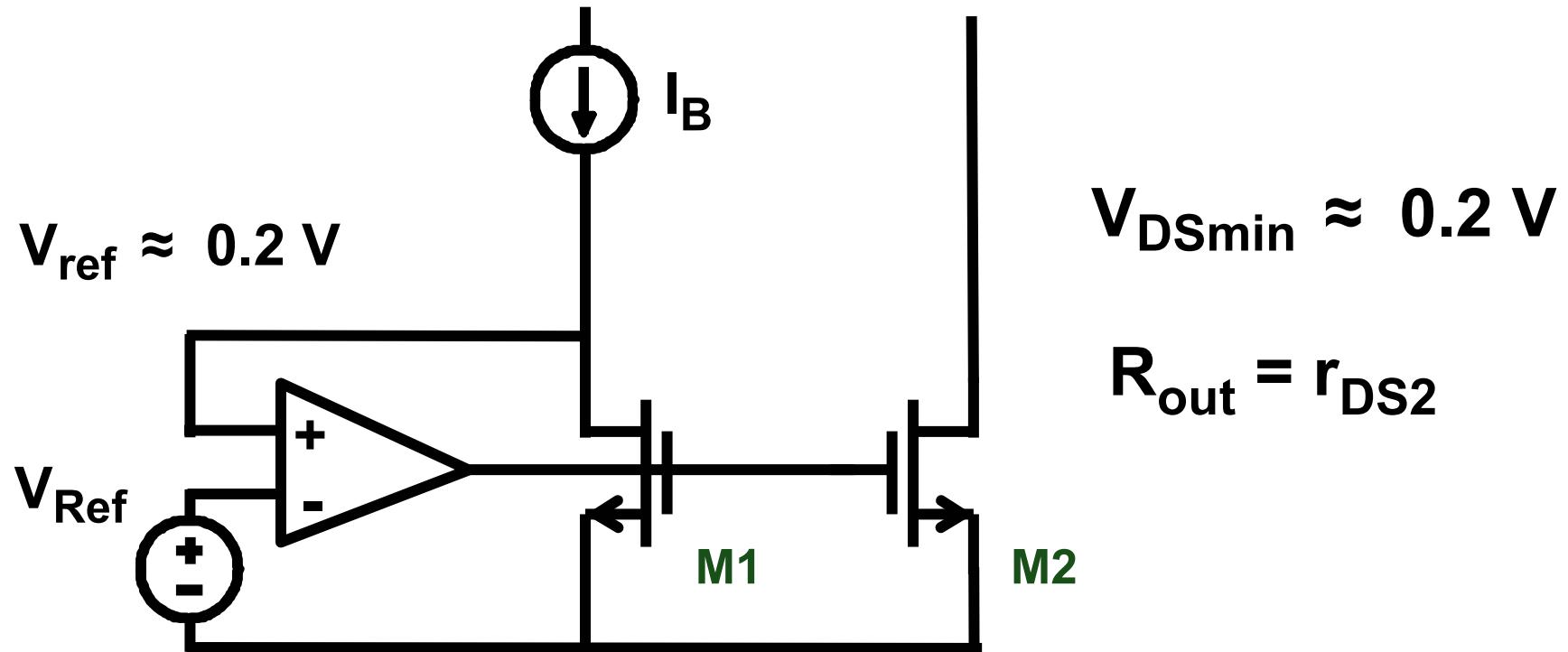

# Lowest-voltage current mirrors

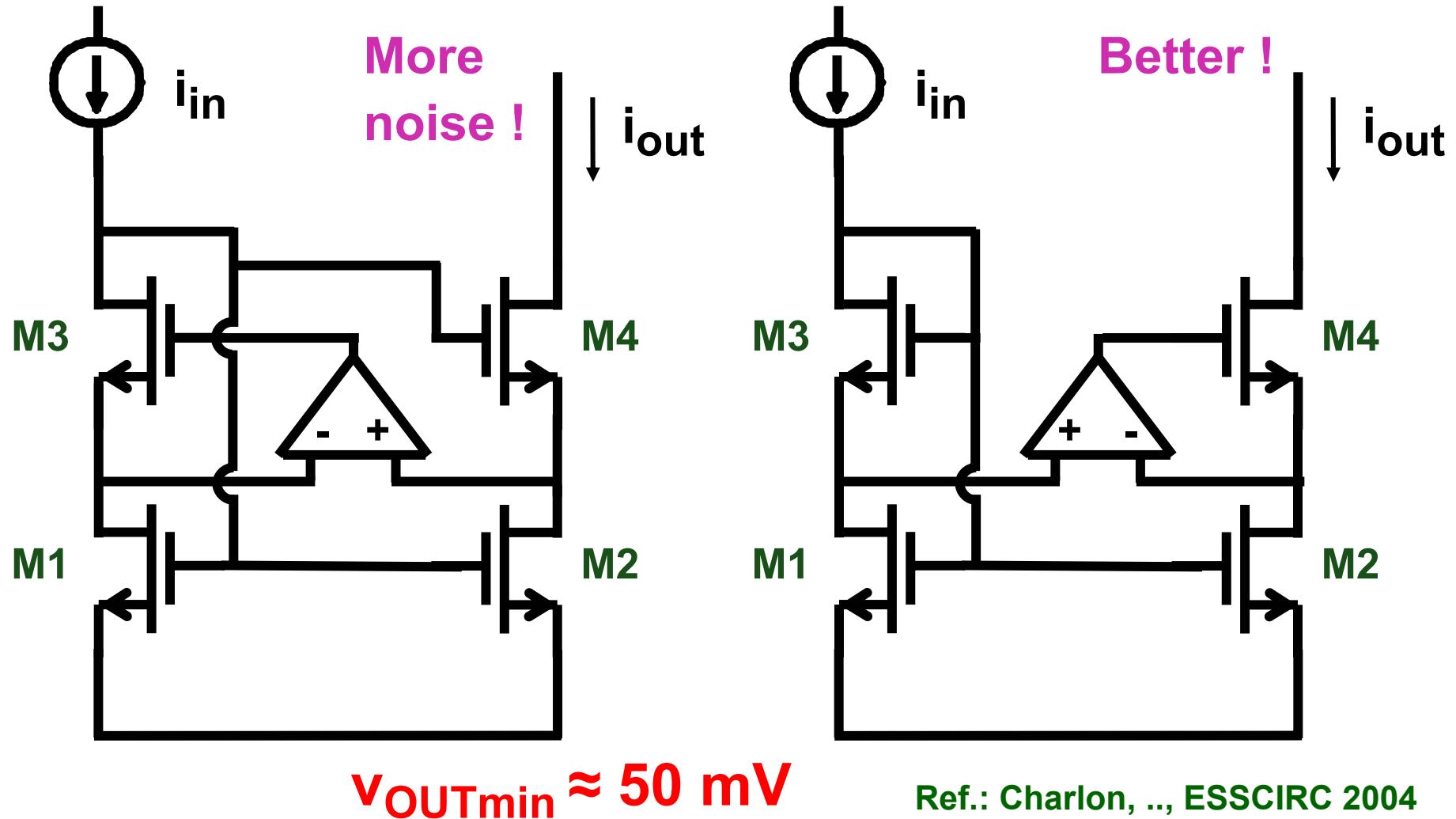

# Current mirror

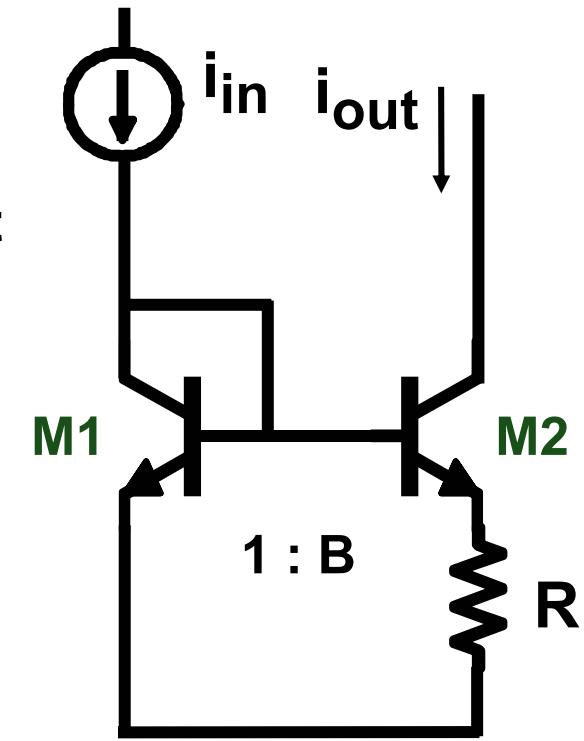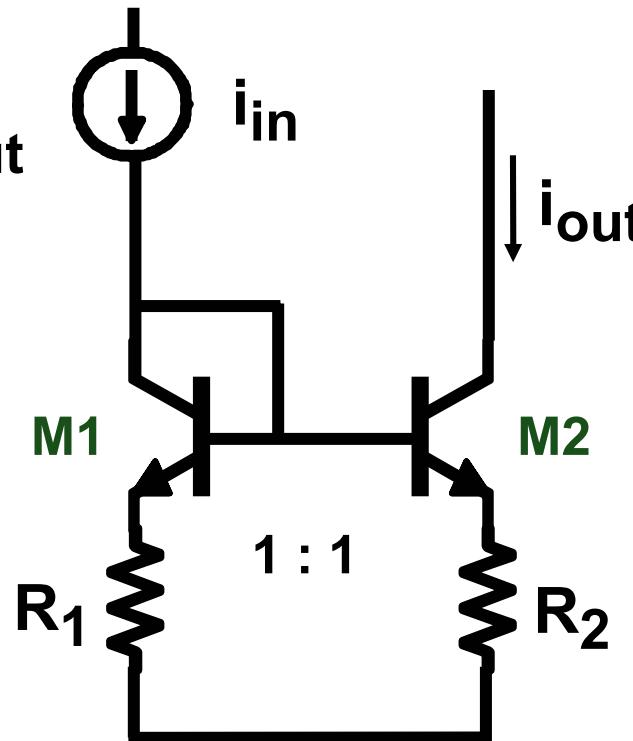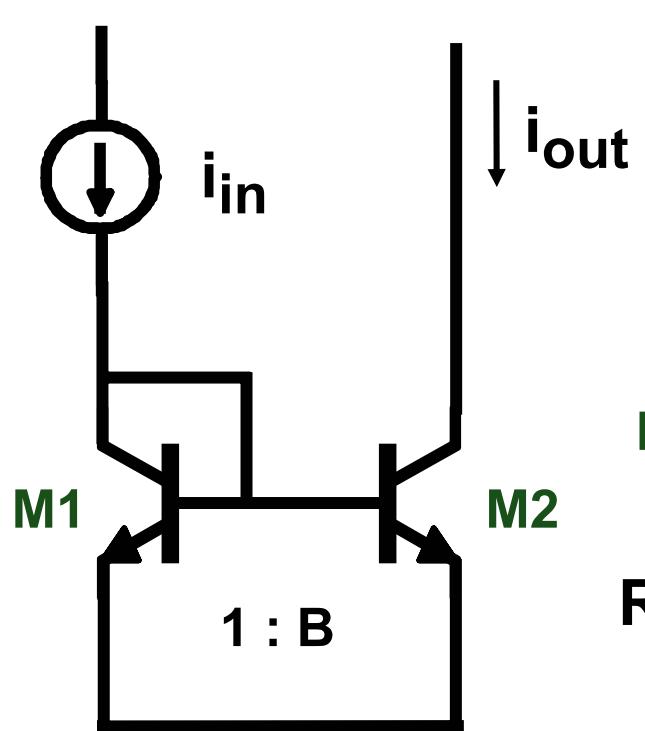


$$i_{out} = B i_{in}$$

$$\frac{i_{out}}{i_{in}} = \frac{R_1}{R_2}$$


$$i_{out} = \frac{kT/q}{R} \ln B \frac{i_{in}}{i_{out}}$$

Ref.: Widlar, JSSC Aug 69, 184-191

# Improved current mirrors


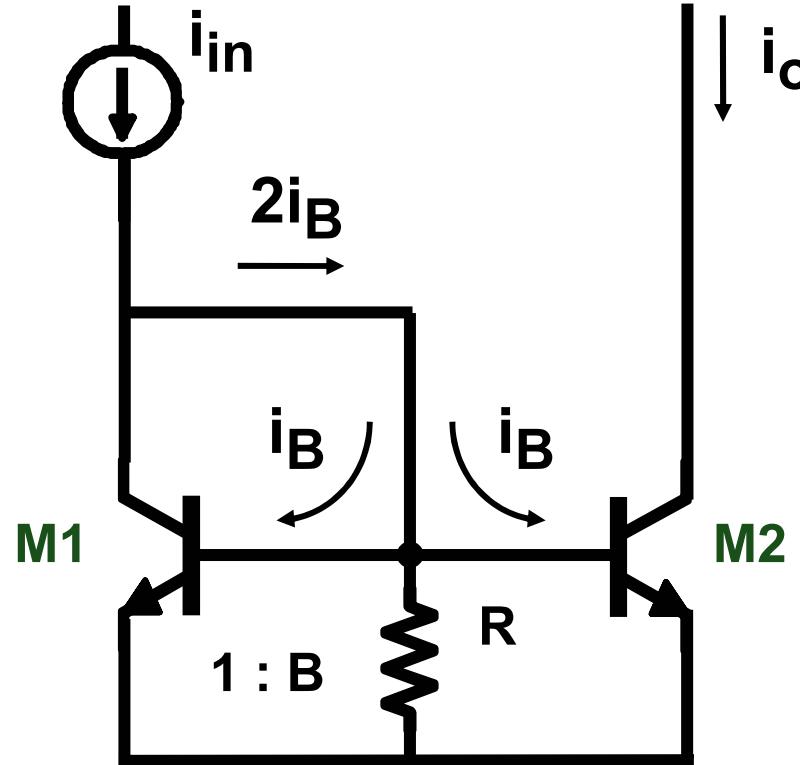


$$\text{Error} \sim \frac{2}{\beta}$$

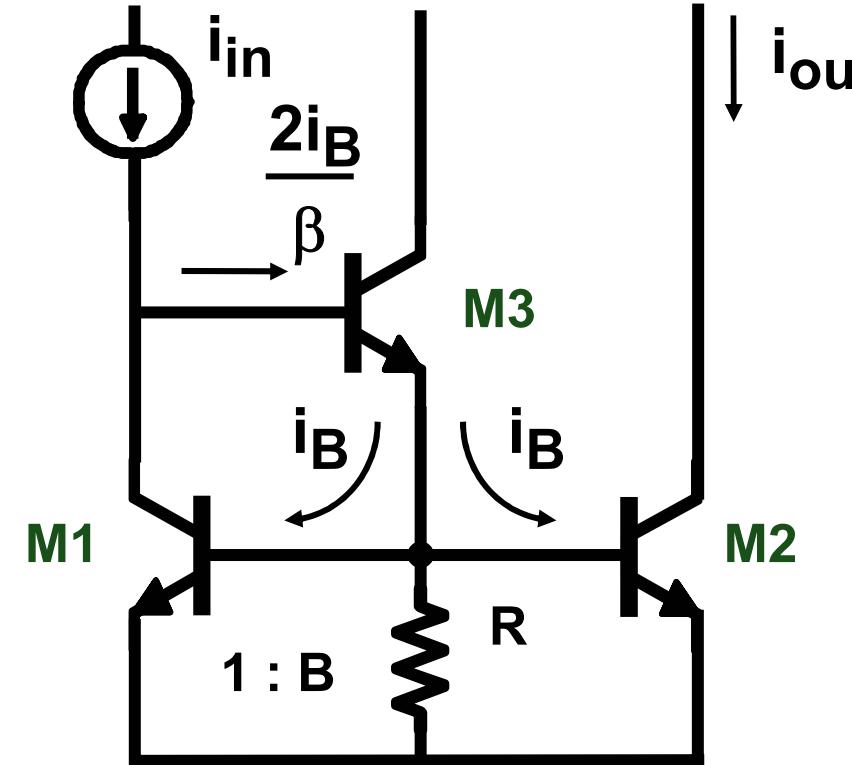

$$\text{Error} \sim \frac{2}{\beta^2}$$

# Improved current mirrors

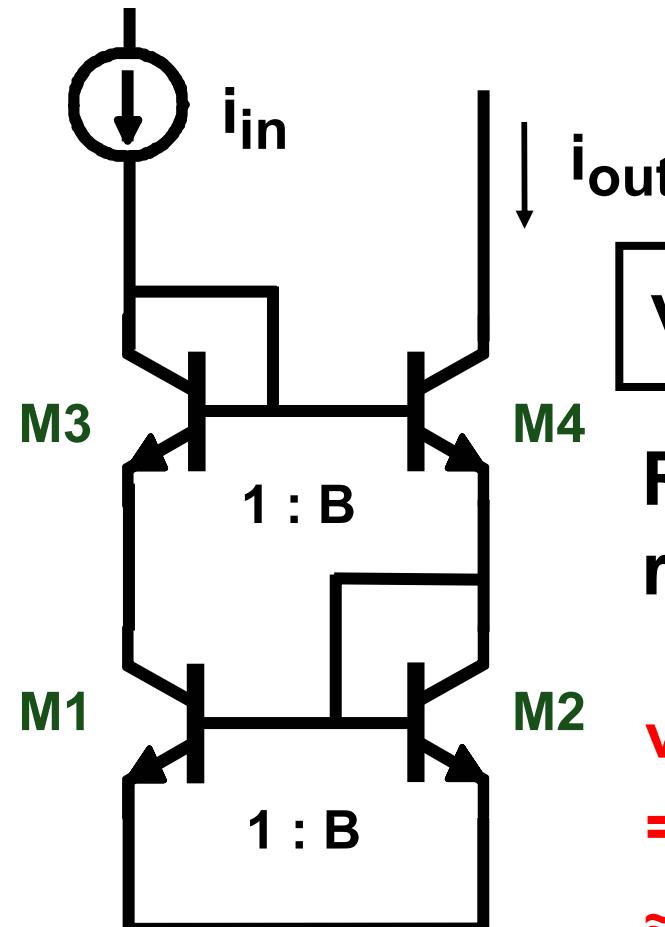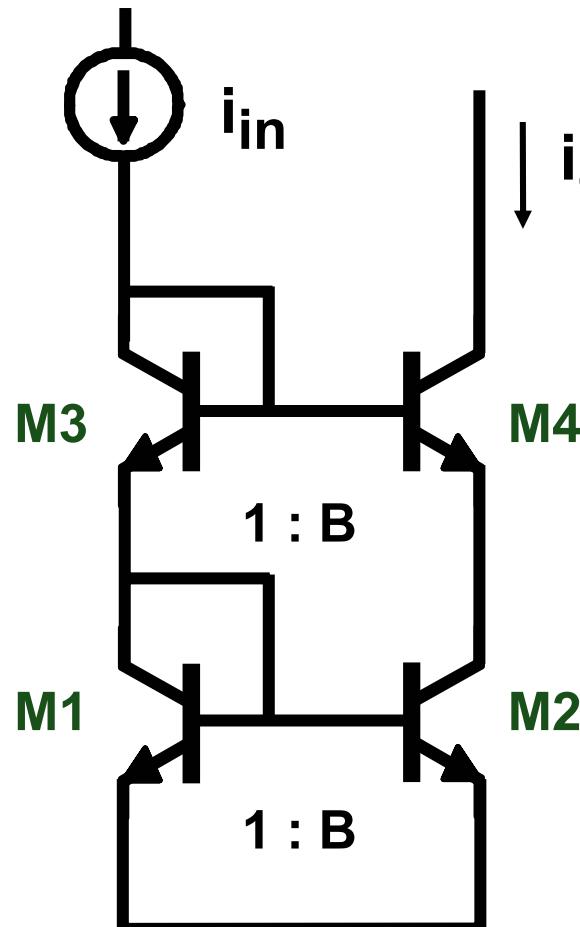

$$V_{CE2} = V_{CE1}$$


$$R_{out} = r_{o2} g_{m4} r_{o4}$$

$$\begin{aligned} V_{OUTmin} &= V_{BE} + V_{CE} \\ &\approx 0.7 + 0.1 = 0.8 \text{ V} \end{aligned}$$

Is too large !

Ref.: Wilson, JSSC Dec.68, 341-348

# Current mirror at high frequencies

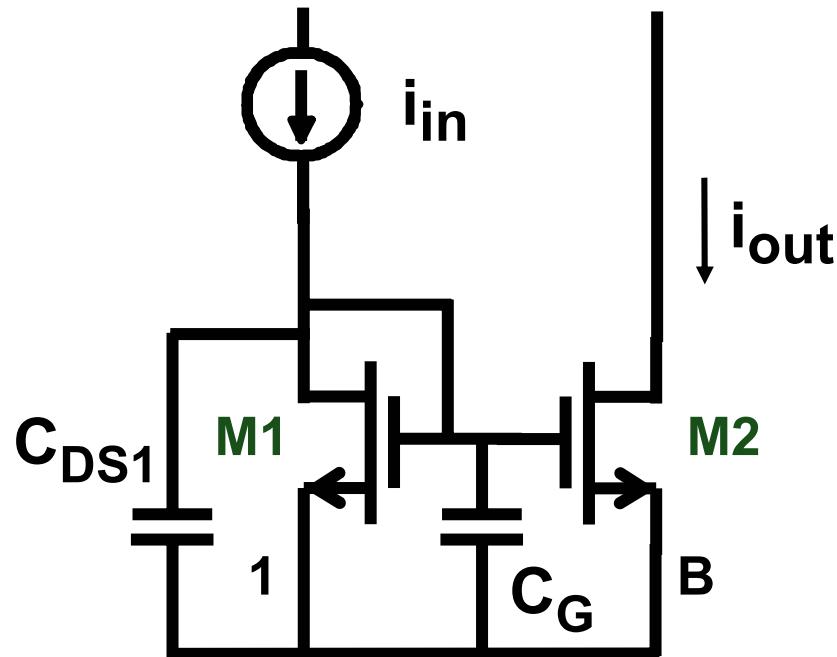

$$i_{out} = B i_{in}$$

$$R_{out} = r_{DS}$$


$$C_G = (1 + B) C_{GS} + C_{DS1}$$

$$BW = \frac{g_m}{2\pi (C_G + C_{DS1})}$$

$$\approx f_T \frac{1}{(2 + B)}$$

Ref.: Gilbert, JSSC Dec.68, 353-365

# Current Miller effect

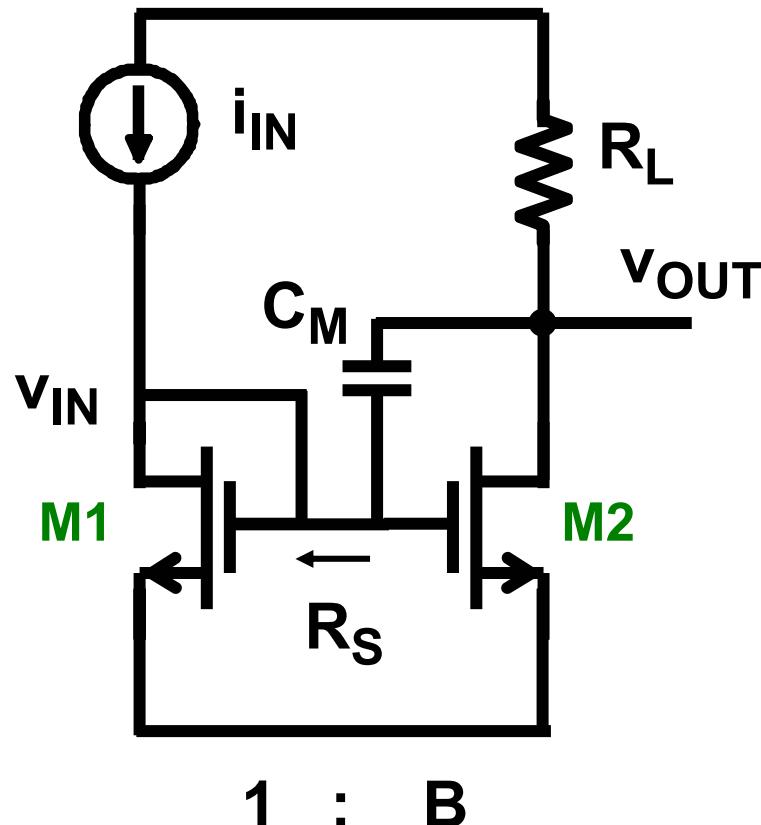

$$A_i = B$$

$$R_{IN} = \frac{1}{g_{m1}}$$


$$R_S = 1/g_{m1}$$

$$v_{IN} \approx i_{IN} R_S$$

$$B = \frac{g_{m2}}{g_{m1}}$$

Ref.: Rincon-Mora, JSSC Jan. 2000, 26-32

# Current Miller equivalent circuit

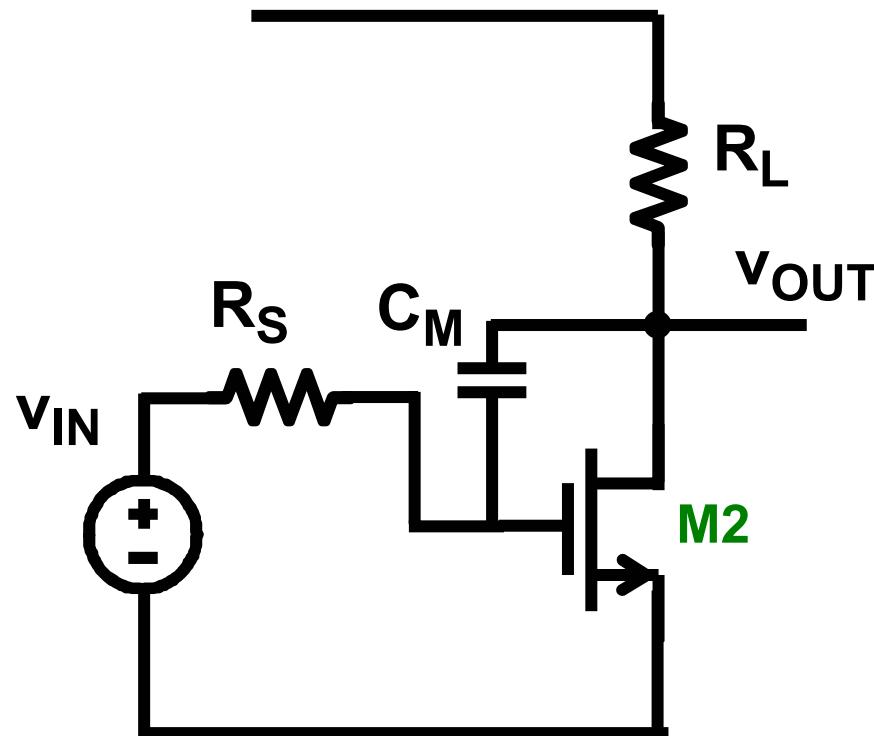

**Miller effect :**

$$f_{-3dB} = \frac{1}{2\pi R_S A_{v2} C_M}$$

$$R_S = 1/g_{m1} \quad A_{v2} = g_{m2} R_L$$

$$f_{-3dB} = \frac{1}{2\pi (1+B) C_M R_L}$$

$$f_z = - \frac{g_{m2}}{2\pi C_M}$$


---

# Table of contents

---

- Current mirrors
- Differential pairs
- Differential voltage and current amps

# Voltage differential amplifier

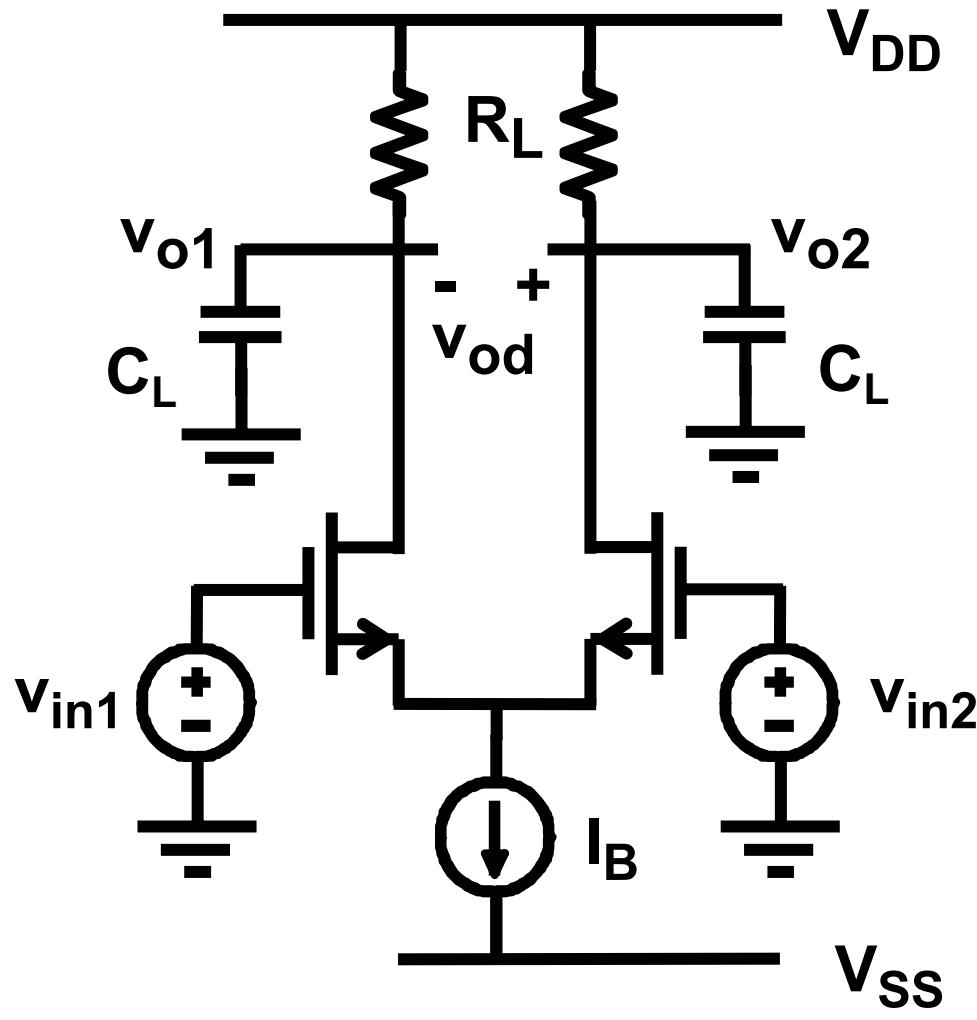

Two equal transistors

Redefine  $v_{in}$  &  $v_o$ :


$$v_{ind} = v_{in1} - v_{in2}$$

$$v_{inc} = \frac{v_{in1} + v_{in2}}{2}$$

$$v_{od} = v_{o1} - v_{o2}$$

$$v_{oc} = \dots$$

# Voltage differential amplifier : DC

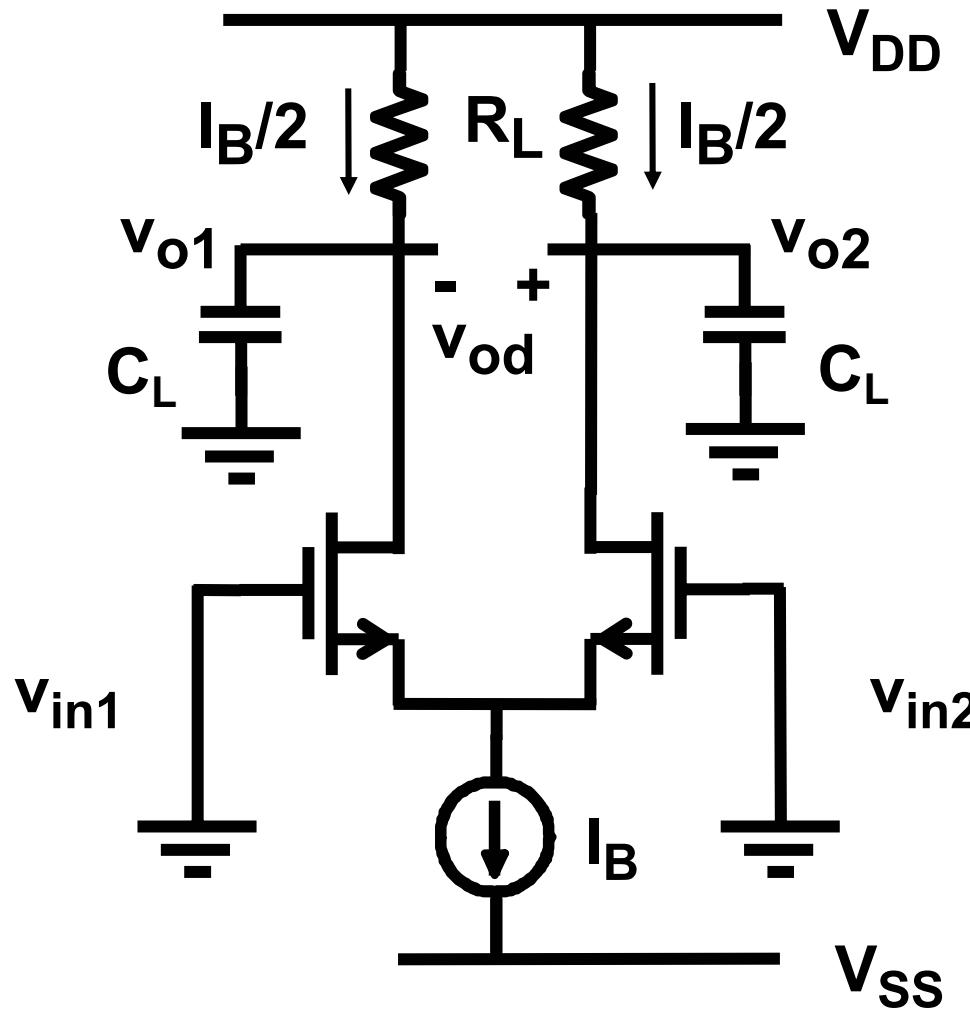


$$v_{in1} = v_{in2} = 0$$

$$\begin{aligned} v_{o1} &= v_{o2} \\ &= V_{DD} - R_L I_B / 2 \end{aligned}$$

$$v_{od} = v_{o1} - v_{o2} = 0$$
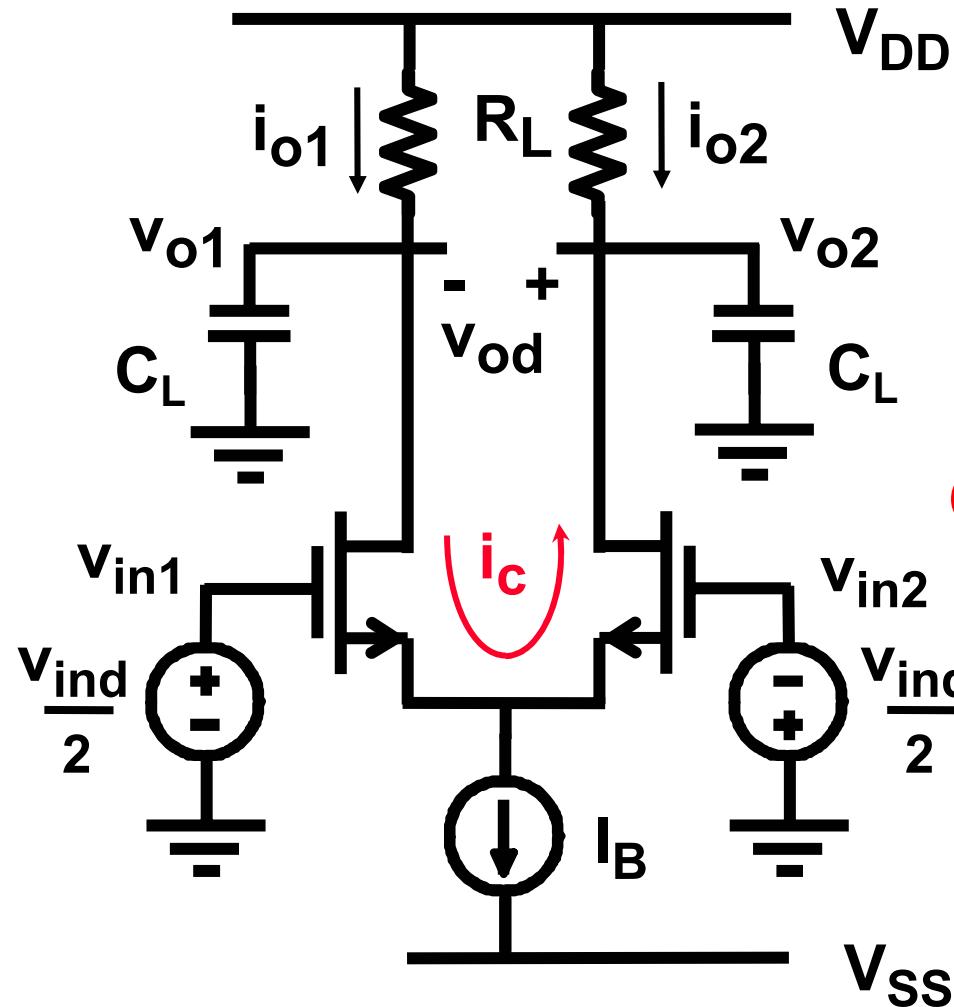
# Voltage differential amplifier : AC Gain



Differential input voltage


$$v_{ind} = v_{in1} - v_{in2}$$

Circular current  $i_c = g_m \frac{v_{ind}}{2}$

$$v_{od} = 2 R_L i_c$$

$$A_v = \frac{v_{od}}{v_{ind}} = g_m R_L$$

# Voltage differential amplifier

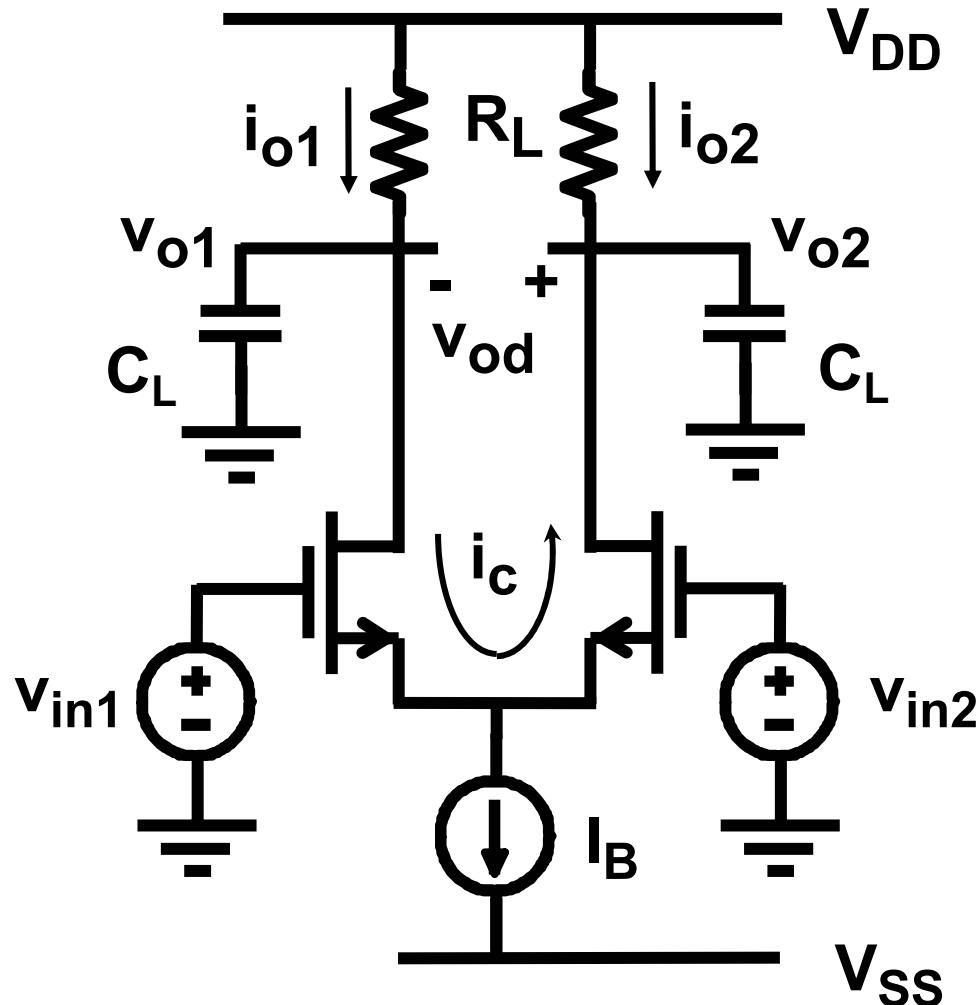

$$A_v = g_m R_L$$

Same as single-tr. !!



Independent of :

Noise on  $V_{DD}$  : PSRR<sub>DD</sub>

Noise on  $V_{SS}$  : PSRR<sub>SS</sub>



Noise on Ground : CMRR
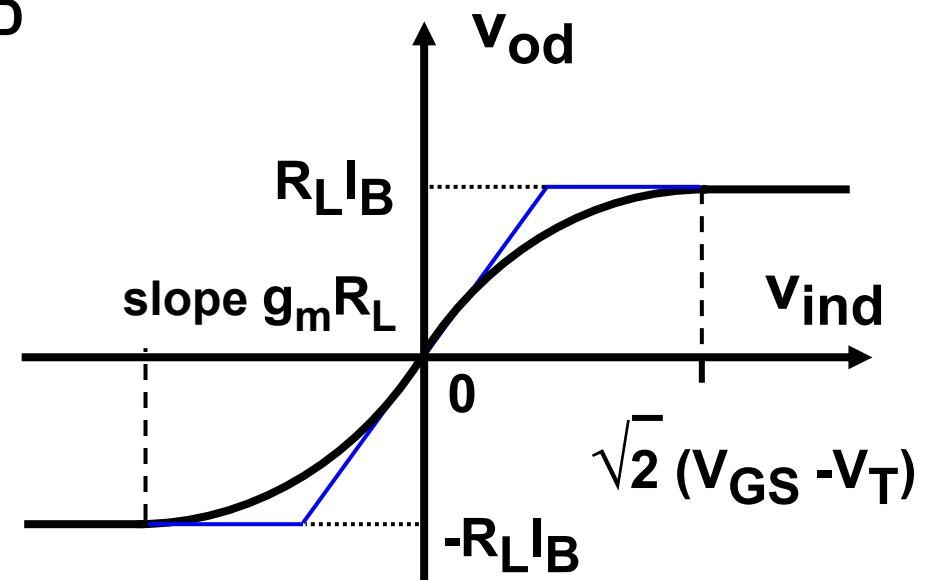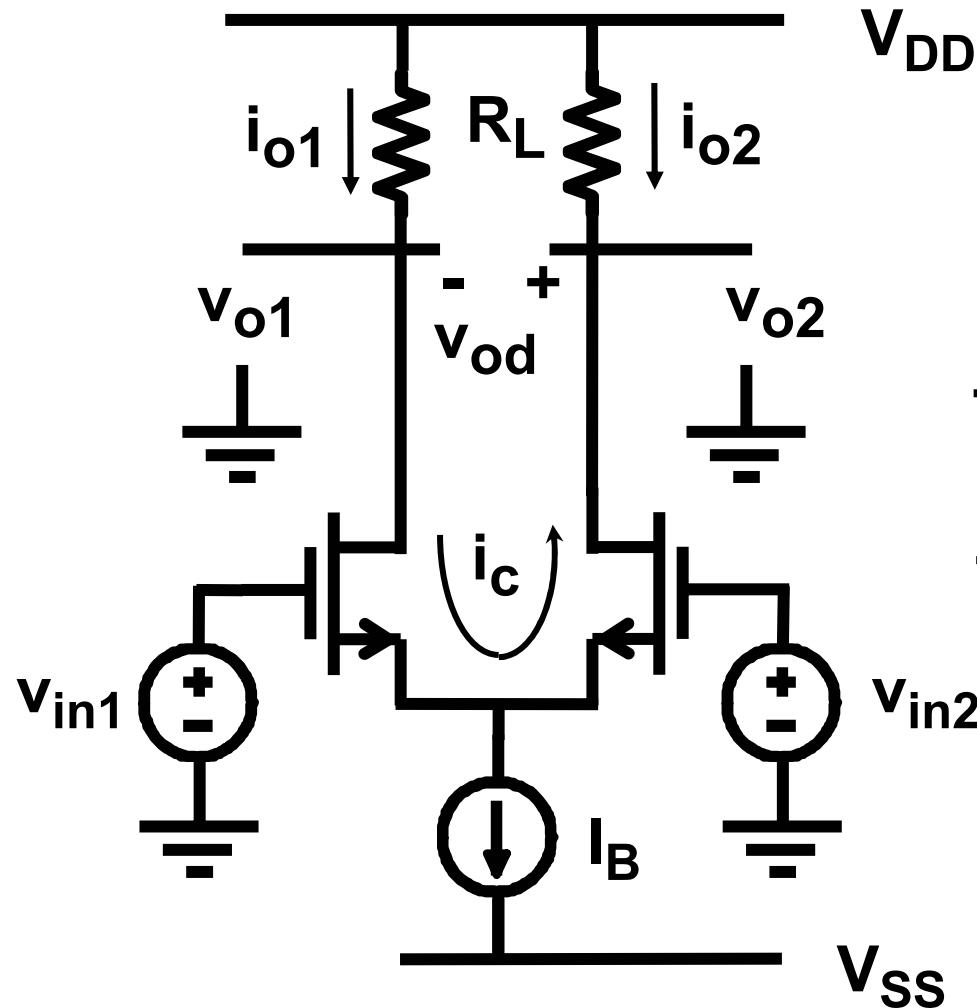
# CMOS Voltage differential amplifier : DC range



$V_{GS} - V_T$  sets slope  
and range  
and .... Gain !
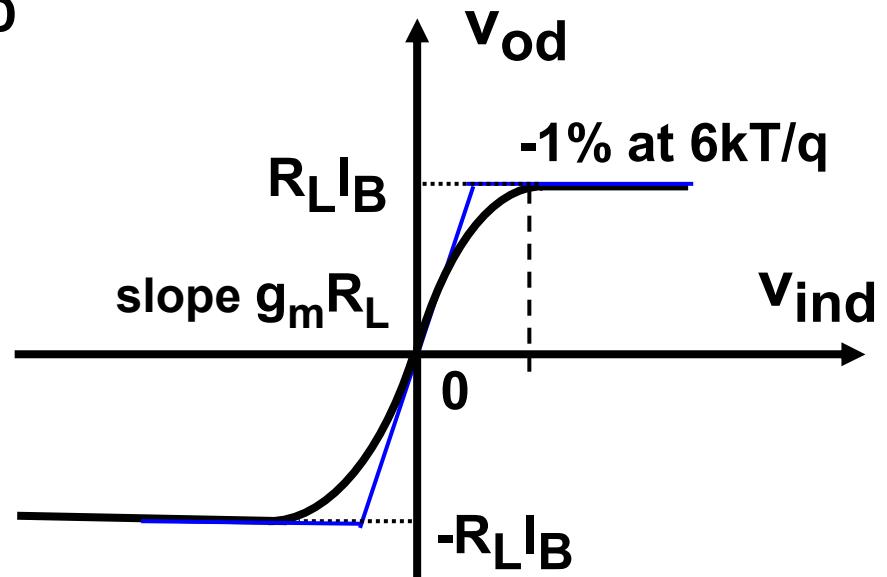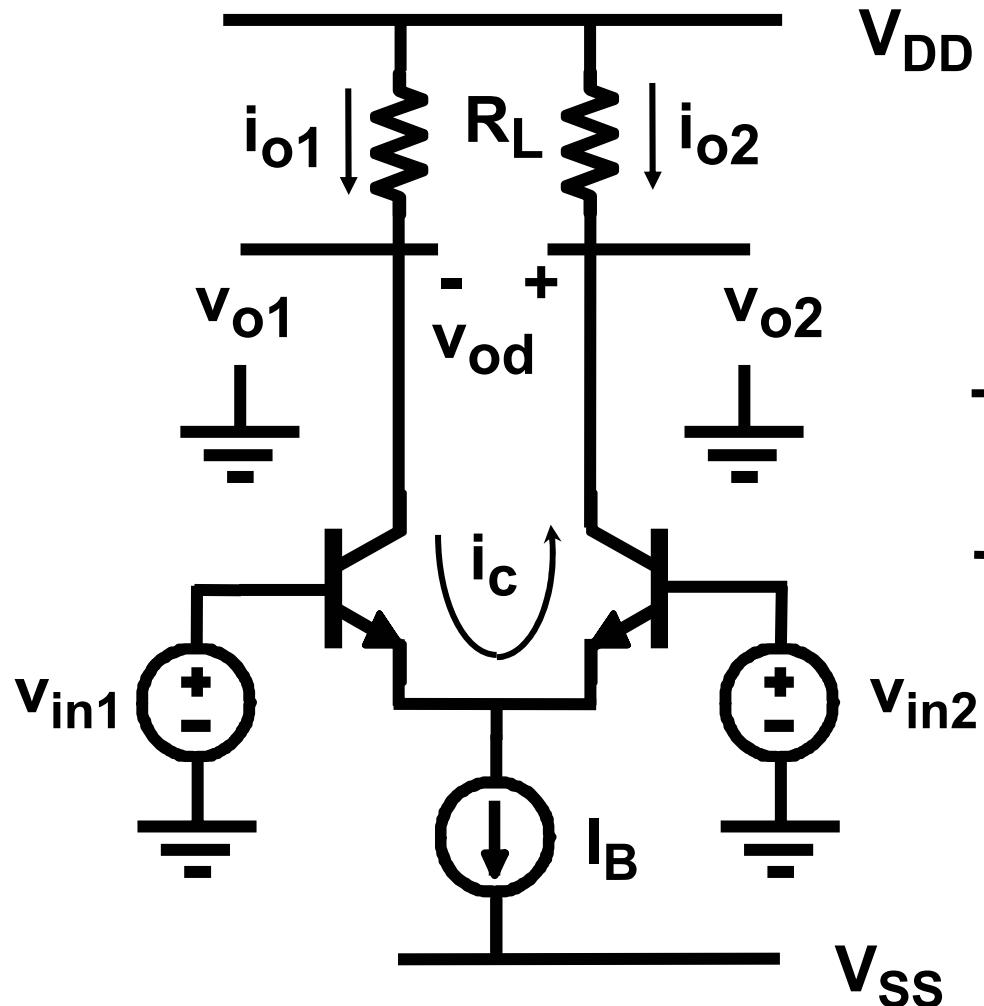
# Bipolar Voltage diff. amplifier : DC range



**kT/q sets slope and Gain  
and range**  
**Insert  $R_E$  to increase range !**

---

# MOST Voltage diff. amplifier : large input signals

---

$$\frac{i_{Od}}{I_B} = \frac{v_{Id}}{(V_{GS}-V_T)} \sqrt{1 - \frac{1}{4} \left( \frac{v_{Id}}{V_{GS}-V_T} \right)^2}$$

$v_{Id}$  is the differential input voltage

$i_{Od}$  is the differential output current ( $g_m v_{Id}$ ) or  
twice the circular current  $g_m v_{Id} / 2$

$I_B$  is the total DC current in the pair

Note that  $g_m = \frac{I_B}{V_{GS} - V_T} = K' W/L (V_{GS} - V_T)$

---

# Bipolar Voltage diff. amp. : large input signals

---

$$\frac{i_{Od}}{I_B} = \tanh \frac{V_{Id}}{2 kT/q}$$

$$\tanh x = \frac{e^x - e^{-x}}{e^x + e^{-x}} = \frac{2e^x - 1}{2e^x + 1}$$


$V_{Id}$  is the differential input voltage

$i_{Od}$  is the differential output current ( $g_m V_{Id}$ ) or  
twice the circular current  $g_m V_{Id} / 2$

$I_B$  is the total DC current in the pair

Note that  $g_m = \frac{I_B}{2 kT/q}$
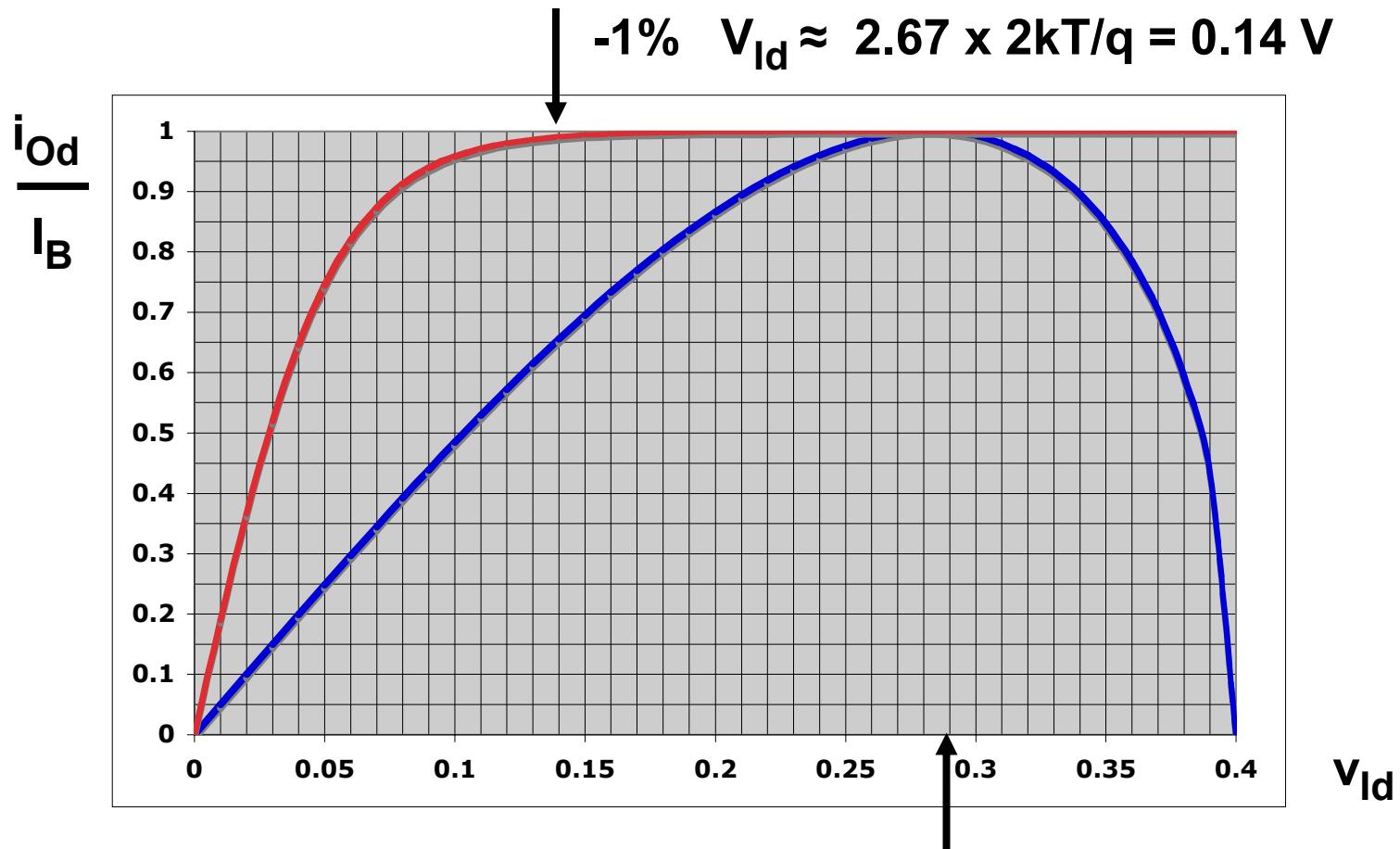
# Voltage differential amplifier: transfer function




$$V_{Id} = \sqrt{2} (V_{GS} - V_T) = \sqrt{2} \times 0.2 \text{ V}$$

---

# Voltage differential amplifier with $g_m r_{DS}$ gain

---

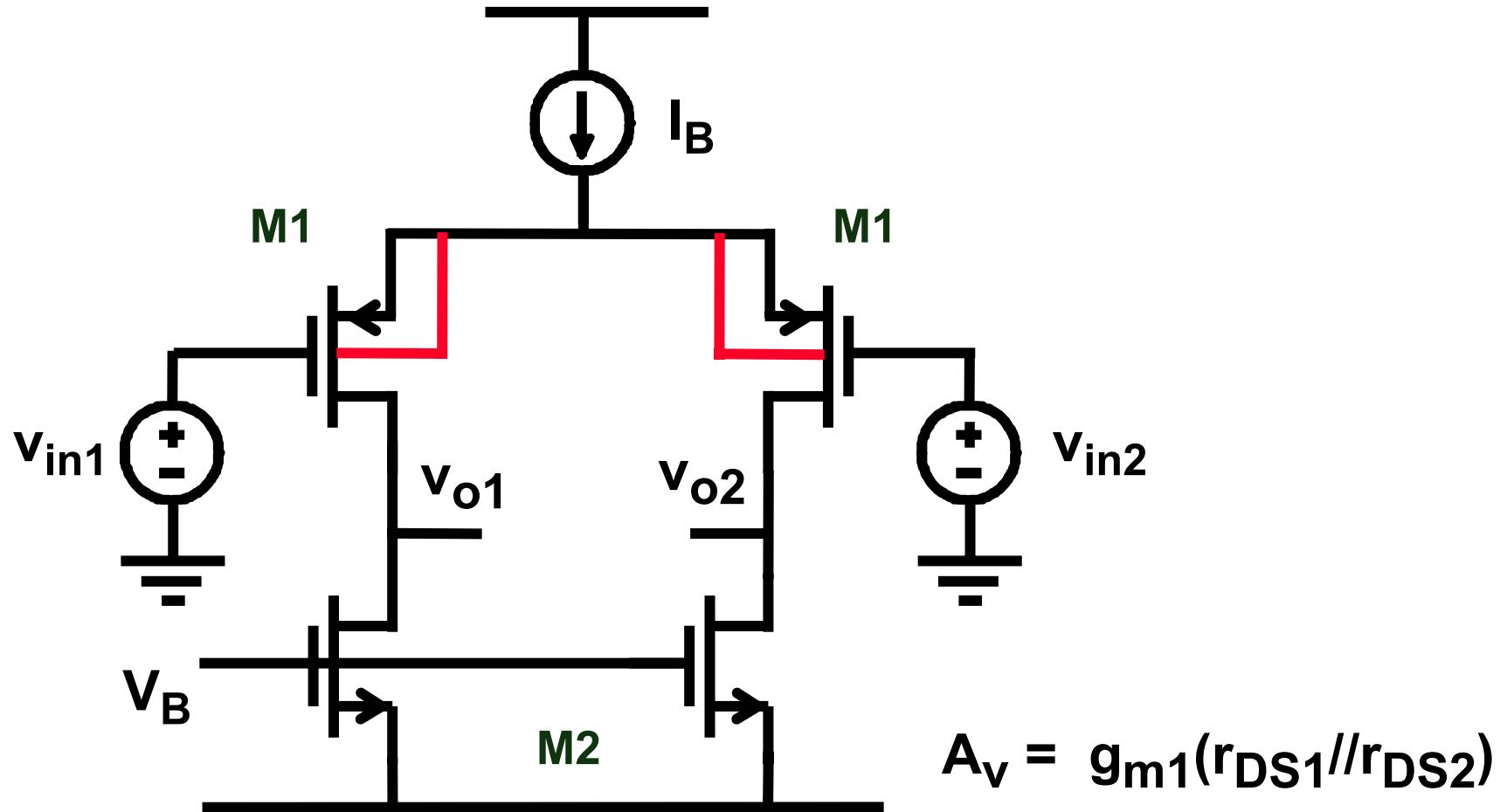


---


# Diode-connected MOSTs with resistors

---


$$\frac{2}{g_m}$$

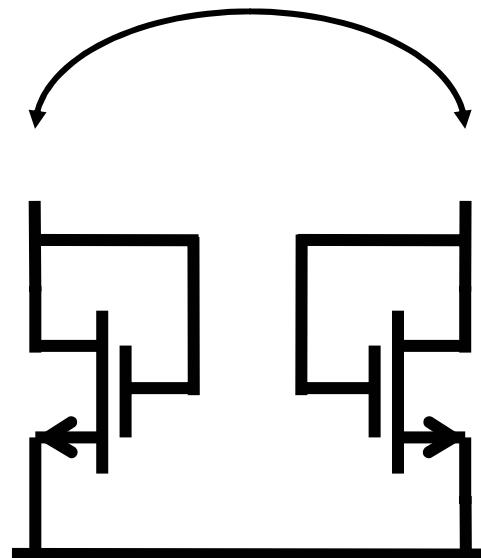

$$2 R//r_o$$

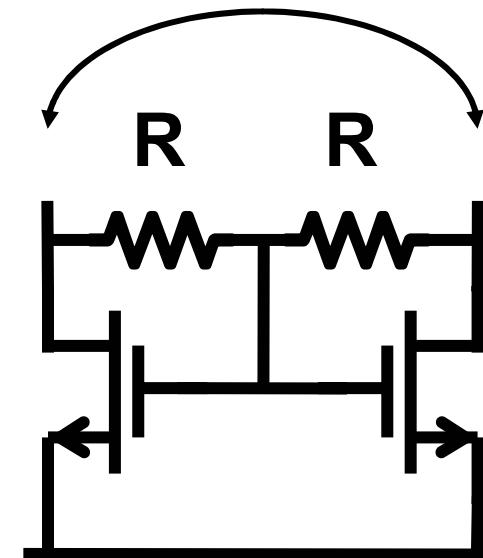
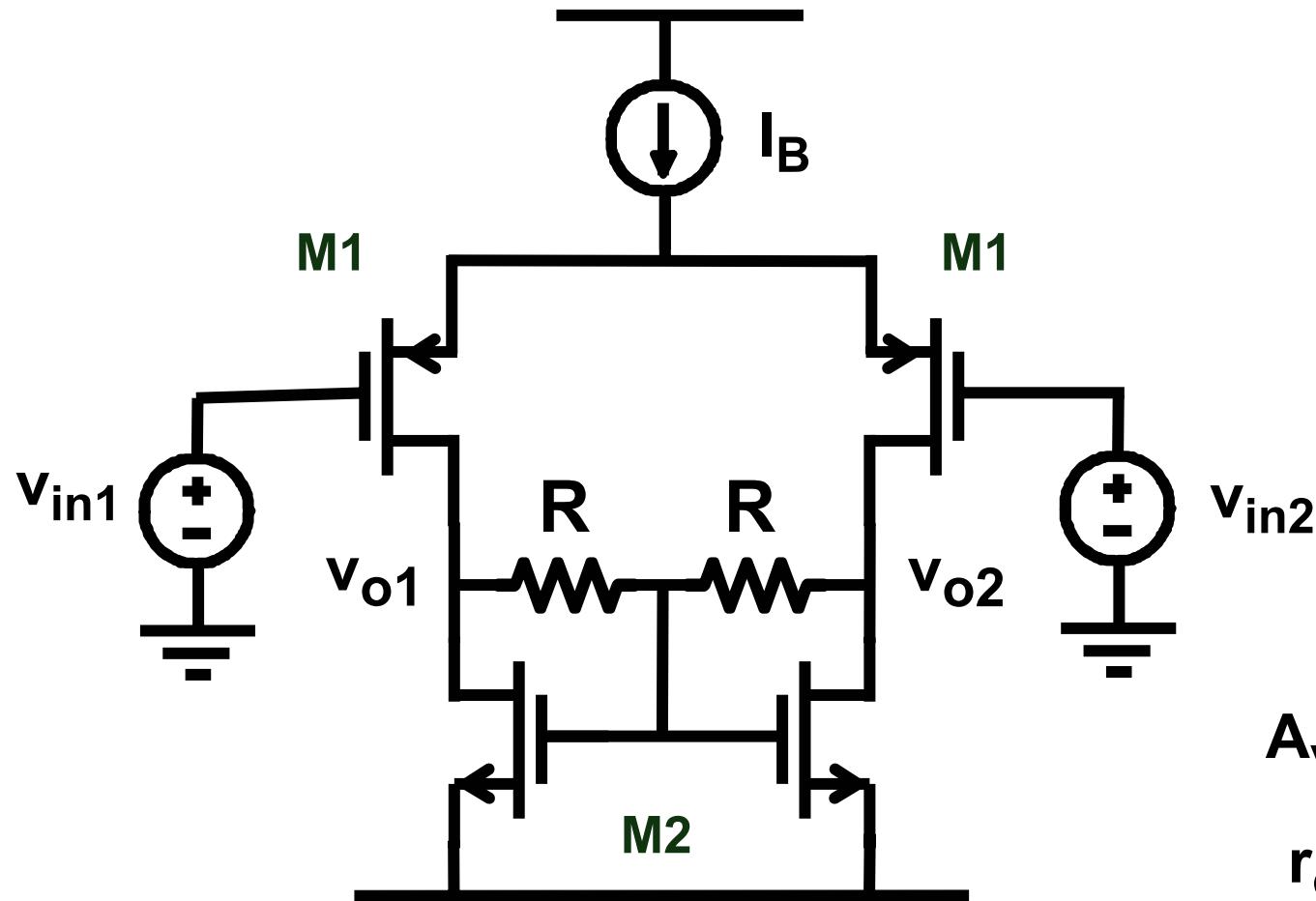
# Voltage differential amplifier with high gain




$$A_v = g_m (R \parallel r_o)$$


$$r_o = r_{o1} \parallel r_{o2}$$

# Differential diode-connected MOSTs


$$\frac{2}{g_m}$$

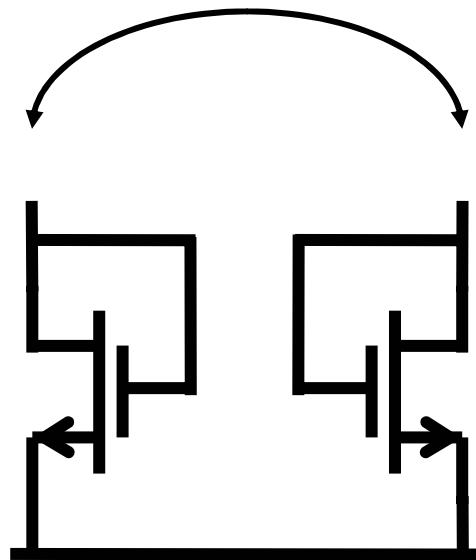

$$-\frac{2}{g_m}$$

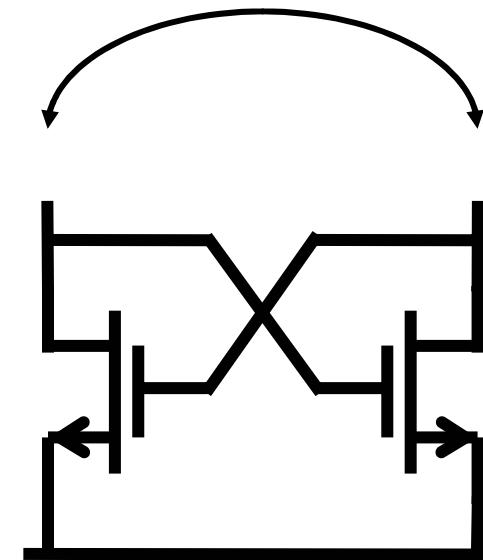

# Differential diode-connected MOSTs

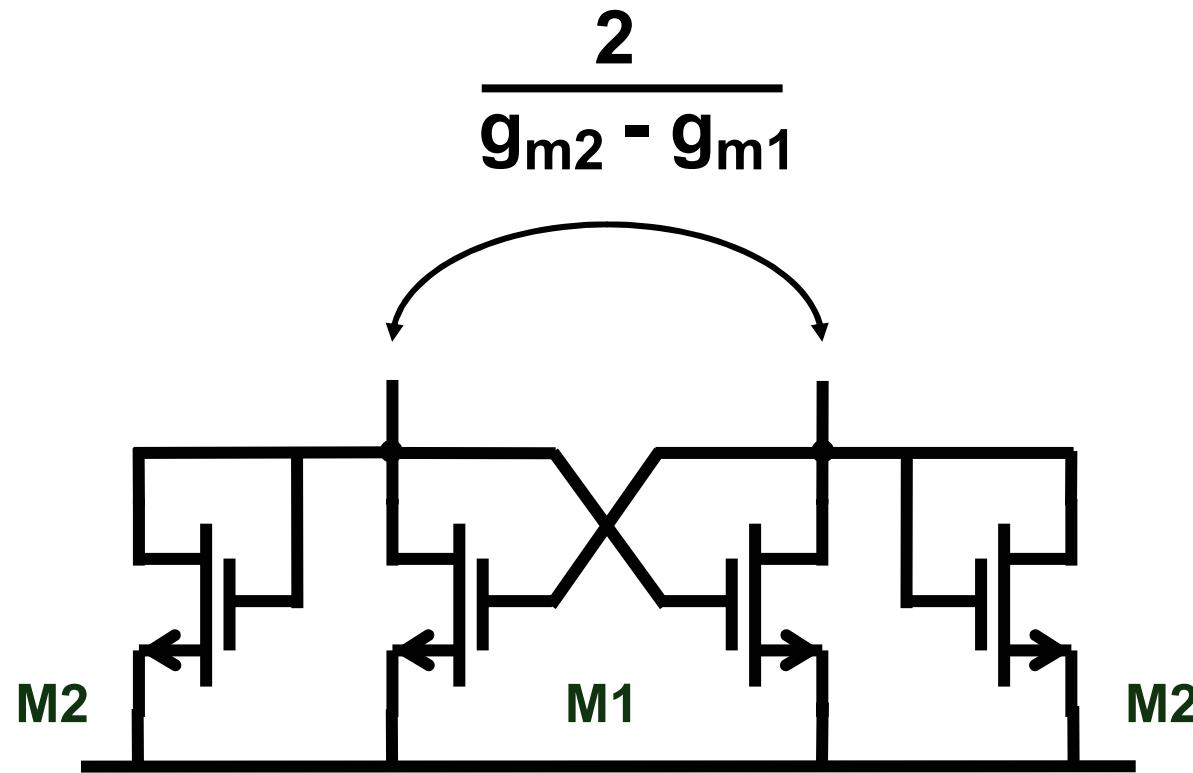


Values close to  $\infty$  !

---

# High gain because of current cancellation



---

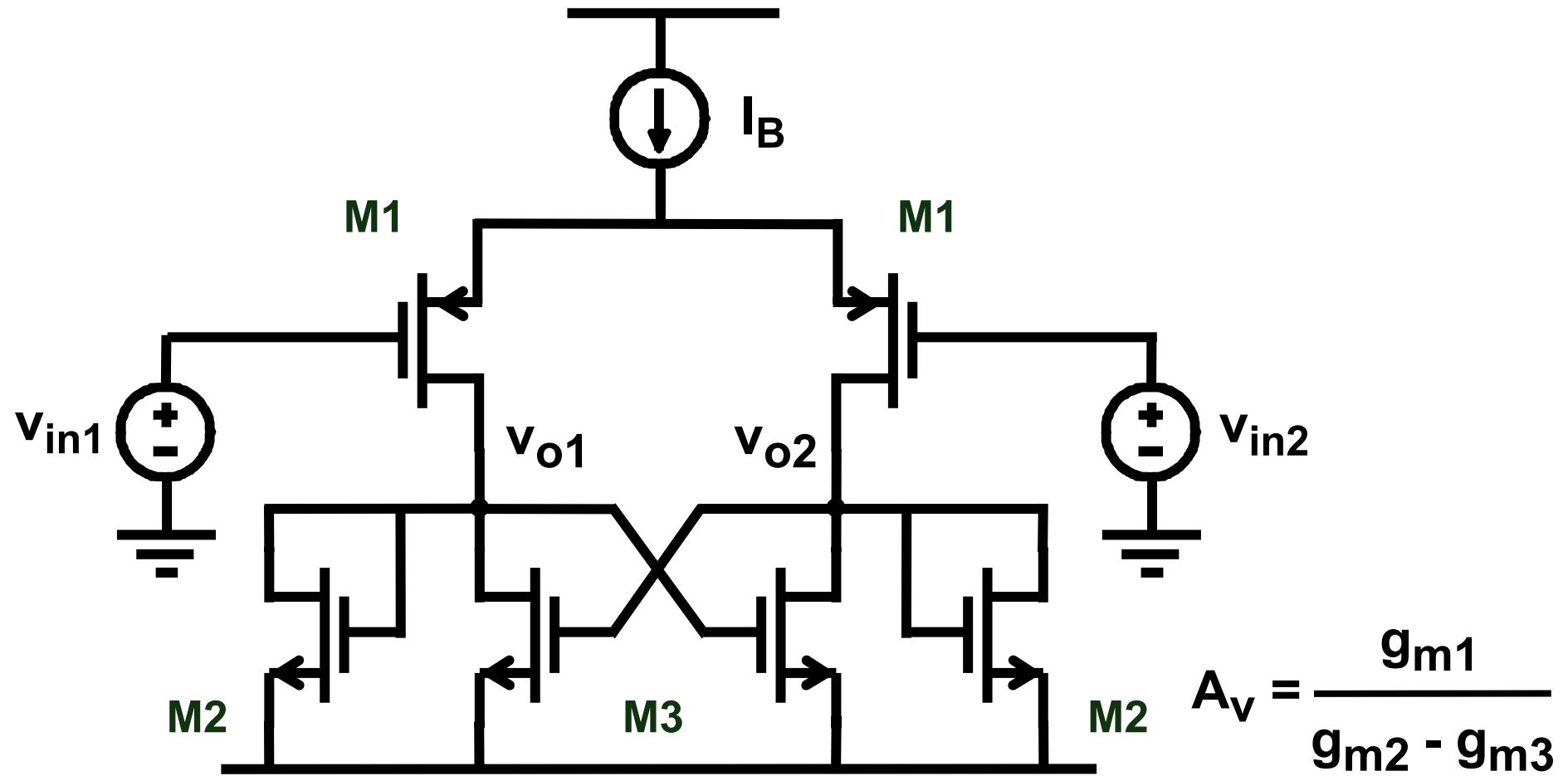

---

# Input impedance


---

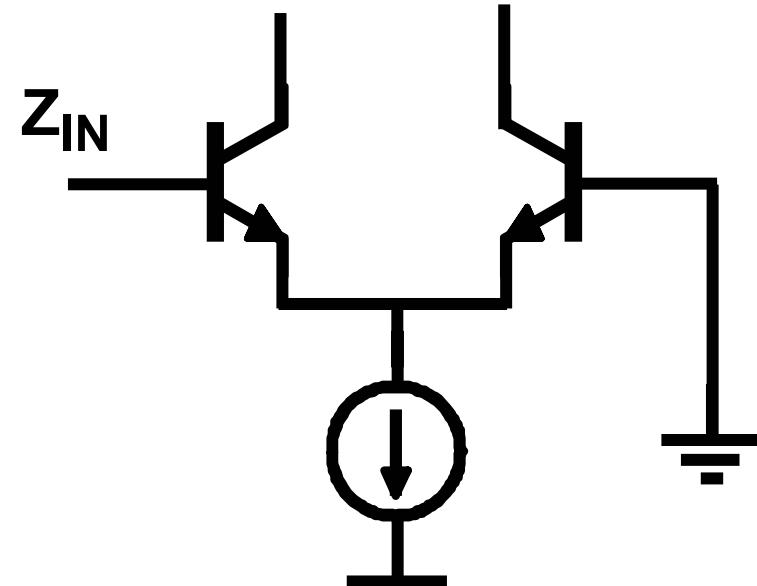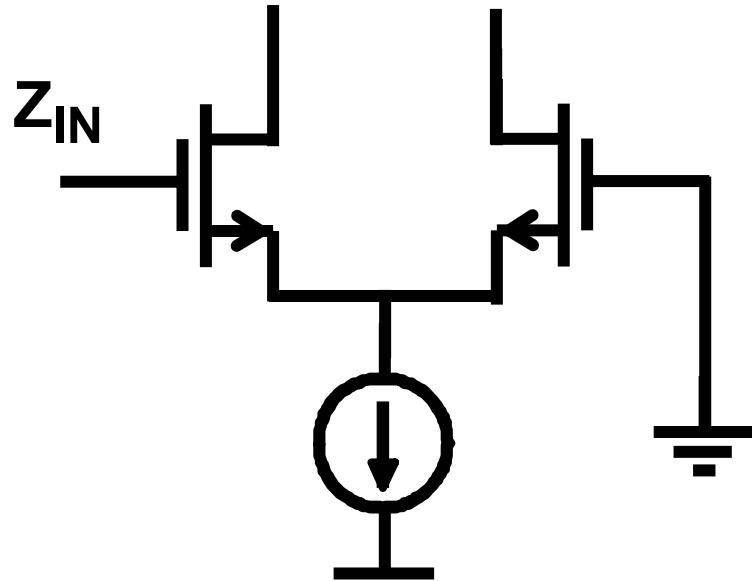

$$C_{IN} = \frac{C_{GS}}{2}$$


$$R_{IN} = 2 r_\pi \quad C_{IN} = \frac{C_\pi}{2}$$
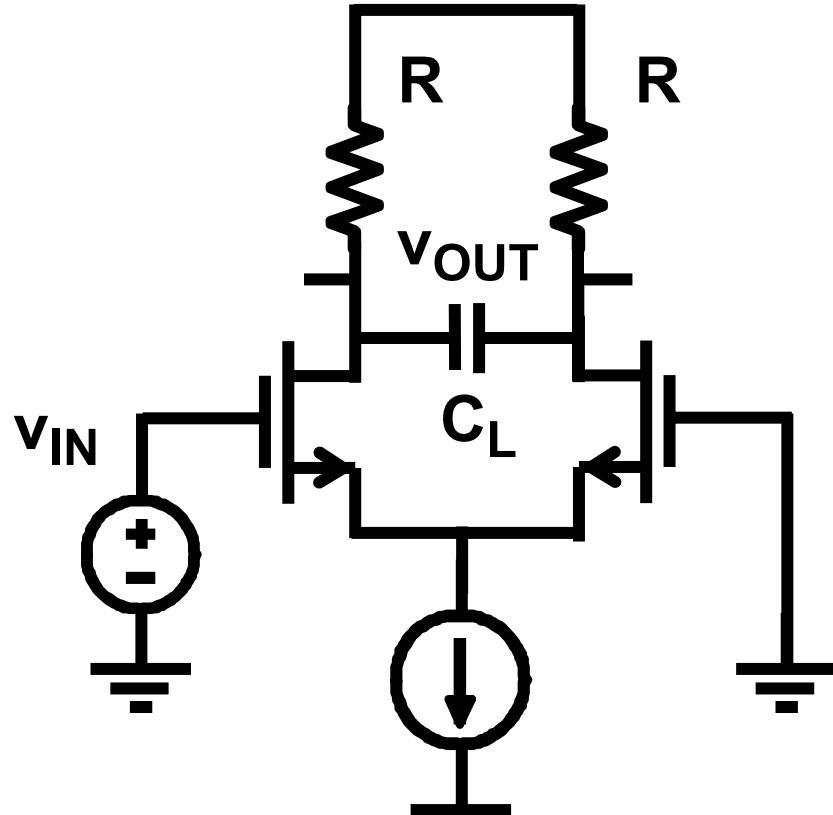
# Low-Pass Voltage Differential amplifier



$$A_{v0} = g_m R$$

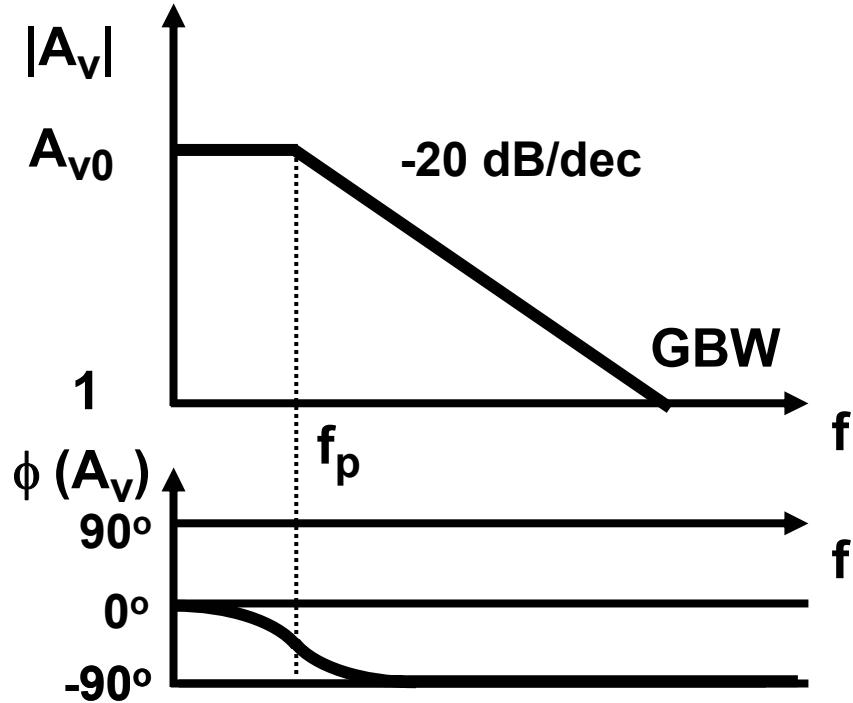
$$A_v = \frac{A_{v0}}{\left(1 + j \frac{f}{f_p}\right)}$$



$$f_p = \frac{1}{2\pi 2RC_L}$$


$$\text{GBW} = \frac{g_m}{2\pi 2C_L}$$
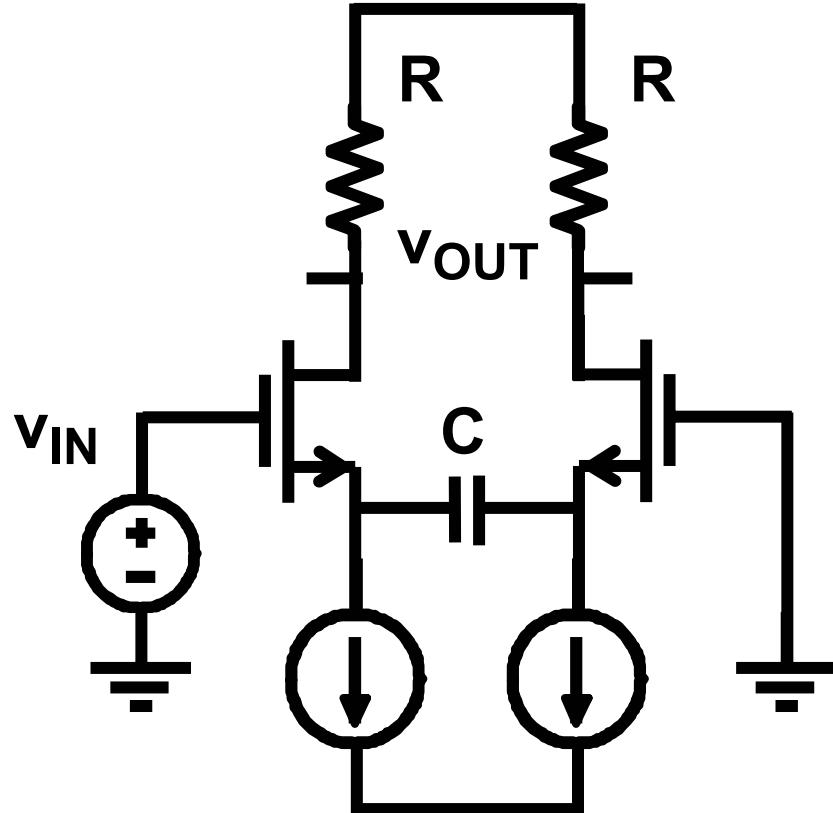
# High-Pass voltage differential amplifier




$$A_{v0} = g_m R$$
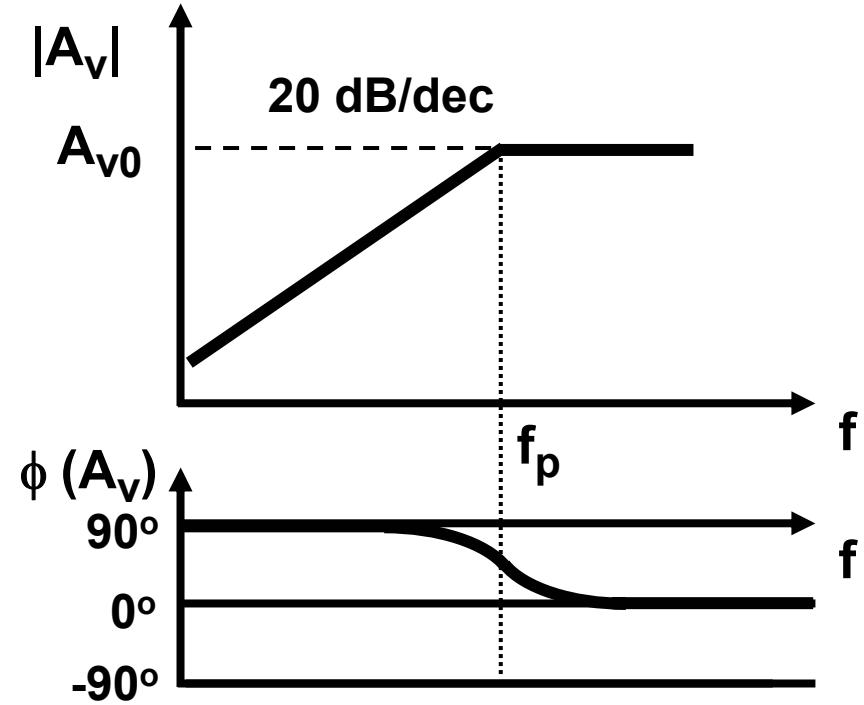
$$A_v = A_{v0} \frac{j \frac{f}{f_p}}{(1 + j \frac{f}{f_p})}$$



$$f_p = \frac{g_m}{2\pi 2C}$$
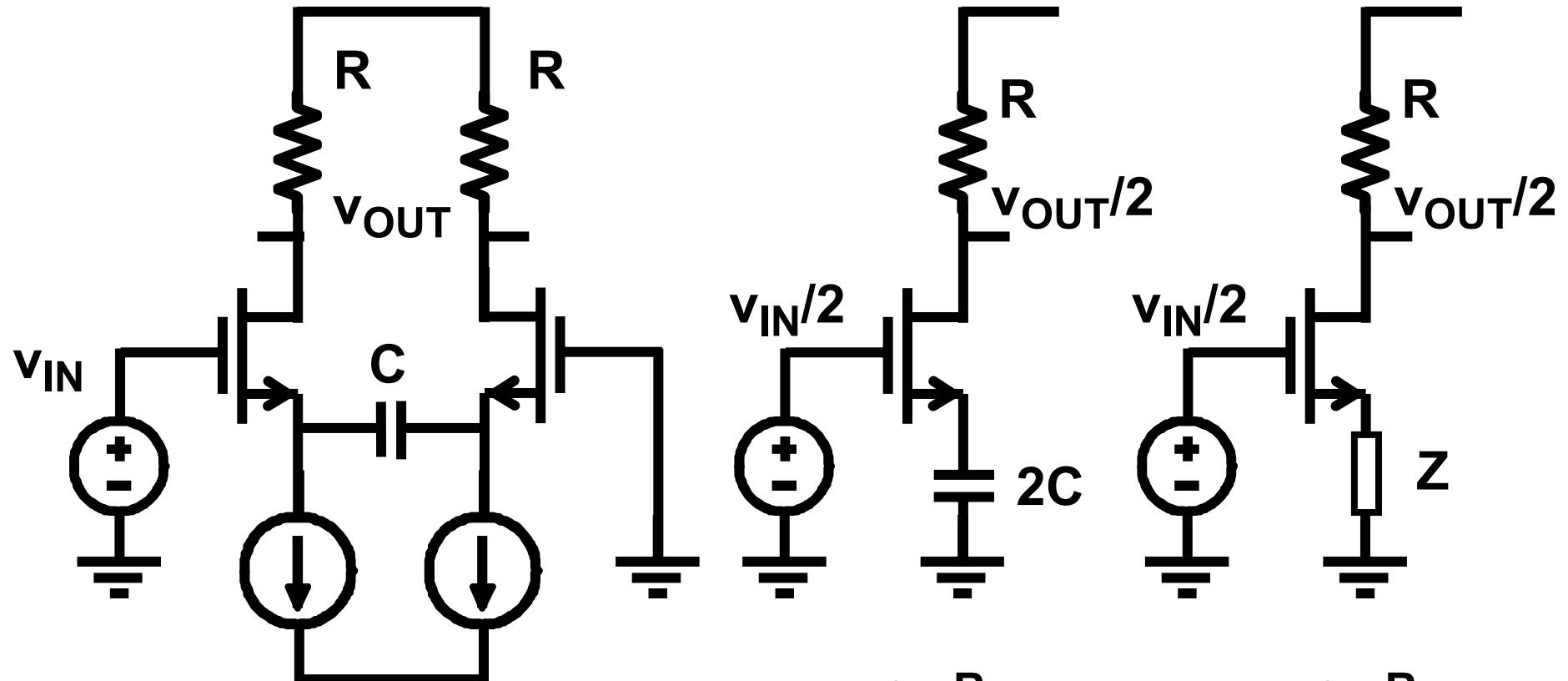
# Calculation High-Pass differential amplifier



$$A_v = \frac{-g_m R}{\left(1 + \frac{g_m}{2C_s}\right)}$$

$$A_v = \frac{-g_m R}{1 + g_m Z}$$


---

# Table of contents

---


- Current mirrors
- Differential pairs
- Differential voltage and current amps
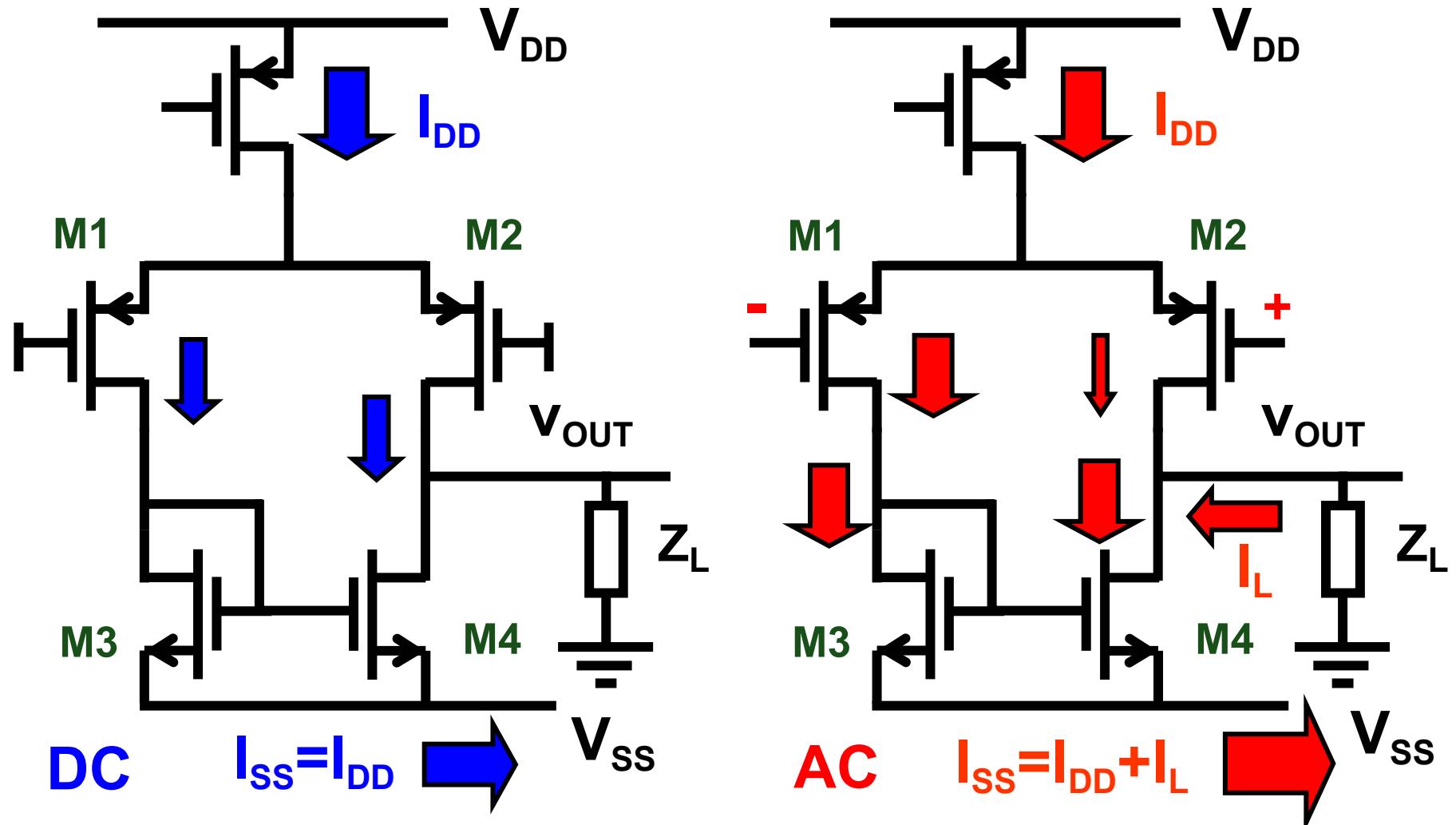
# Operational Transconductance Amplifier (OTA)



# Single-stage OTA: operation


∞

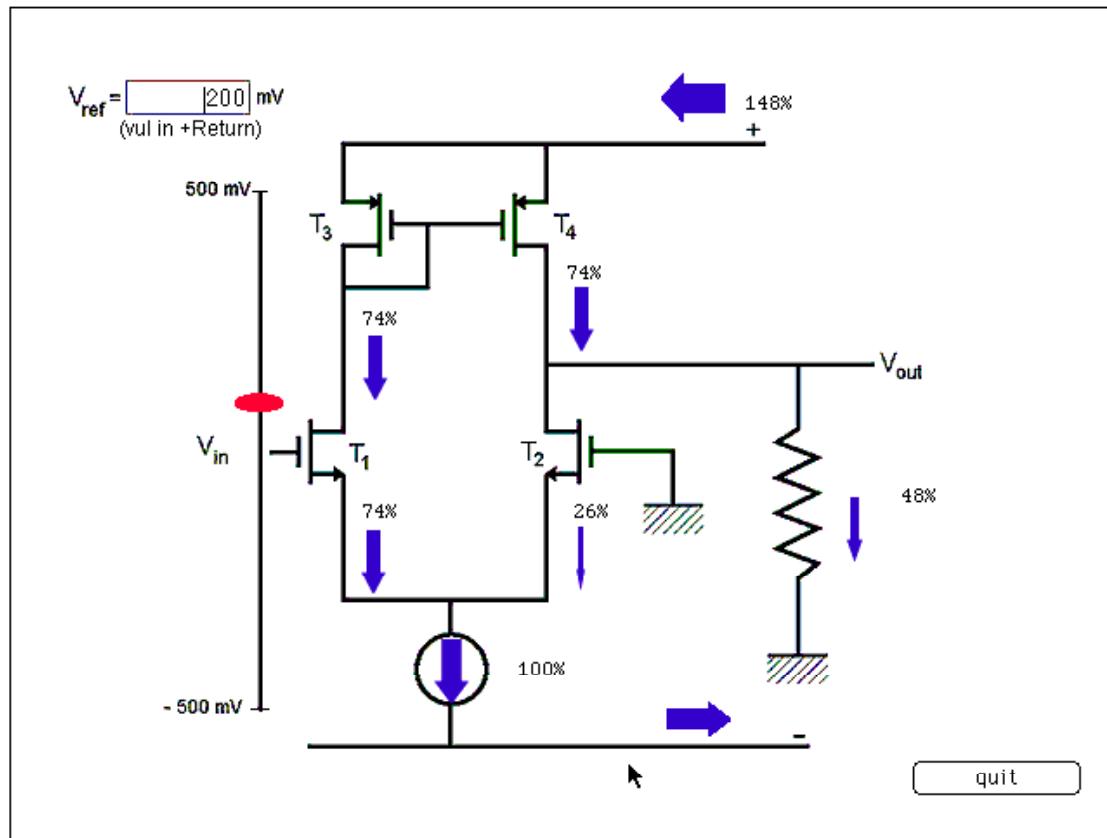

---

# Single-stage OTA

---

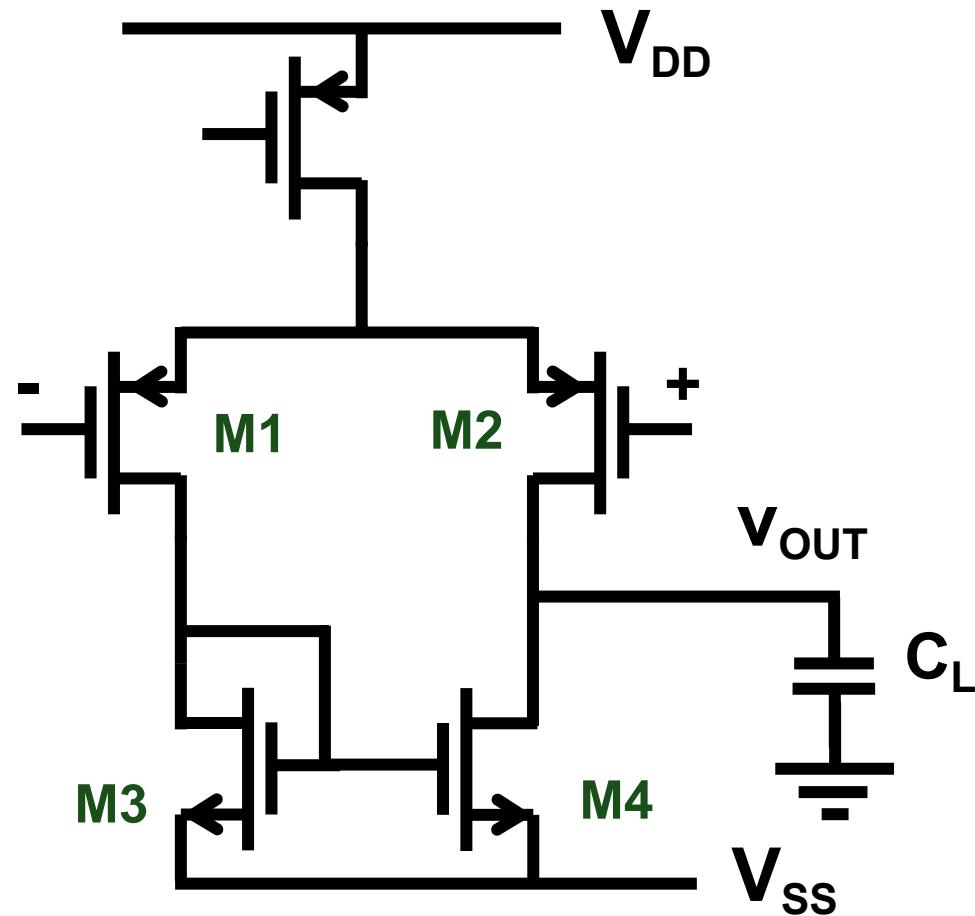

$$A_v = g_{m1} R_{out}$$

$$R_{out} = r_{DS2} // r_{DS4}$$


$$BW = \frac{1}{2\pi R_{out} C_L}$$

$$GBW = \frac{g_{m1}}{2\pi C_L}$$

---


# Bootstrapping for low input capacitance

---

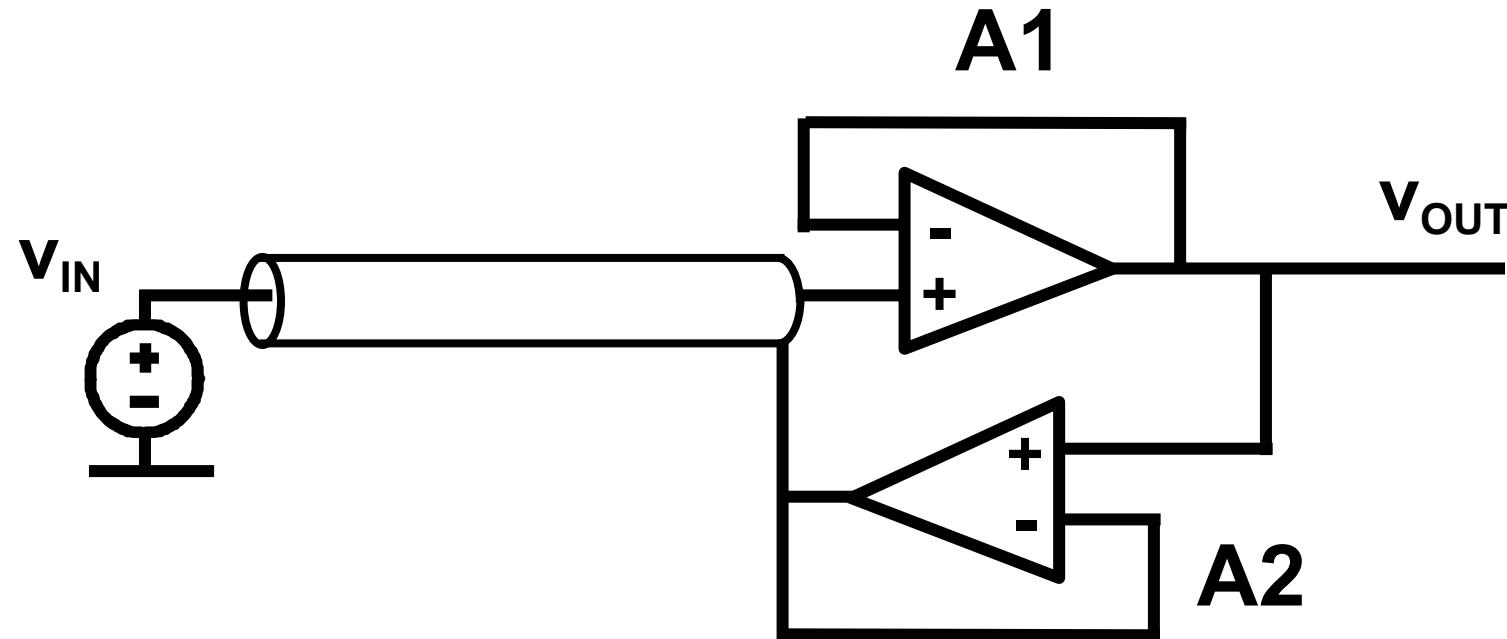


$C_{coax} \approx 0 \text{ !!!}$

# Bootstrapping for high input impedance

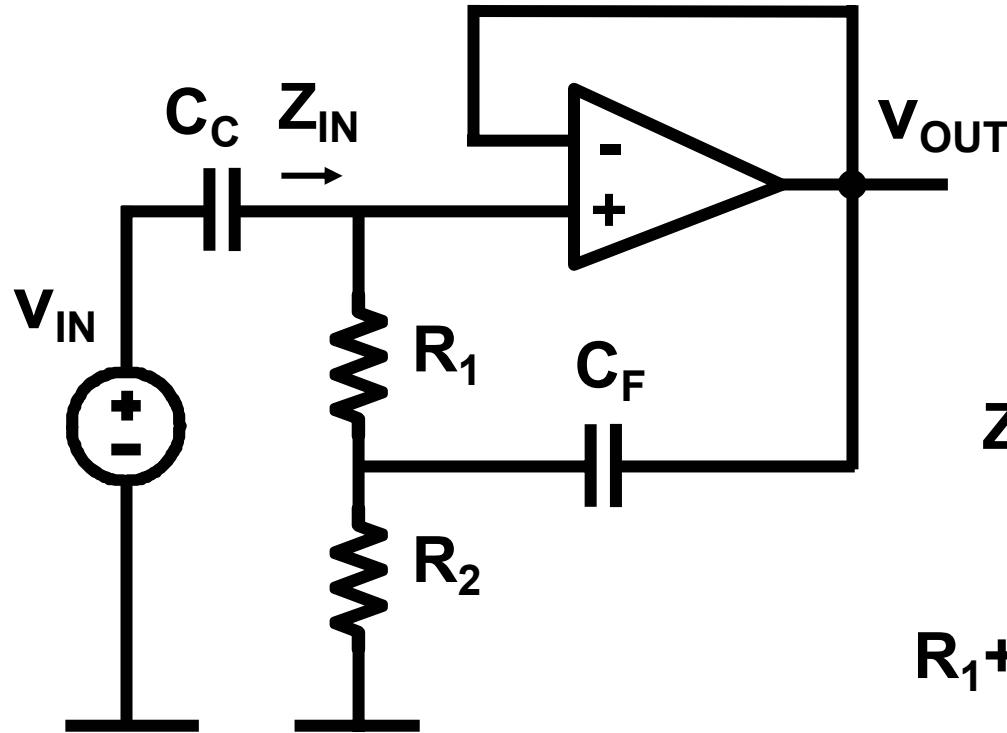

$$f_z = \frac{1}{2\pi (R_1+R_2)C_F}$$


$$f_2 = \frac{1}{2\pi R_2 C_F}$$

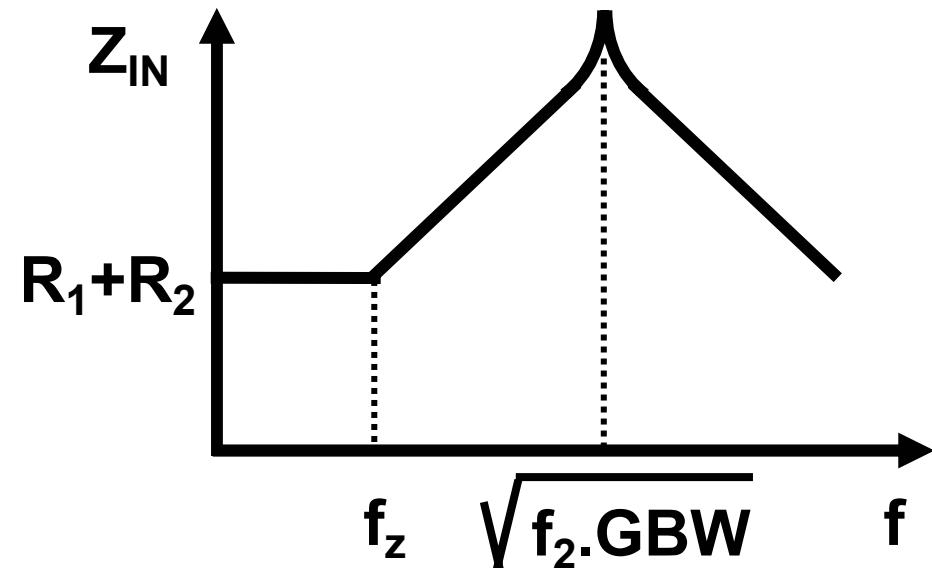


---

# Bootstrapping for high input impedance

---

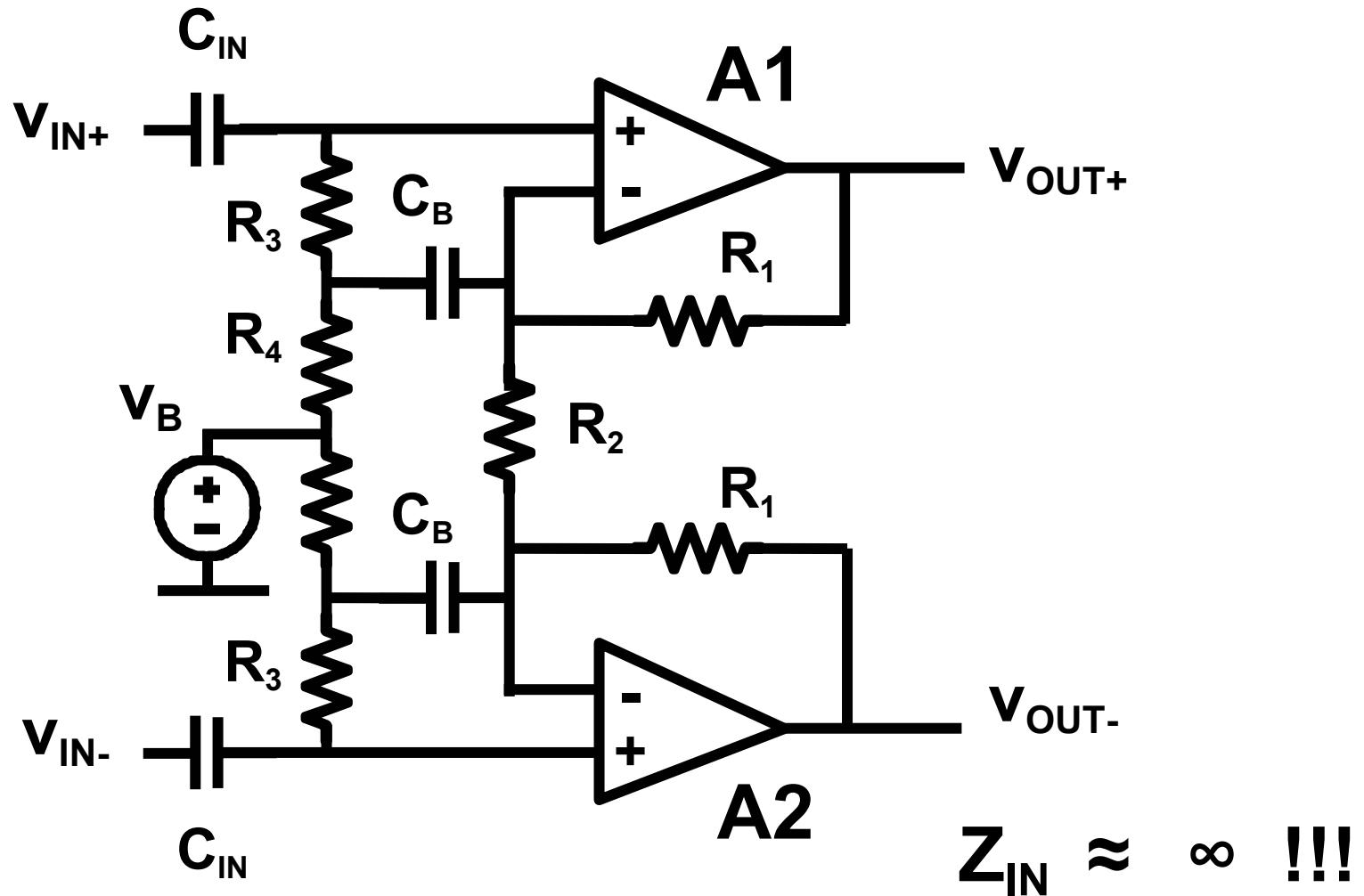


# Bootstrapping out a load resistance R

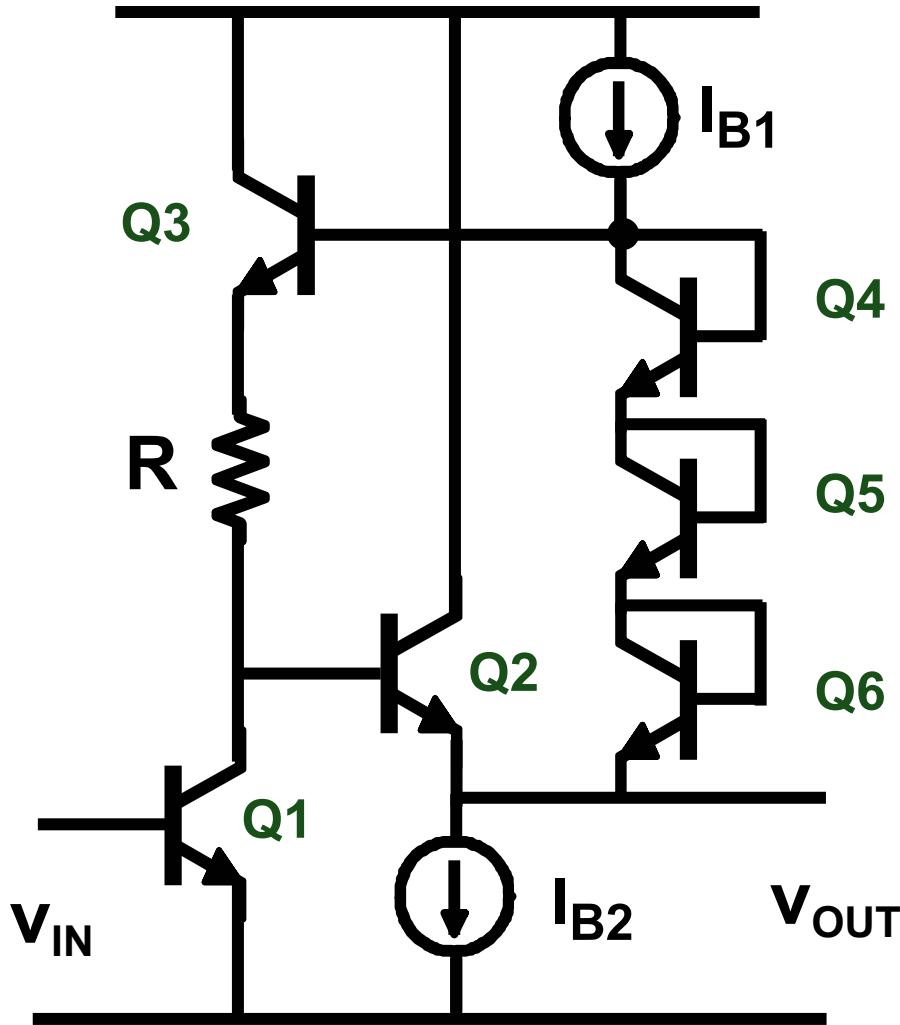

**R is  
bootstrapped out :  
Very high gain !**

Ref.: Nordholt  
JSSC June 85, 688-696

# Bootstrapping out an output resistance

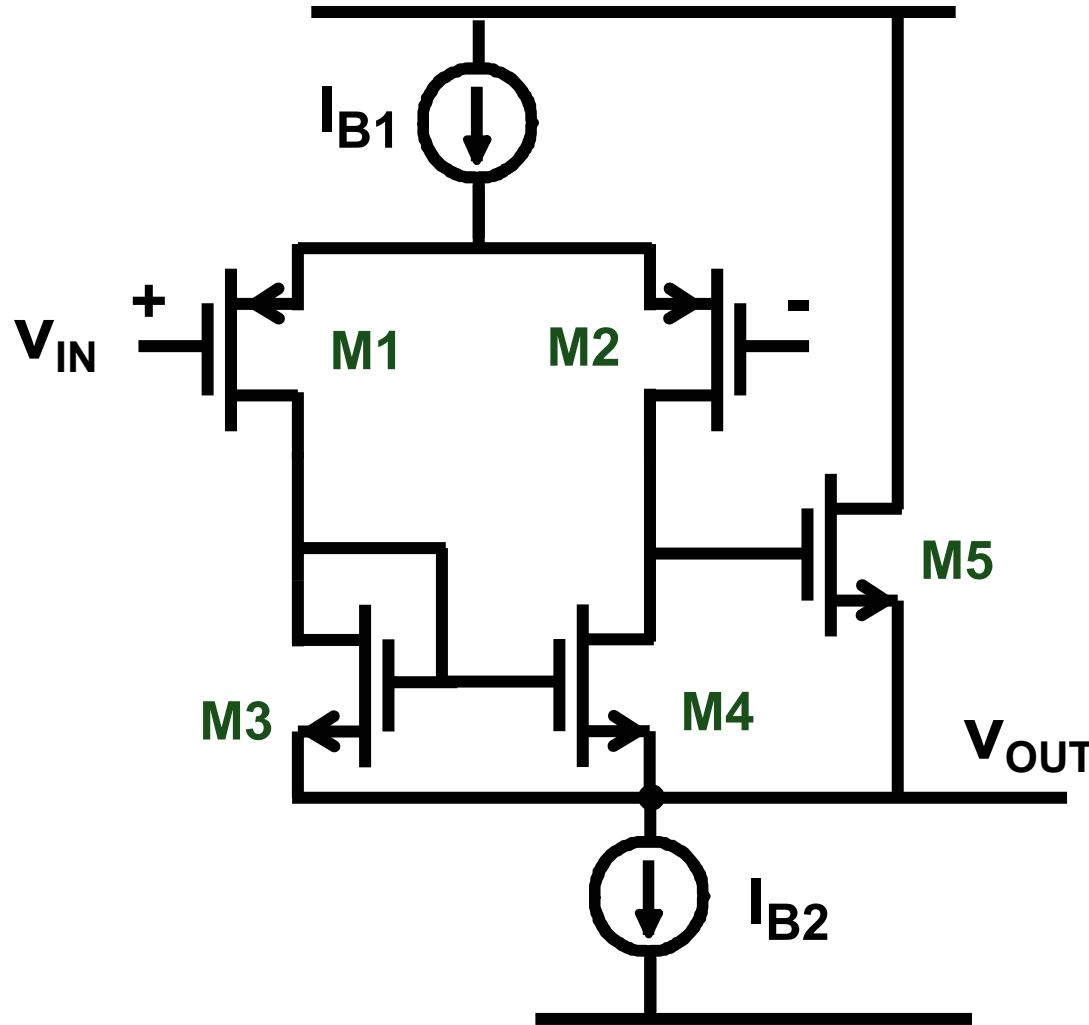


$r_{o4}$  is  
bootstrapped out !

$$A_v \approx g_{m1} r_{o2}$$

Same GBW !

# Bootstrap for high gain $A_{v2}$

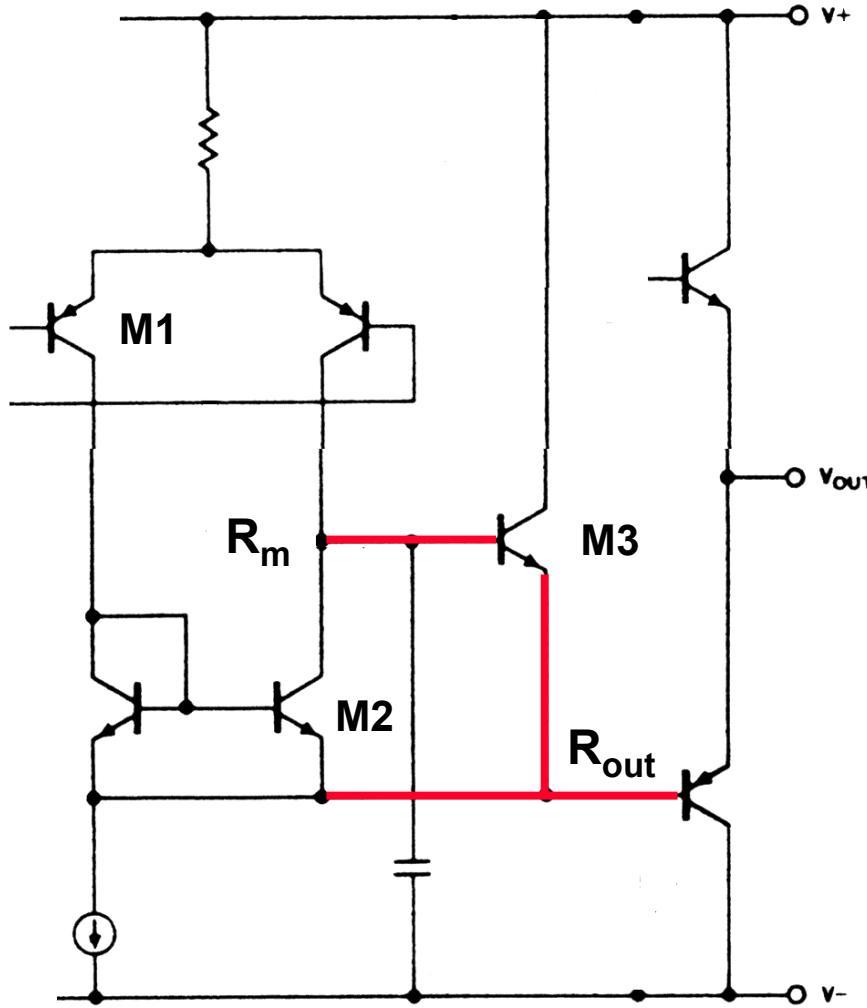

$$R_m \rightarrow x \beta_3$$


$$R_{out} \rightarrow x \frac{1}{\beta_3}$$

$$A_{v2} \approx g_{m1} r_{o2} x \beta_3$$

Same GBW !

Ref. De Man JSSC June 77, pp. 217-222  
LT1008, LT1012

# Current differential amplifier

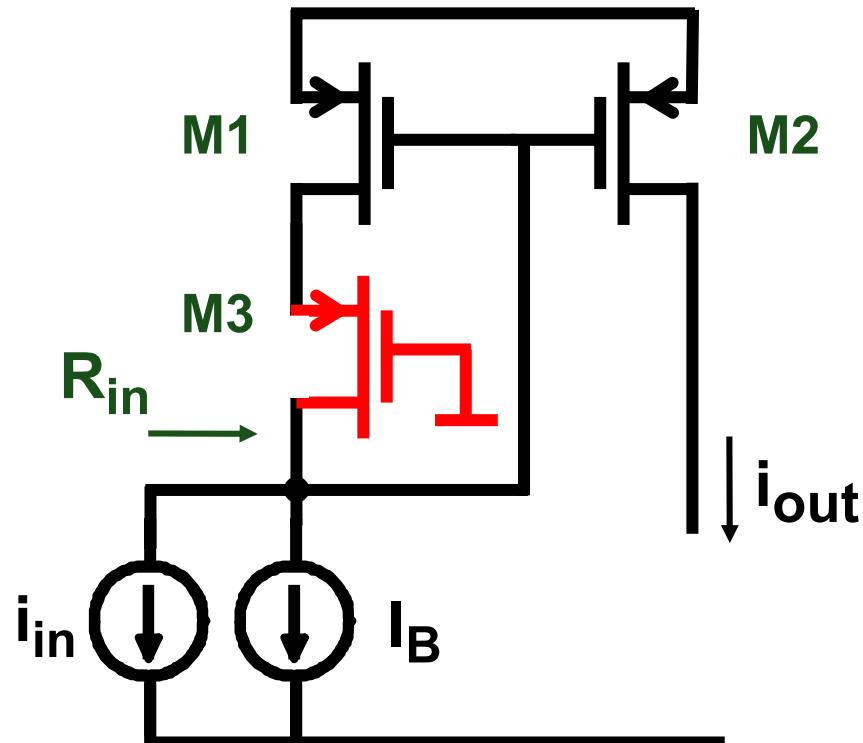


$$i_{out} = I_B + i_{in} \quad R_{in} = \frac{1}{g_{m1}}$$


Is the same !



# Current differential amplifier

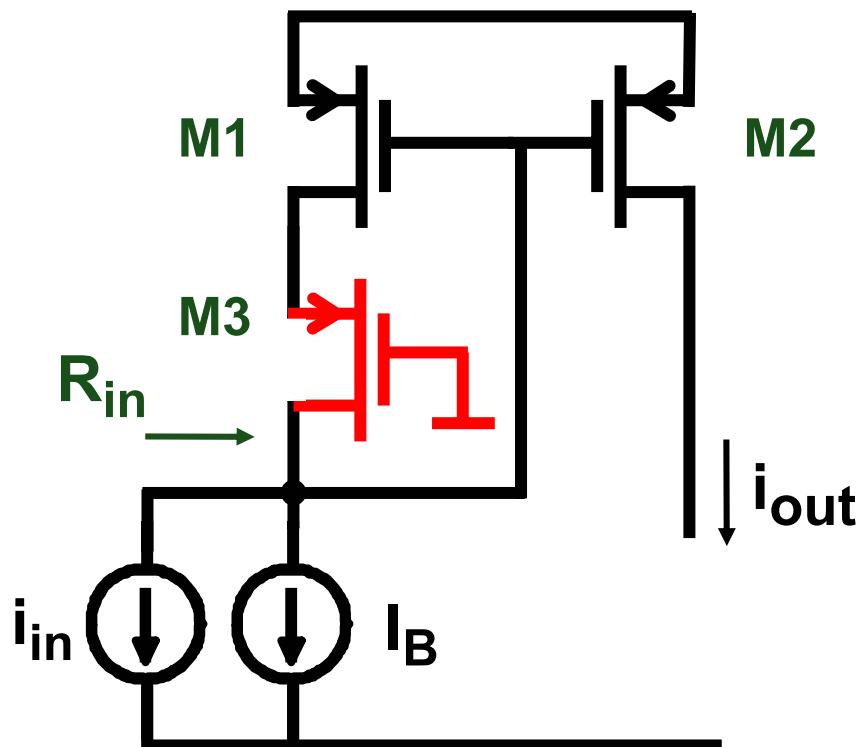

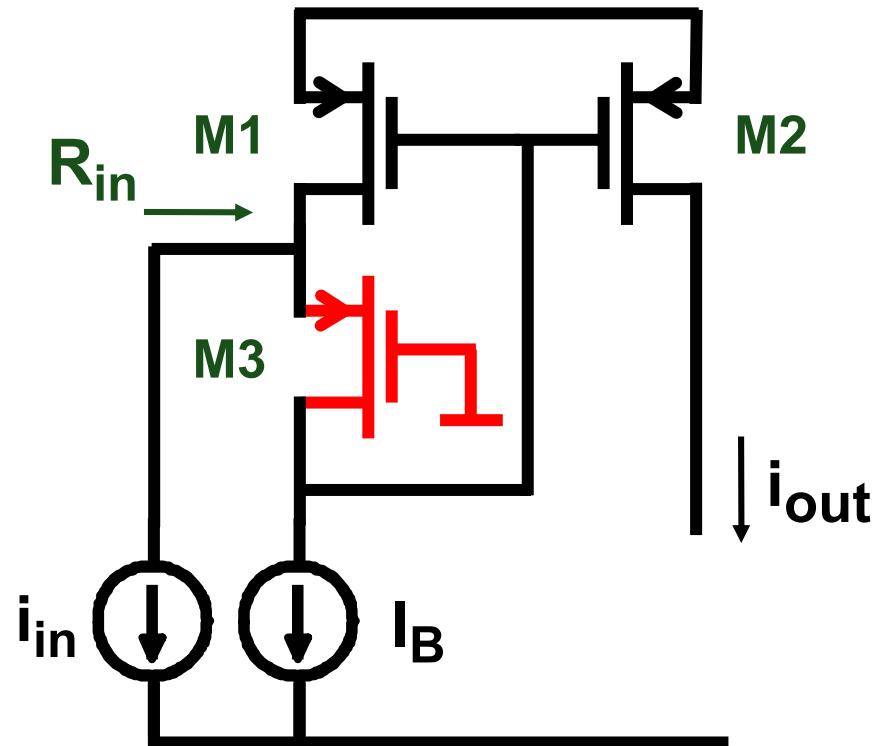
$$i_{out} = I_B + i_{in} \quad R_{in} = \frac{1}{g_{m1}}$$



$$R_{in} = \frac{1}{g_{m1}} \frac{1}{g_{m3}r_{o3}}$$

# Current differential amplifier

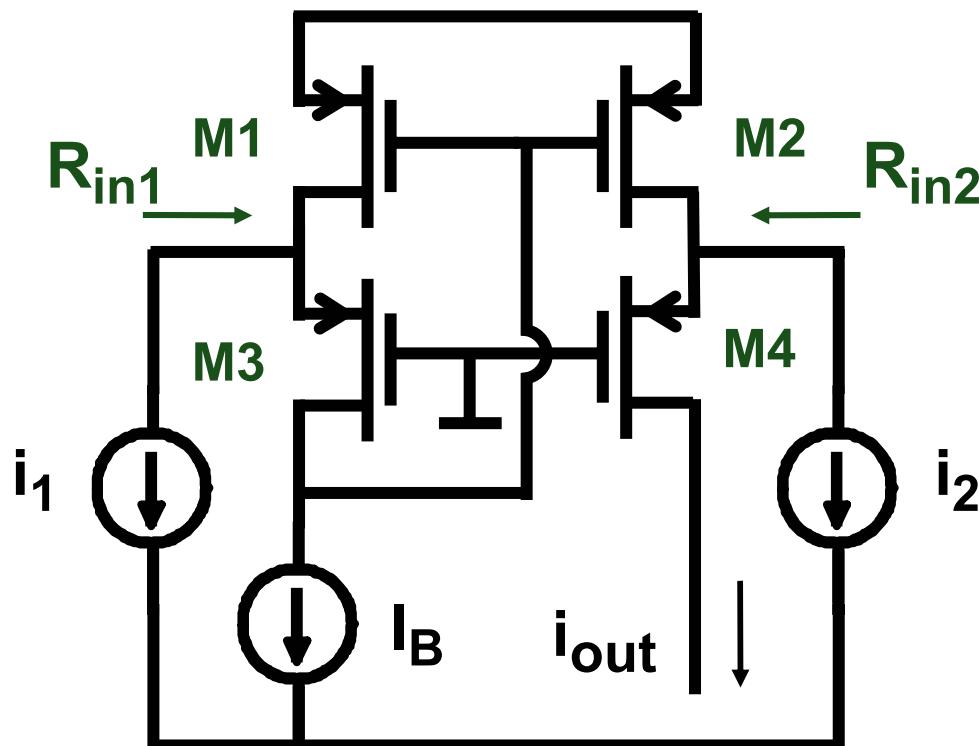

$$i_{out} = I_B + i_1 - i_2$$

$$R_{in1} = \frac{1}{g_{m1}} \frac{1}{g_{m3}r_o3}$$


$$R_{in2} = \frac{1}{g_{m4}}$$

Ref. Fischer, JSSC June 87, 330-340


---

# 4-input current amplifier

---

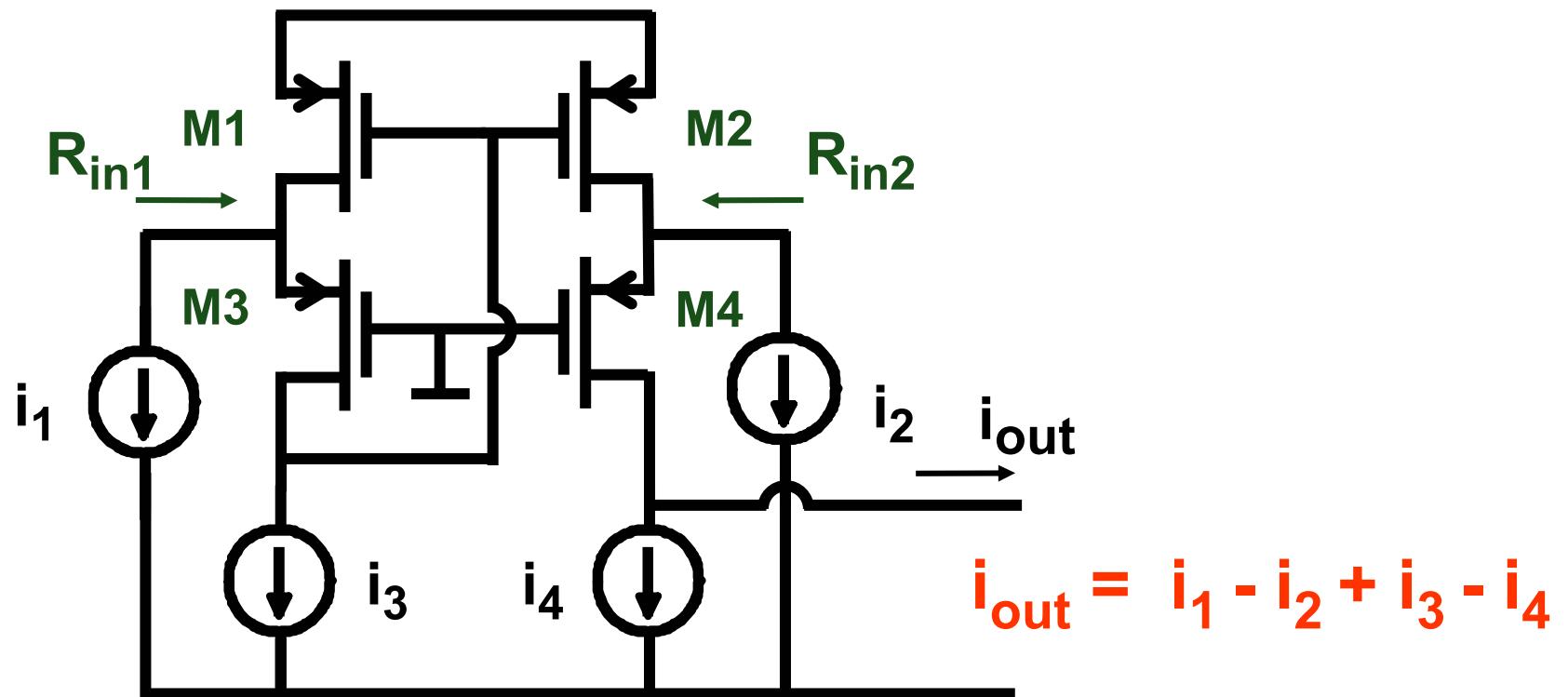

# Low voltage operation

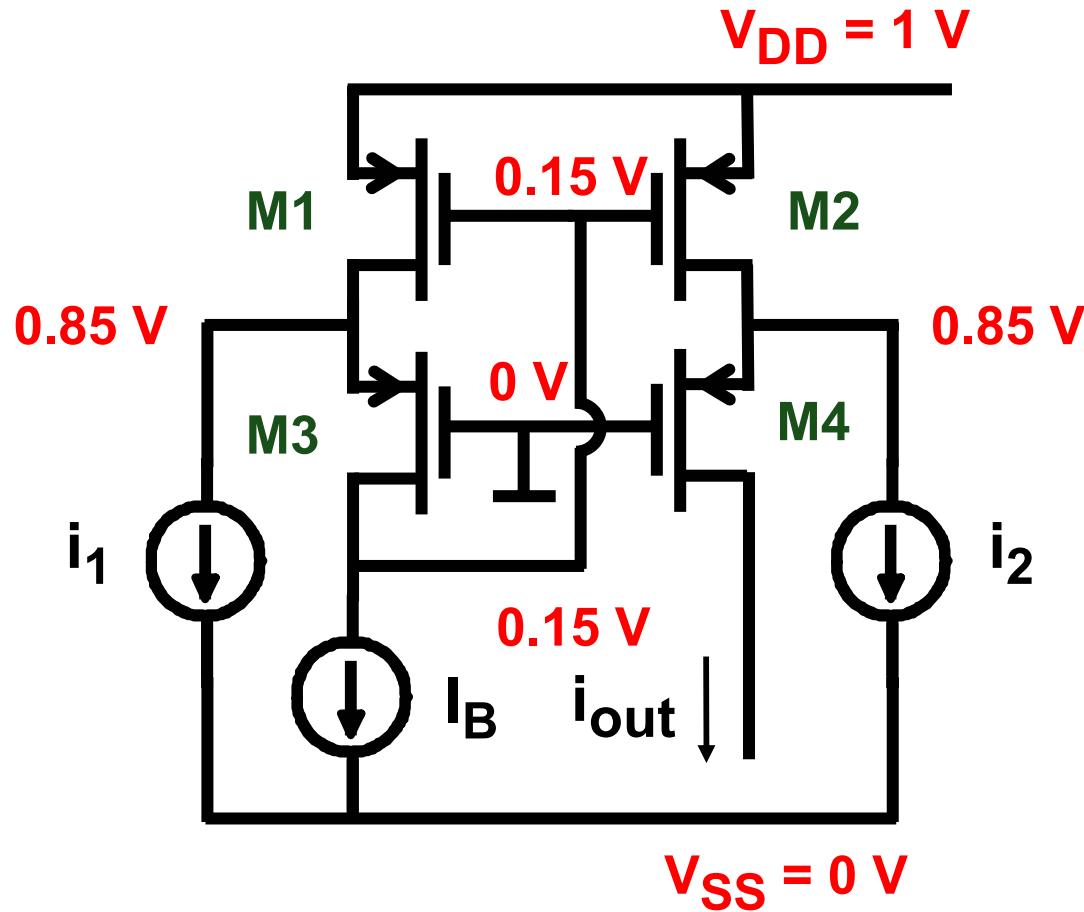

$$i_{out} = i_B + i_1 - i_2$$

$$V_{GS} = 0.85\text{ V}$$

$$V_{DSsat} = 0.15\text{ V}$$

$$V_{outmax} = 0.7\text{ V}$$

$$\text{For } V_T = 0.7\text{ V}$$

$$V_{DDmin} \approx 0.6\text{ V}$$

$$\text{For } V_T = 0.3\text{ V}$$

$$V_{DDmin} \approx 0.6\text{ V}$$

---

# Table of contents

---

- Current mirrors**
- Differential pairs**
- Differential voltage and current amps**