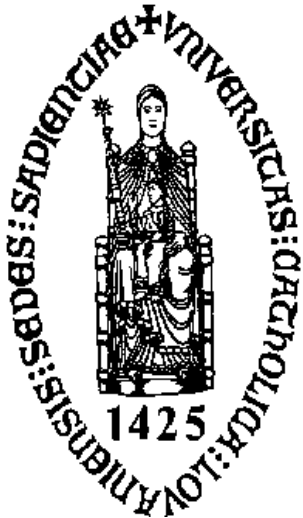


---

---

# Fully-differential amplifiers



**Willy Sansen**

**KULeuven, ESAT-MICAS**

**Leuven, Belgium**

[willy.sansen@esat.kuleuven.be](mailto:willy.sansen@esat.kuleuven.be)



---

# Table of contents

---



- **Requirements**

- **Fully-diff. amps with linear MOSTs**
- **FDA's with error amp.& source followers**
- **Folded cascode OTA without SF's**
- **Other fully-differential amps**
- **Exercise**


---

# Single-stage OTA

---

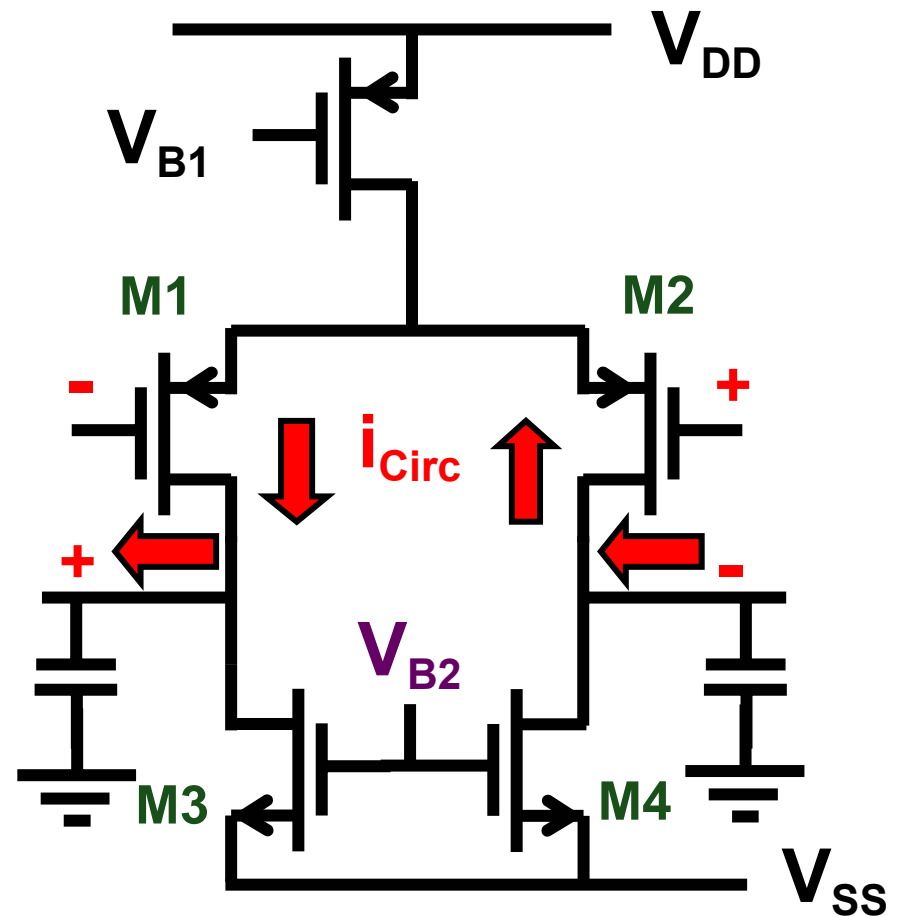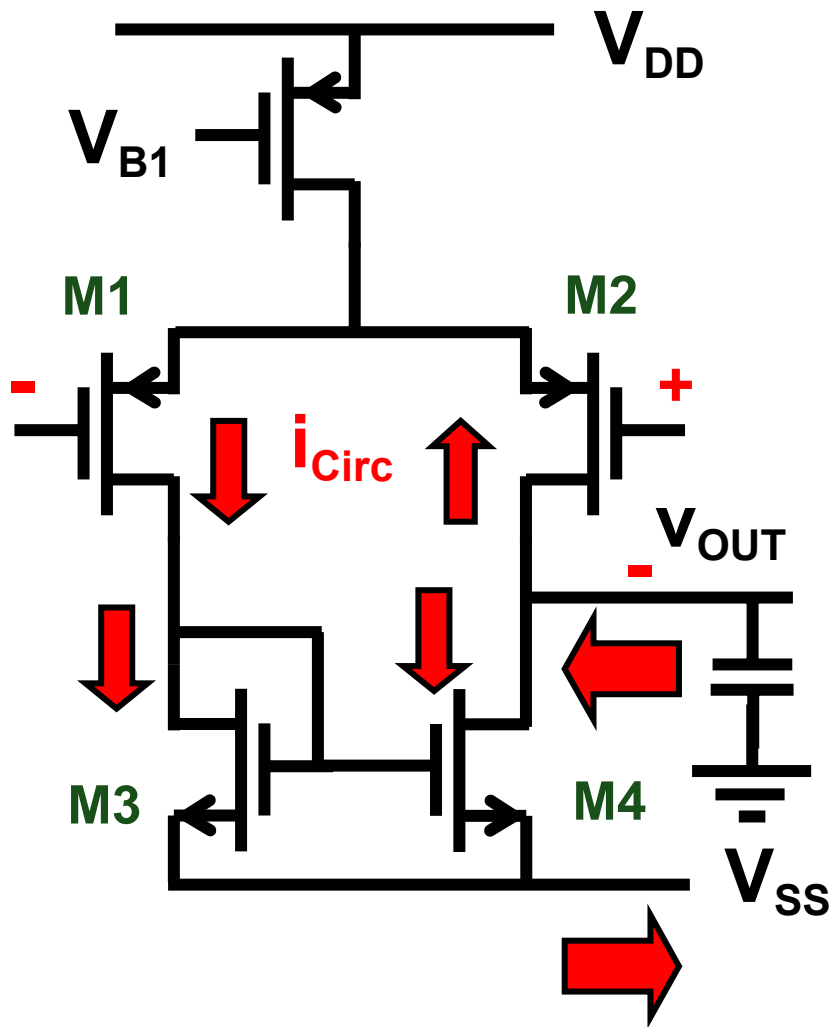

# Simple CMOS fully-differential OTA

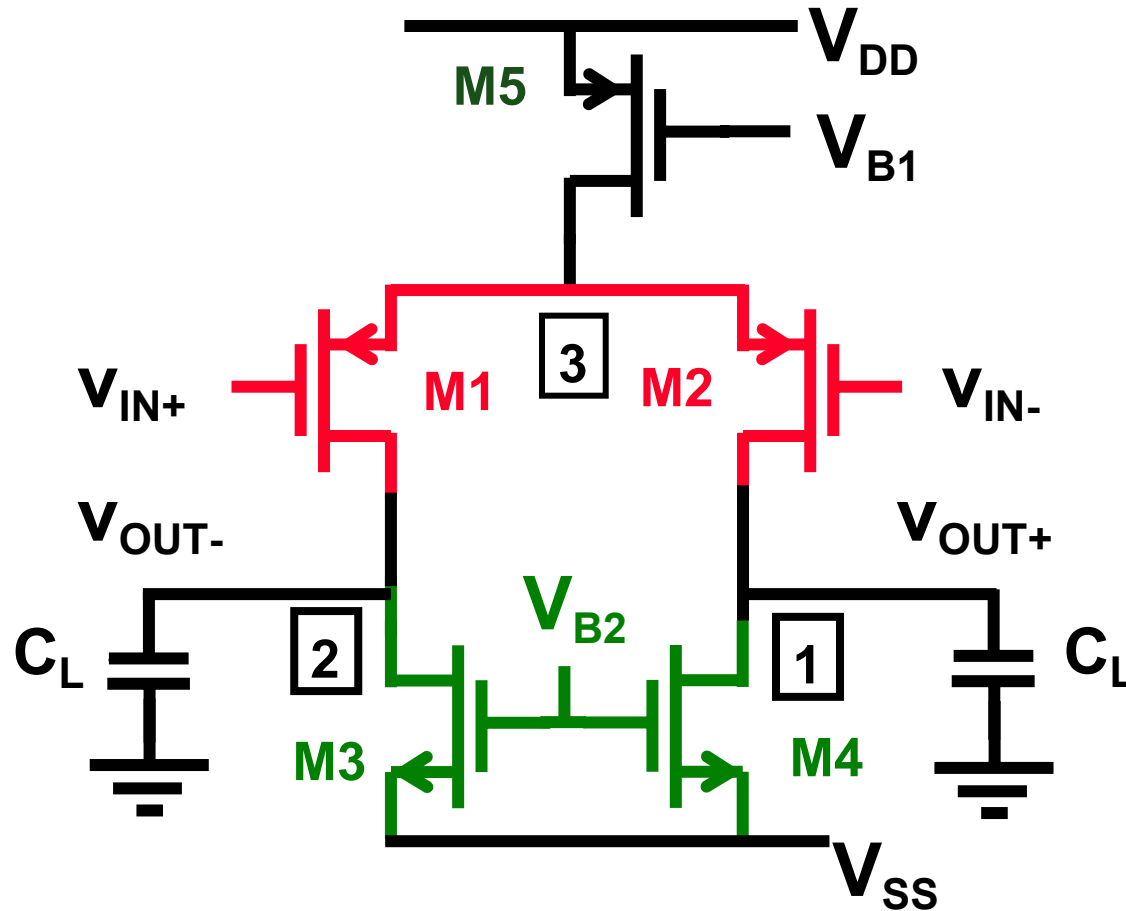


Differential pair  
No current mirror

$$GBW = \frac{g_{m1}}{2\pi C_L}$$


Problem:  
keep M1-4 in  
saturation:

Control  $V_{OUTCOM}$   
Control  $I_{DS5}$
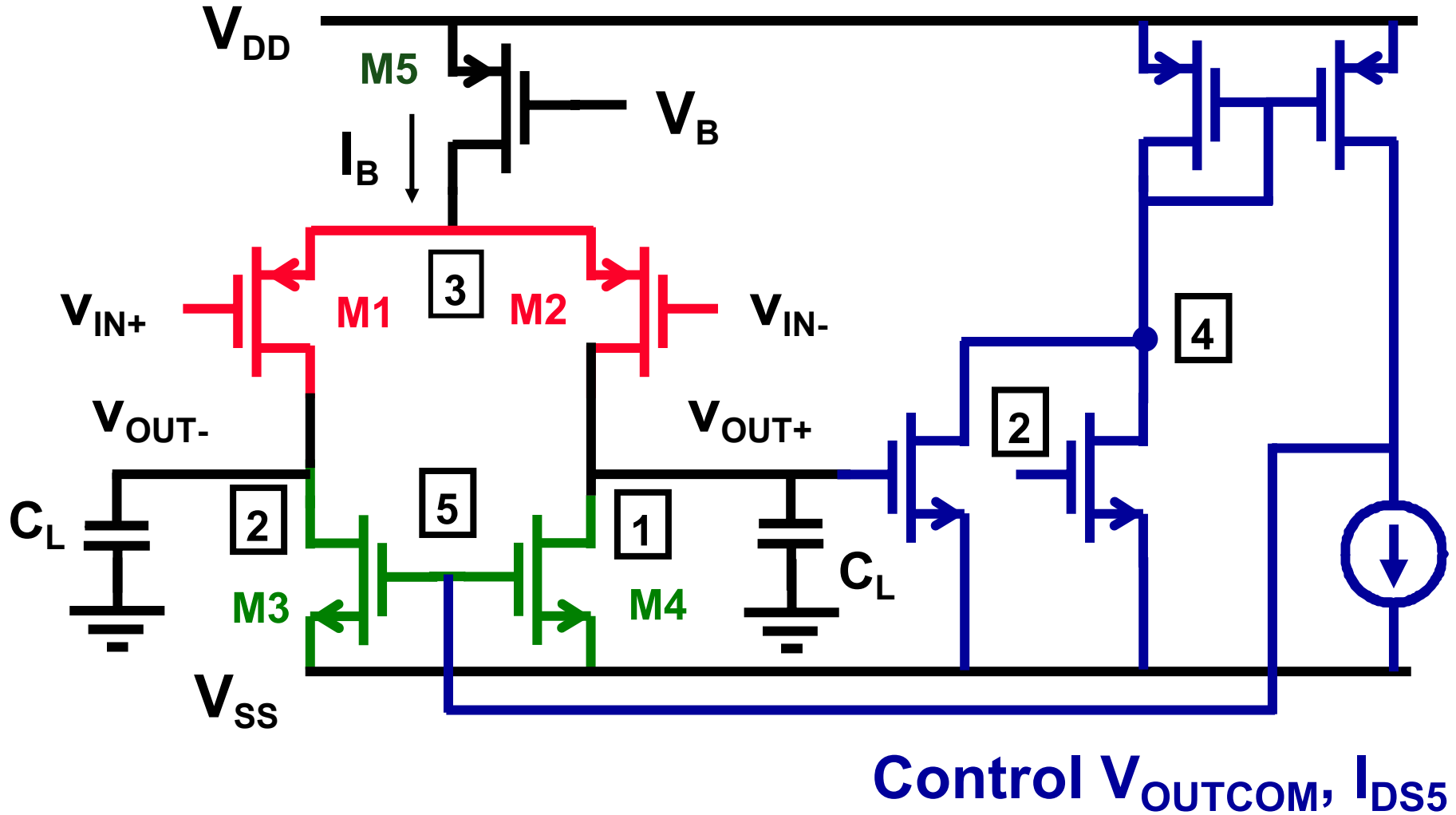
# Simple CMOS fully-diff. OTA with CMFB - 1



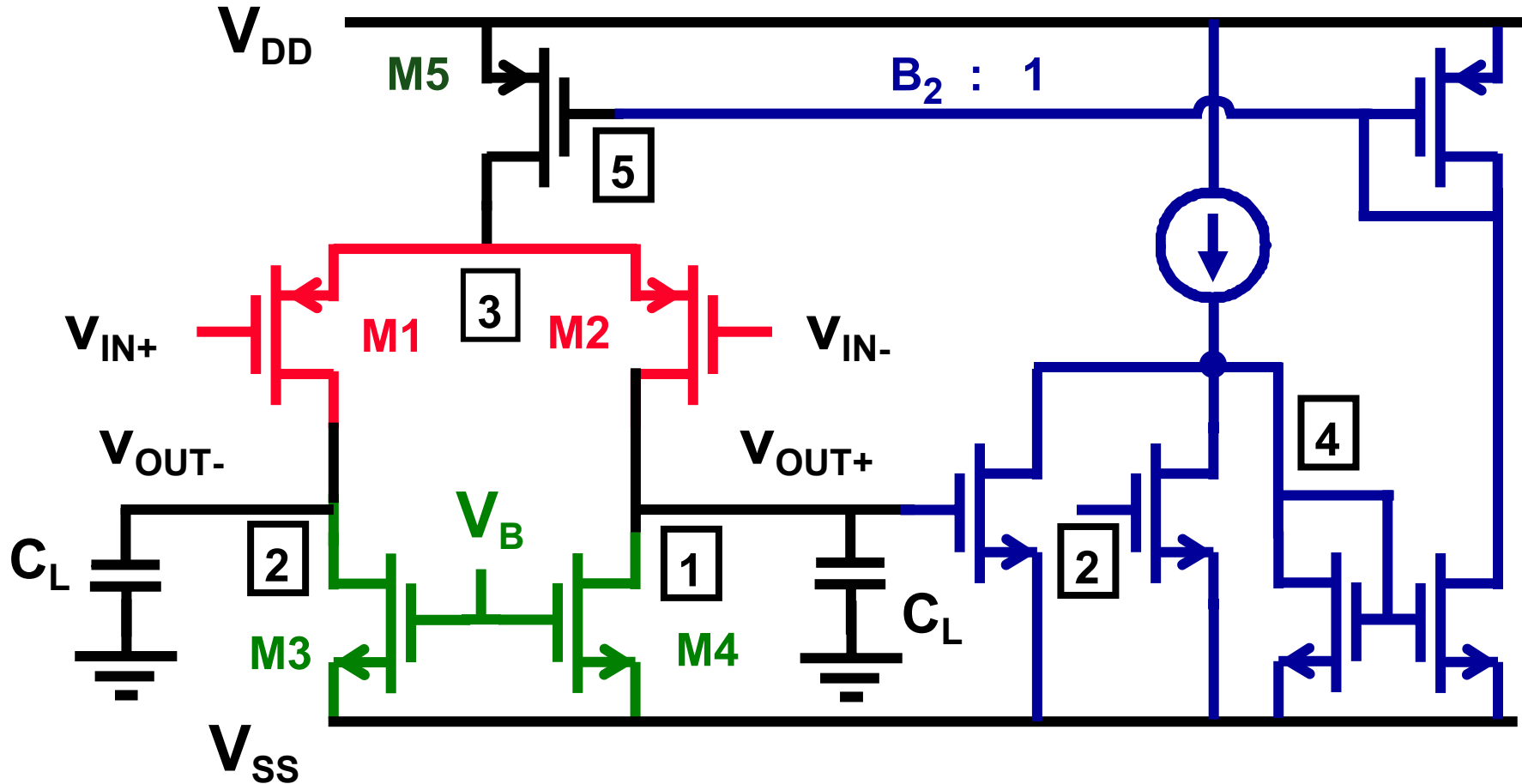
# Simple CMOS fully-diff. OTA withy CMFB - 2



Control  $V_{OUTCOM}$ ,  $I_{DS5}$

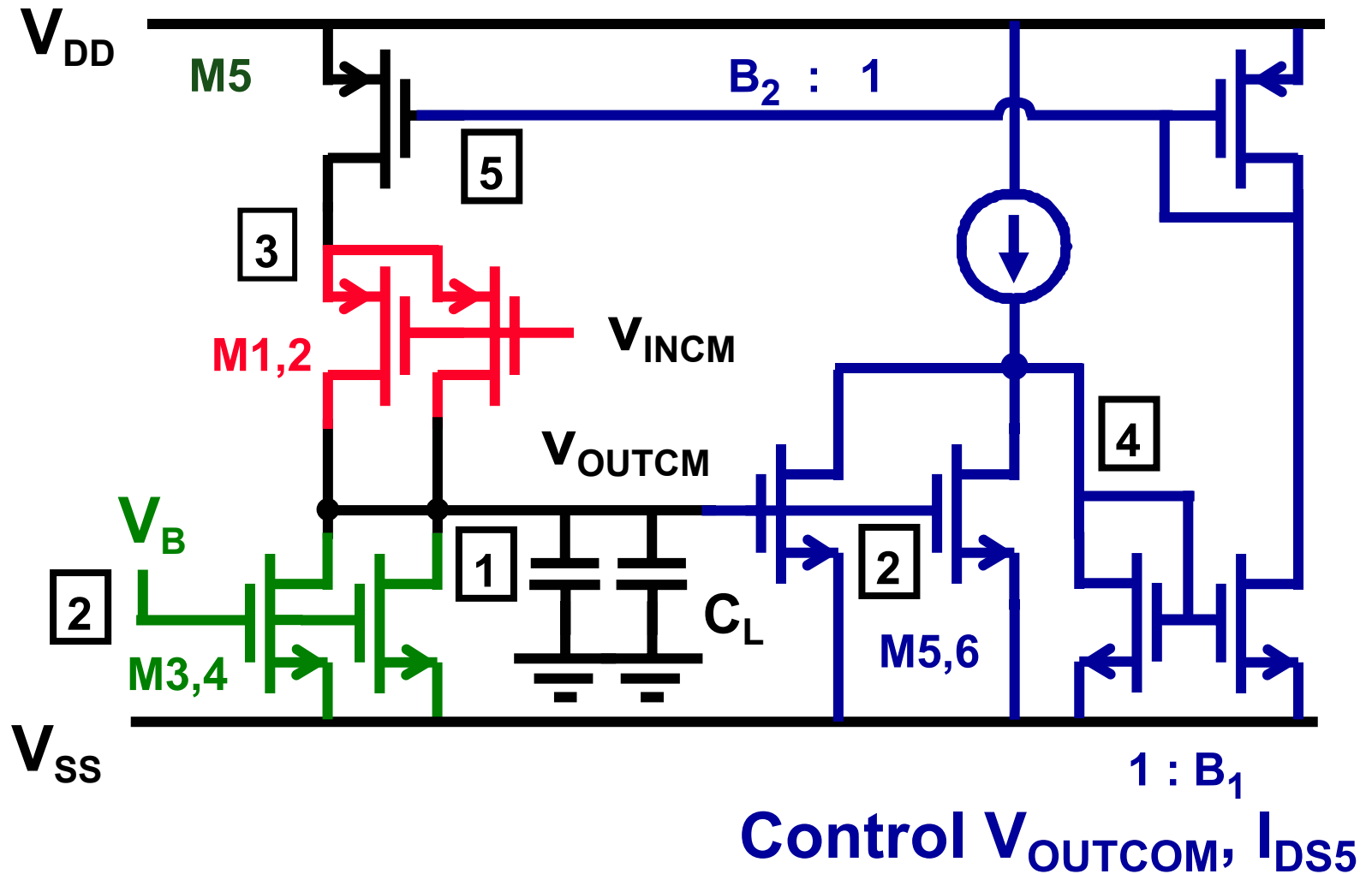
# Common-mode feedback equivalent circuit



---

# Common-mode feedback CMFB

---

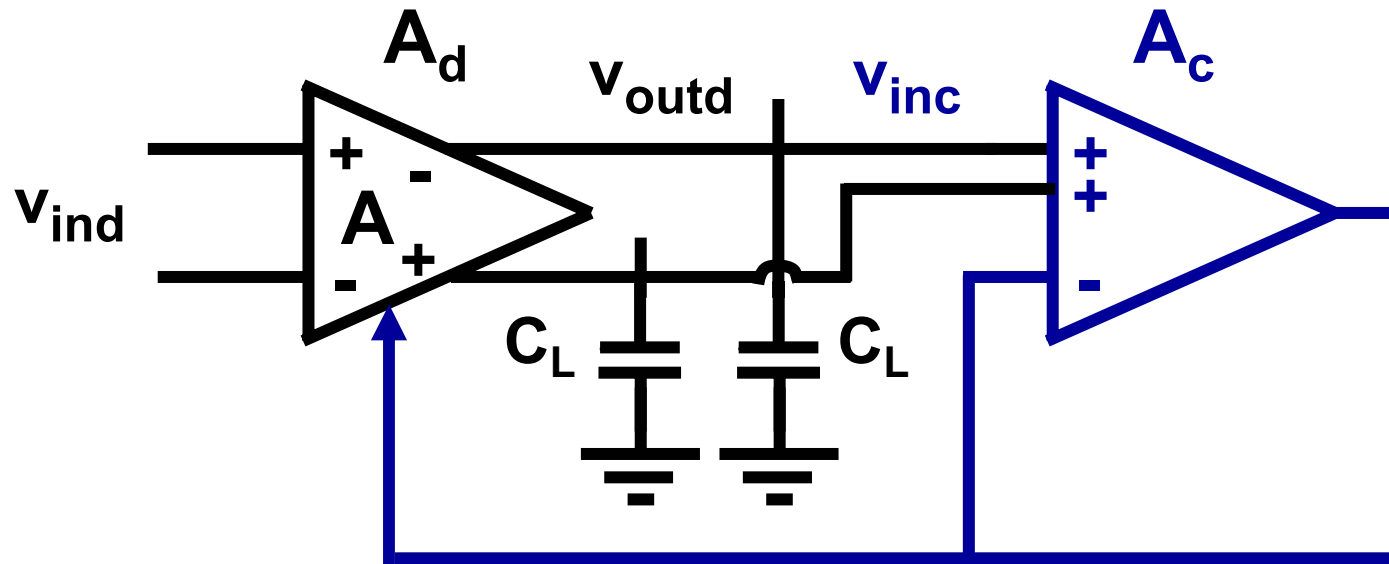

**CMFB in unity gain :  $CMRR = A_{vCM}$**

- Three tasks :**
- 1. Measure the output voltages**
  - 2. Cancel out the differential signals**
  - 3. Close the CMFB loop**



---

# Requirements fully-differential amplifiers


---

- High speed :  $GBW_{CM} > GBW_{DM}$
- Matching
- Output swing limited by :
  - Output swing of differential-mode amp
  - Input range of common-mode amp
- Low power  $P_{CM} < P_{DM}$

---

# Load capacitance ?


---

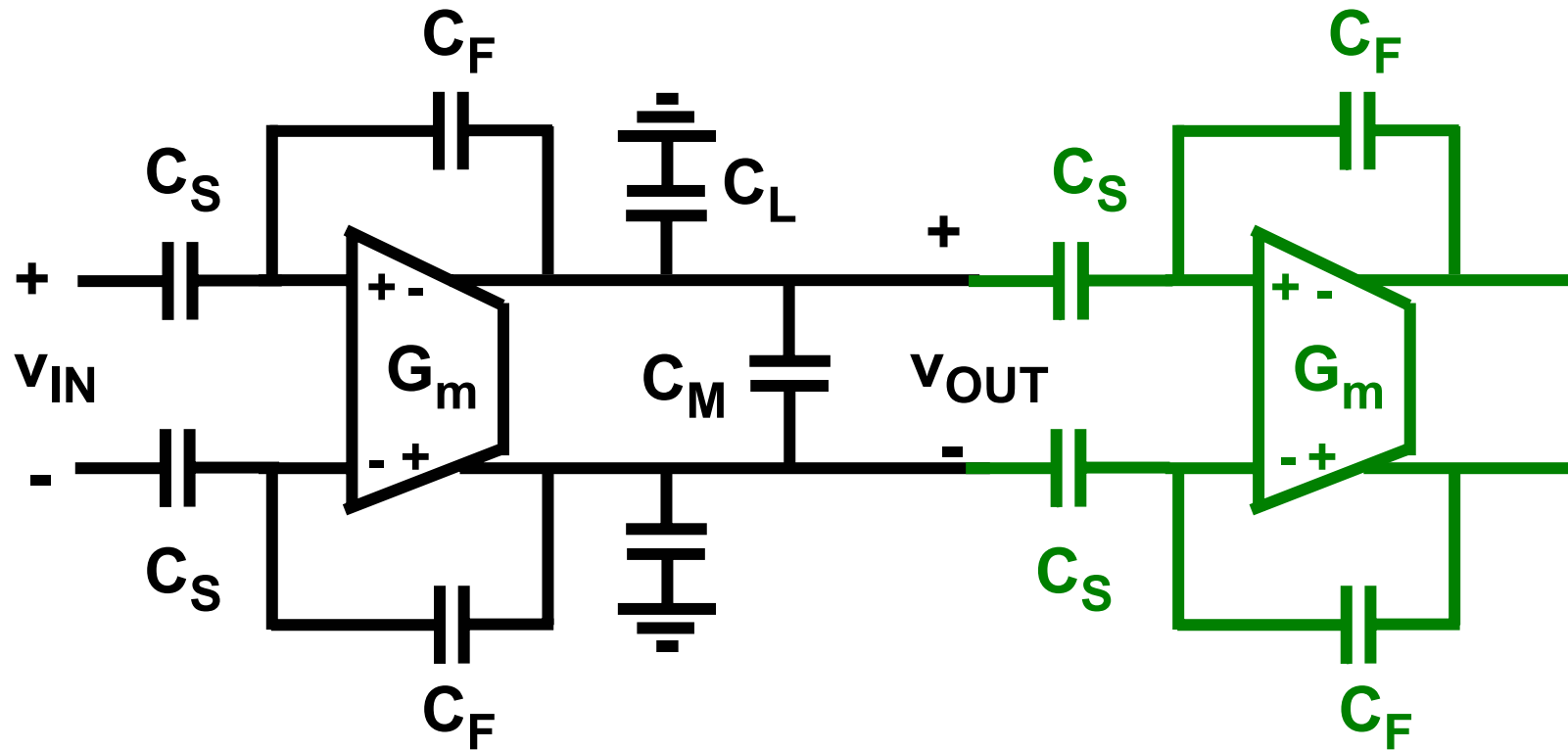

---

# Load capacitance $C_{IN}$


---

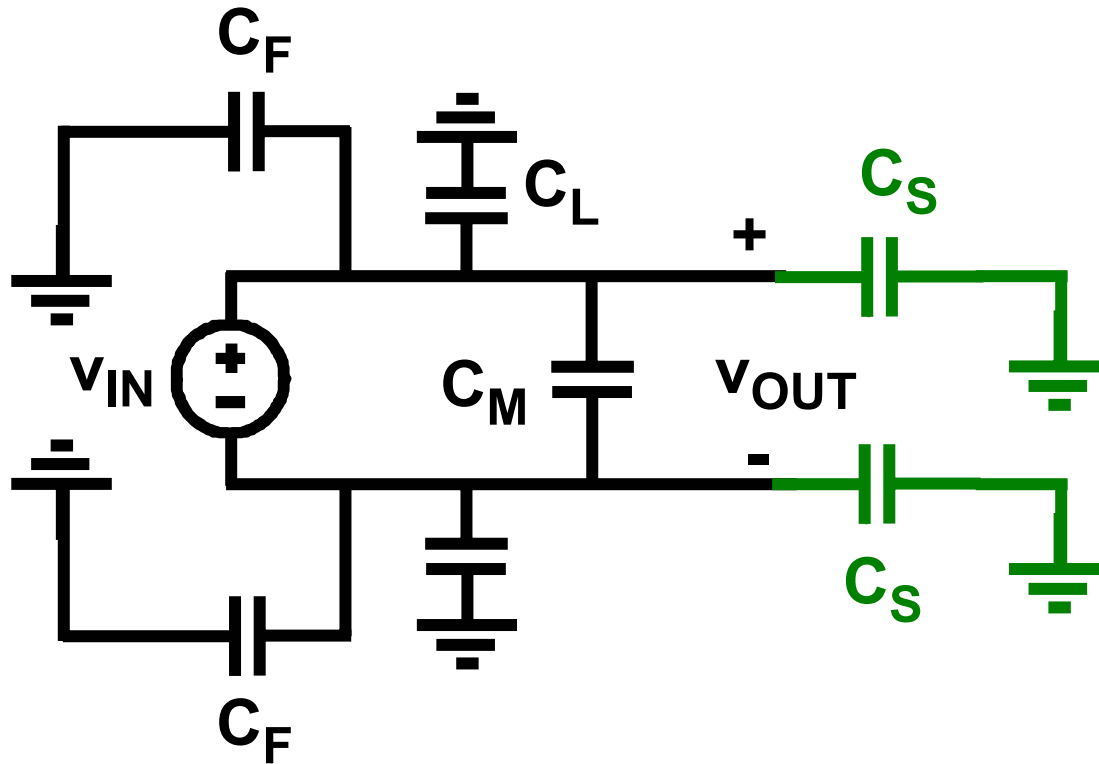

---

# Load capacitance $C_{\text{INDM}}$

---

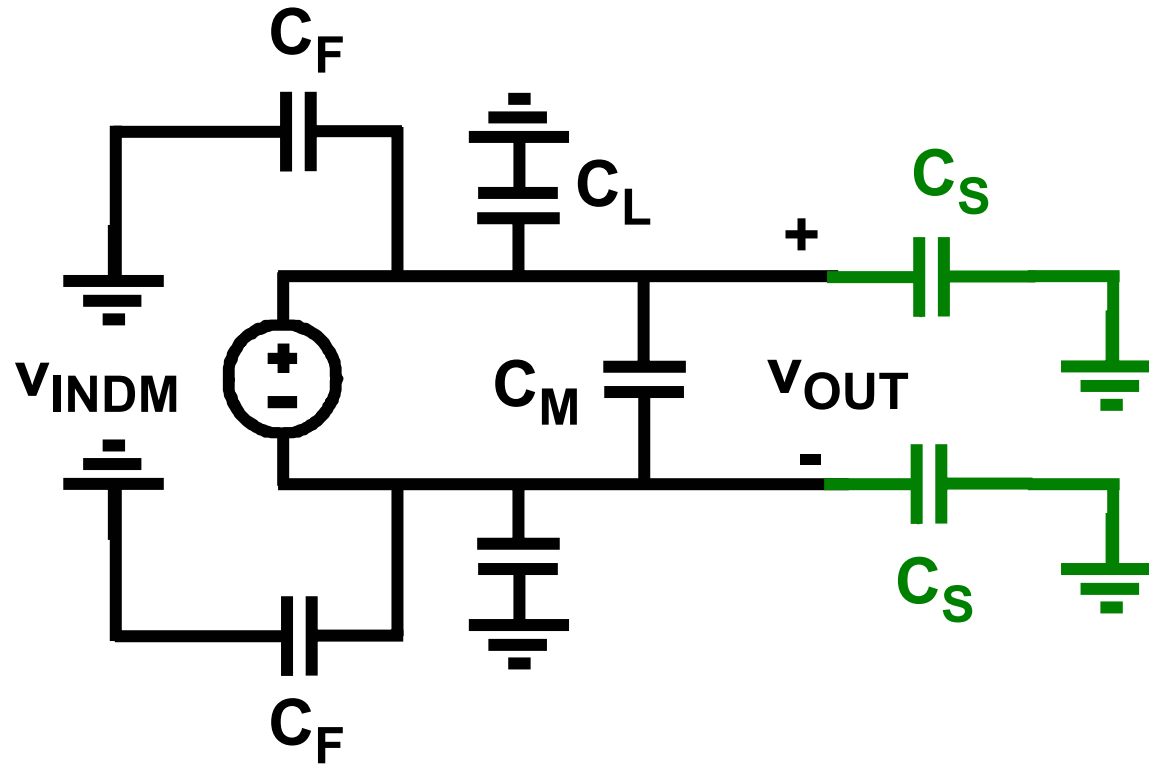


$$C_{\text{INDM}} = C_M + \frac{C_F + C_L + C_S}{2}$$

---

# Load capacitance $C_{INCM}$

---

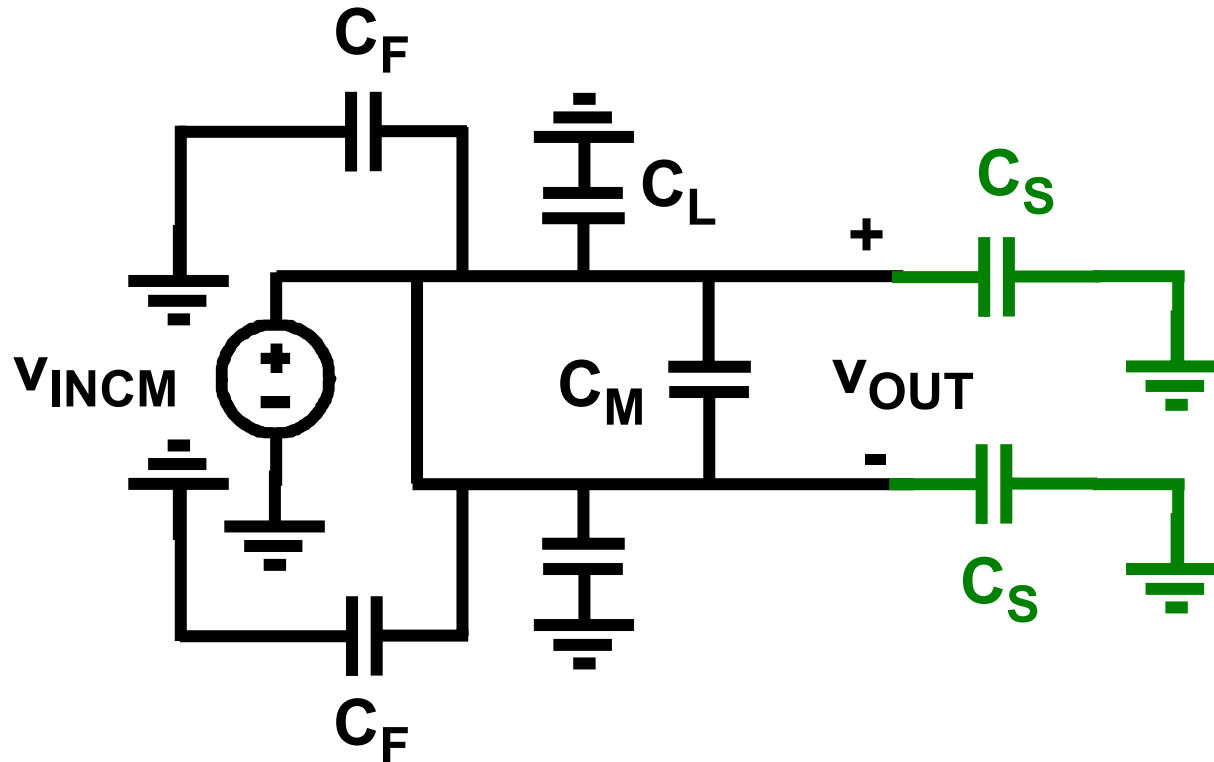


$$C_{INCM} = 2 (C_F + C_L + C_S) > C_{INDM}$$

---


# GBW<sub>DM</sub> & GBW<sub>CM</sub>

---

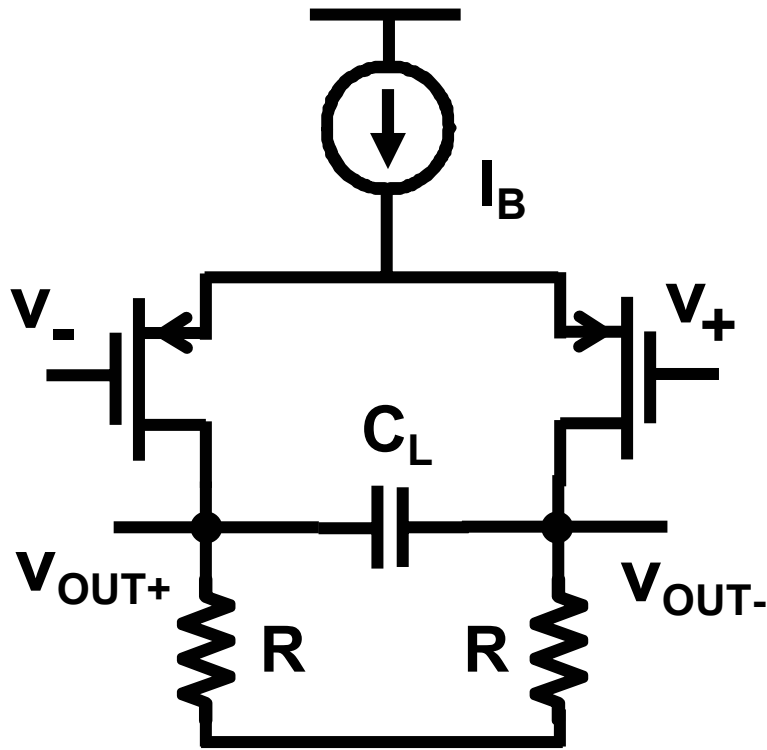

$$GBW_{DM} = \frac{g_m}{2\pi \cdot 2C_L}$$

$$C_{LCM} = 0$$

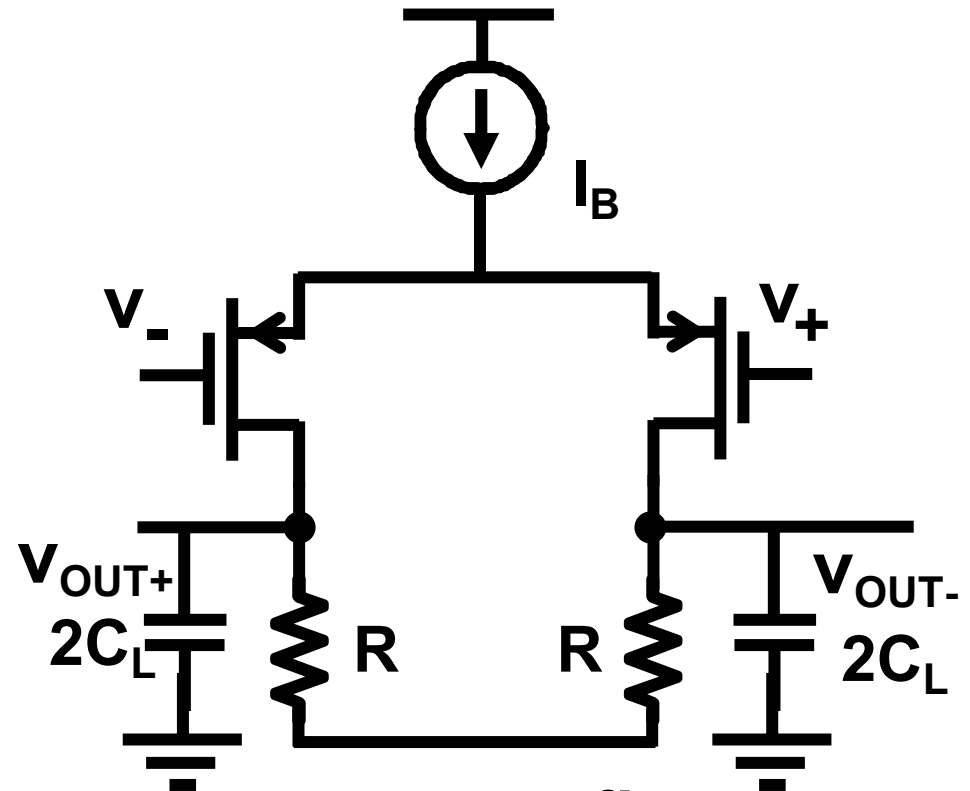

$$GBW_{DM} = \frac{g_m}{2\pi \cdot 2C_L}$$

$$C_{LCM} = 4 C_L$$


---

# Table of contents

---

- Requirements
- Fully-diff. amps with linear MOSTs
- FDA's with error amp.& source followers
- Folded cascode OTA without SF's
- Other fully-differential amps
- Exercise

# CMFB amplifier with linear MOSTs

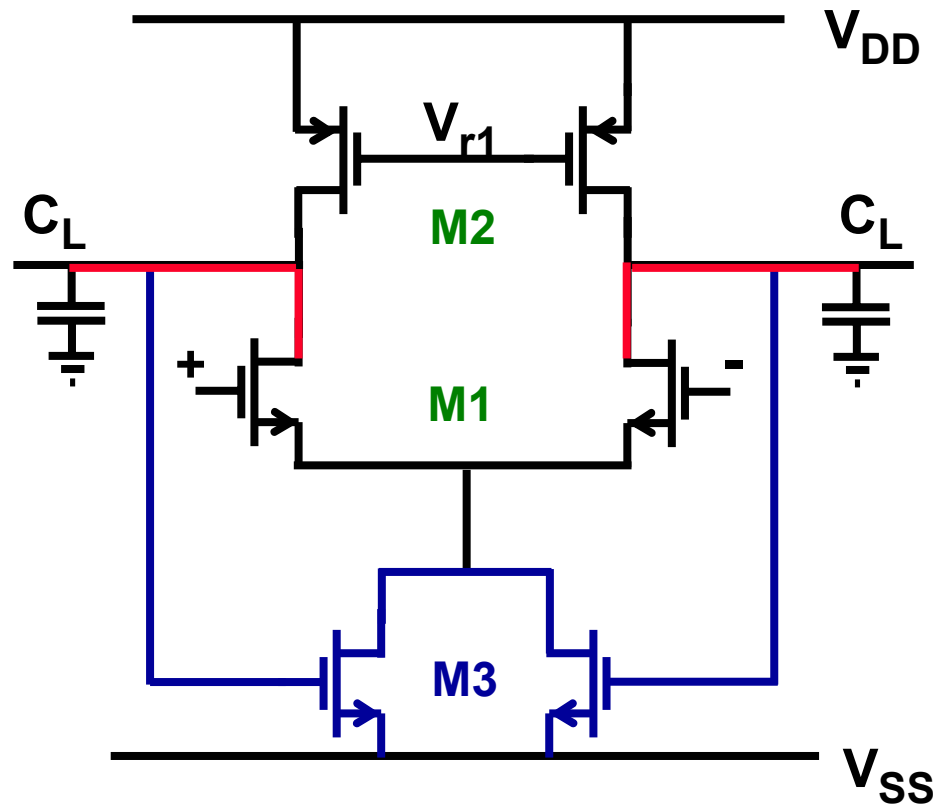

Linear MOSTs:

$$V_{DS3} \approx 200 \text{ mV}$$

$$I_{DS} = \beta V_{DS}(V_{GS} - V_T)$$

$$g_{m3} = \beta V_{DS3}$$


$$GBW_{DM} = \frac{g_{m1}}{2\pi C_L}$$

$$GBW_{CM} = \frac{g_{m3}}{2\pi C_L}$$

is always smaller !


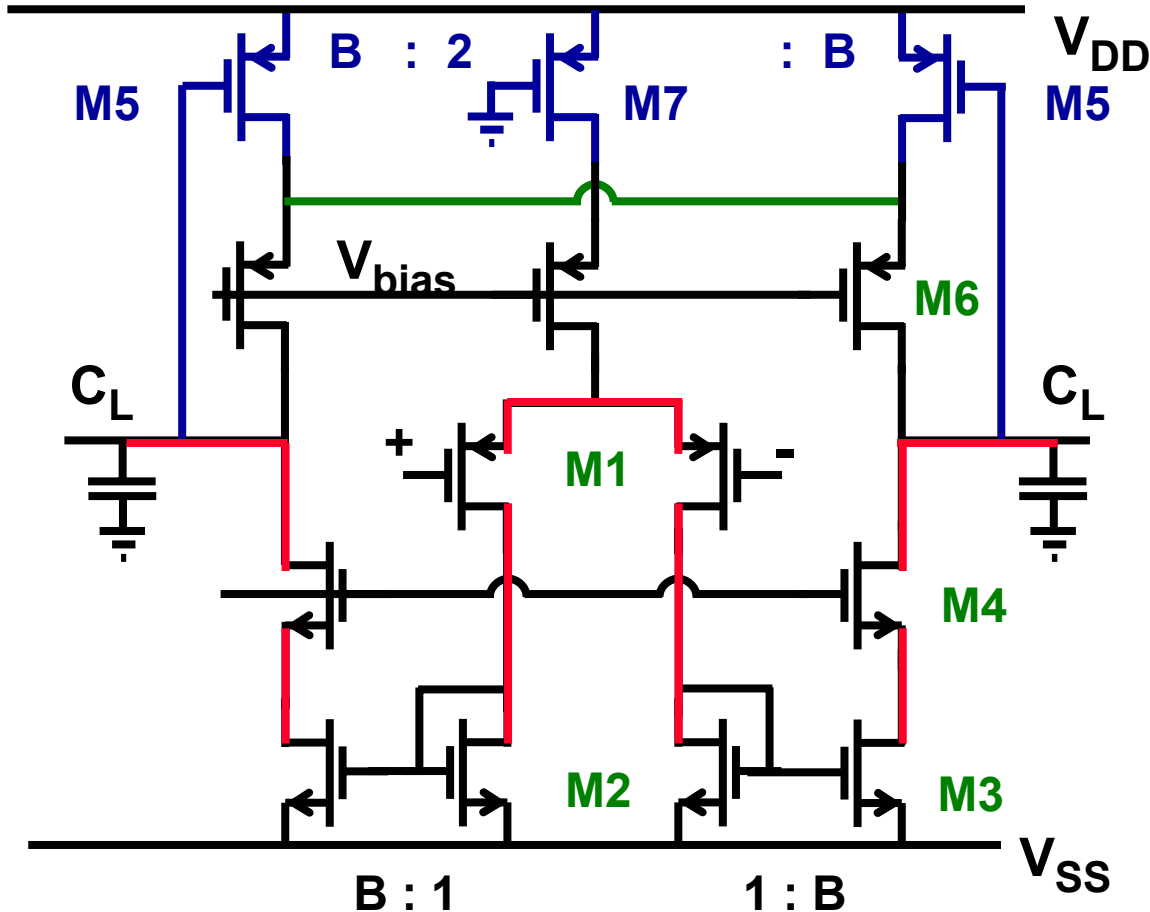
# Fully-differential amp. with linear MOSTs



Linear MOSTs:  
 $V_{DS5} \approx 200 \text{ mV}$


Cancel diff. signals

$$GBW_{DM} = B \frac{g_{m1}}{2\pi C_L}$$

$$GBW_{CM} = \frac{g_{m5}}{2\pi C_L}$$

is always smaller !  
 even with M5 in wi !
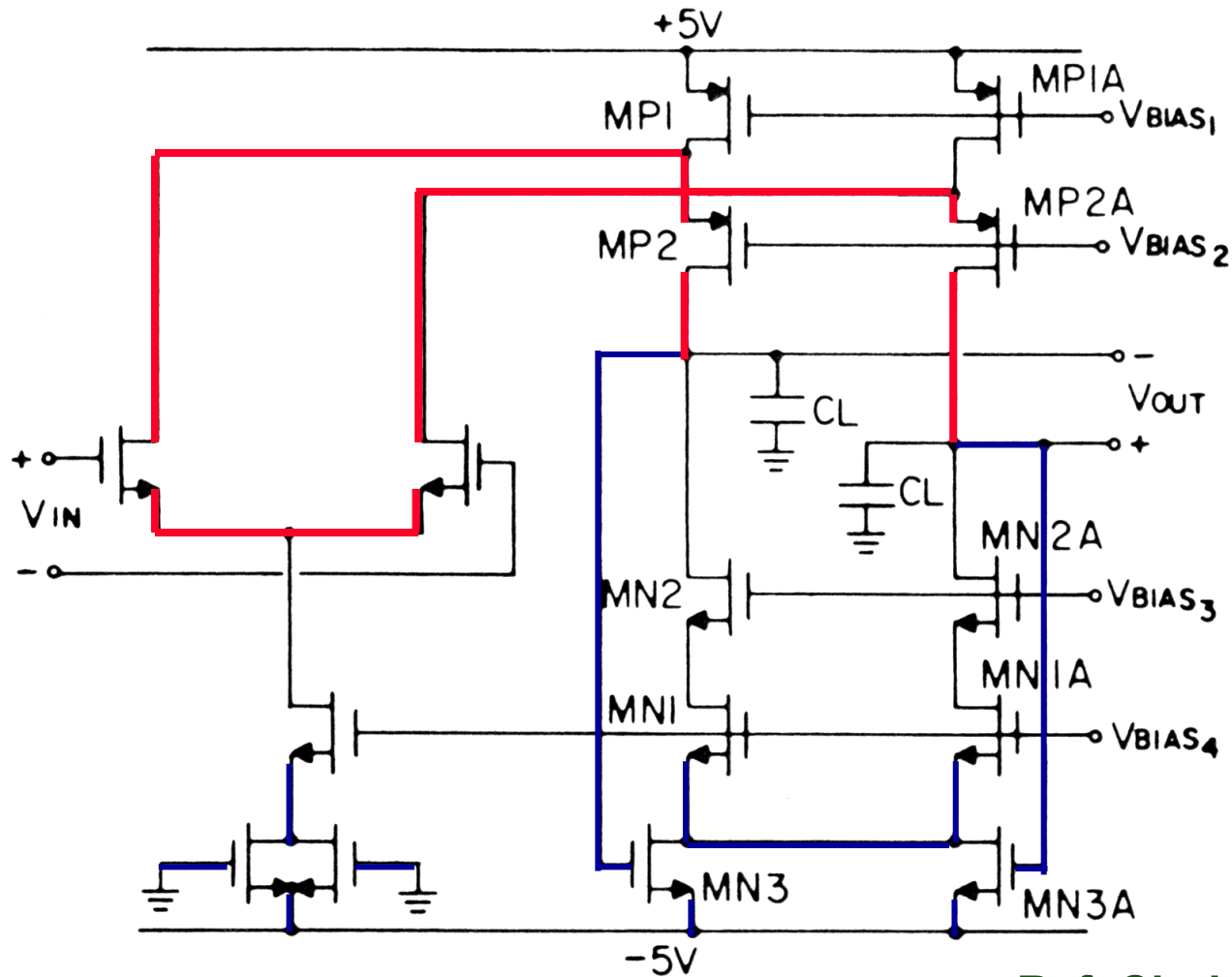
# Fully-differential amp. with linear MOSTs




**Linear MOSTs:**  
 $V_{DS3} \approx 200 \text{ mV}$

Ref. Choi, JSSC, Dec.83, 652-653

---


# Total amplifier schematic

---

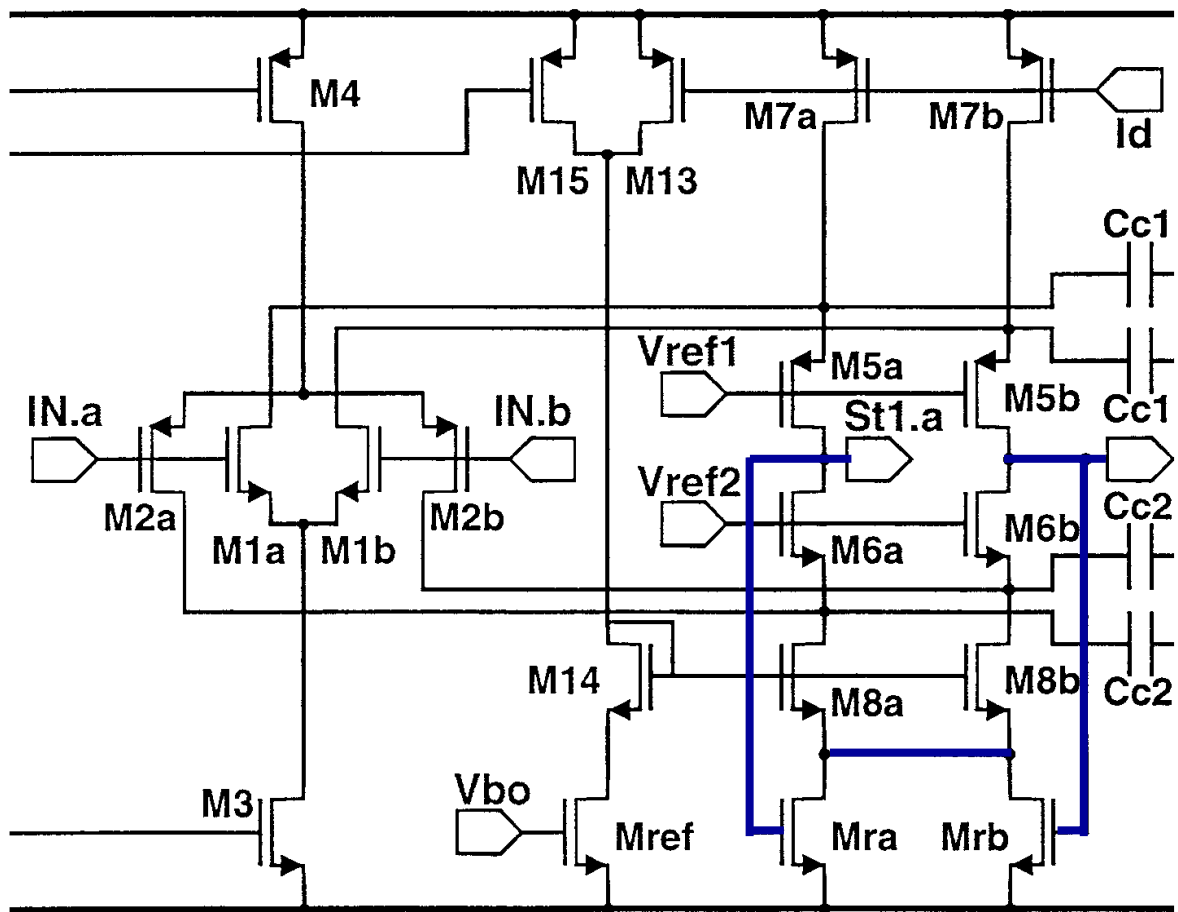


E.Peeters etal, CICC 1997

# Fully-differential OTA with FF

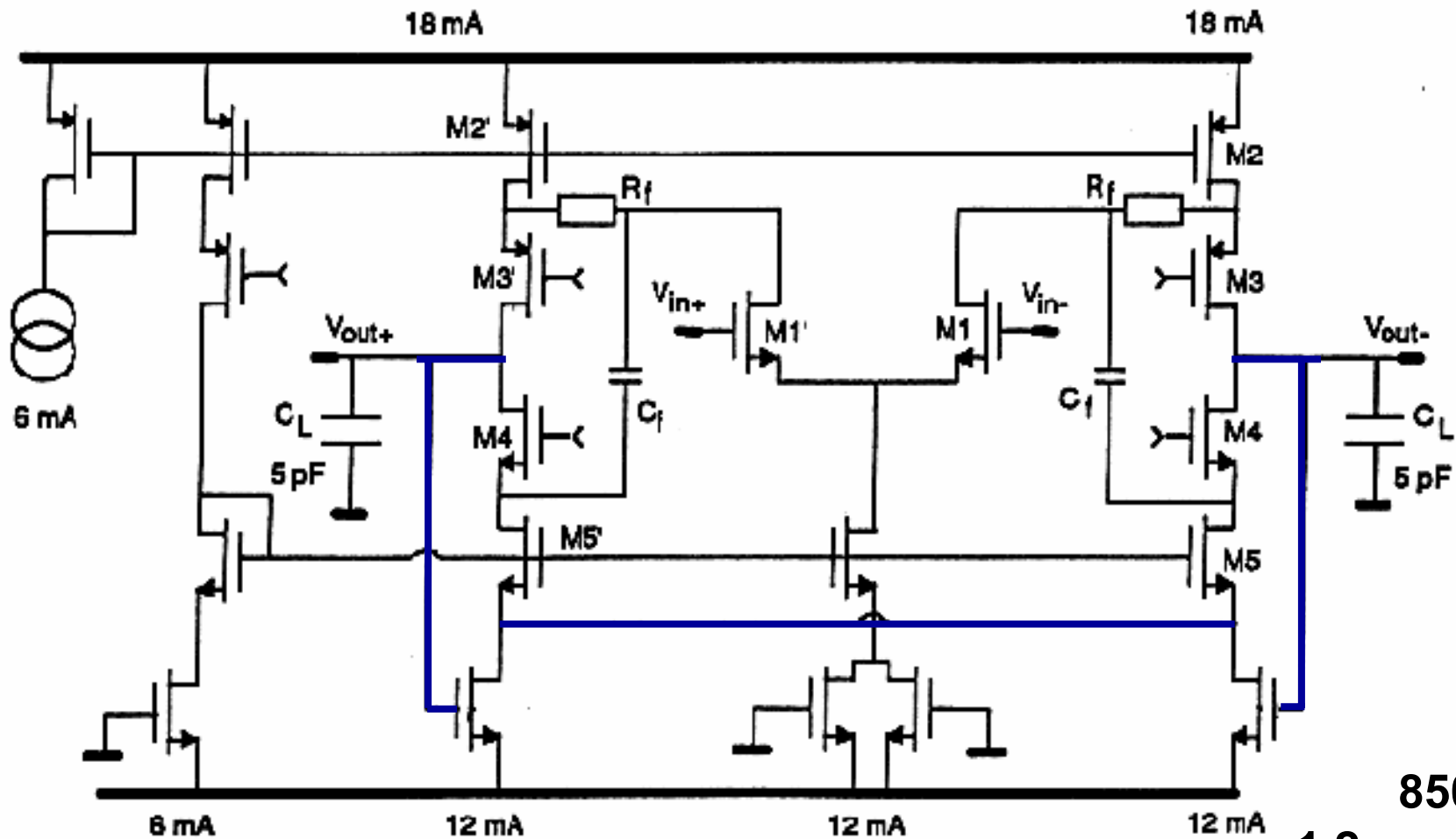

F. Op't Eynde, Kluwer Ac. 1993

# Transconductor with $C_{DG}$ compen.

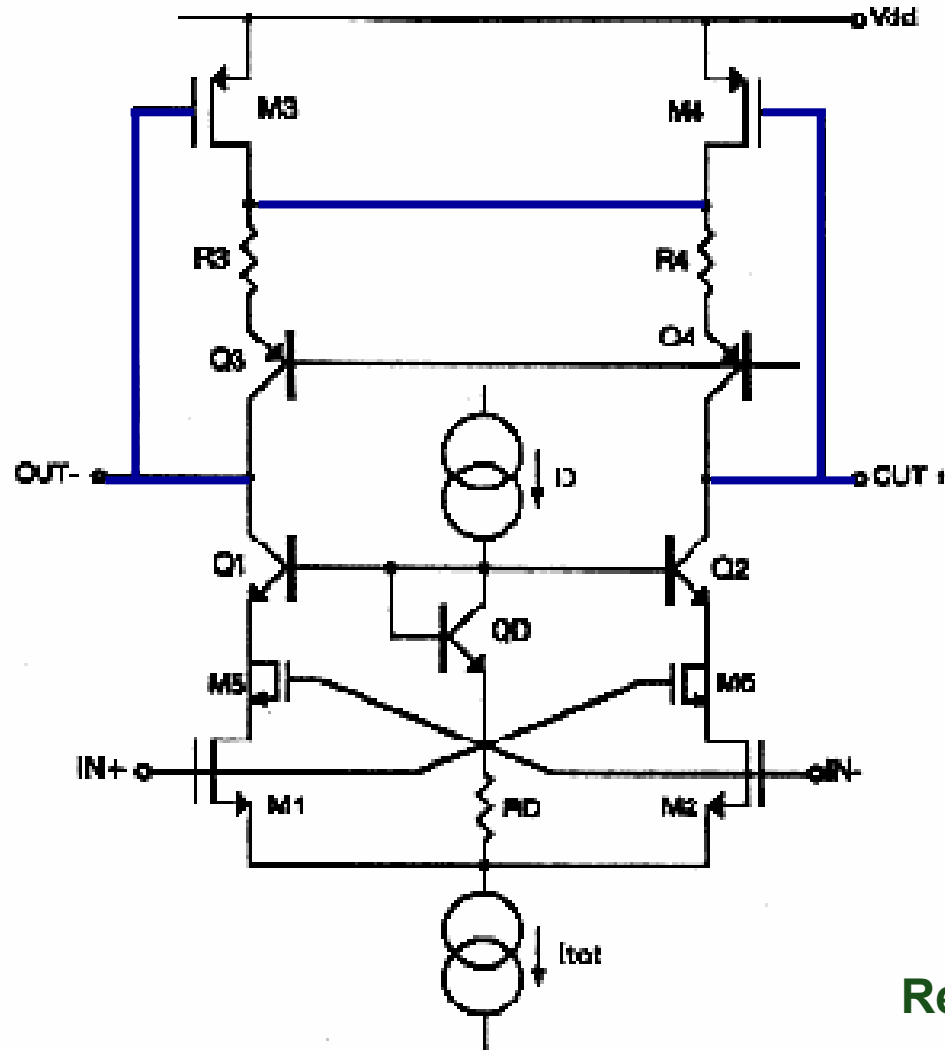

$$V_{DS1} = R_D I_D \approx 0.2 \text{ V}$$

$$I_{DS1} = \beta_1 V_{DS1} (V_{GS1} - V_T)$$

$$g_{m1} = \beta_1 V_{DS1} \text{ is constant}$$

Ref. Alini, JSSC, Dec.92, pp.1905-1915

---

# Table of contents


---

- Requirements
- Fully-diff. amps with linear MOSTs
- **FDA's with error amp.& source followers**
- Folded cascode OTA without SF's
- Other fully-differential amps
- Exercise


---

# Fully-differential amplifier with resistive CMFB

---

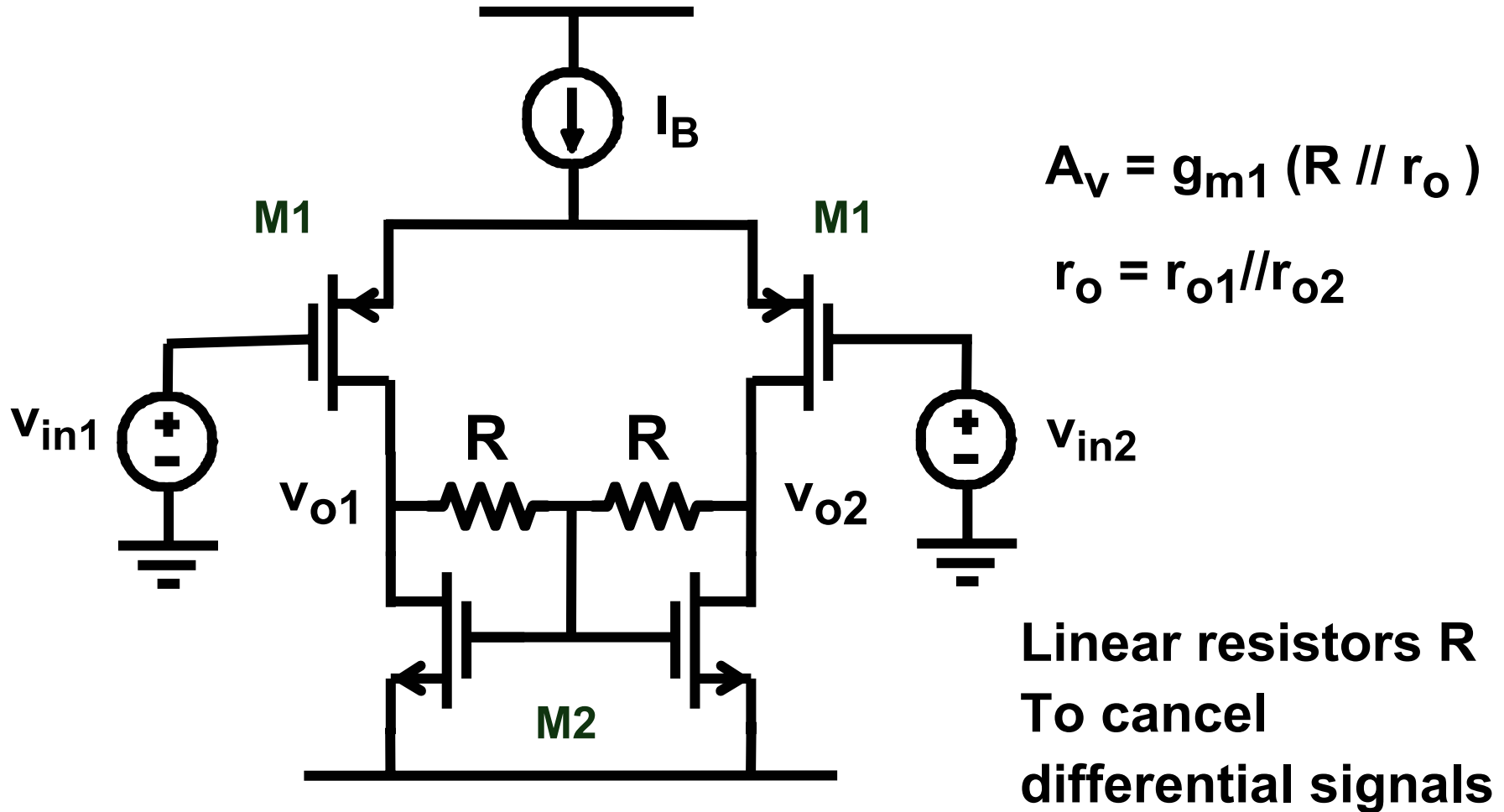
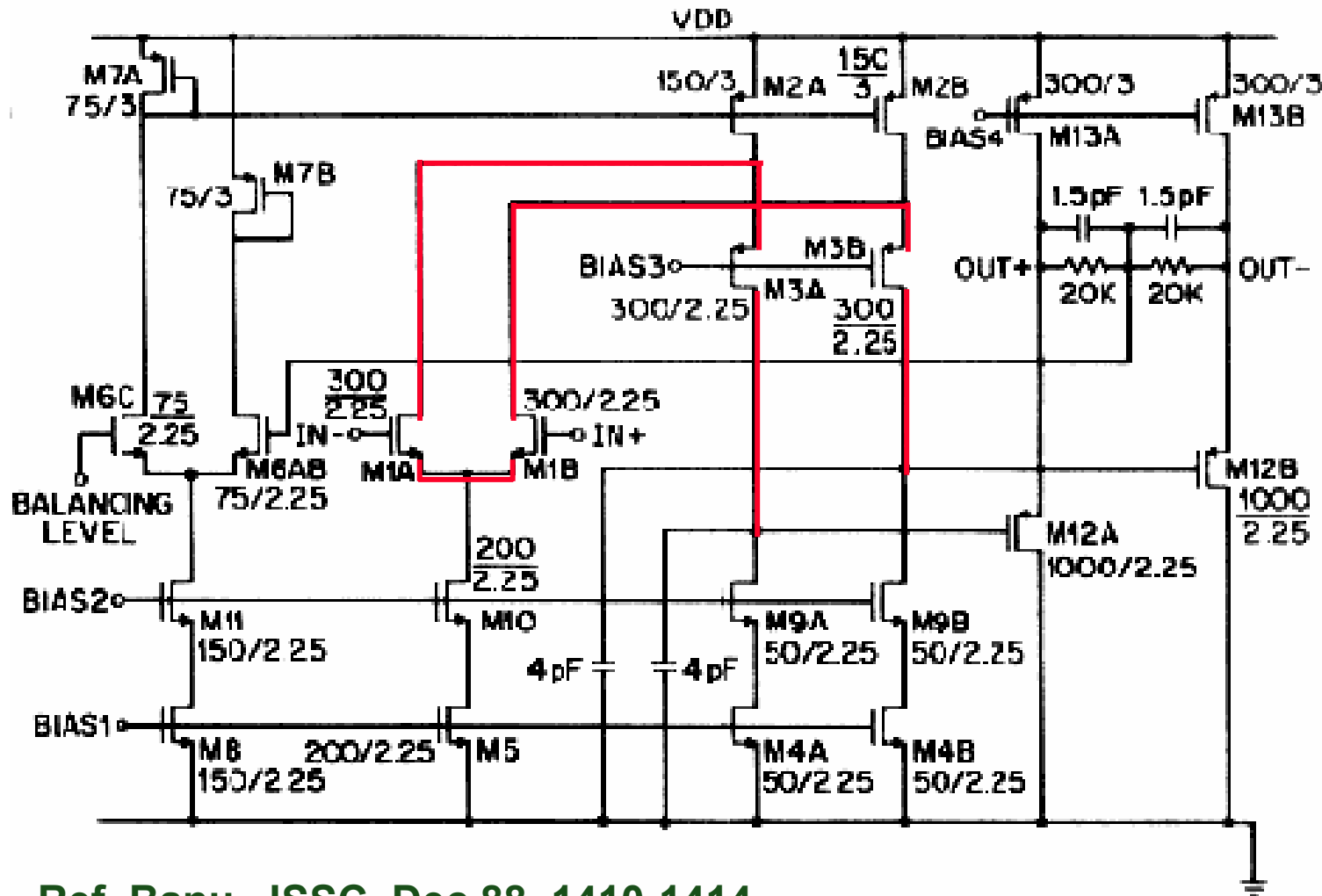
# Fully-diff. amp. with source followers: Diff. mode




$$GBW_{DM} = \frac{g_{m1}}{2\pi C_L}$$

$$C_L = 4 \text{ pF}$$

Ref. Banu, JSSC, Dec.88, 1410-1414


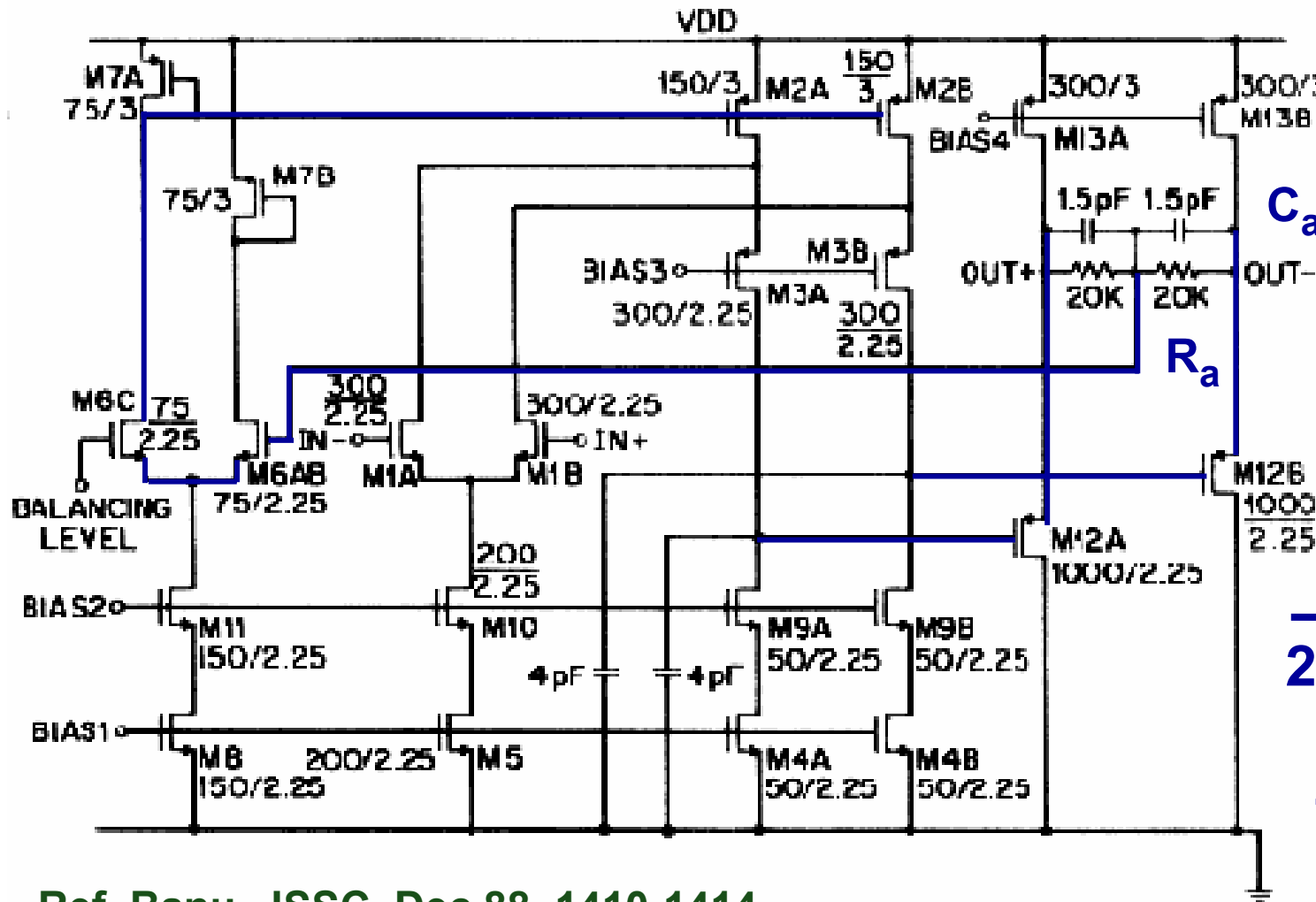
# Fully-diff. amp. with source followers: CM



$$GBW_{CM} = \frac{g_{m6}}{4\pi C_L}$$

$$f_{ndCM} = \frac{4}{2\pi R_a (C_{GS6} + C_a)}$$

$$f_z = \frac{1}{2\pi R_a C_a}$$

Ref. Banu, JSSC, Dec.88, 1410-1414


---

# Table of contents

---

- Requirements
- Fully-diff. amps with linear MOSTs
- FDA's with error amp.& source followers
- **Folded cascode OTA without SF's**
- Other fully-differential amps
- Exercise

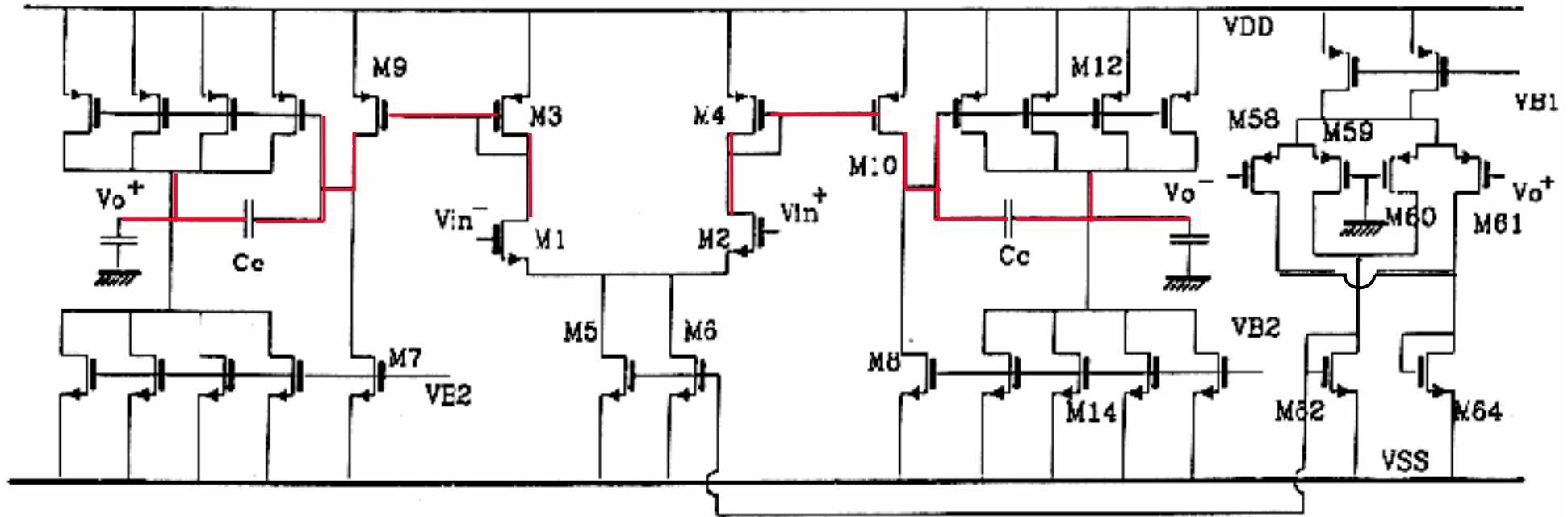
# Fully-diff amp. with error amplifier: Diff. mode



$$GBW_{DM} = \frac{g_{m1}}{2\pi C_c}$$

Ref. Ribner, CICC 85; Haspeslagh, CICC 88
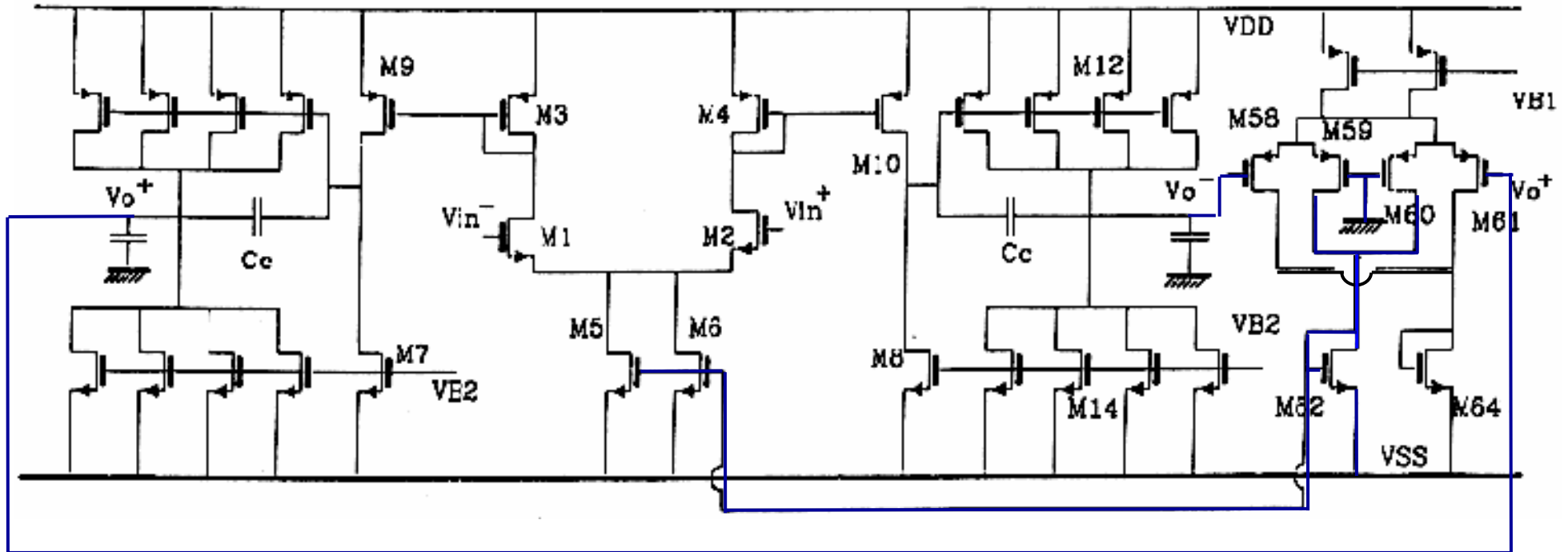
# Fully-diff amp. with error amp. : Common mode



Nonlinear !


$$GBW_{CM} = \frac{g_{m58}}{4\pi C_c}$$

Ref. Ribner, CICC 85; Haspeslagh, CICC 88

---

# Class AB fully-differential amplifier

---

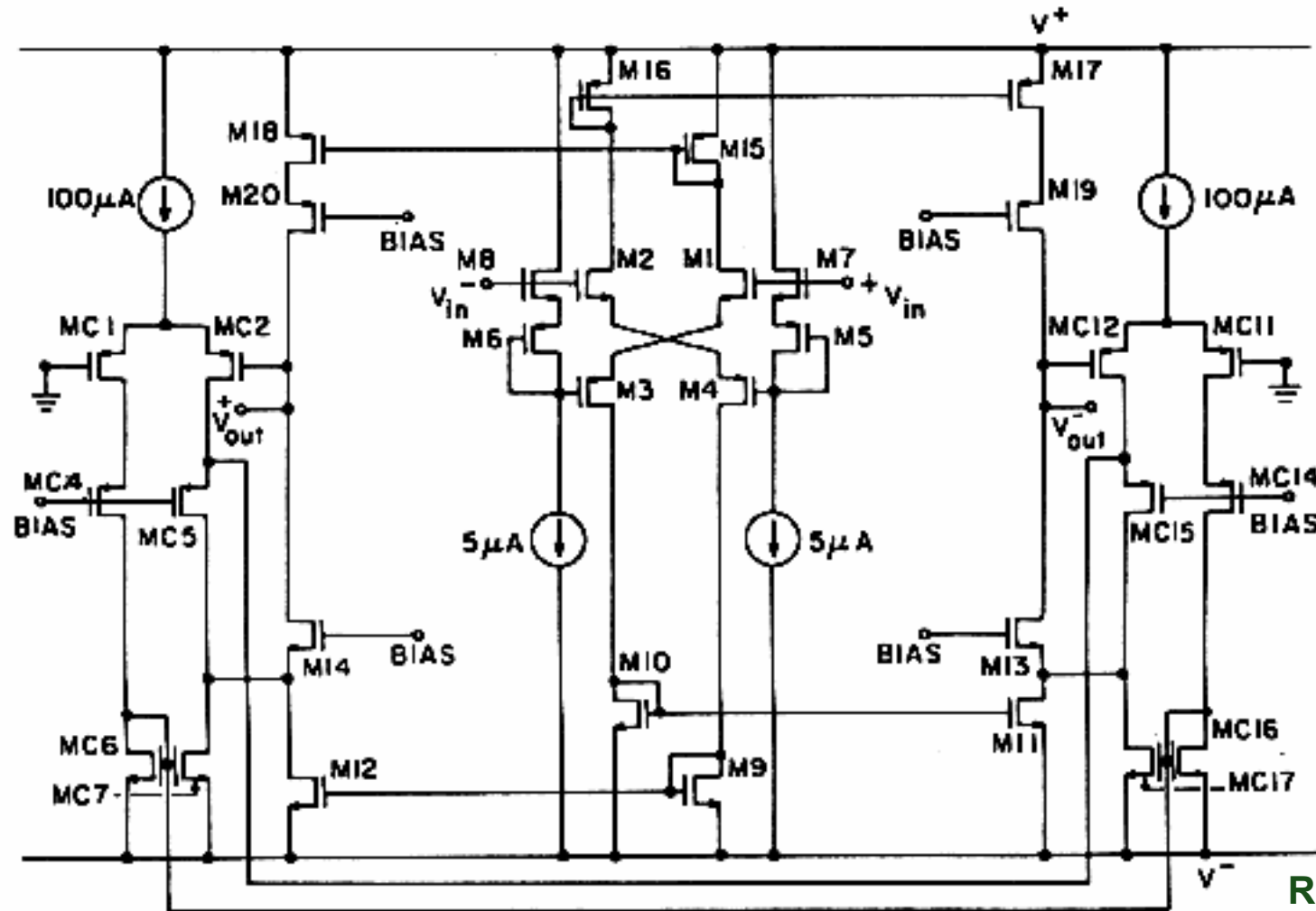

Ref. Lee, JSSC  
Dec.85, 1103-1113

---

# Comparison

---

<b>Criterion</b>	<b>Linear MOST</b>	<b>Error amp Source foll.</b>	<b>Error amp. Quad amp.</b>
<b><math>GBW_{CM}/GBW_{DM}</math></b>	<b>&lt; 0.1</b>	<b>&gt; 1</b>	<b>&gt; 1</b>
<b>Required tol.</b>	<b>&lt; 1 %</b>	<b>&lt; 6 %</b>	<b>&lt; 6 %</b>
<b>Diff.output swing Is limited by</b>	<b>0.8 <math>V_{DDSS}</math> cascodes</b>	<b>0.4 <math>V_{DDSS}</math> source foll.</b>	<b>0.4 <math>V_{DDSS}</math> cm input</b>
<b>Power dissipation</b>	<b>1 amp</b>	<b>3 amps</b>	<b>2 amps</b>


---

# Table of contents

---

- Requirements
- Fully-diff. amps with linear MOSTs
- FDA's with error amp.& source followers
- Folded cascode OTA without SF's
- Other fully-differential amps
- Exercise
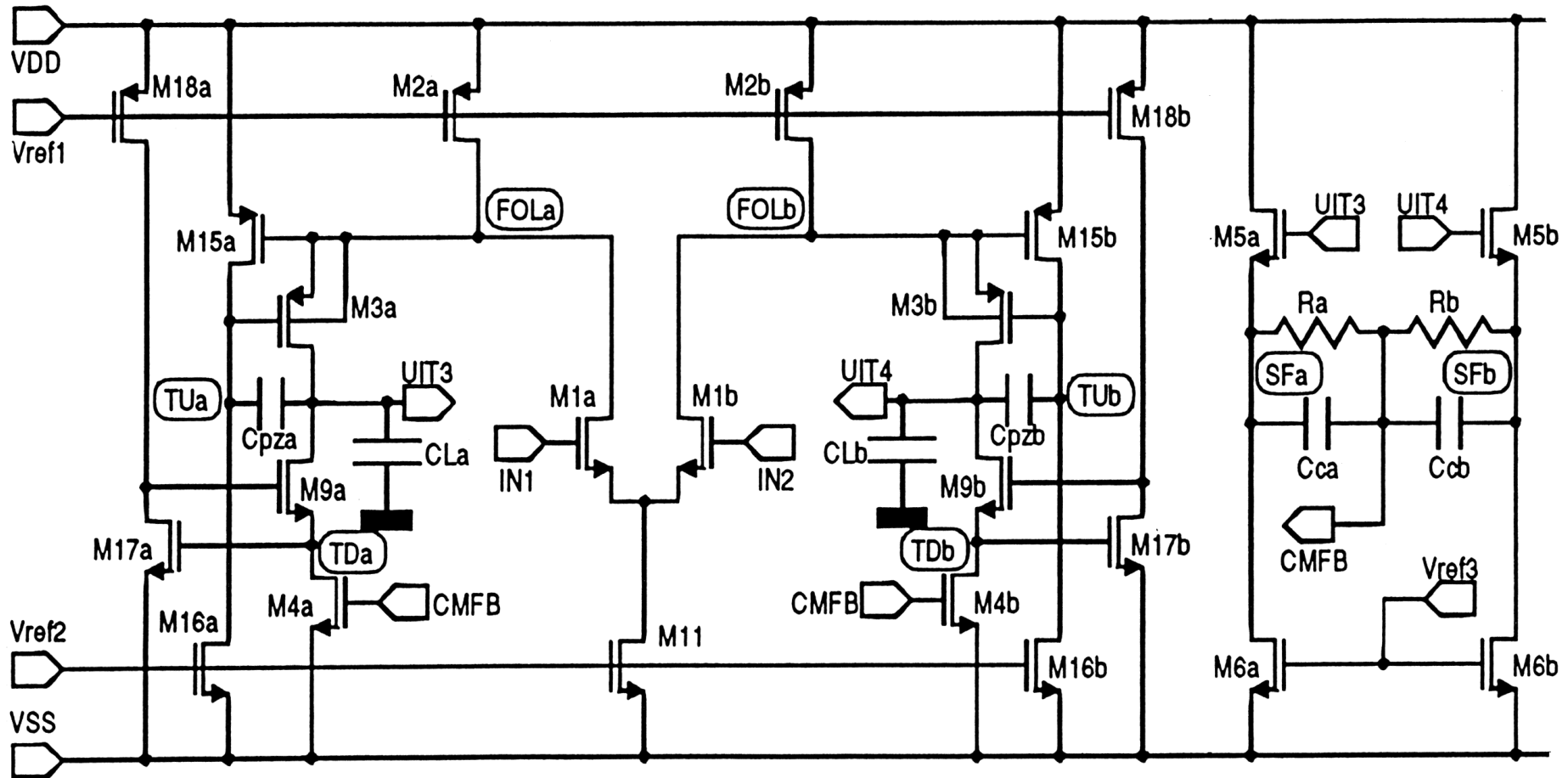
# Fully-differential amplifier with gain boosting






---

# Low-voltage (1.1 V) DIDO

---

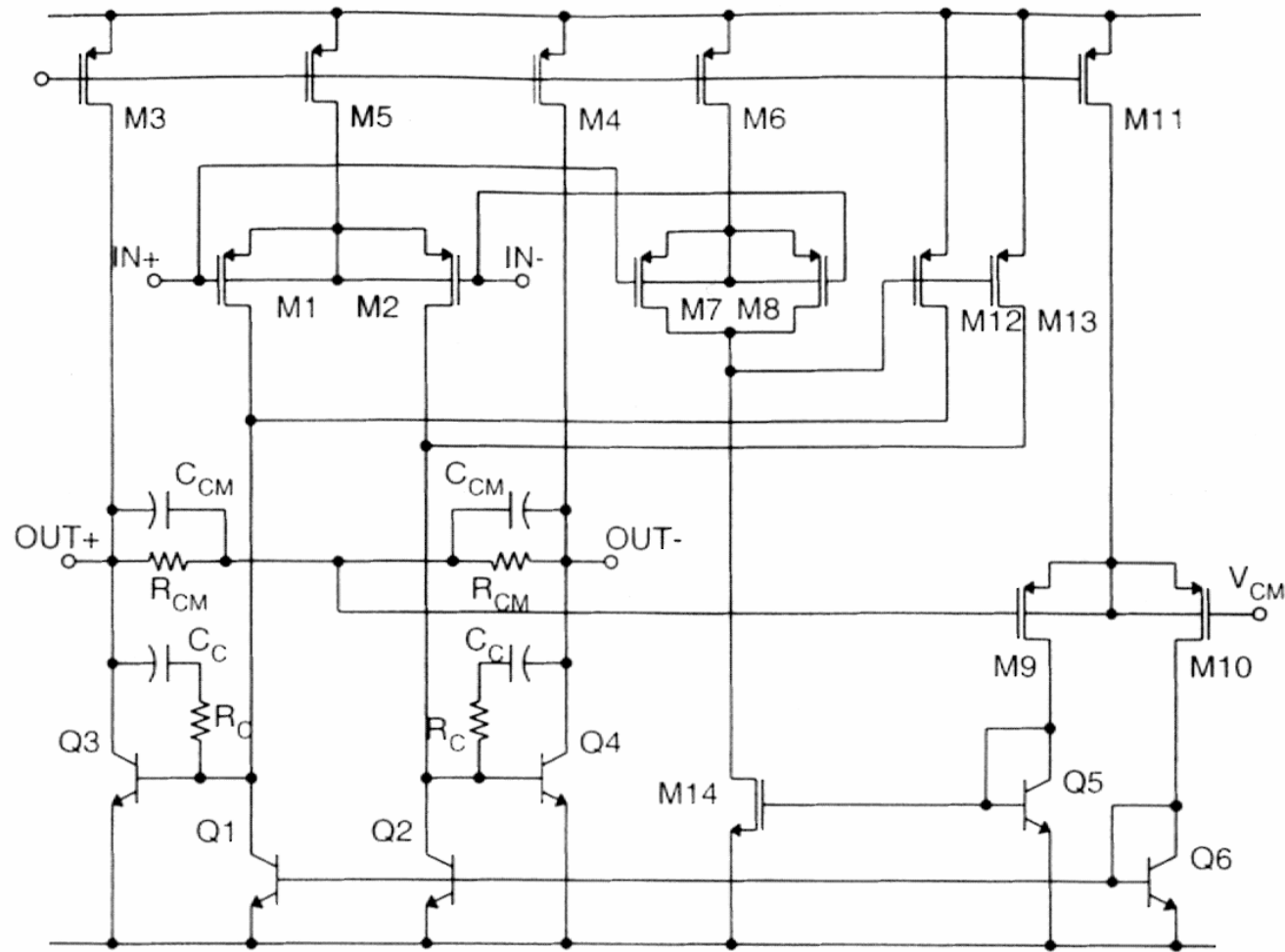


Gata, JSSC Dec.02  
1670-1678

---

# Linear CM amplifier


---

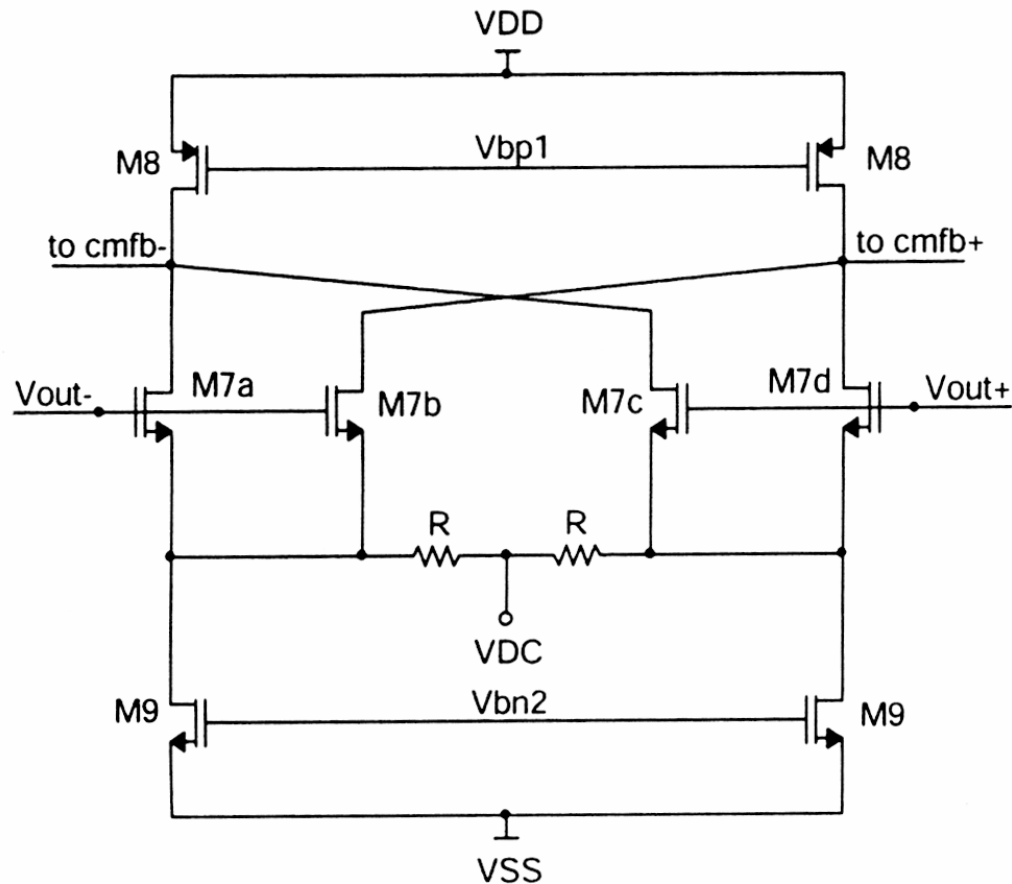

$$V_{outCM} = VDC + V_{GS7}$$

Ref. Hernandez, JSSC  
Aug.05, 1610-1617
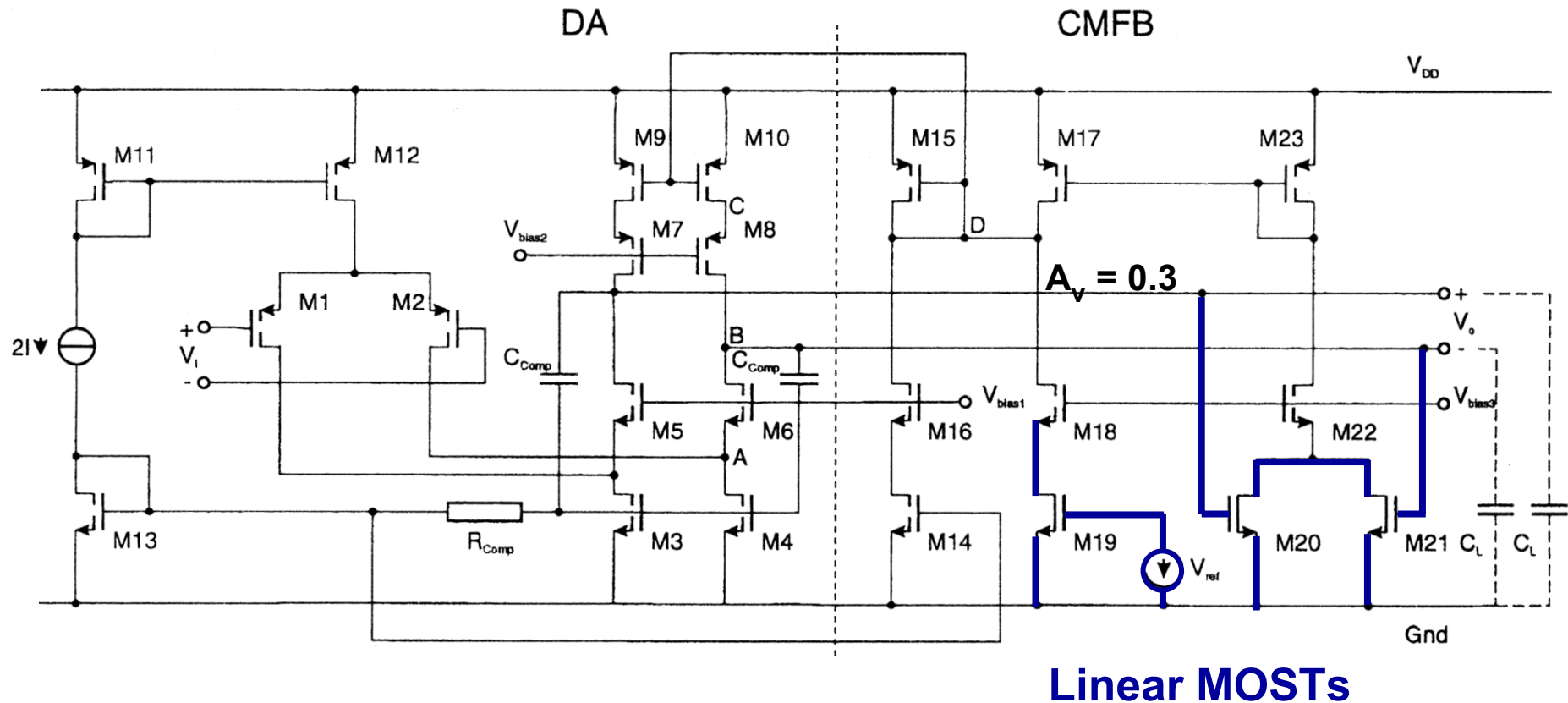
# Fully-diff.amp. with separate linear trans.CMFB




24 MHz/ 3 pF    3 V/ 5 mA     $I_{DS1} = 0.25 \text{ mA}$     Comp 4 k $\Omega$ / 2 pF > 20 MHz

Ref. Pasch, AICSP, 2000

---

# CMFB over 2 or more amplifiers

---

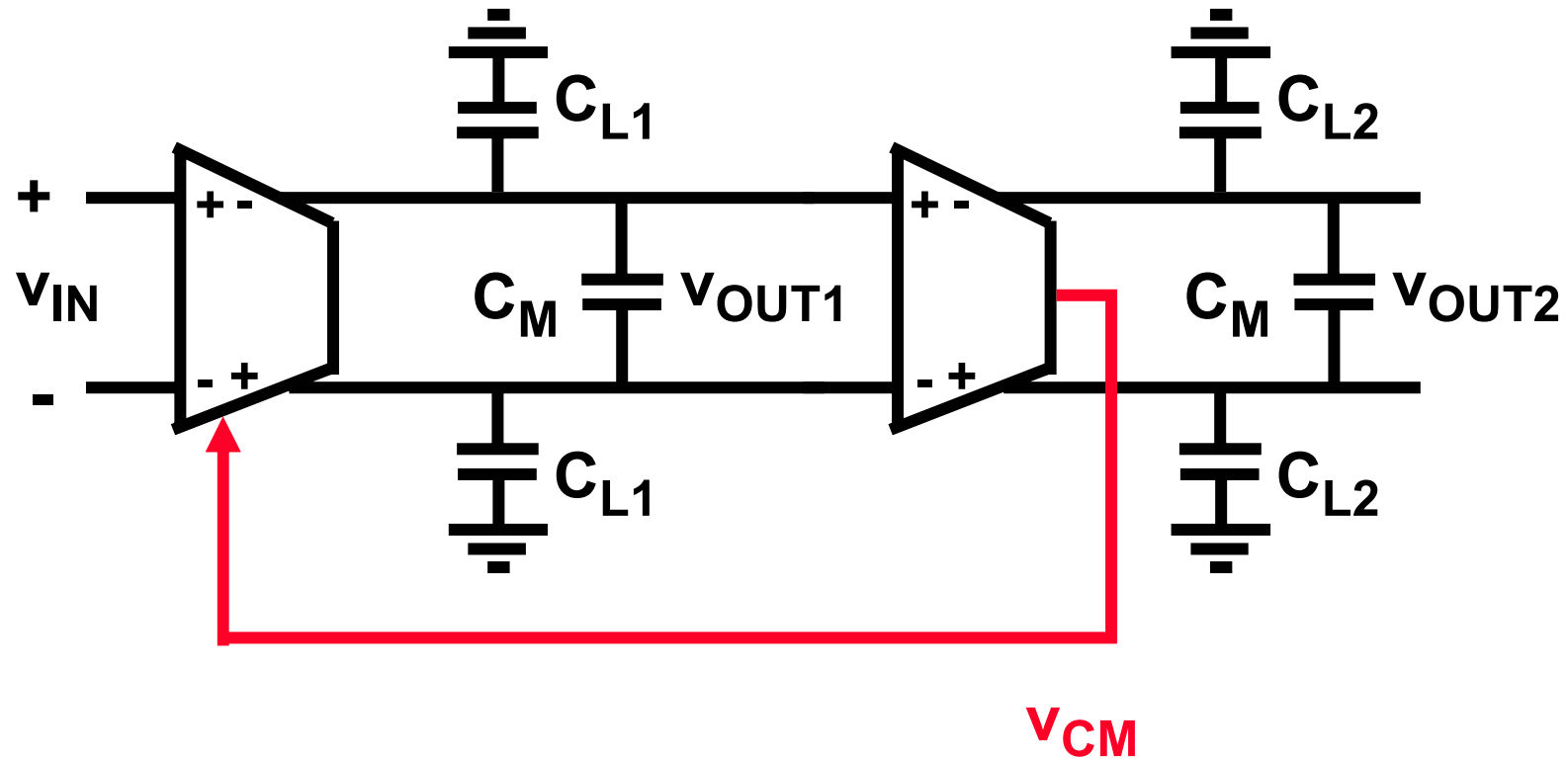


**Efficient use of 2nd amplifier !**

Ref. Mohieldin, JSSC April 2003, 663-668


---

# CMFB over 2 pseudo-differential amps


---

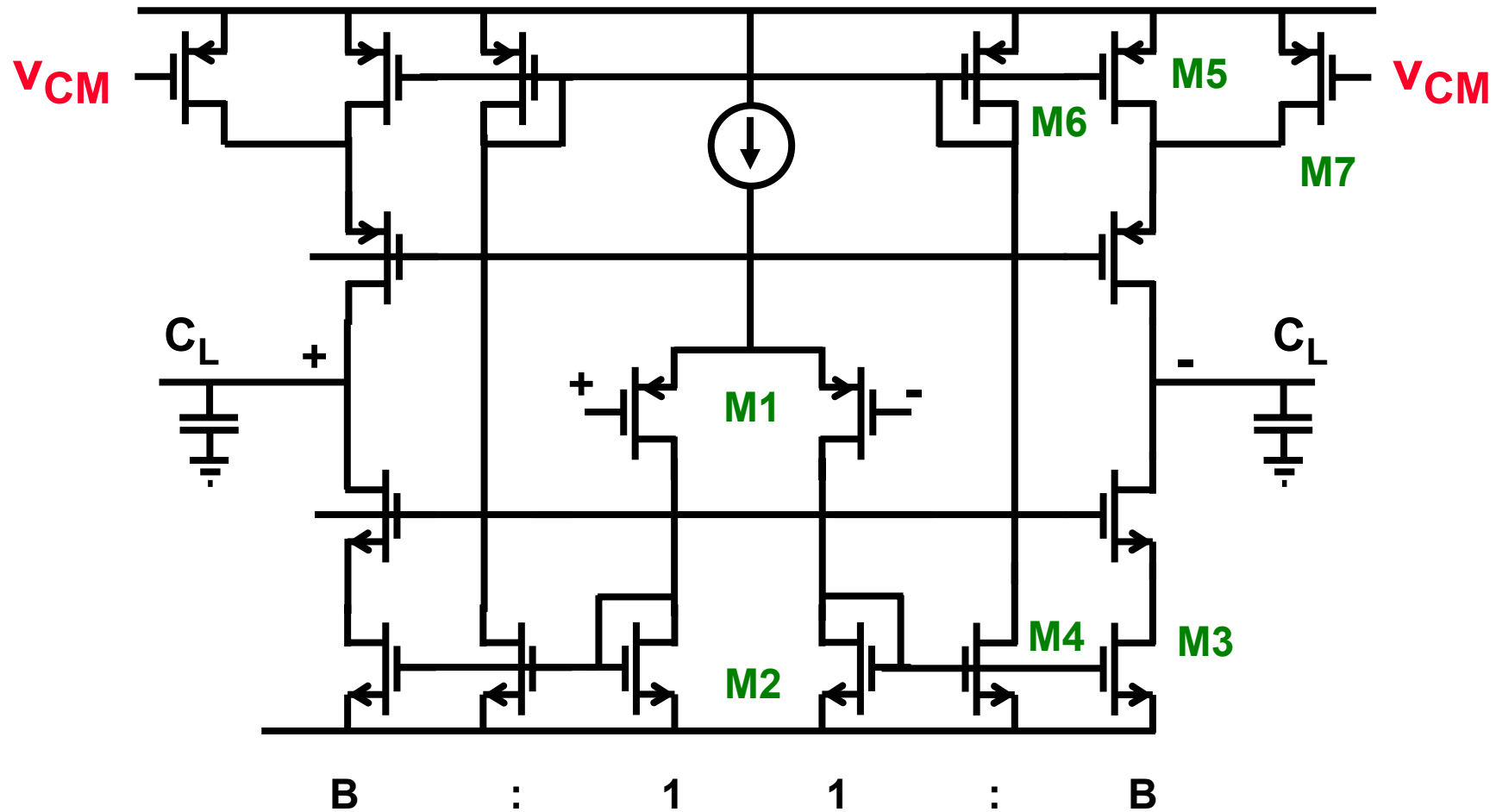
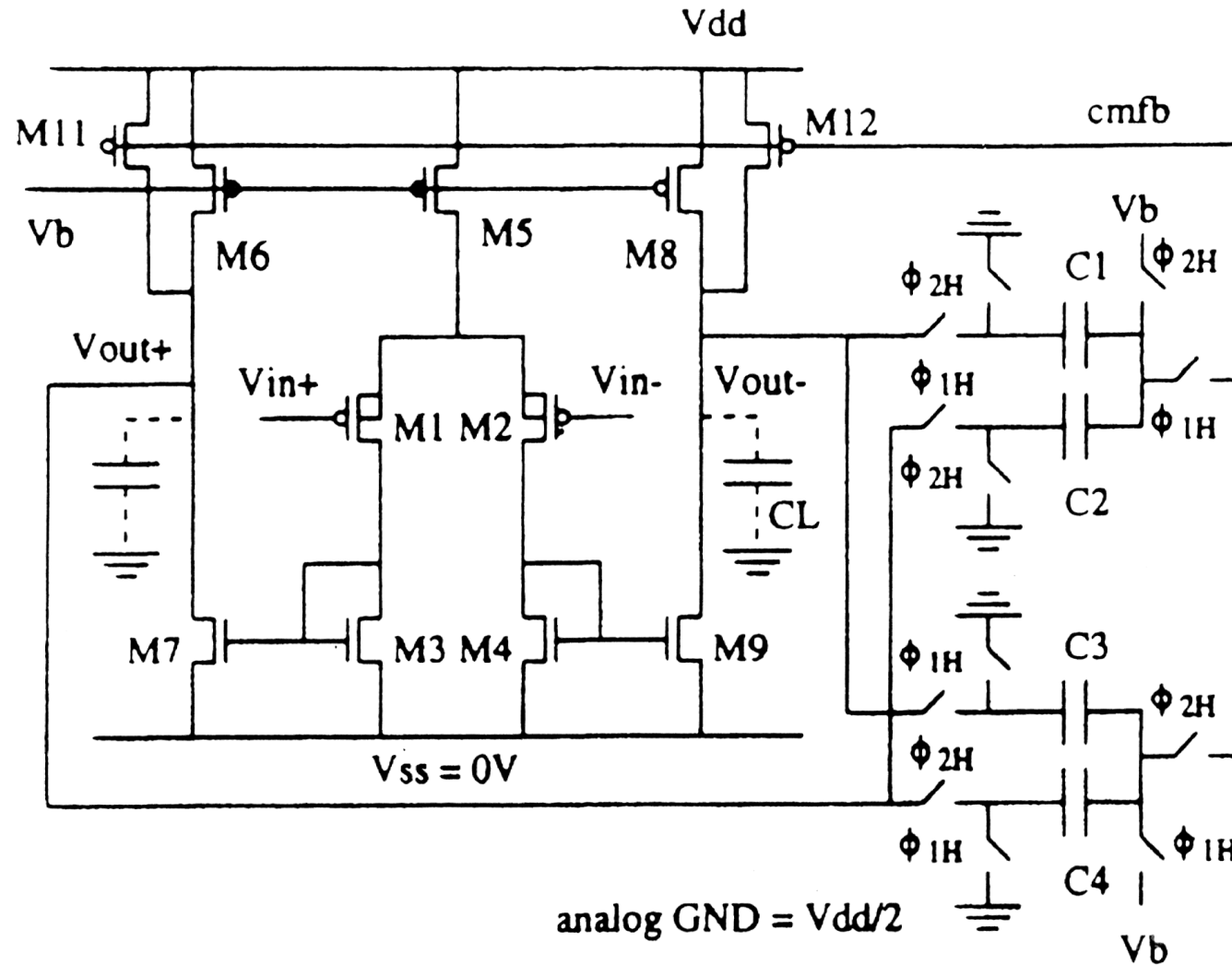
# Fully-differential amplifier with SC CMFB



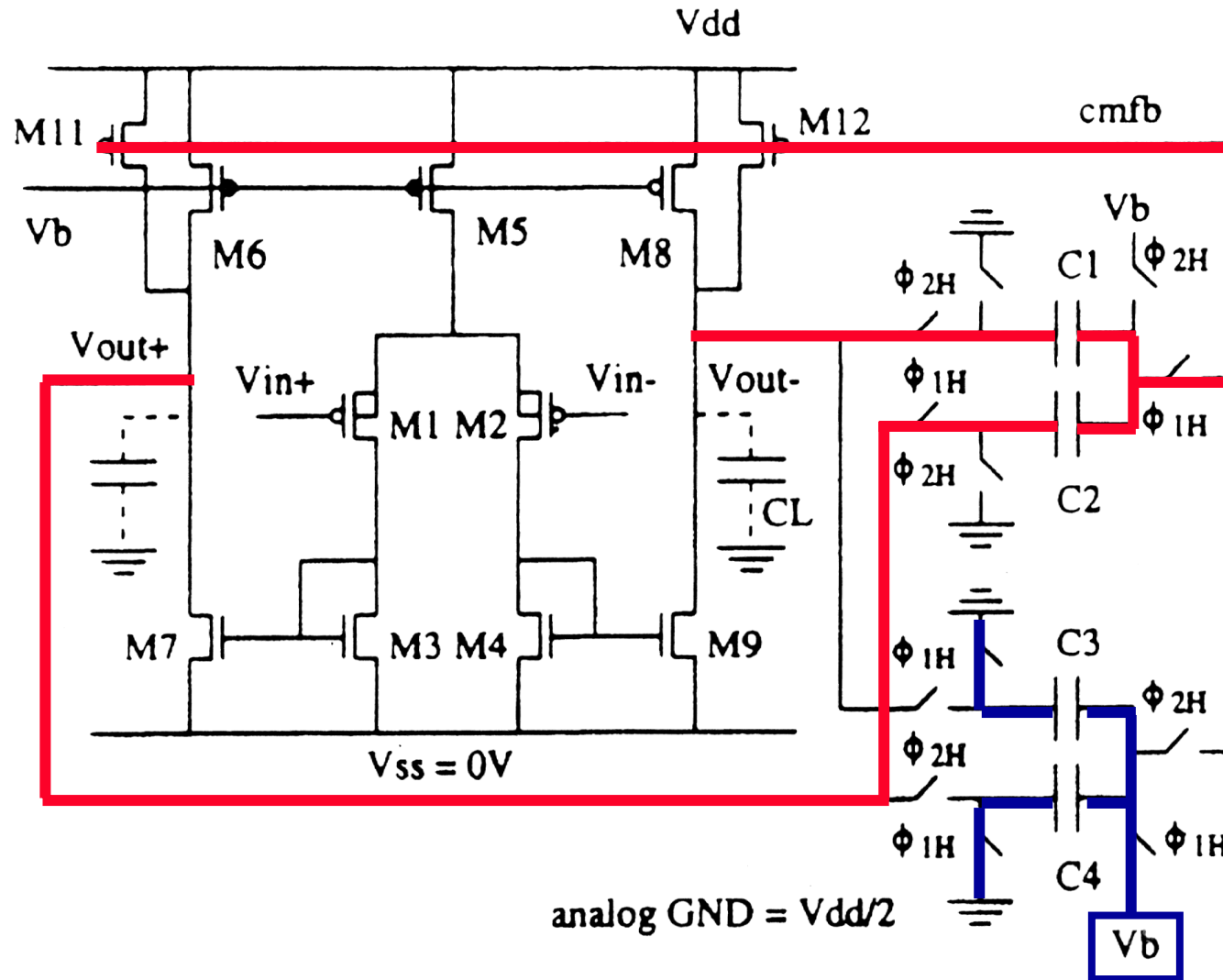
# Fully-differential amp. with SC CMFB : $\Phi 1$



**Switches**  
 $\phi_{1H}$  closed  
 gives CMFB  
 and  
 precharge C
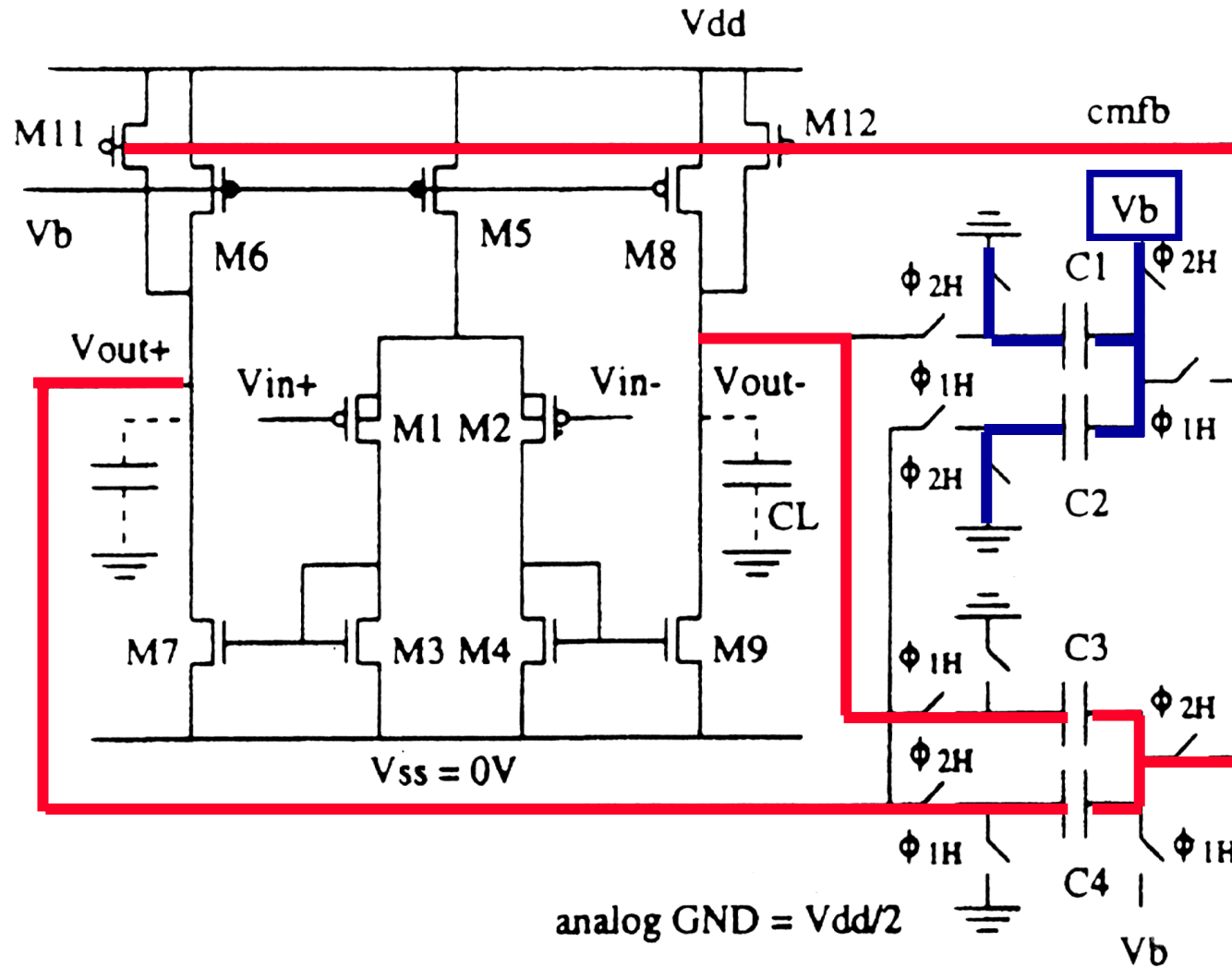
# Fully-differential amp. with SC CMFB : $\Phi_2$



**Switches**  
 $\phi_{2H}$  closed  
 gives CMFB  
 and  
 precharge C




---

# Table of contents

---

- **Requirements**
- **Fully-diff. amps with linear MOSTs**
- **FDA's with error amp.& source followers**
- **Folded cascode OTA without SF's**
- **Other fully-differential amps**
- **Exercise**
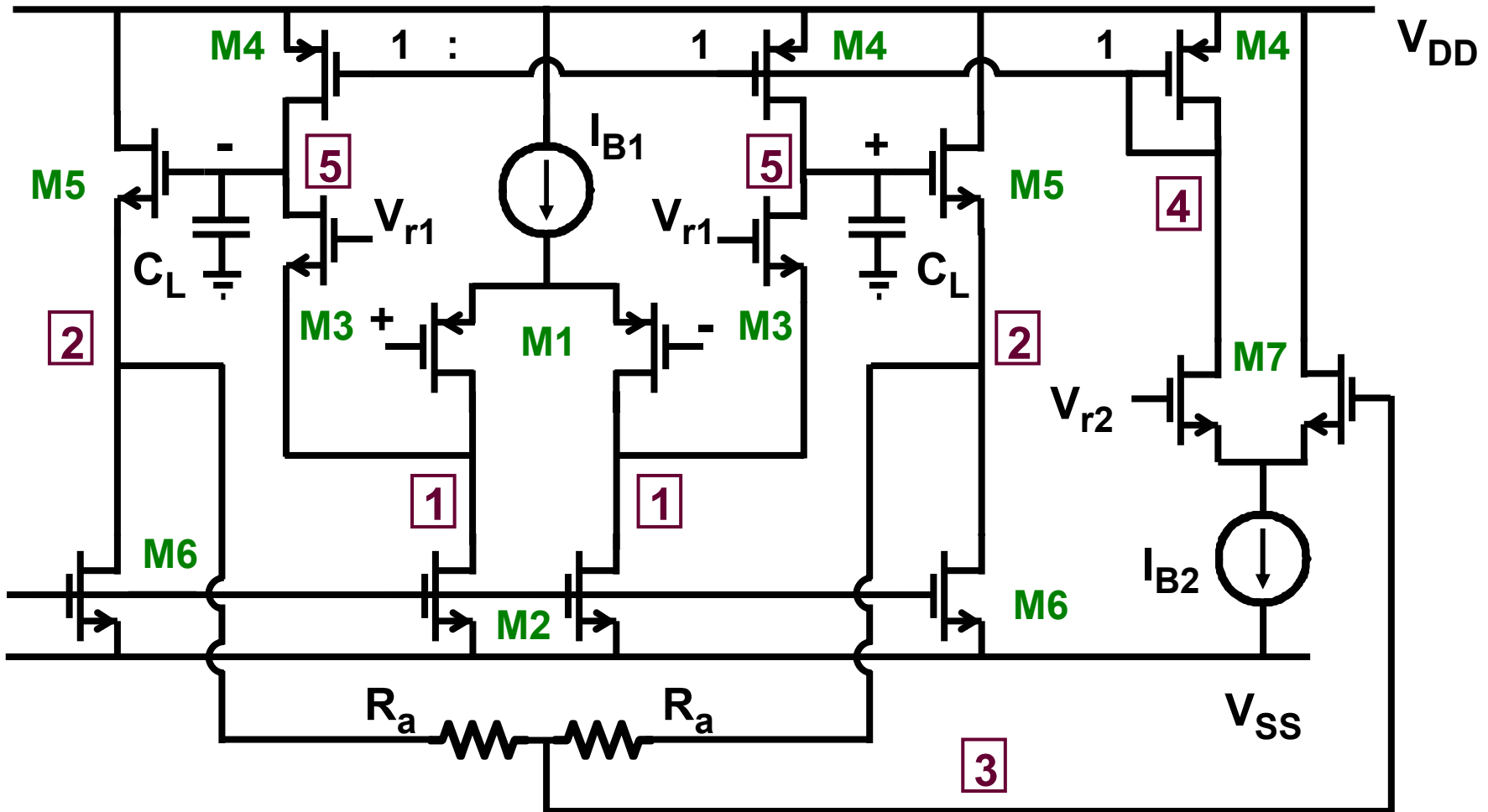
# Fully-differential folded cascode with source foll.



---

# Fully-diff. amp. : Specifications


---

Techn: **CMOS**     $L_{\min} = 0.8 \mu\text{m}$  ;  $V_T = 0.7 \text{ V}$   
 $K'_n = 60 \mu\text{A/V}^2$  &  $K'_p = 30 \mu\text{A/V}^2$   
 $V_{En} = 4 \text{ V}/\mu\text{m}$  &  $V_{Ep} = 6 \text{ V}/\mu\text{m}$

Specs:             $\text{GBW}_{\text{DM}} = 10 \text{ MHz}$      $C_L = 3 \text{ pF}$   
 $\text{GBW}_{\text{CM}} = 20 \text{ MHz}$   
all PM > 70°  
 $V_{\text{DD}}/V_{\text{SS}} = \pm 1.5 \text{ V}$   
**Maximum**  $V_{\text{swingptp}} = V_{\text{outmax}} - V_{\text{outmin}}$   
**Minimum**  $I_{\text{tot}}$

Verify:            Slew Rate, Noise, ...

# Fully-diff. folded cascode in BICMOS

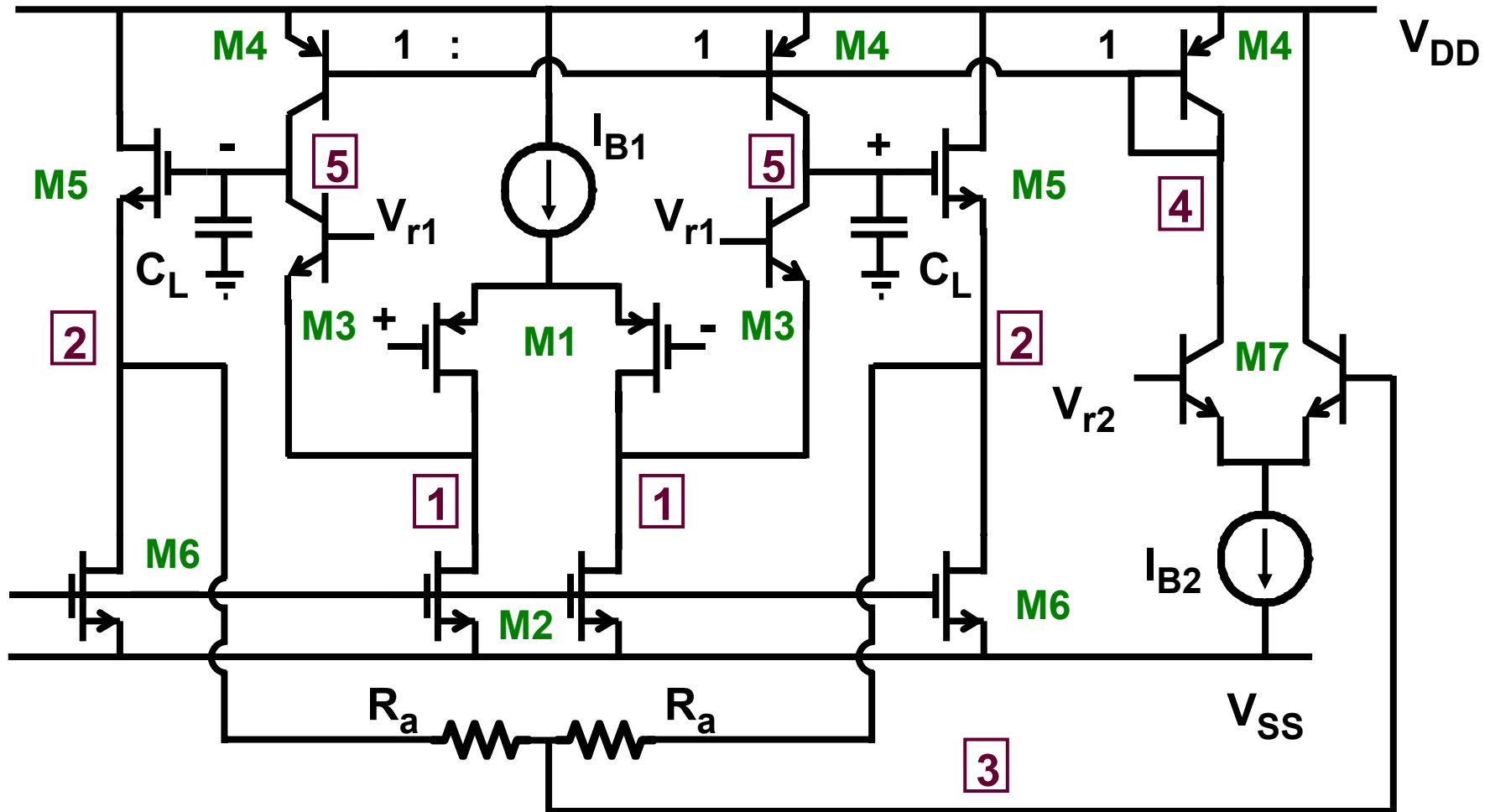

---

# Fully-diff. amp. : Specifications

---

Techn: **BICMOS**     $L_{\min} = 0.8 \mu\text{m}$  ;  $V_T = 0.7 \text{ V}$   
 $K'_n = 60 \mu\text{A/V}^2$  &  $K'_p = 30 \mu\text{A/V}^2$   
 $V_{En} = 4 \text{ V}/\mu\text{m}$  &  $V_{Ep} = 6 \text{ V}/\mu\text{m}$   
 $f_{Tn} = 12 \text{ GHz}$  &  $f_{Tp} = 4 \text{ GHz}$

Specs:             $\text{GBW}_{\text{DM}} = 10 \text{ MHz}$      $C_L = 3 \text{ pF}$   
 $\text{GBW}_{\text{CM}} = 20 \text{ MHz}$   
all PM > 70°  
 $V_{\text{DD}}/V_{\text{SS}} = \pm 1.5 \text{ V}$   
**Maximum  $V_{\text{swingtp}} = V_{\text{outmax}} - V_{\text{outmin}}$**   
**Minimum  $I_{\text{tot}}$**

Verify:            Slew Rate, Noise, ...

---

# Table of contents

---

- **Requirements**
- **Fully-diff. amps with linear MOSTs**
- **FDA's with error amp.& source followers**
- **Folded cascode OTA without SF's**
- **Other fully-differential amps**
- **Exercise**