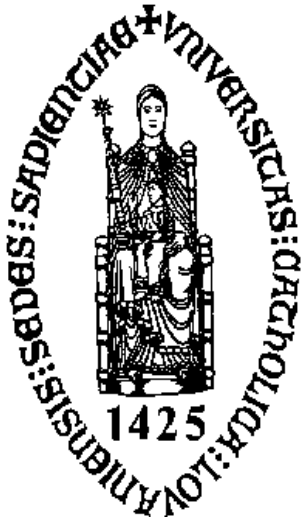

Current-input Operational Amplifiers



Willy Sansen

**KULeuven, ESAT-MICAS
Leuven, Belgium**


willy.sansen@esat.kuleuven.be




Table of contents

- **Operational current amplifier**
- **Configurations current amplifiers**

Current or voltage amplifier

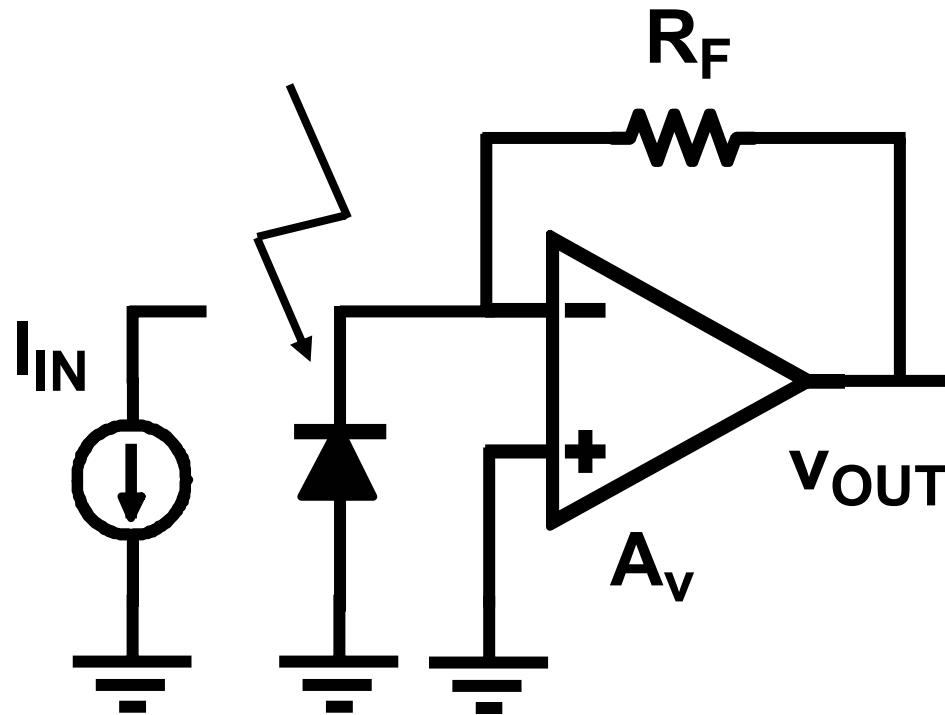


$$V_{OUT} = R_F I_{IN}$$

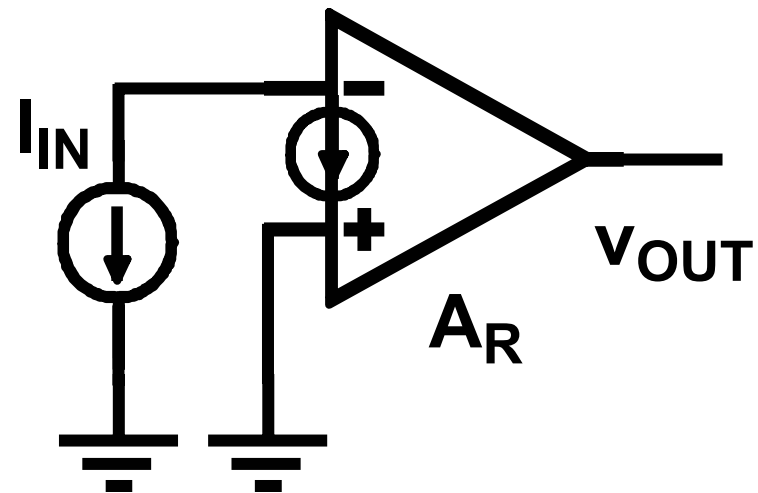

$$V_{OUT} = A_R I_{IN}$$

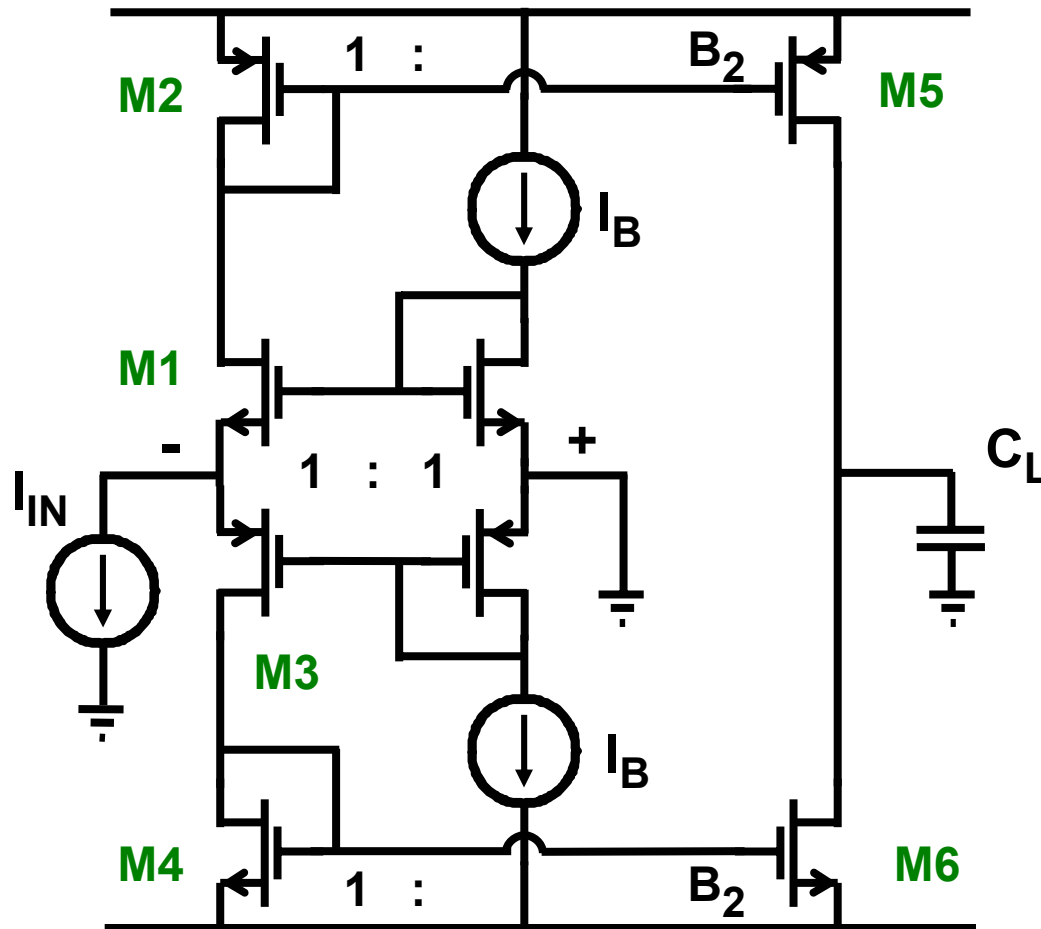Operational current amplifier Gain & Speed




$$A_R = B_2 R_{OUT} = B_2 r_{o5} // r_{o6}$$

$$BW = \frac{1}{2\pi C_L R_{OUT}} \sim I_{DS} \uparrow$$

$$A_R BW = \frac{B_2}{2\pi C_L}$$

$$SR = B_2 \frac{I_{IN}}{C_L} \quad I_{DS} \uparrow$$

Operational current amplifier : noise

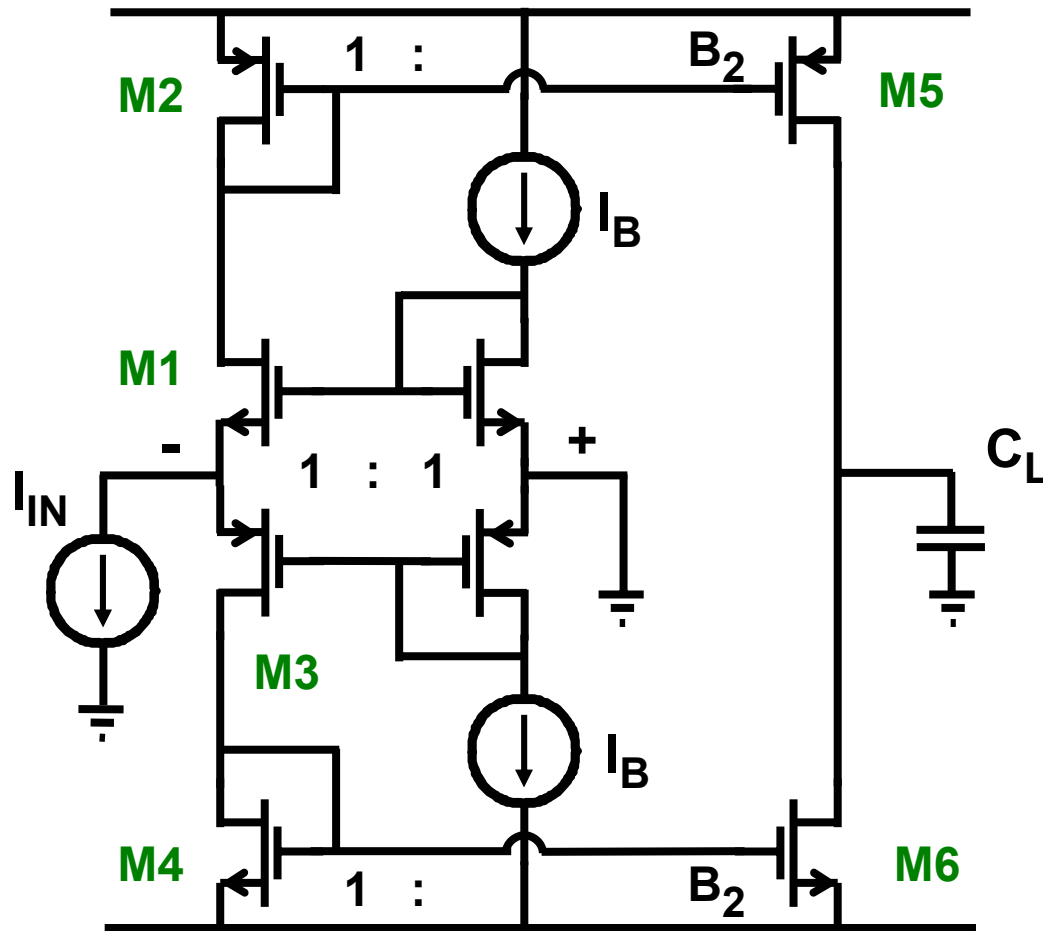

$$SR = B_2 \frac{I_{IN}}{C_L} \quad I_{DS} \uparrow$$


$$\overline{di_{DS}^2} = 4kT \frac{2}{3} g_m df$$

$$\overline{di_{IN}^2} \approx 2 \overline{di_{DS}^2}$$

$$\frac{S}{N} = \frac{I_{IN}}{\sqrt{\overline{di_{IN}^2} BW} \frac{\pi}{2}}$$

$$\frac{S}{N} \sim \frac{I_{IN}}{\sqrt{I_{DS}}} \quad I_{DS} \downarrow$$

Gain and noise in MOST cascodes

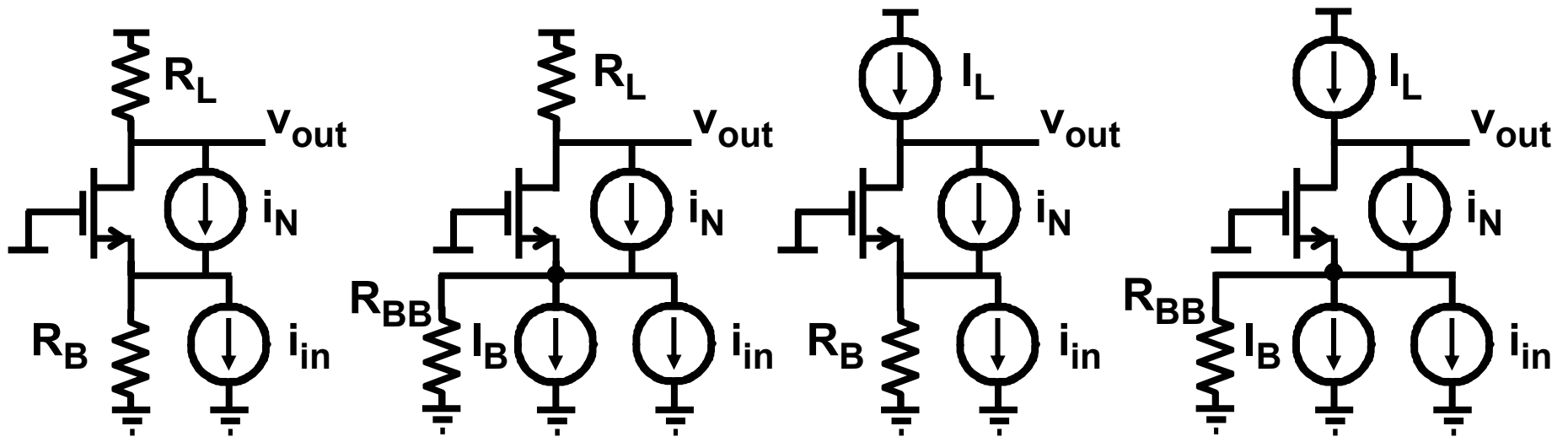

$$r_{DS} > R_L$$

$$R_{BB} > R_L$$

$$g_m r_{DS} > 1$$

$$\frac{V_{out}}{i_{in}}$$

$$g_m R_L \frac{R_B}{1 + g_m R_B}$$

$$R_L$$

$$g_m r_{DS} R_B$$

$$g_m r_{DS} R_{BB}$$

$$\frac{V_{out}}{i_N}$$

$$\frac{R_L}{1 + g_m R_B}$$

$$\frac{R_L}{g_m R_{BB}}$$

$$R_B$$

$$r_{DS}$$

$$\frac{i_{in}}{i_N}$$


$$\frac{1}{g_m R_B}$$

$$\frac{1}{g_m R_{BB}}$$

$$\frac{1}{g_m r_{DS}}$$

$$\frac{1}{g_m R_{BB}}$$


OTA in feedbackloop

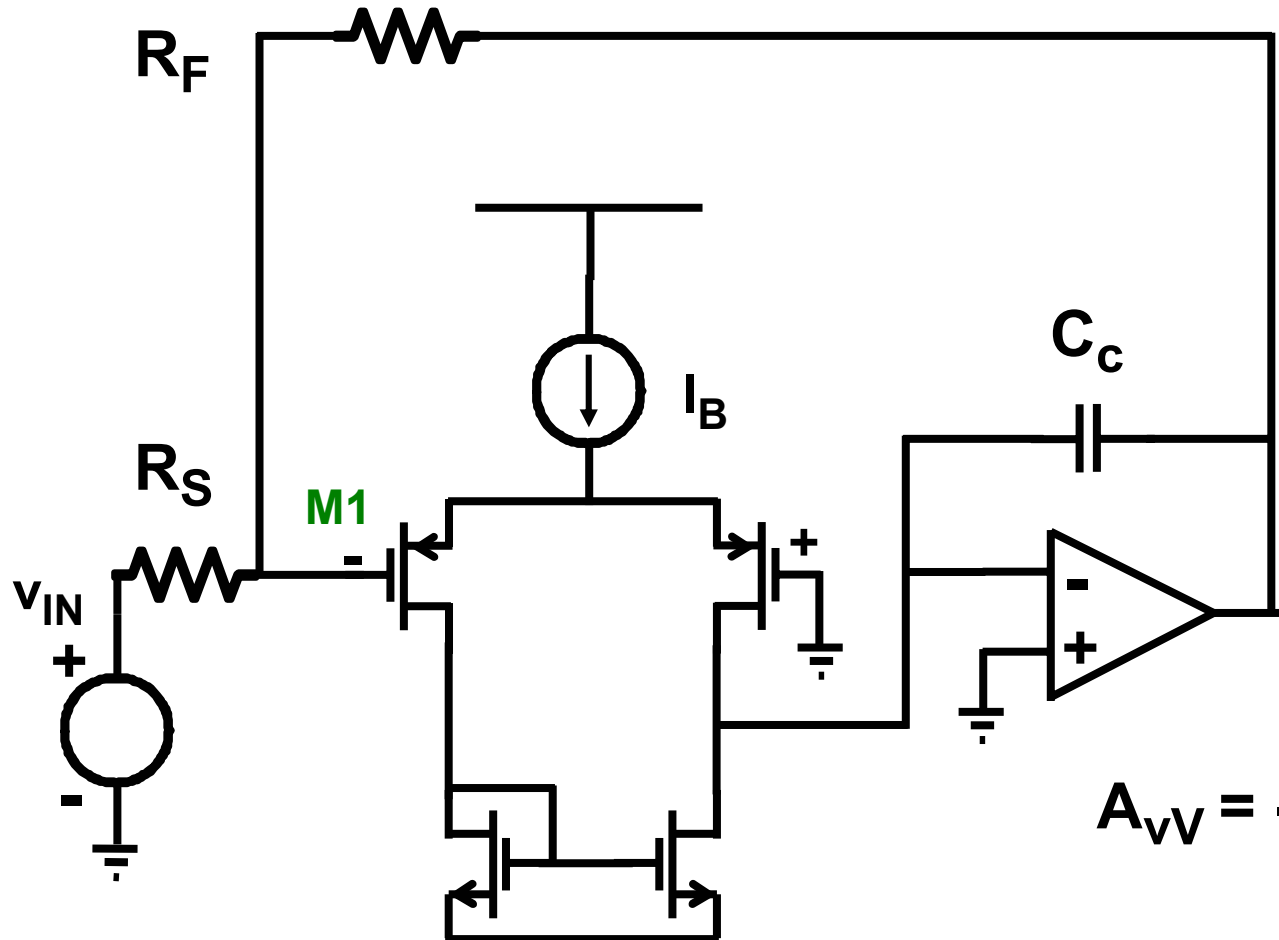

$$GBW = \frac{g_{m1}}{2\pi C_c}$$

$$A_{vV} = - \frac{R_F}{R_S} \frac{1}{1 + \frac{R_F j\omega C_c}{R_S g_{m1}}}$$



OCA in feedbackloop

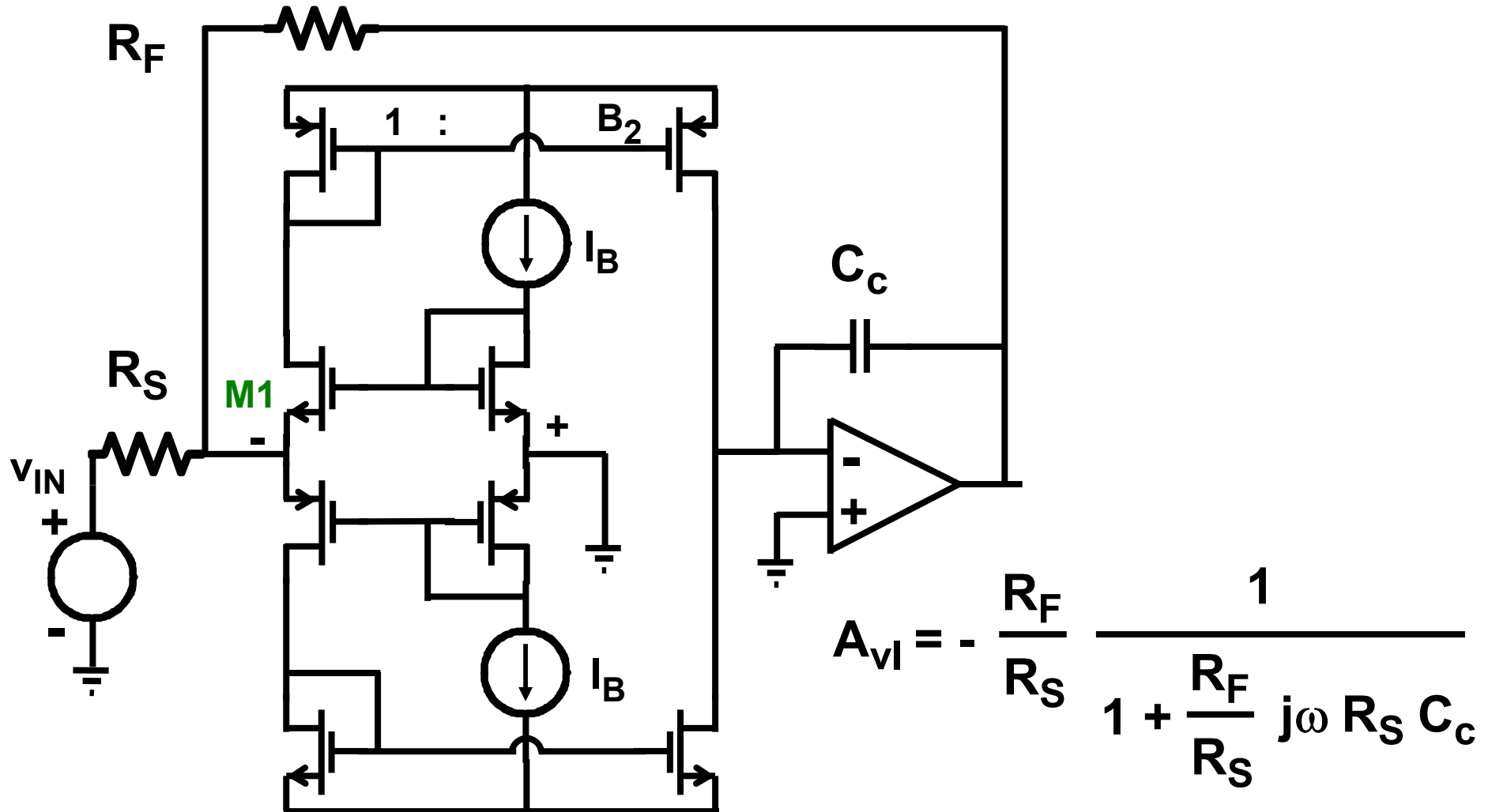

Comparison A_{vV} and A_{vI}

$$A_{vV} = - \frac{R_F}{R_S} \frac{1}{1 + \frac{R_F}{R_S} \frac{j\omega C_c}{g_{m1}}}$$

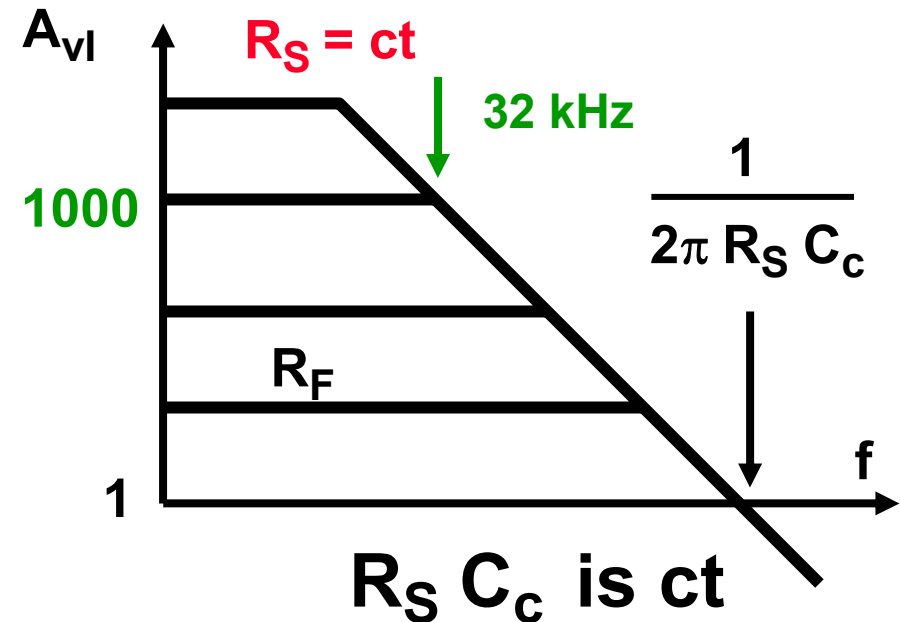
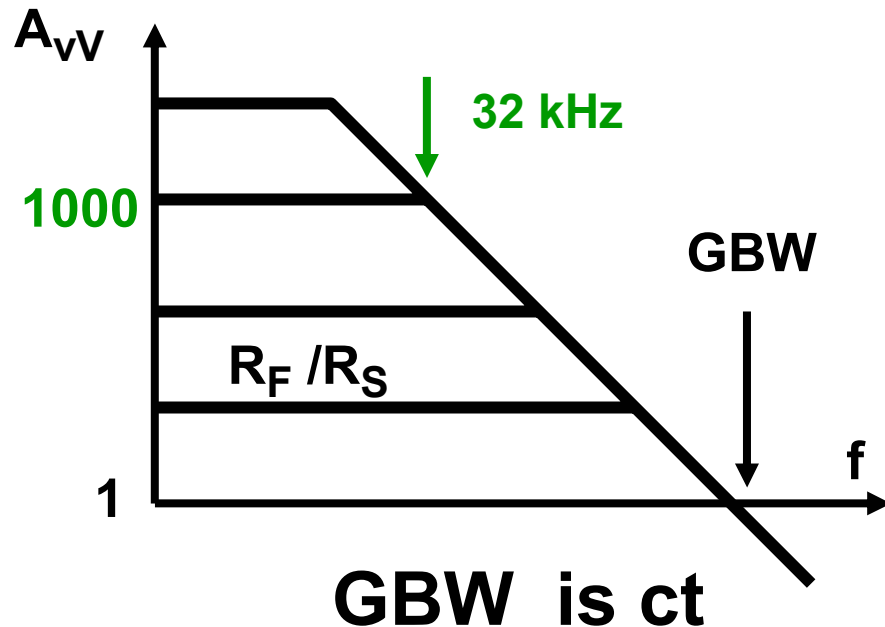
$$A_{vI} = - \frac{R_F}{R_S} \frac{1}{1 + \frac{R_F}{R_S} j\omega R_S C_c}$$



$g_{m1} = 0.2 \text{ mS}; C_c = 1 \text{ pF}; \text{GBW} = 32 \text{ MHz}; A_{vV} = 1000; \text{BW} = 32 \text{ kHz}$


Advantage A_{vI}
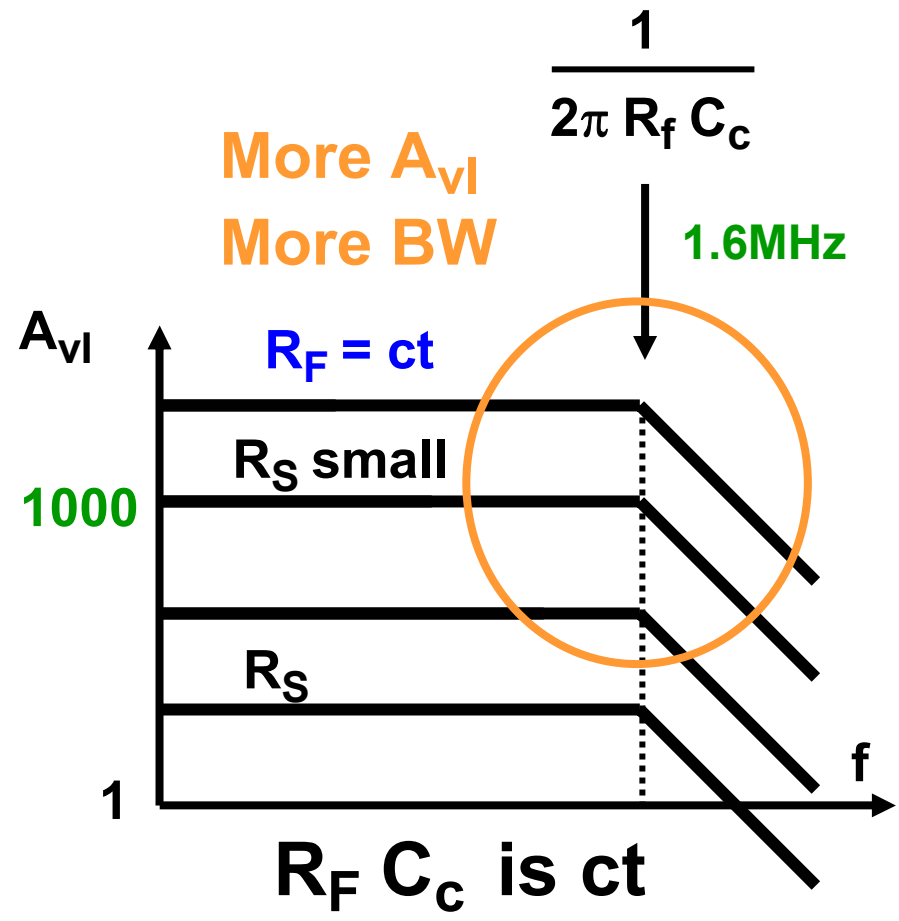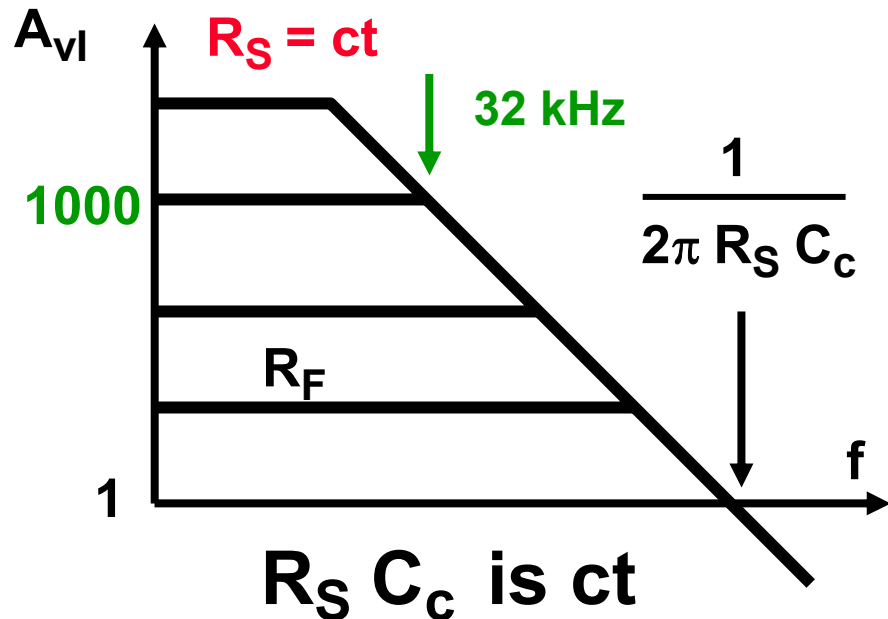
$$A_{vI} = - \frac{R_F}{R_S} \frac{1}{1 + \frac{R_F}{R_S} j\omega R_S C_C}$$



$C_C = 1 \text{ pF}; R_S = 100 \text{ } \Omega; R_F = 100 \text{ k } \Omega; BW = 1.6\text{MHz} \square$

Limitations advantage A_{vI}

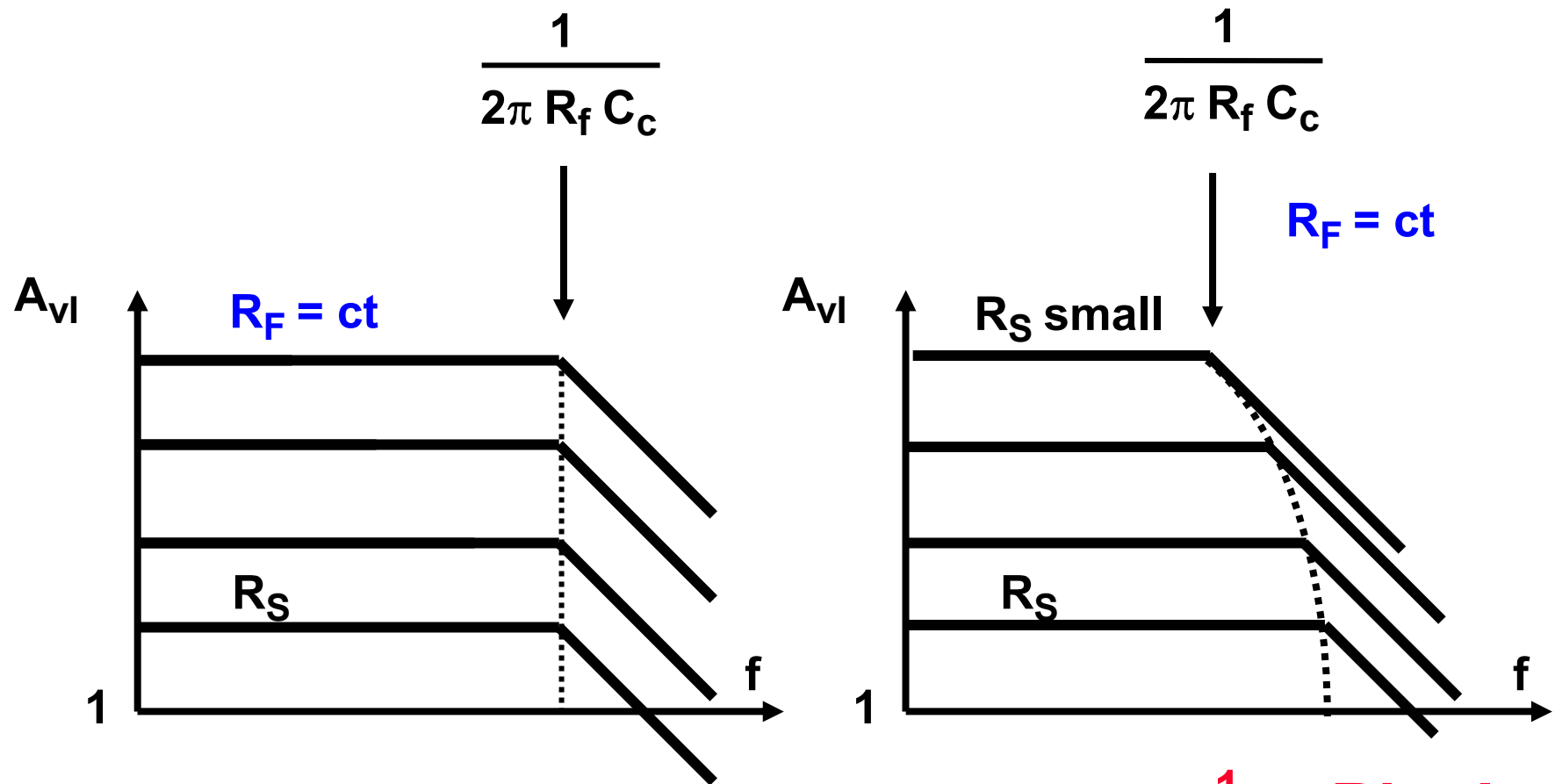


R_S limited to $R_S + \frac{1}{2g_{m1}}$: **Bipolar**

Table of contents

- **Operational current amplifiers**
- **Configurations Current amplifiers**

Single-stage OCA- 1 (AD846)

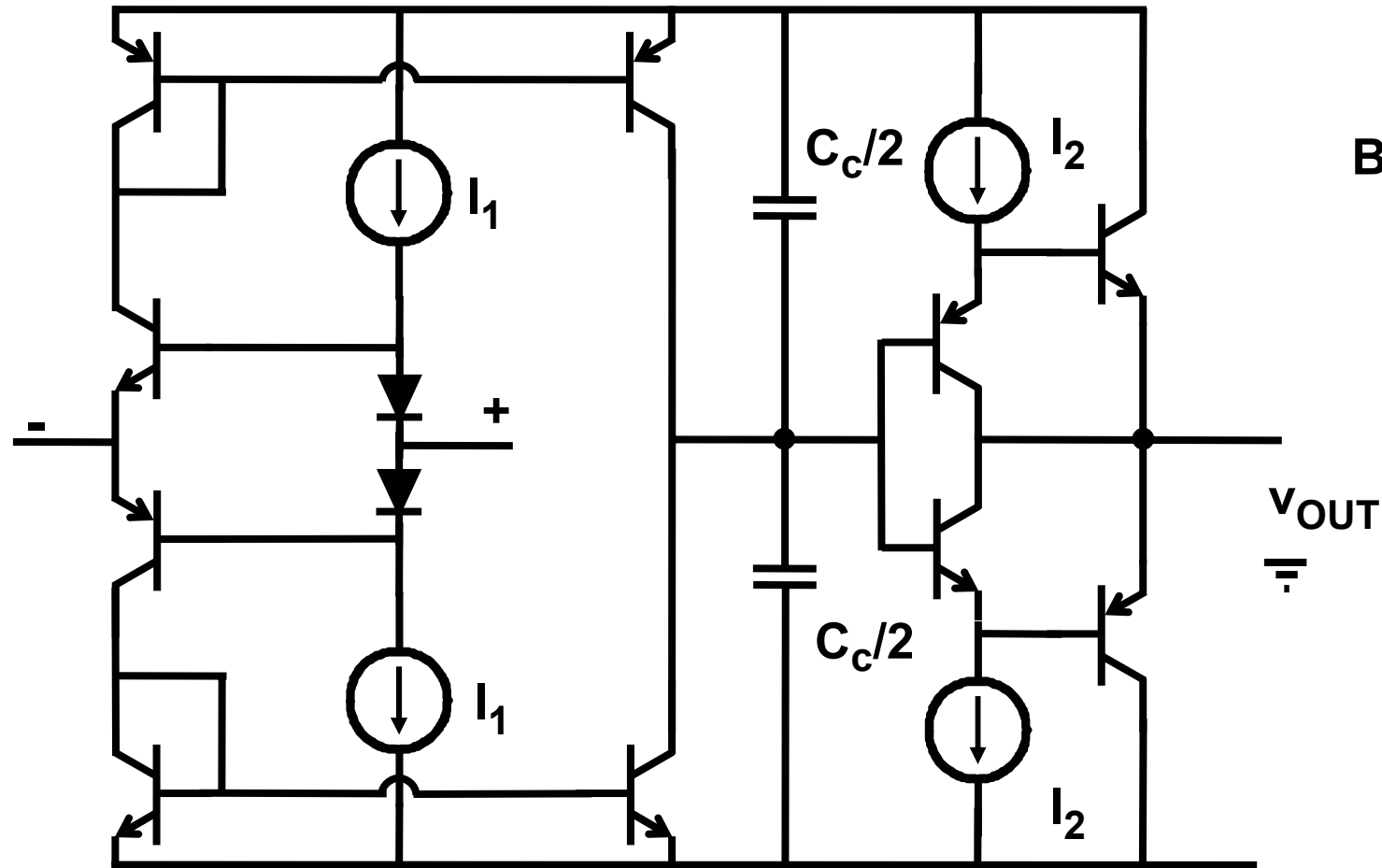


BW = 80 MHz

**SR (G=1) =
450 V/ μ s**

**6.5 mA (5V)
0.45 μ A**

Single-stage OCA- 2 (AD846)

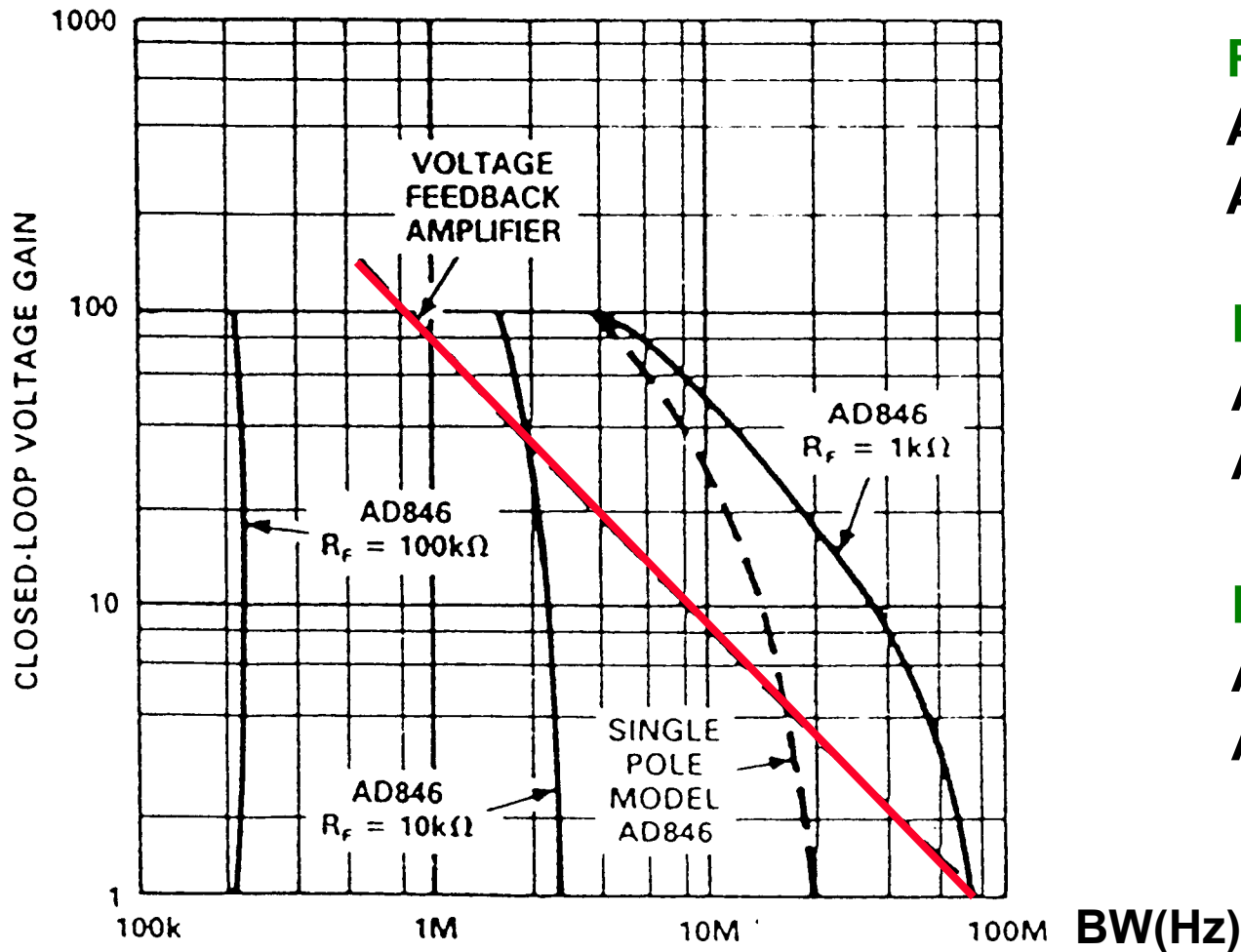

$$R_F = 100 \text{ k}\Omega$$

$$A = 10 : R_S = 10 \text{ k}\Omega$$

$$A = 100 : R_S = 1 \text{ k}\Omega$$

$$R_F = 10 \text{ k}\Omega$$

$$A = 10 : R_S = 1 \text{ k}\Omega$$

$$A = 100 : R_S = 100 \Omega$$


$$R_F = 1 \text{ k}\Omega$$

$$A = 10 : R_S = 100 \Omega$$


$$A = 100 : R_S = 10 \Omega$$

$$R_S + \frac{1}{g_{m1}} > 10 \Omega$$


Two-stage OCA- 1 (AD8011 bipolar)

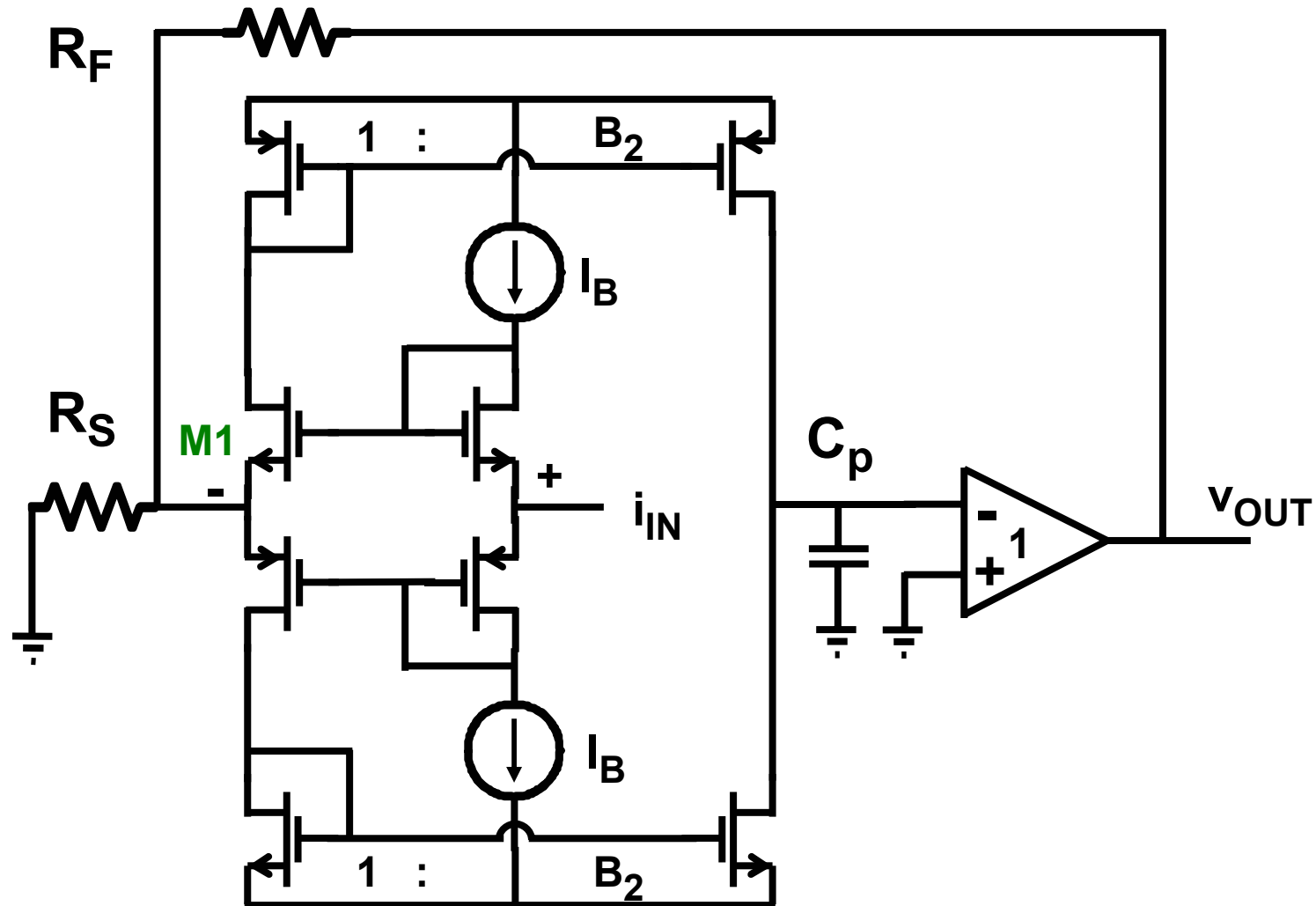


Two-stage OCA- 2 (AD8011 bipolar)

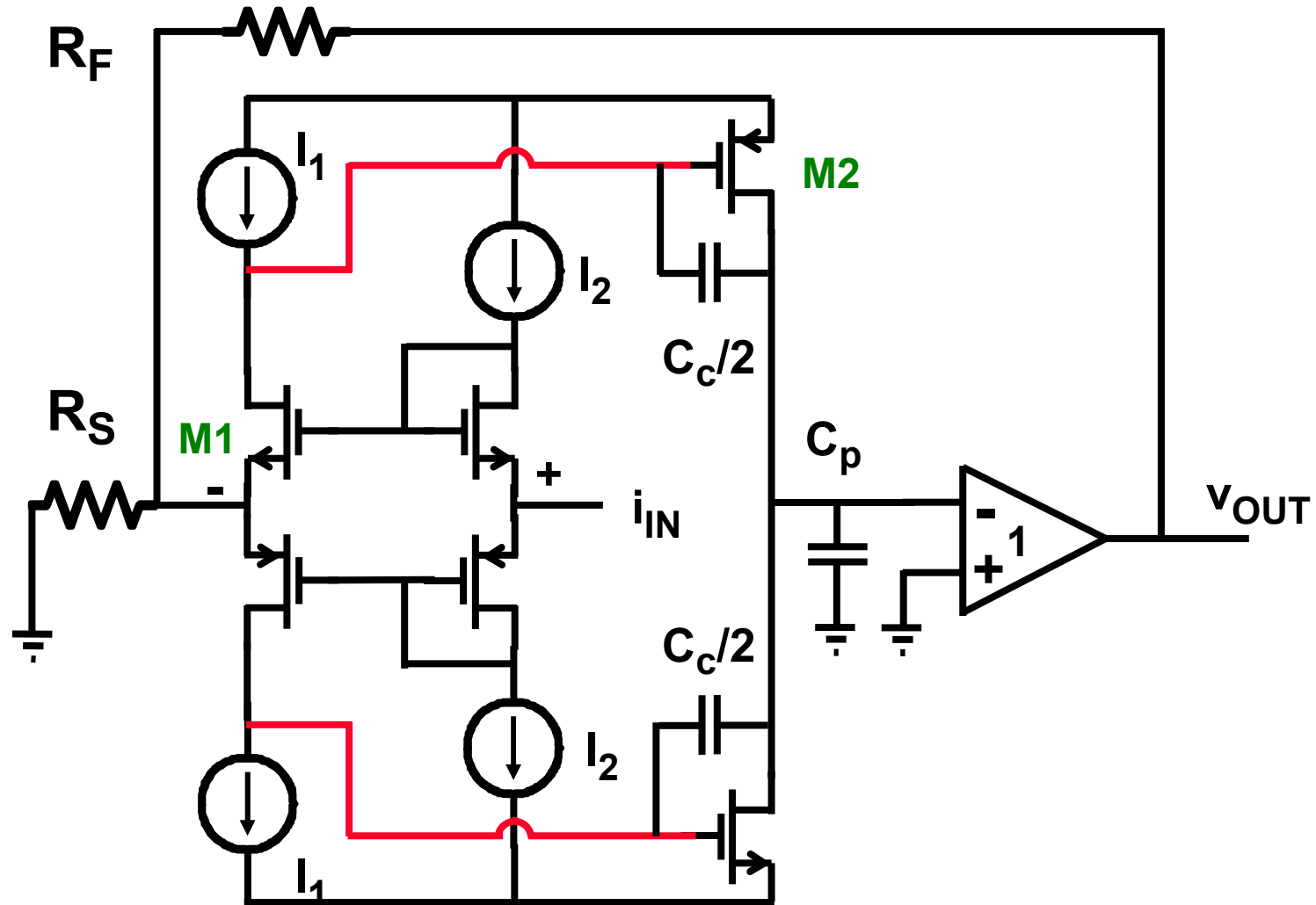

Two-stage OCA : AD8011

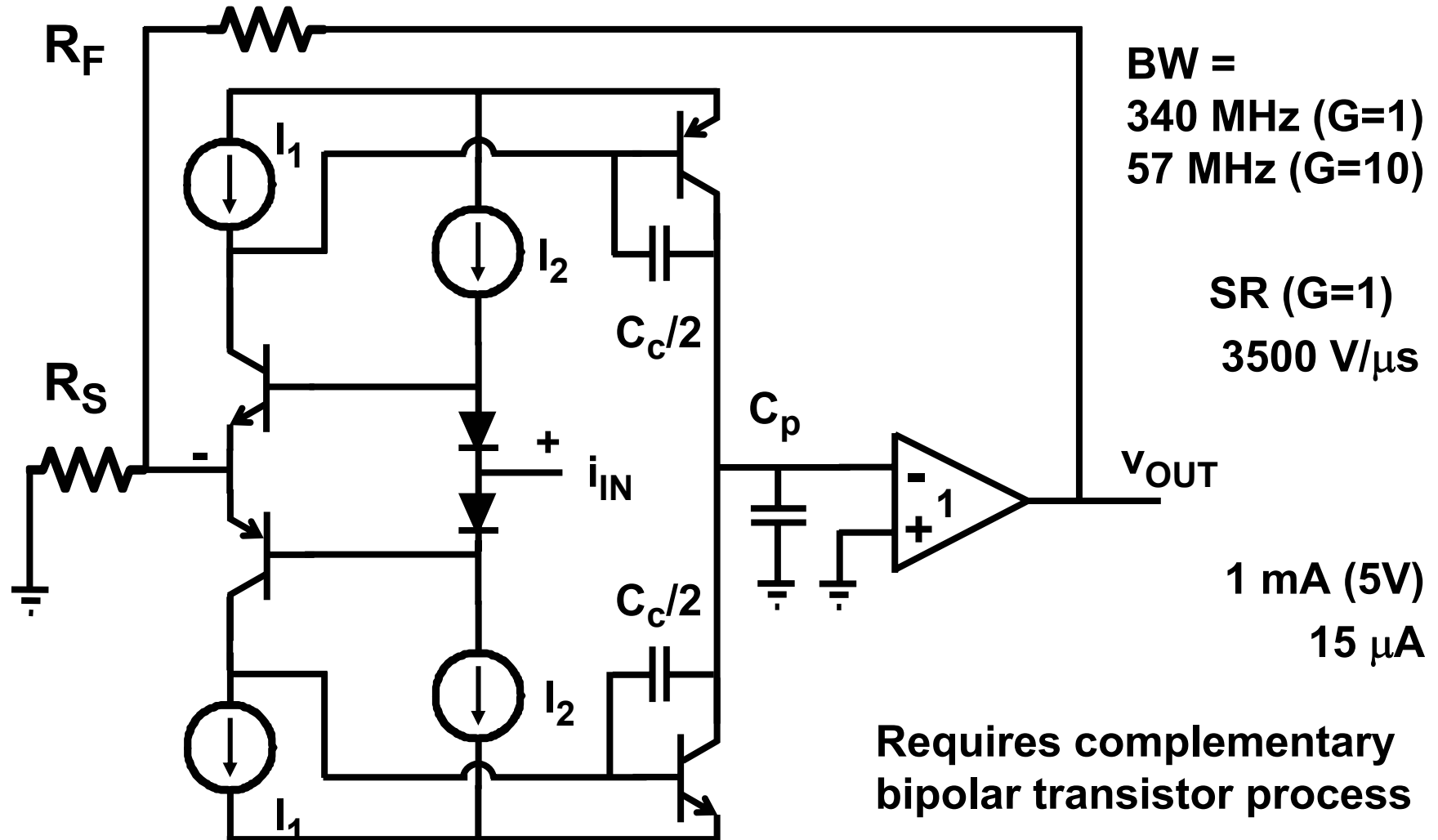

Two-stage OCA (LM3900)

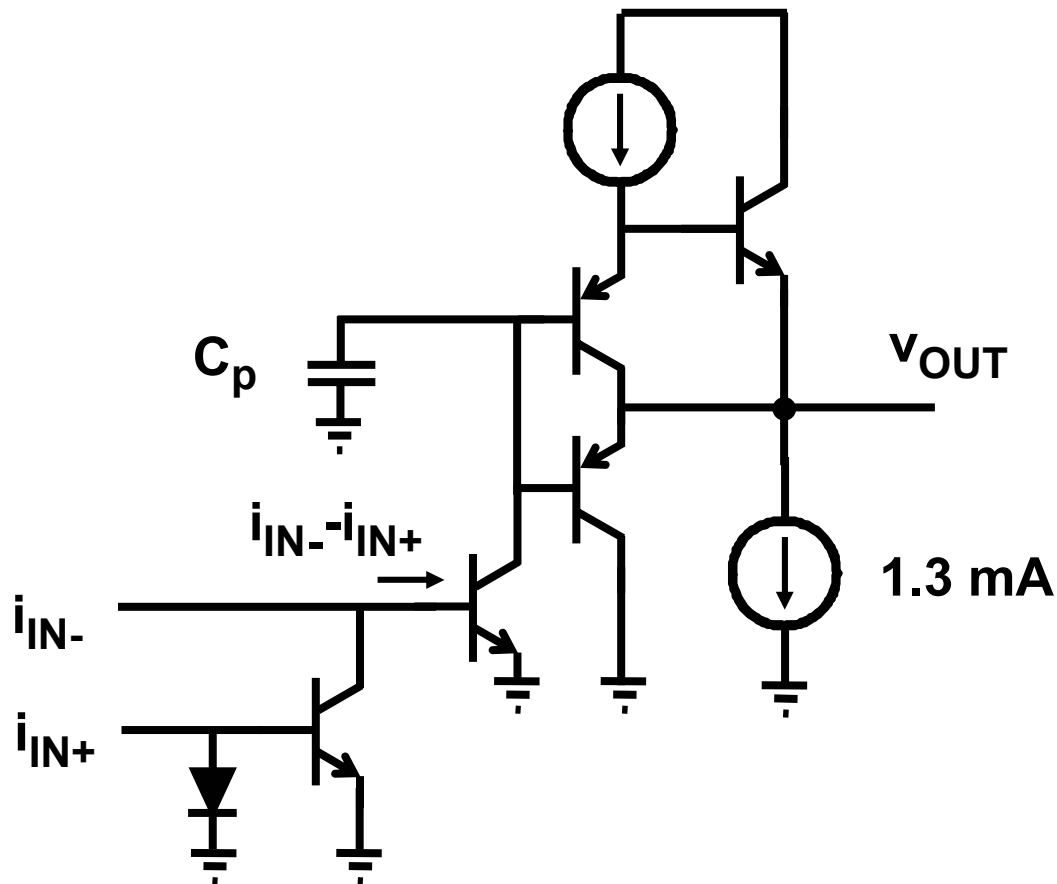


GBW = 2.5 MHz

**SR (G=1) =
0.5 V/ μ s**

**1.4 mA (4-36V)
0.03 μ A**

Current feedback opamp

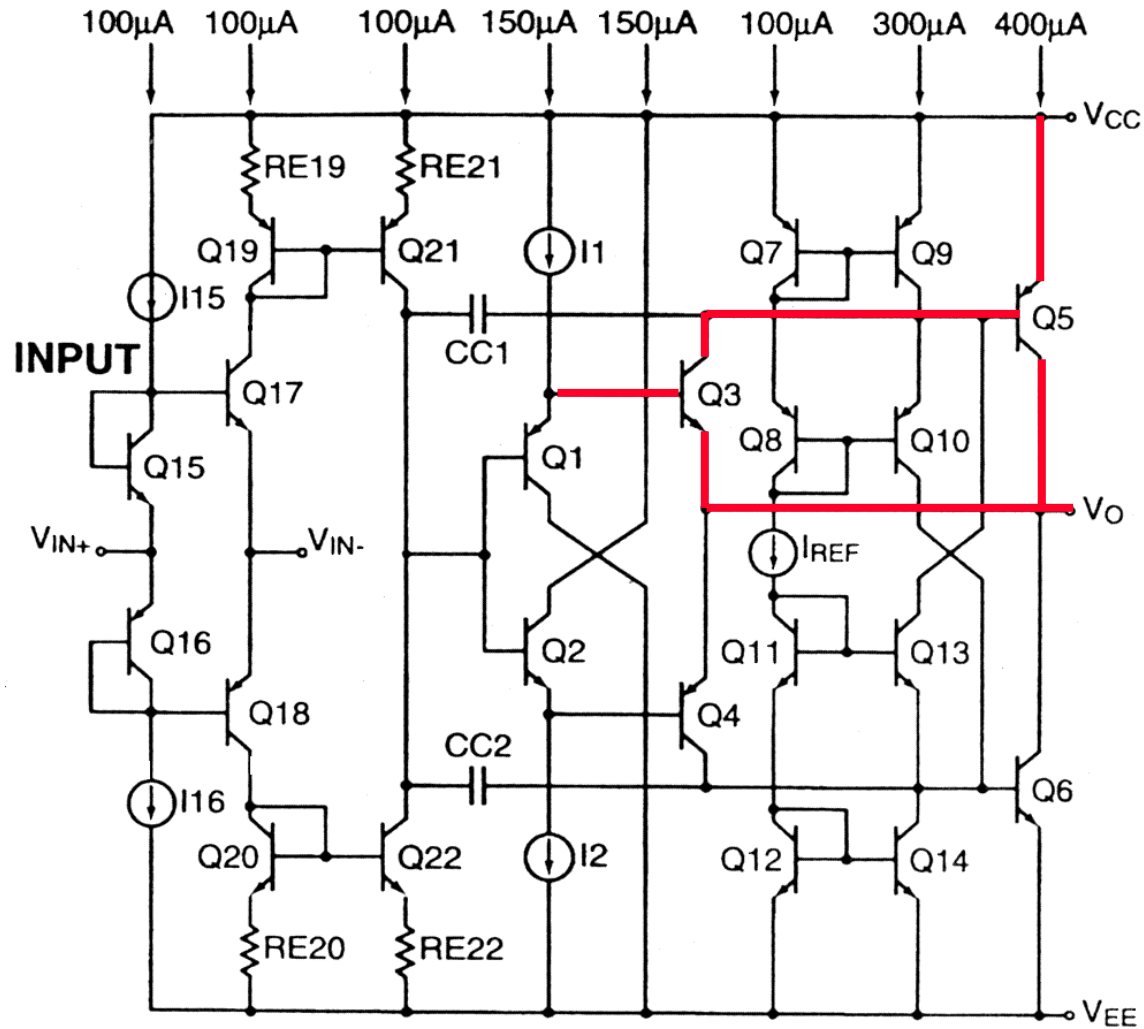

110 MHz/ 1.5 mA

230 V/µs

$A_v = 2$ in 100 Ω

$f_T = 3.8$ GHz

Ref. Bales, JSSC
Sept. 97, 1470-1474

Table of contents

- **Operational current amplifiers**
- **Other current amplifiers**