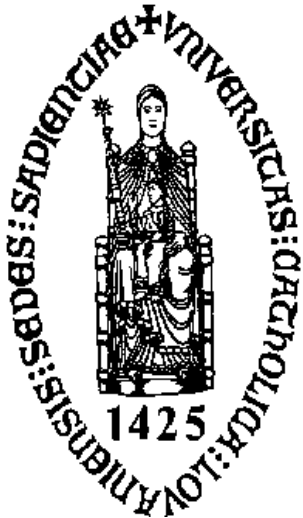

Feedback

Transimpedance & Current

Amplifiers



Willy Sansen

KULeuven, ESAT-MICAS

Leuven, Belgium

willy.sansen@esat.kuleuven.be



Table of contents

- **Introduction**
- **Shunt-shunt FB for Transimpedance amps.**
- **Shunt-series FB for Current amplifiers**
- **Transimpedance amplifiers for
low noise and high frequencies**

Input- & output impedances

$$\frac{1}{H} =$$

Output

Shunt

Series

Input

$$R_{OUT} = \frac{R_{OUTOL}}{1+LG}$$

$$R_{OUT} = R_{OUTOL}(1+LG)$$

Shunt $R_{IN} = \frac{R_{INOL}}{1+LG}$

$$\frac{v_{OUT}}{i_{IN}} = A_R$$

$$\frac{i_{OUT}}{i_{IN}} = A_I$$

Series $R_{IN} = R_{INOL}(1+LG)$


$$\frac{v_{OUT}}{v_{IN}} = A_V$$

$$\frac{i_{OUT}}{v_{IN}} = A_G$$

Table of contents

- Introduction
- **Shunt-shunt FB for Transimpedance amps.**
- Shunt-series FB for Current amplifiers
- Transimpedance amplifiers for
low noise and high frequencies

Shunt-shunt FB configuration

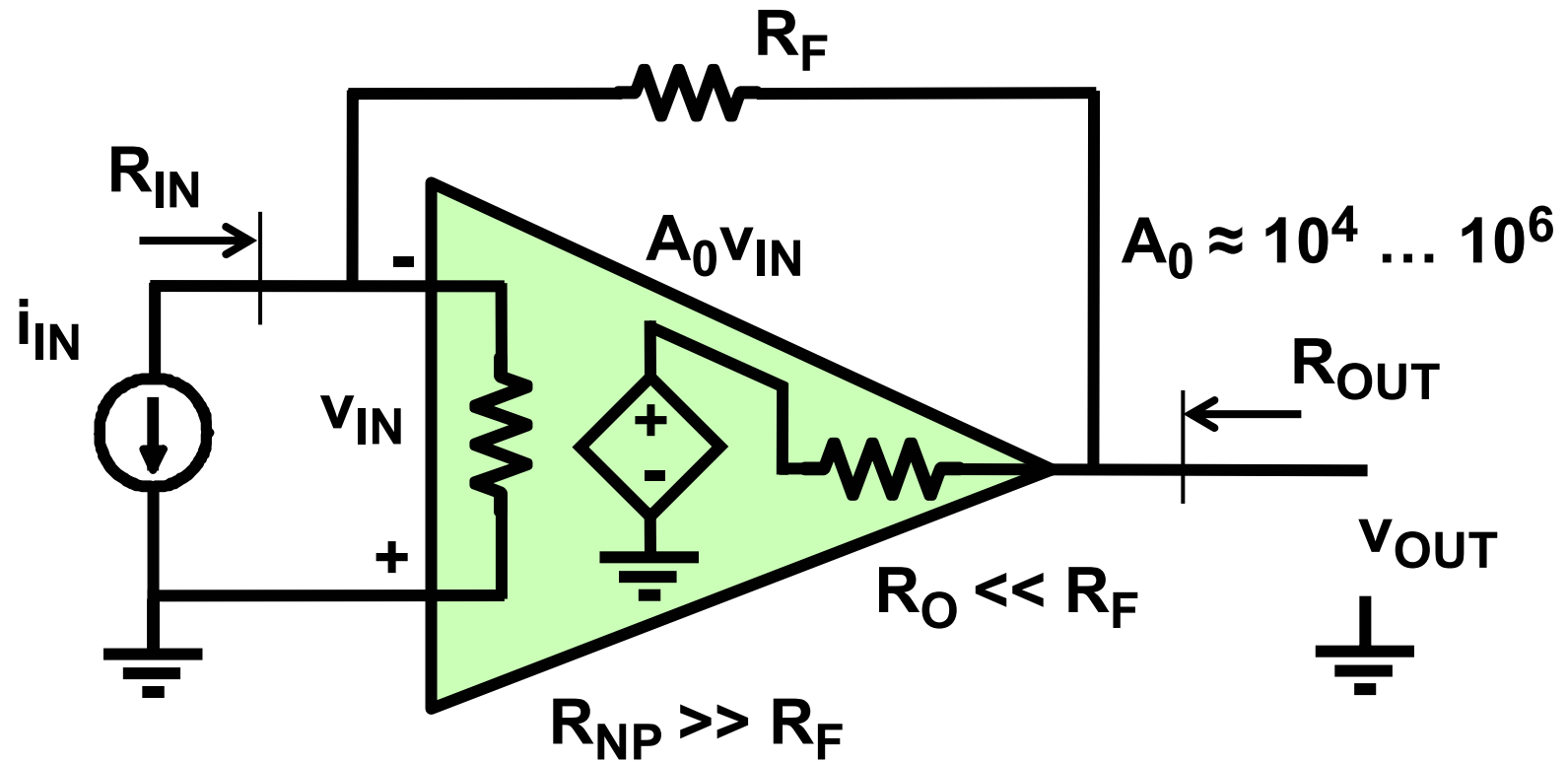


$$A_R = \frac{V_{OUT}}{i_{IN}} = R_F$$

$$R_{IN} \approx 0$$


$$R_{OUT} \approx 0$$

Shunt-shunt FB : loop gain

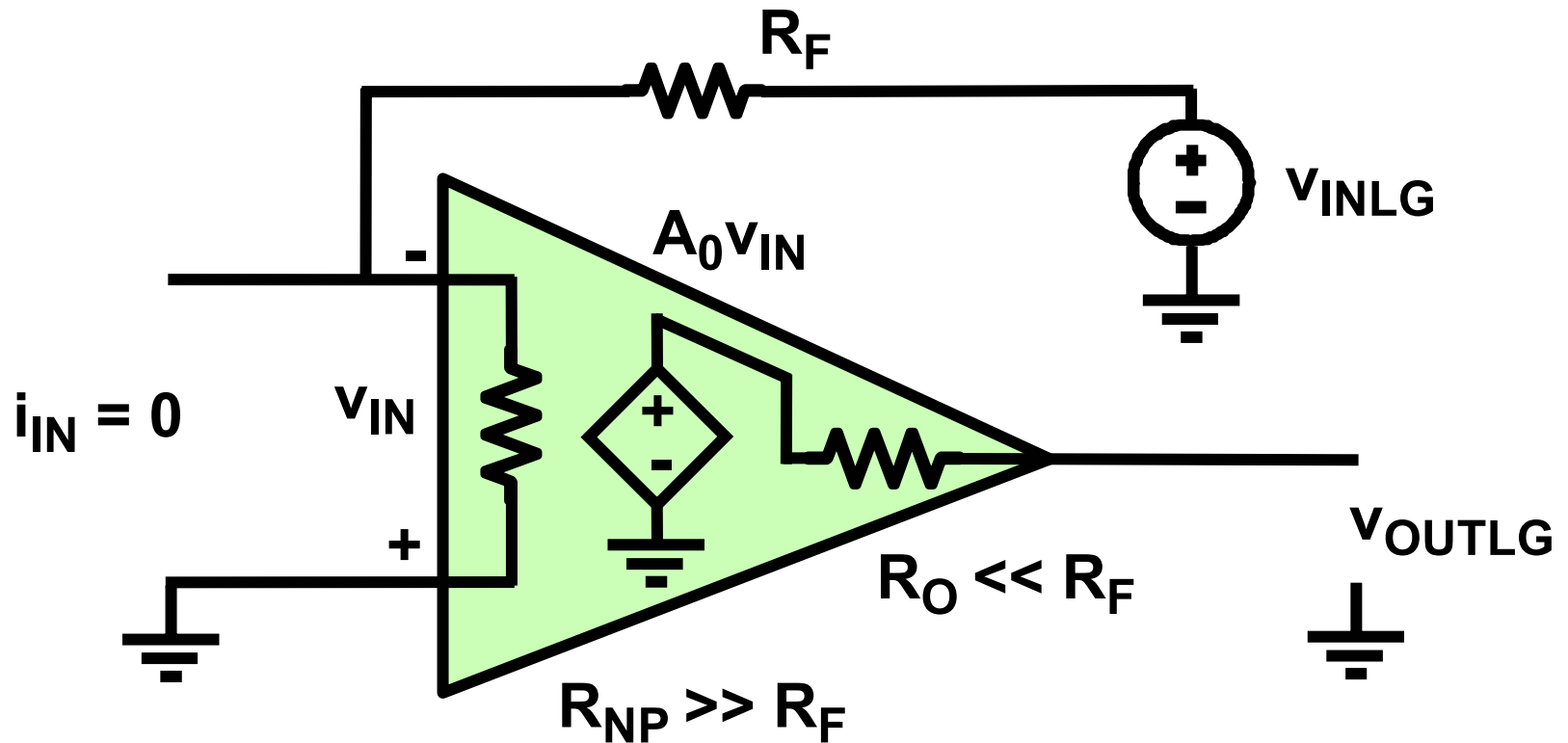


$$LG = \frac{V_{OUTLG}}{V_{INLG}} \approx A_{vOL} \approx A_0 \approx 10^4 \dots 10^6$$

Shunt-shunt FB : input resistance

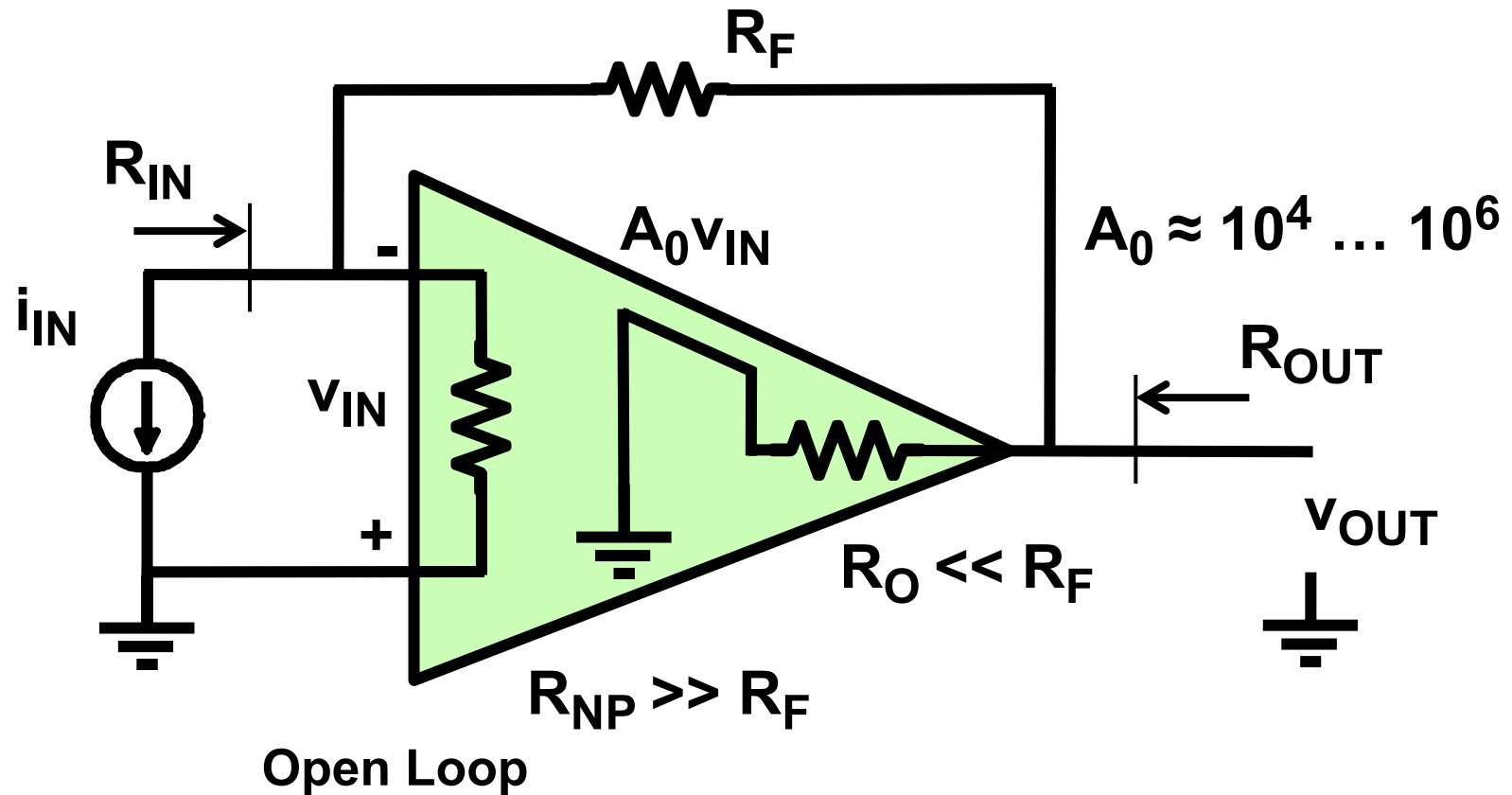

$$R_{IN} = \frac{v_{IN}}{i_{IN}} = \frac{R_{INOL}}{LG} \approx 0 \quad R_{INOL} = R_{IN} (A_v = 0) = R_{NP} // (R_F + R_O) \approx R_F$$


Shunt-shunt FB : output resistance

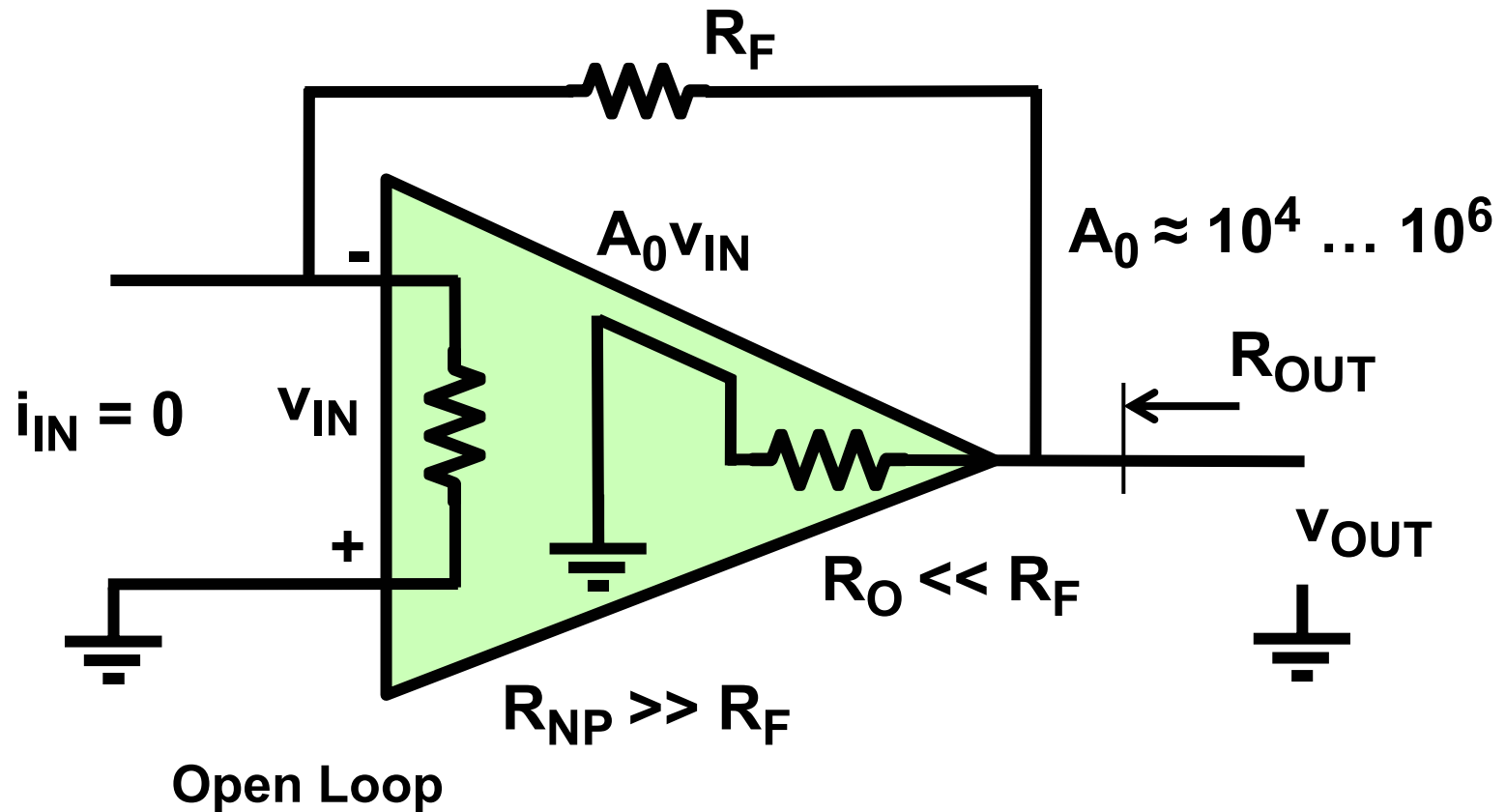

$$R_{OUT} = \frac{R_{OUTOL}}{LG} \approx 0$$

$$\begin{aligned}
 R_{OUTOL} &= R_{OUT} (A_v = 0) \\
 &= R_O // (R_F + R_{NP}) \approx R_O
 \end{aligned}$$

Shunt-shunt FB pair

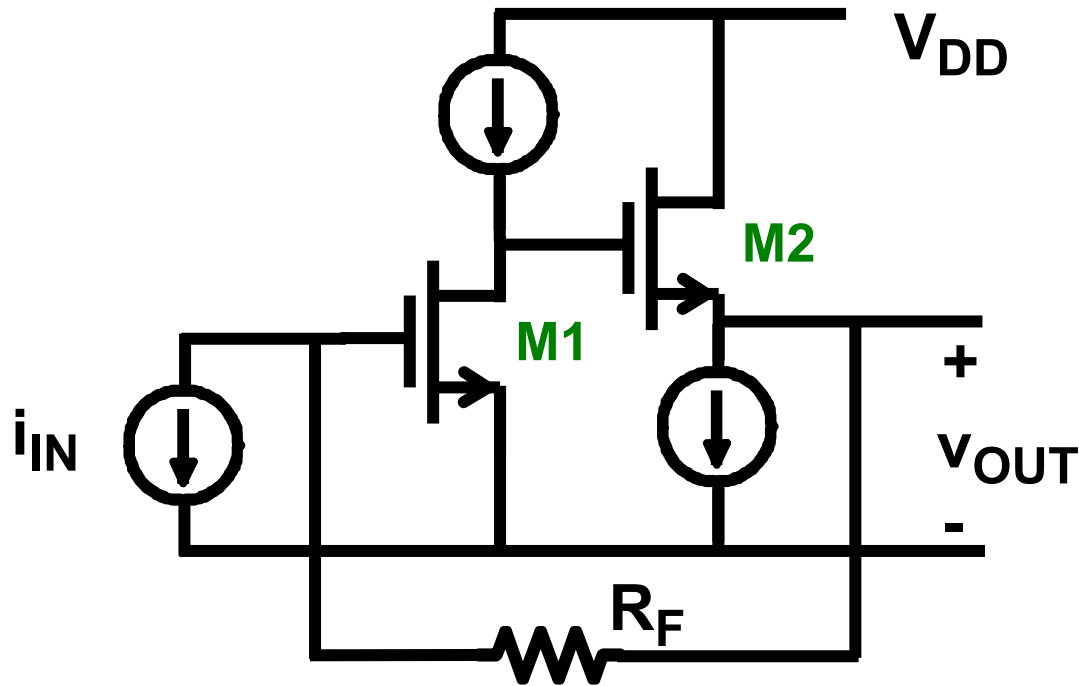


$$A_R = \frac{v_{OUT}}{i_{IN}} = R_F$$

$$LG = g_{m1}r_{o1}$$


$$R_{IN} = \frac{R_F}{LG} \approx 0 \text{ ?}$$

$$R_{OUT} = \frac{1/g_{m2}}{LG} \approx 0$$

Shunt-shunt FB pair with resistors

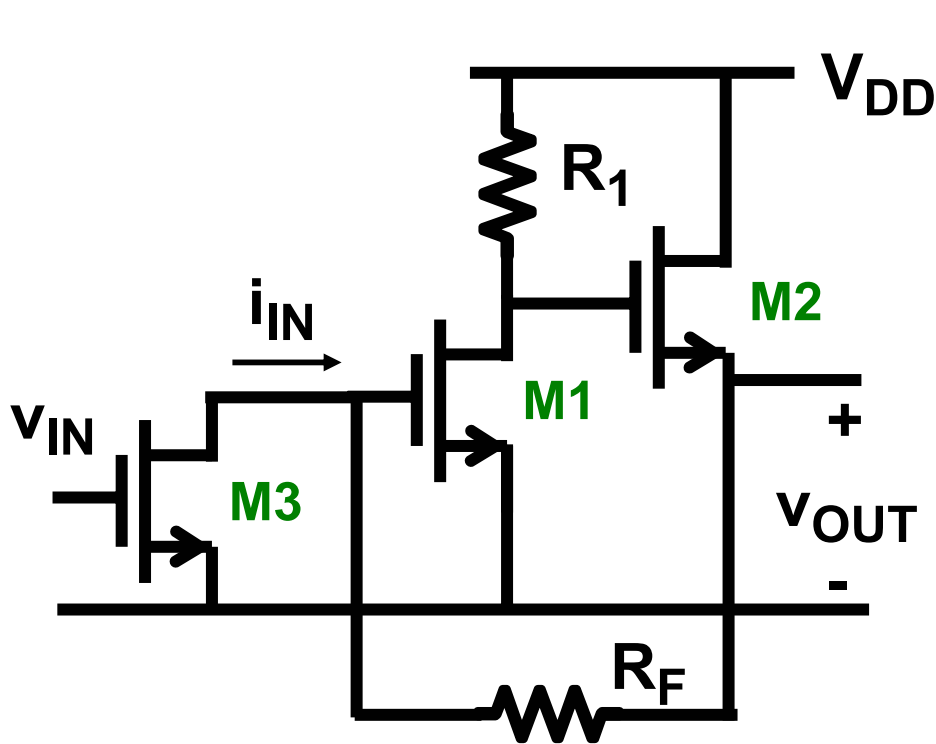


$$A_R = \frac{V_{OUT}}{i_{IN}} = R_F$$

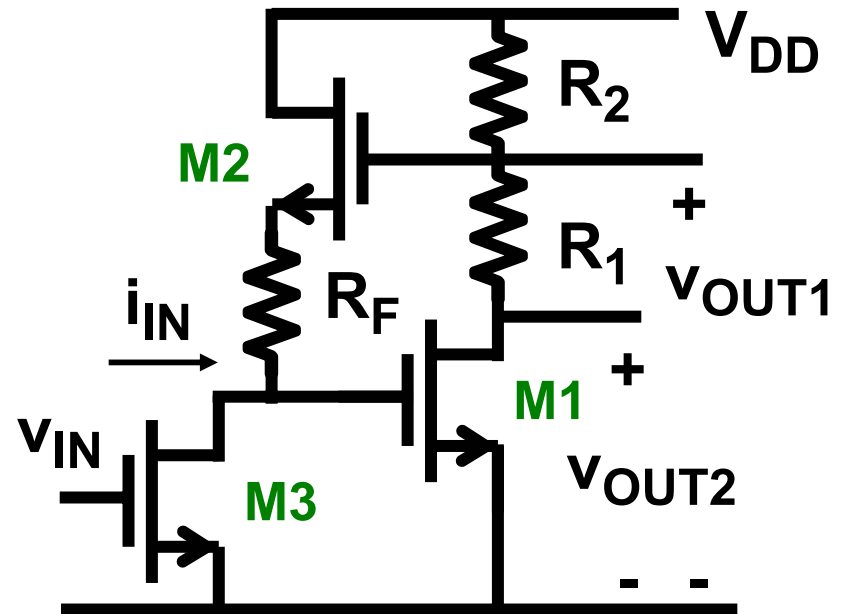

$$A_{R1} = R_F \quad A_{R2} = R_F \frac{R_1 + R_2}{R_2}$$

Ref. Cherry, Proc. IEE, Feb.63, 375-389; Holdenried, JSSC Nov.04, 1959-1967


Current detector with voltage amp.

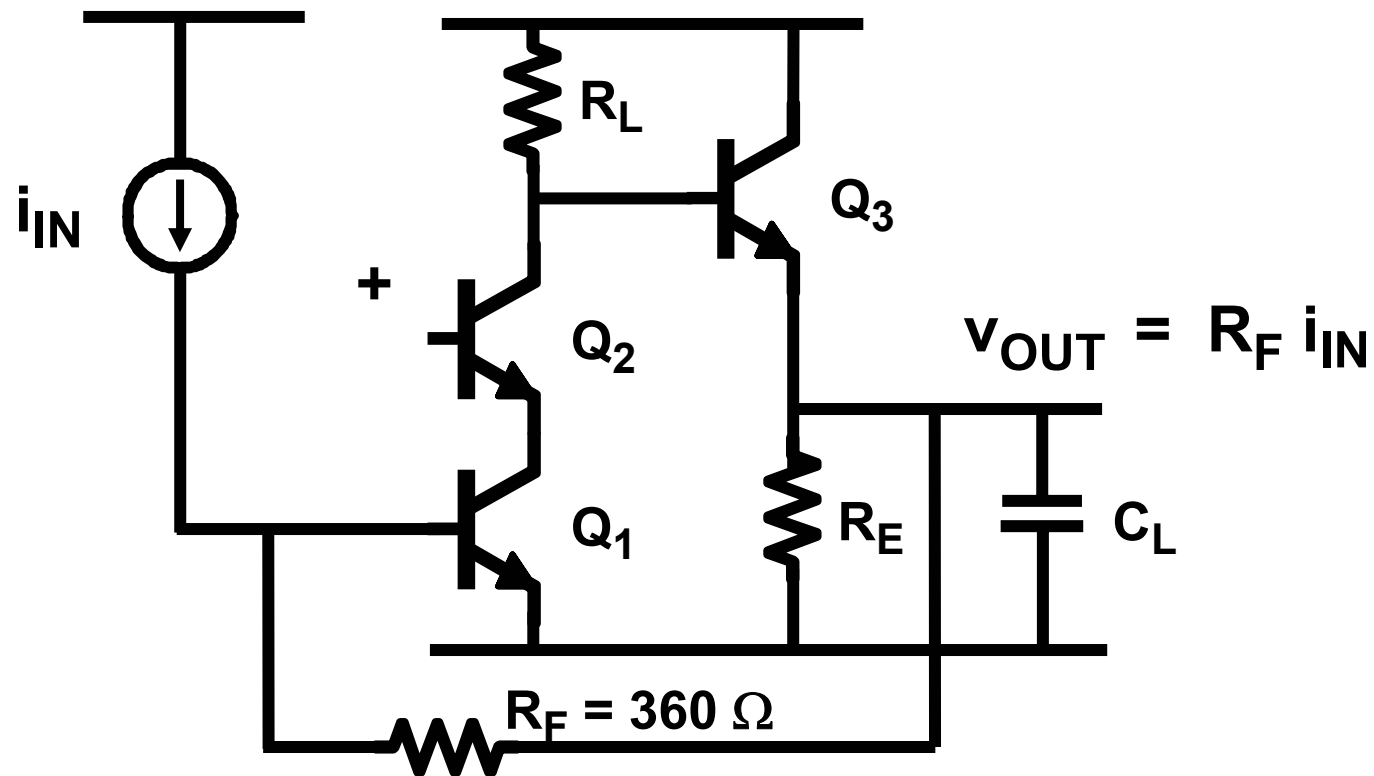

$f_T = 40 \text{ GHz}$ $r_B = 20 \Omega$ $BW = 10 \text{ GHz}$ $I_{TOT} = 10 \text{ mA}$

Ref. Baureis, JSSC
June 1993, 701-706

Shunt-shunt FB triple

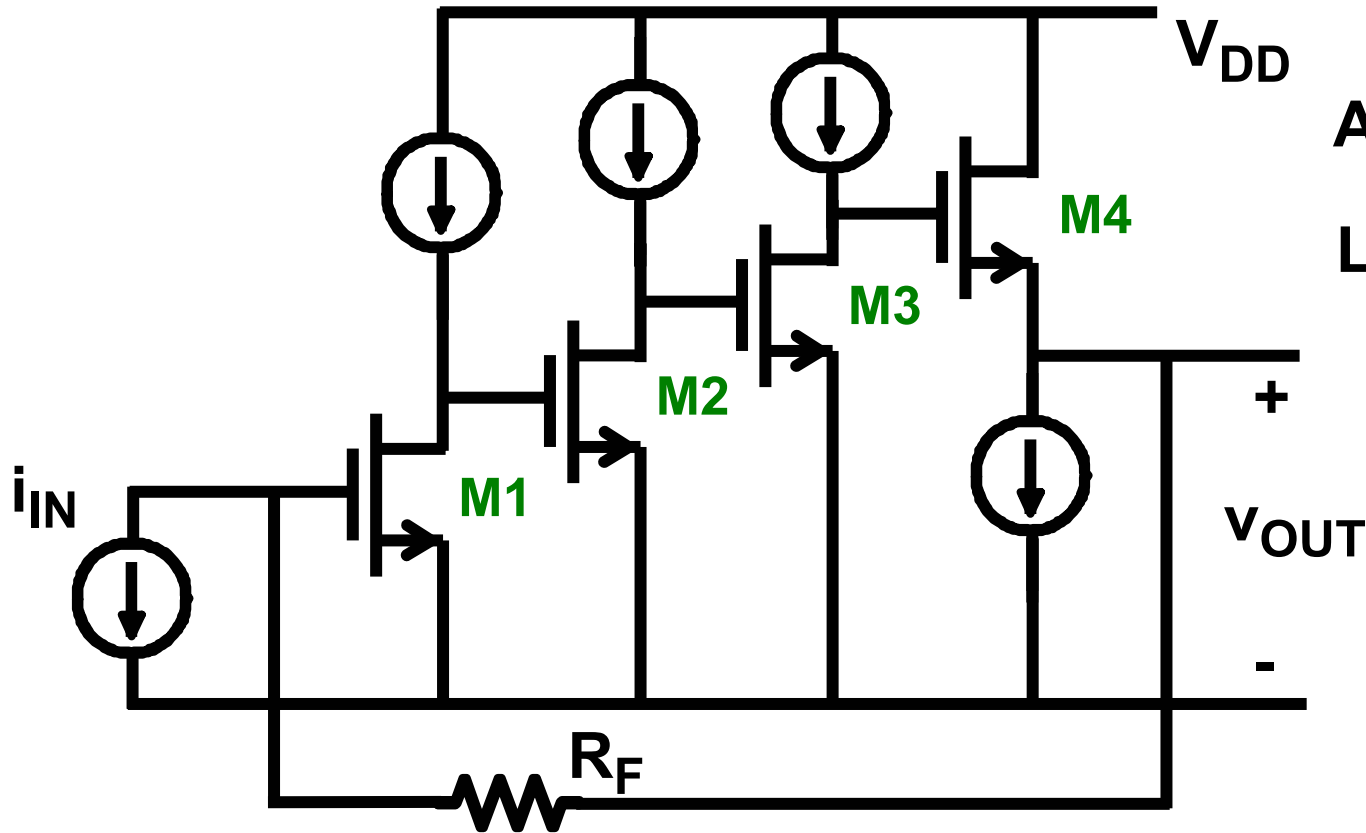


$$A_R = R_F$$

$$LG = A_{v1}A_{v2}A_{v3}$$

$$A_{vi} = g_{mi}r_{oi}$$

$$R_{IN} = \frac{R_F}{LG} \approx 0 \quad R_{OUT} = \frac{1/g_{m4}}{LG} \approx 0$$

Shunt-shunt FB triple: easier biasing

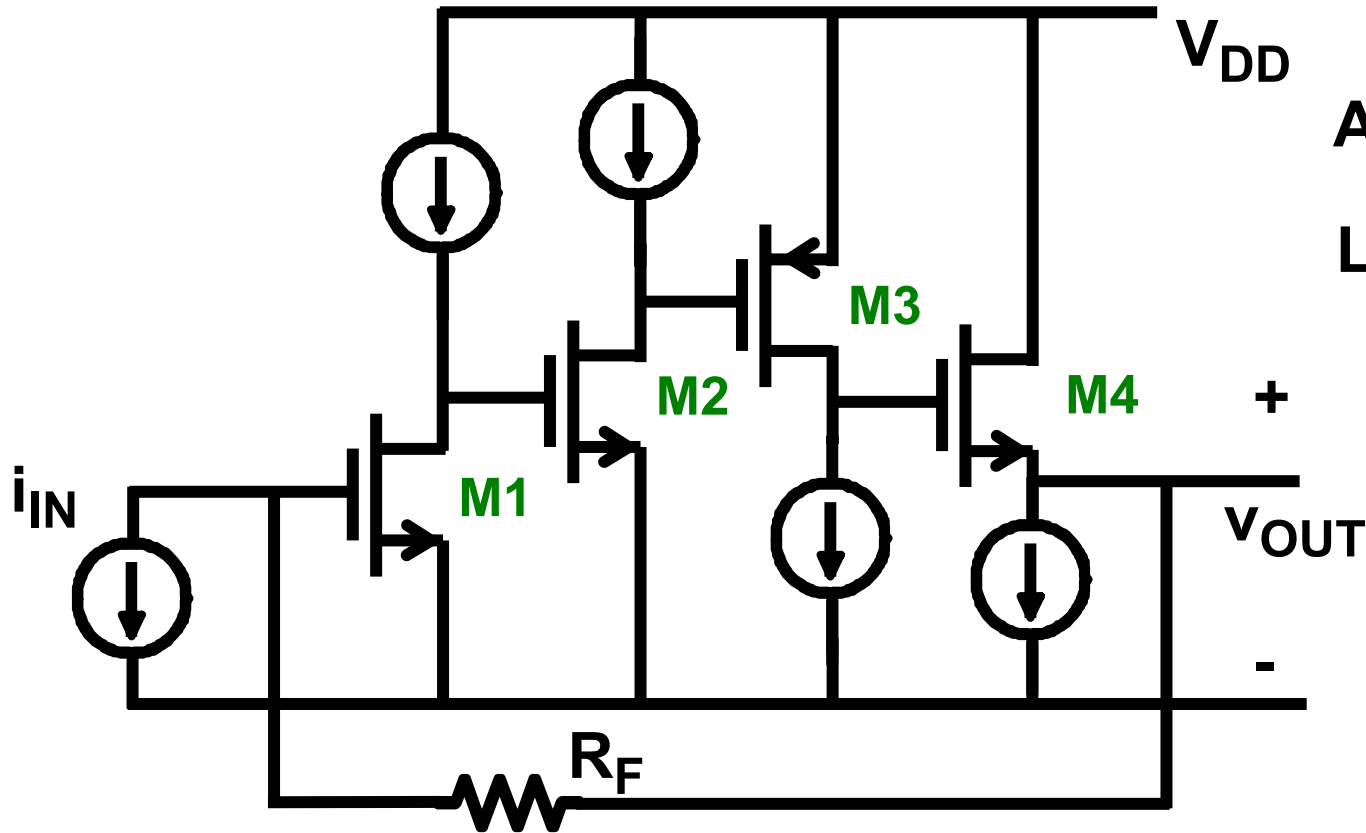

$$A_R = R_F$$

$$LG = A_{v1}A_{v2}A_{v3}$$

$$A_{vi} = g_{mi}r_{oi}$$

$$R_{IN} = \frac{R_F}{LG} \approx 0 \quad R_{OUT} = \frac{1/g_{m4}}{LG} \approx 0$$

Differential shunt-shunt FB pair

$$A_R = R_F$$


$$LG = A_{v1}A_{v2}$$

$$A_{v1} = g_{m1}r_{o1}$$

$$A_{v2} = g_{m2}r_{o2}$$

$$R_{IN} = \frac{2R_F}{LG} \approx 0 \quad R_{OUT} = \frac{2/g_{m3}}{LG} \approx 0$$

Current detector with voltage amplifier

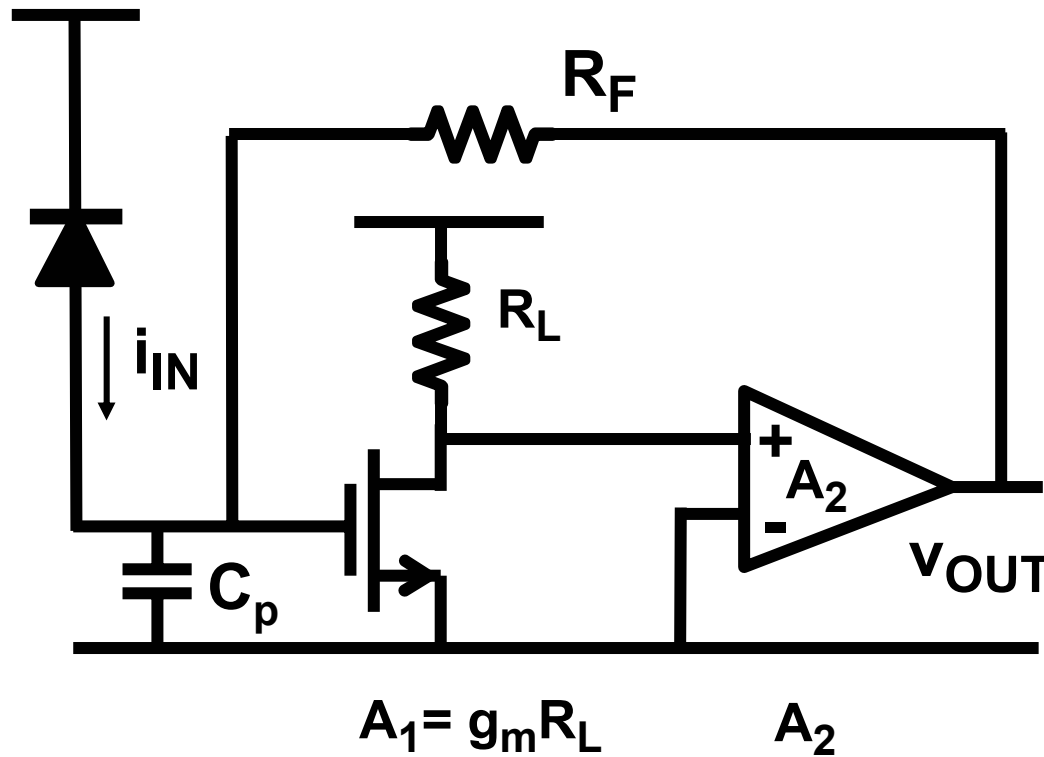


$$R_{IN} = \frac{V_{IN}}{i_{IN}} = \frac{R_F}{A_1 A_2}$$

$$A_R = \frac{V_{OUT}}{i_{IN}} = R_F$$

$$LG = A_1 A_2$$

$$f_{-3dB} = \frac{1}{2\pi R_{IN} C_p}$$

Single MOST with shunt-shunt FB

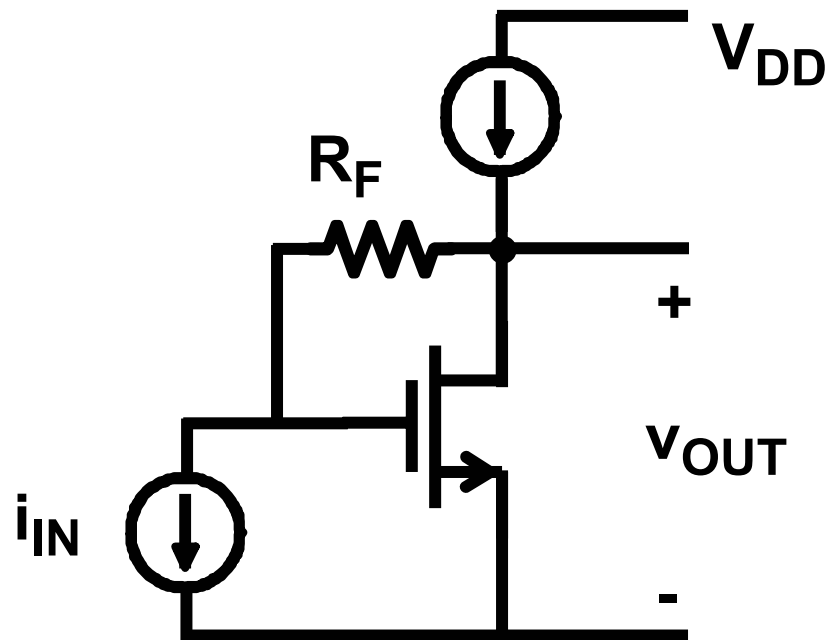

$$A_R = R_F \quad (\text{if } \gg 1/g_m)$$


$$LG = g_m r_o$$

$$R_{IN} = \frac{R_F + r_o}{LG} \approx 0 \quad ?$$

$$R_{OUT} = \frac{r_o}{LG} \approx 0 \quad ?$$

Ref.Cherry, Proc. IEE, Feb.63, 375-389

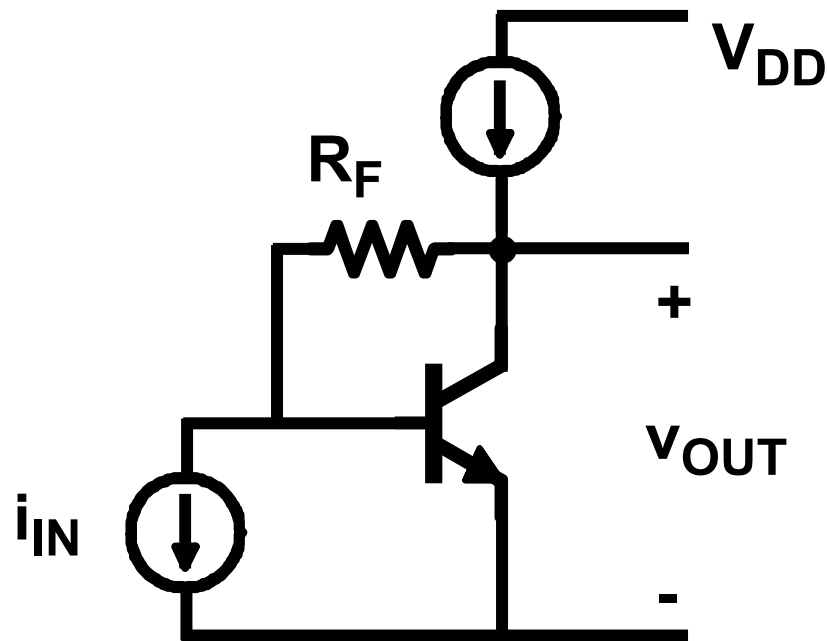Single bipolar transistor with shunt-shunt FB



$$A_R = R_F \quad (\text{if } \gg 1/g_m)$$

$$LG = \frac{g_m r_o r_\pi}{r_o + R_F + r_\pi}$$

$$R_{IN} = \frac{(R_F + r_o) // r_\pi}{LG} \approx 0 ?$$


$$R_{OUT} = \frac{r_o // (R_F + r_\pi)}{LG} \approx 0 ?$$

Far from ideal !!

Output loading : $R_F + r_\pi \approx r_o$

reduces the LG !!

Cascode with shunt-shunt FB

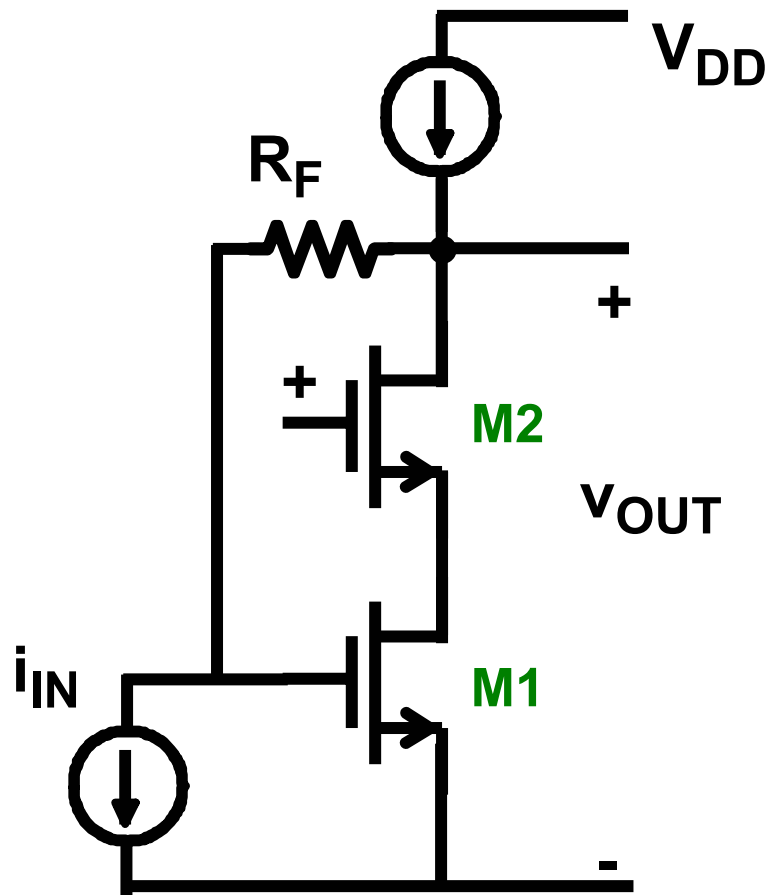

$$A_R = R_F$$


$$LG = g_{m1}r_{o1} g_{m2}r_{o2}$$

$$R_{IN} = \frac{R_F + r_{OUT}}{LG} \approx \frac{1}{g_{m1}} \approx 0$$

$$r_{OUT} = r_{o1}g_{m2}r_{o2}$$

$$R_{OUT} = \frac{r_{OUT}}{LG} \approx \frac{1}{g_{m1}} \approx 0$$

MOST Shunt-shunt FB triple

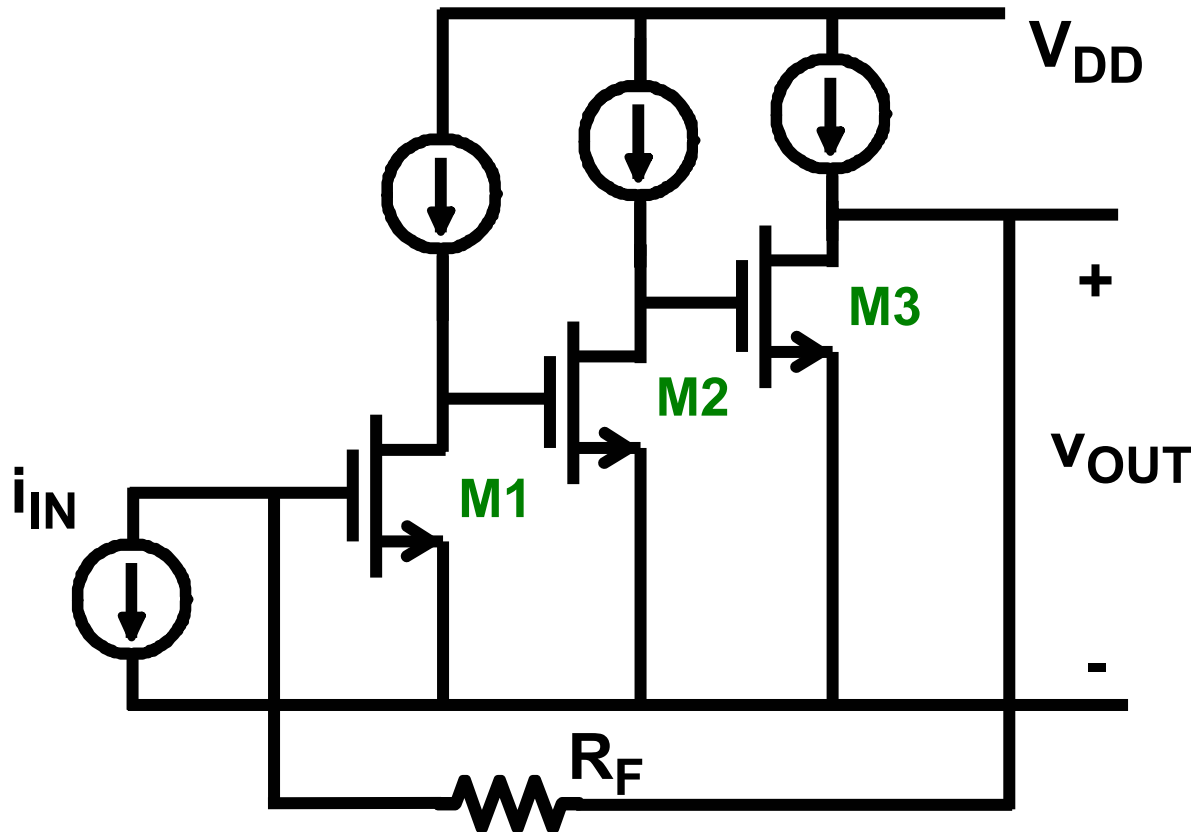

$$A_R = R_F$$


$$LG = A_{v1}A_{v2}A_{v3}$$

$$A_{vi} = g_{mi}r_{oi}$$

$$R_{IN} = \frac{R_F + r_{o3}}{LG} \approx 0$$

$$R_{OUT} = \frac{r_{o3}}{LG} \approx 0$$

Bipolar Transistor Shunt-shunt FB triple

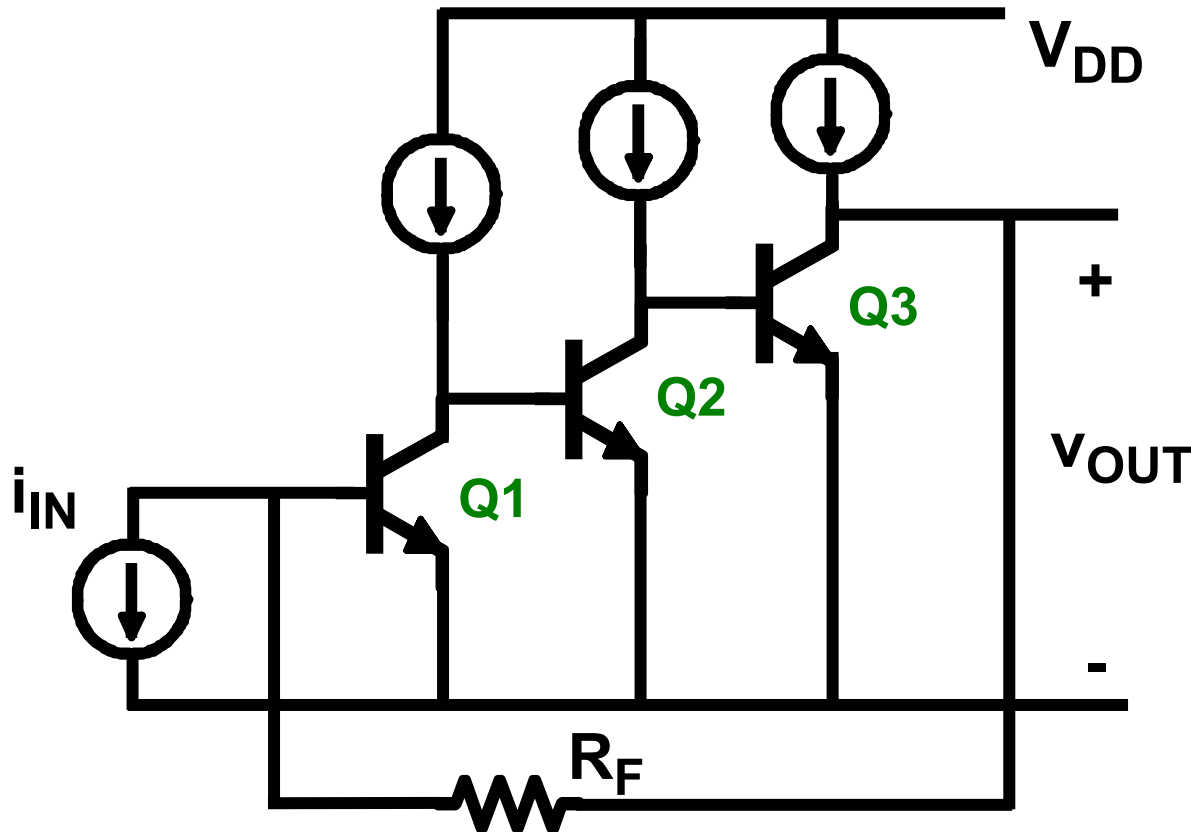

$$A_R = R_F$$

$$LG = A_{v1}A_{v2}A_{v3}$$

$$A_{v1} = g_{m1}(r_{o1} // r_{\pi2})$$

$$A_{v2} = g_{m2}(r_{o2} // r_{\pi3})$$

$$A_{v3} = g_{m3} R_{OUTOL}$$


$$R_{OUTOL} = r_{o3} // (R_F + r_{\pi1})$$

$$R_{OUT} = \frac{R_{OUTOL}}{LG} \approx 0$$

$$R_{IN} = \frac{(R_F + r_{o3}) // r_{\pi1}}{LG} \approx 0$$

**Output loading : $R_F + r_{\pi3} \approx r_{o3}$
reduces the LG !!**

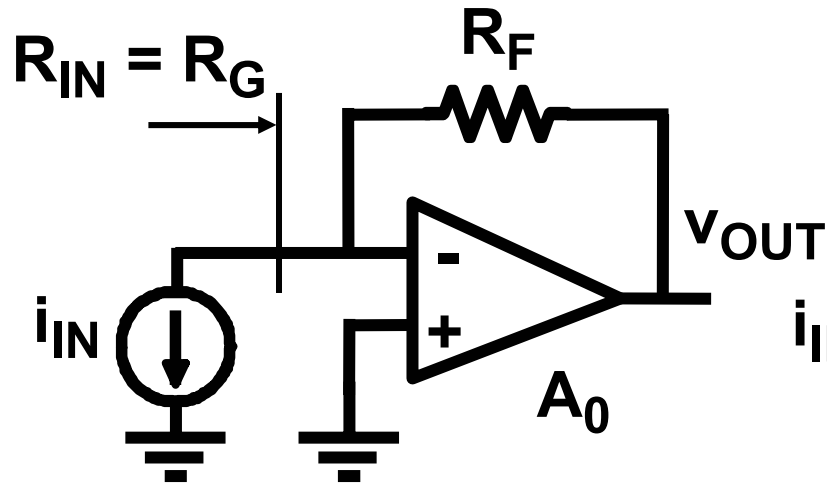
Shunt-shunt FB with non-ideal current source



$$A_R = R_F$$

$$LG = A_0$$

$$R_{IN} = \frac{R_F}{A_0}$$

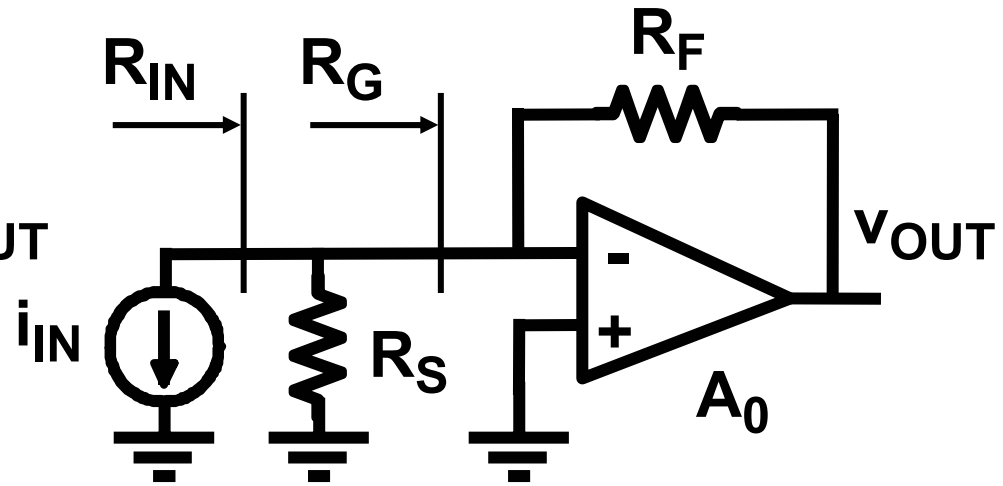

$$A_R = R_F$$


$$LG = A_0$$

$$R_G = \frac{R_F}{A_0}$$

if $R_S > \frac{R_F}{A_0}$

$$R_{IN} = R_G // R_S$$

Shunt-shunt FB with voltage source

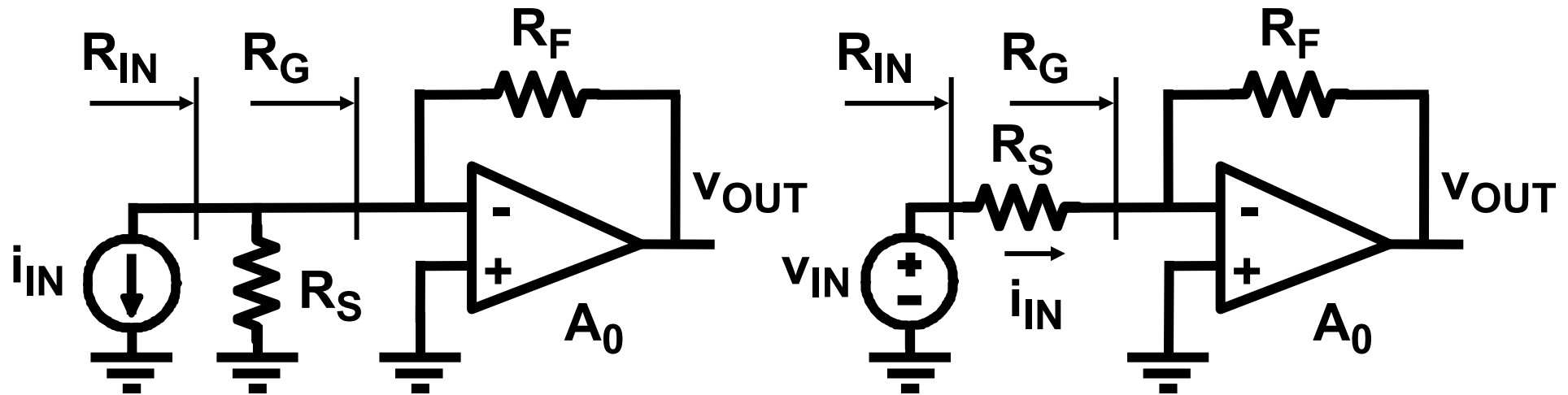

$$A_R = R_F \quad \text{if } R_S > \frac{R_F}{A_0}$$

$$LG = A_0$$


$$R_G = \frac{R_F}{A_0} \quad R_{IN} = R_G // R_S$$

$$A_R = R_F \quad \text{if } R_S > \frac{R_F}{A_0}$$

$$LG = A_0$$

$$R_G = \frac{R_F}{A_0} \quad R_{IN} = R_G + R_S$$

Shunt-shunt feedback : Gain and R_{OUT}

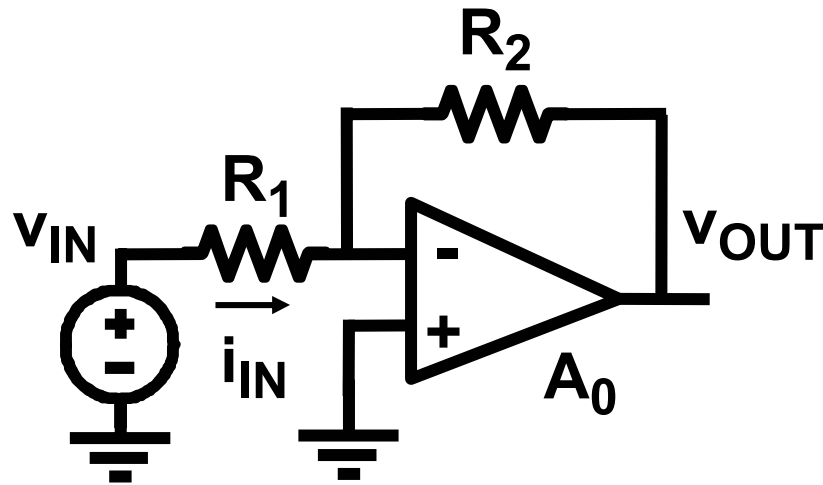

$$LG = A_0 \quad A_0 \approx 10^4 \dots 10^6$$

$$A_R = R_2 \quad \text{if } R_1 > \frac{R_2}{A_0}$$


$$\frac{V_{OUT}}{V_{IN}} = \frac{V_{OUT}}{i_{IN}} \frac{i_{IN}}{V_{IN}}$$

$$A_V = -A_R \frac{1}{R_1}$$

$$A_V = -\frac{R_2}{R_1}$$

$$R_{OUT} = \frac{R_{OUT0L}}{LG}$$

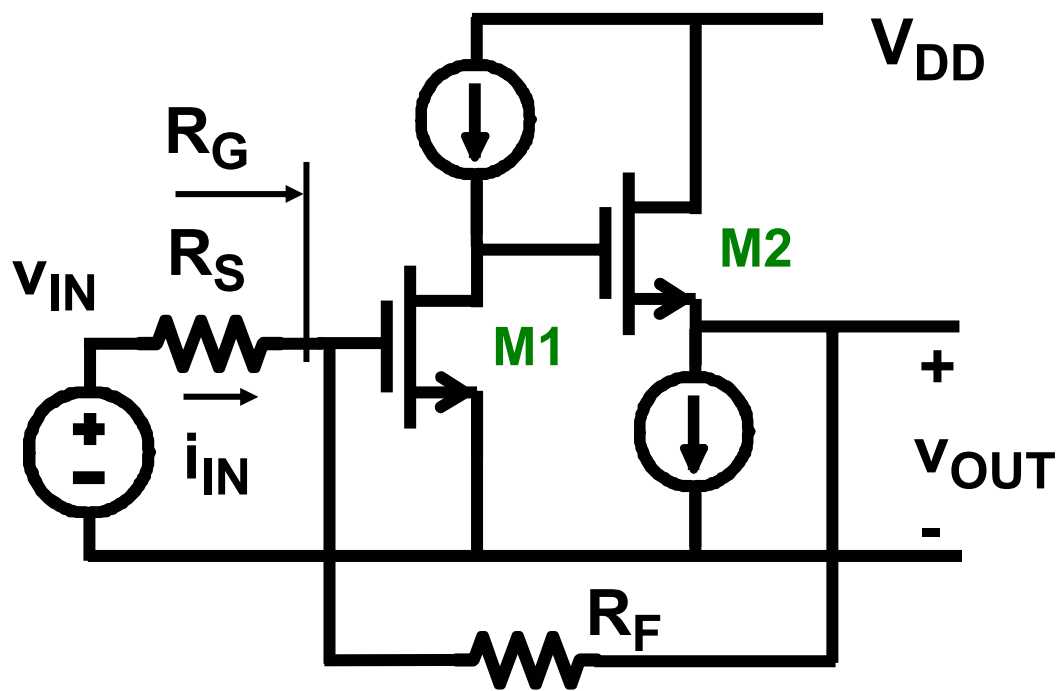Shunt-shunt FB pair with with voltage source



$$A_R = R_F \quad A_V = -\frac{R_F}{R_S}$$

$$LG = g_{m1}r_{o1}$$


$$R_{IN} = R_S + R_G$$

$$R_G = \frac{R_F}{LG} = \frac{R_F}{g_{m1}r_{o1}} \approx 0$$

$$R_{OUT} = \frac{1/g_{m2}}{LG} \approx 0$$

if $R_S > \frac{R_F}{A_0}$

Shunt-shunt FB pair with input loading

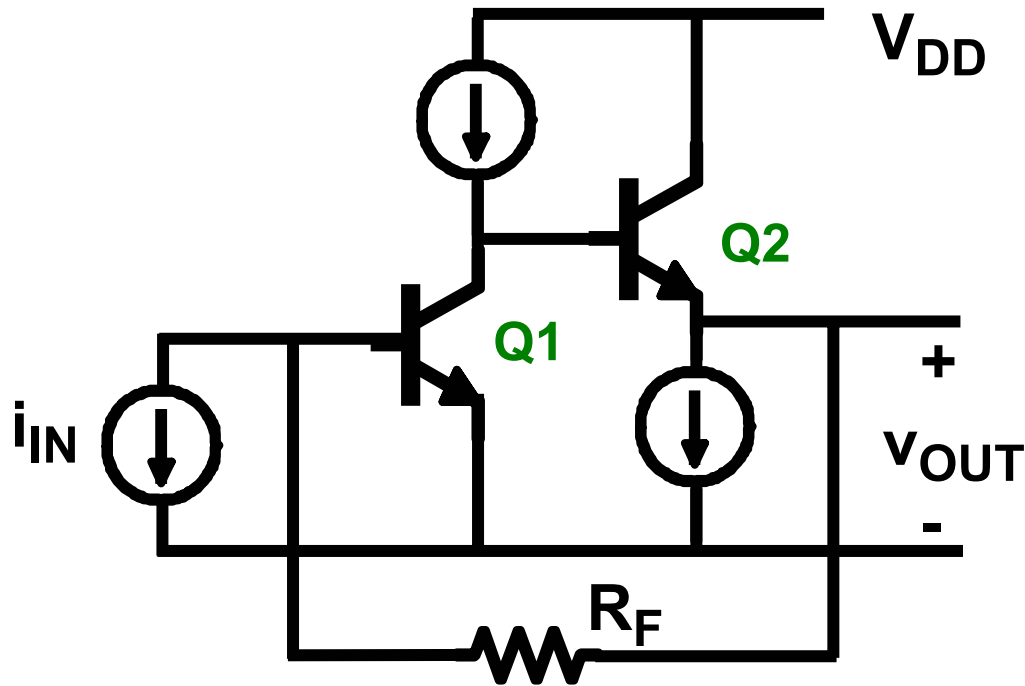

Input loading : $R_F \approx r_{\pi 1}$

$$A_R = R_F$$


$$LG = g_{m1} r_{o1} \frac{r_{\pi 1}}{R_F + r_{\pi 1}}$$

$$R_{IN} = \frac{R_F // r_{\pi 1}}{LG} = \frac{R_F}{g_{m1} r_{o1}} \approx 0$$

$$R_{OUT} = \frac{R_{OUTOL}}{LG} \approx 0$$

$$R_{OUTOL} = \frac{1}{g_{m2}} + \frac{r_{o1}}{\beta}$$

Shunt-shunt FB pair with voltage source

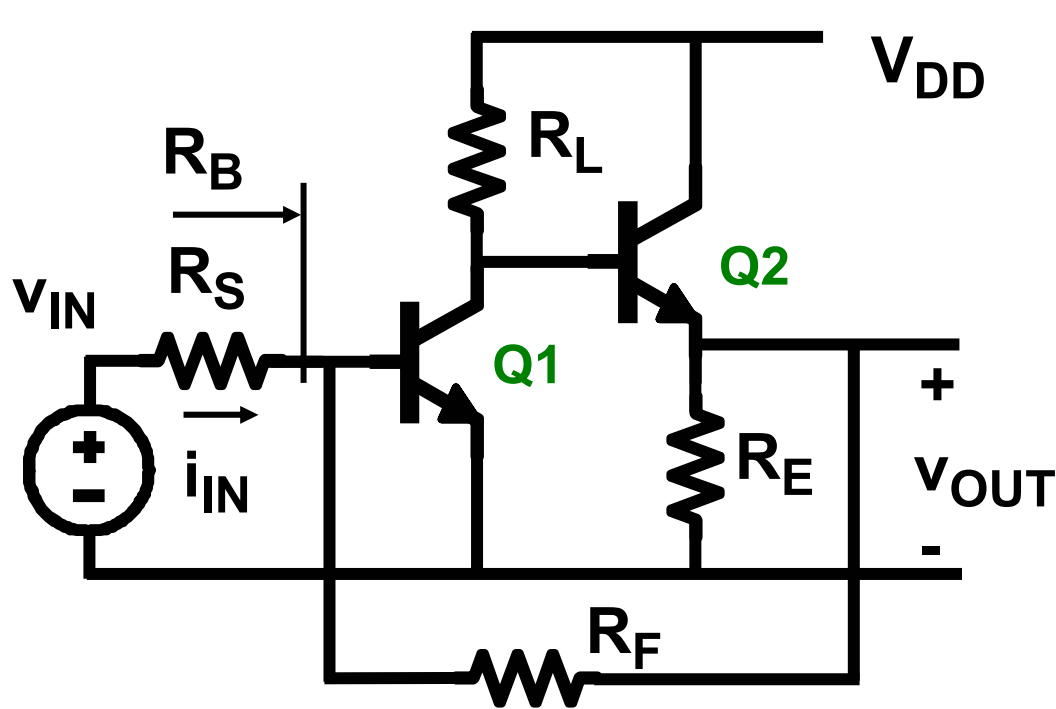

$$A_R = -R_F \quad A_V = -\frac{R_F}{R_S}$$

$$LG = g_{m1} R_L \frac{r_{\pi 1}}{R_F + r_{\pi 1}}$$

$$R_B = \frac{R_F // r_{\pi 1}}{LG} \approx 0$$


$$R_{IN} = R_S + R_B$$

Input loading :

$$R_F \approx r_{\pi 1}$$

$$R_{OUT} = \frac{R_{OUTOL}}{LG} \approx 0 \quad R_{OUTOL} = \frac{1}{g_{m2}} + \frac{R_L}{\beta}$$

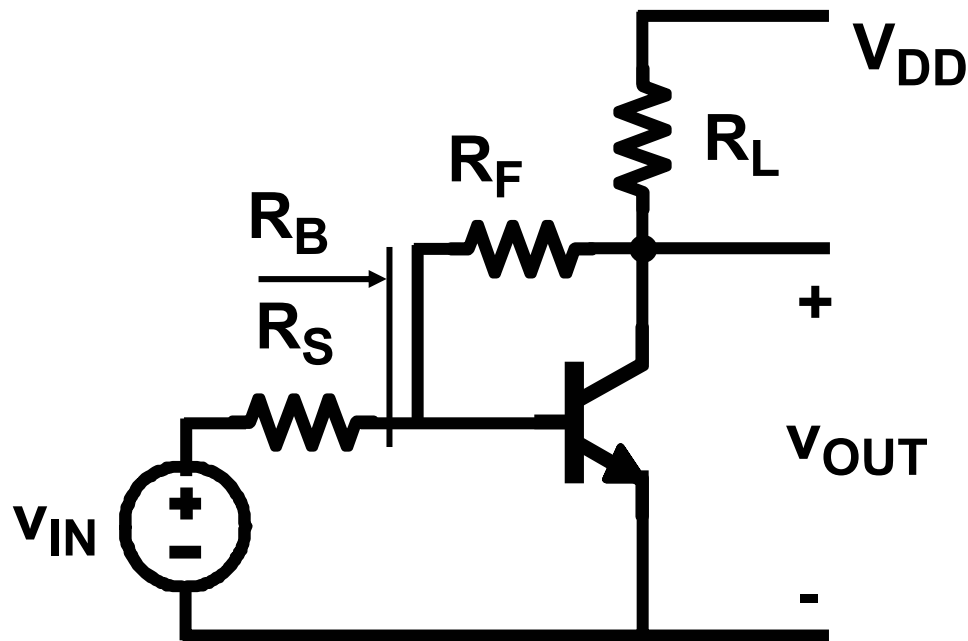Non-ideal single-transistor shunt-shunt FB



$$A_R \approx R_F \quad A_V \approx -\frac{R_F}{R_S}$$

$$LG \approx g_m r_{oLF}$$

$$R_{IN} = R_S + R_B$$


$$R_B \approx \frac{r_{\pi} // (R_F + r_{oL})}{LG} \approx 0$$

$$R_{OUT} \approx \frac{r_{oLF}}{LG} \approx 0 \quad ??$$

Output loading : $R_F \approx r_{oL}$ $r_{oL} = r_o // R_L$ $r_{oLF} = r_o // R_L // R_F$

Input loading : $R_F \approx r_{\pi}$

Non-ideal single-transistor Feedback

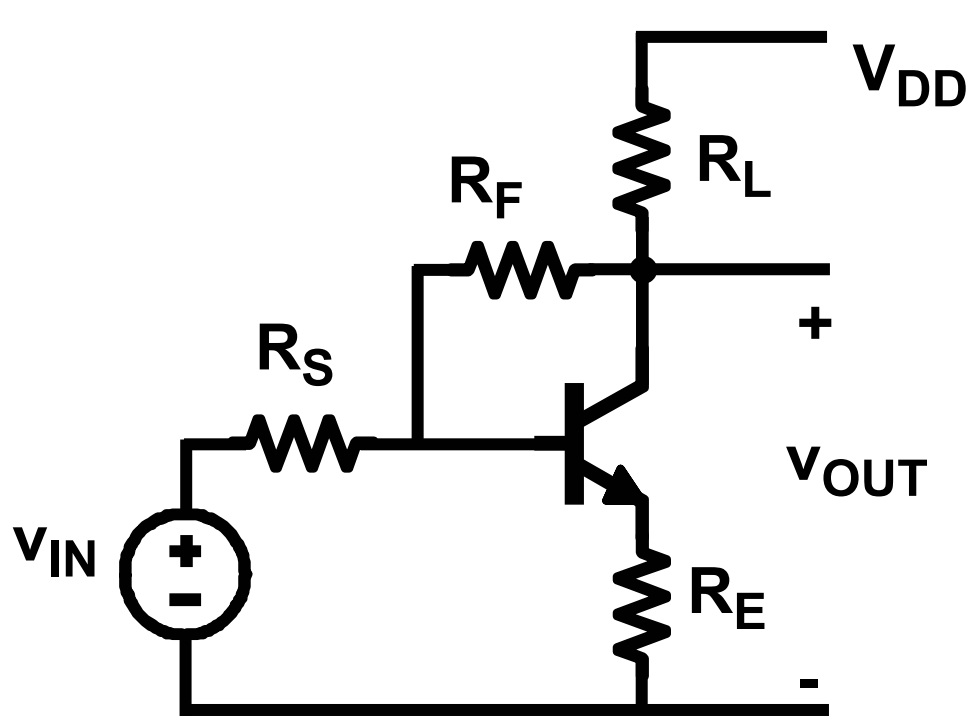

$$A_R = R_F \quad A_V = -\frac{R_F}{R_S}$$

$$LG = ?$$


$$R_{IN} = ?$$

$$R_{OUT} = ?$$


Output loading : $R_F \approx r_{oL}$ $r_{oL} = r_o // R_L$

Input loading : $R_F \approx r_\pi$

Shunt-shunt feedback in Right-leg drive

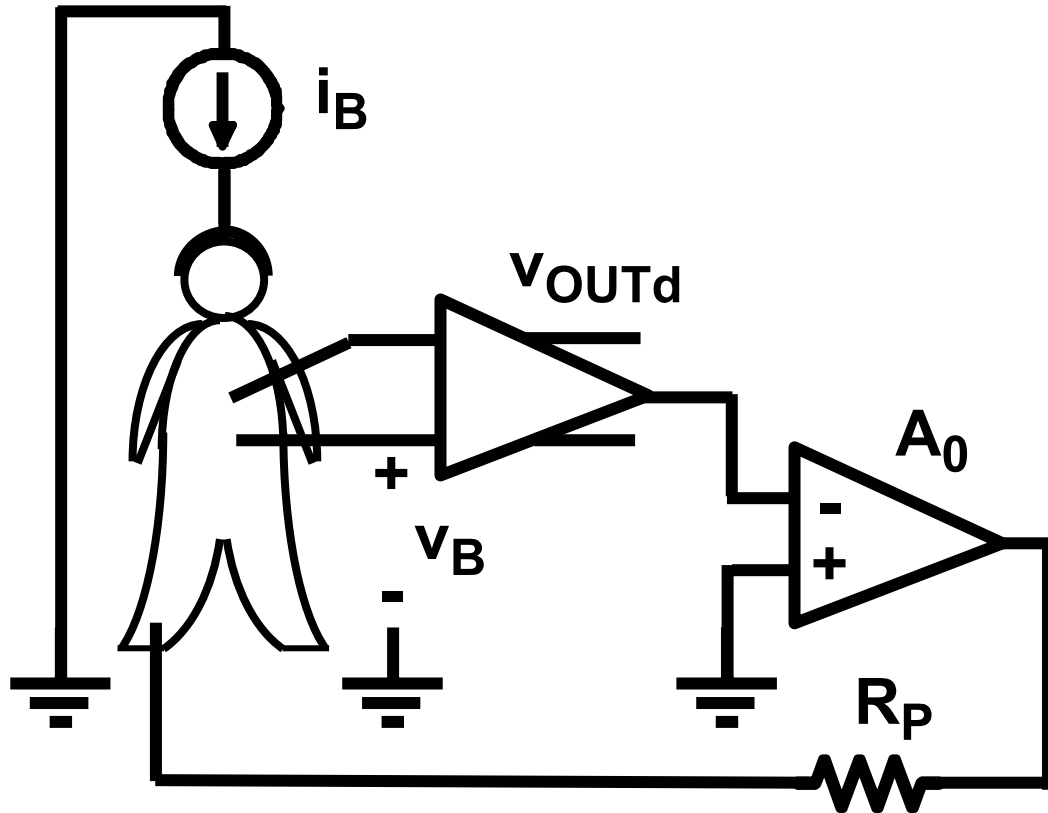

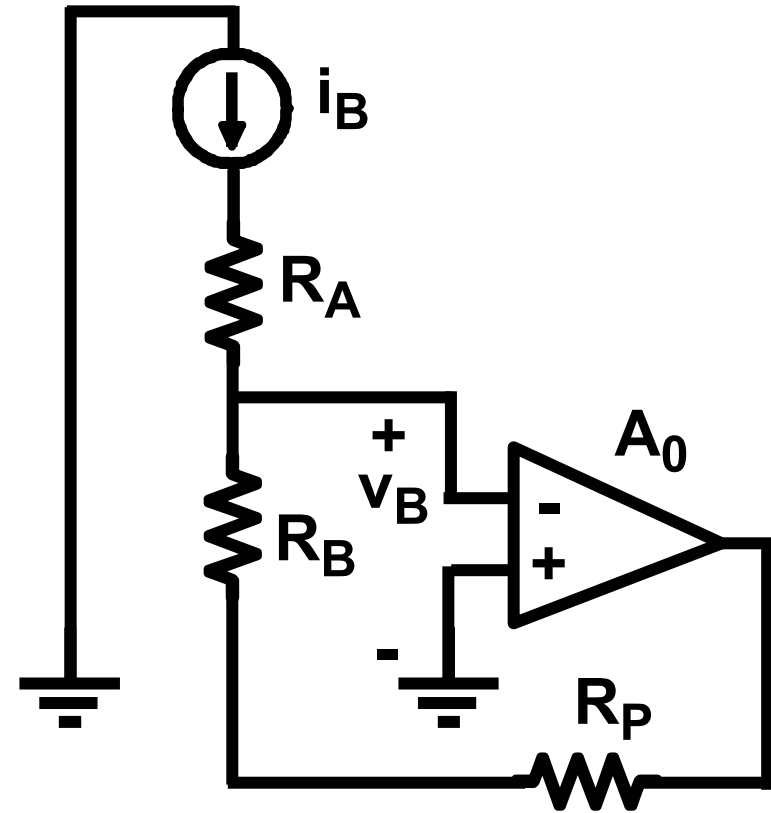$i_B \approx 10 \mu A_{RMS}$
 for 220 V_{RMS} (50 Hz) through 150 pF




$$\frac{V_B}{i_B} = \frac{R_p + R_B}{A_0 + 1}$$

Table of contents

- Introduction
- Shunt-shunt FB for Transimpedance amps.
- **Shunt-series FB for current amplifiers**
- Transimpedance amplifiers for
low noise and high frequencies

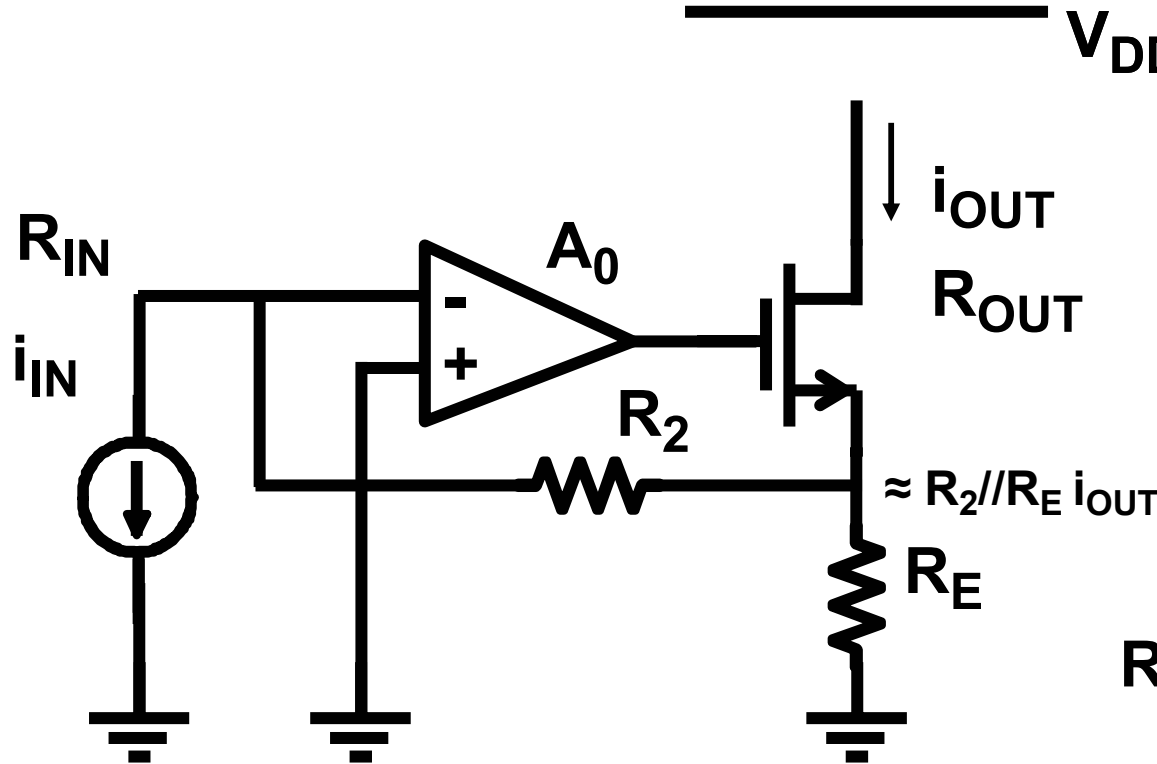Shunt-series feedback : Gain, R_{IN} & R_{OUT}



$$V_{DD} \quad LG = A_0$$

$$A_1 = 1 + \frac{R_2}{R_E}$$

$$R_{IN} = \frac{R_2^*}{LG} \approx 0$$


$$R_{OUTOL} = r_o (1 + g_m R_E)$$

$$R_{OUT} = R_{OUTOL} LG \approx \infty$$

$$R_2^* = R_2 + R_E / (1 + g_m R_E) \approx R_2$$

$$R_E > 1/g_m \quad R_2 > 1/g_m$$

Shunt-series feedback with load R_L

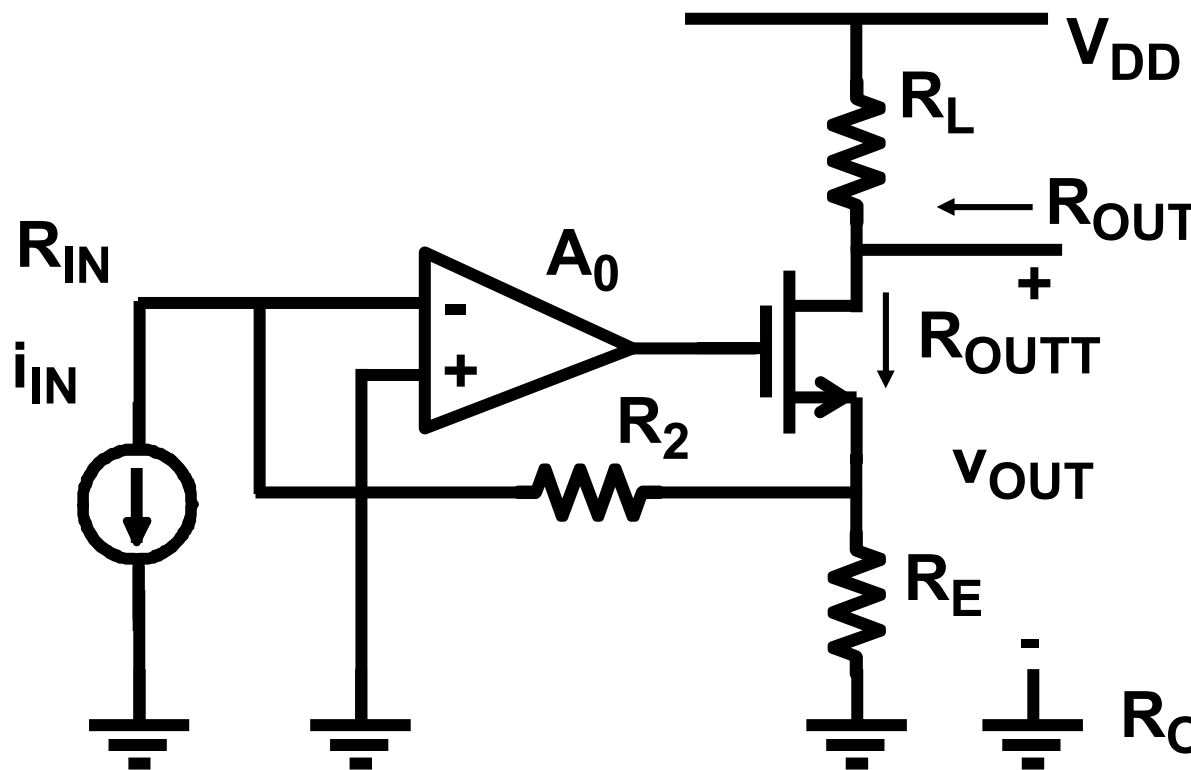

$$LG = A_0$$

$$A_I = 1 + \frac{R_2}{R_E}$$

$$A_R = A_I R_L$$

$$R_{IN} = \frac{R_2}{LG} \approx 0$$


$$R_{OUT} = R_{OUTT} // R_L \approx R_L$$

$$R_{OUTT} = R_{OUTTOL} LG \approx \infty$$

$$R_{OUTTOL} = r_o (1 + g_m R_E)$$

$$R_E > 1/g_m \quad R_2 > 1/g_m$$

Ideal current buffer

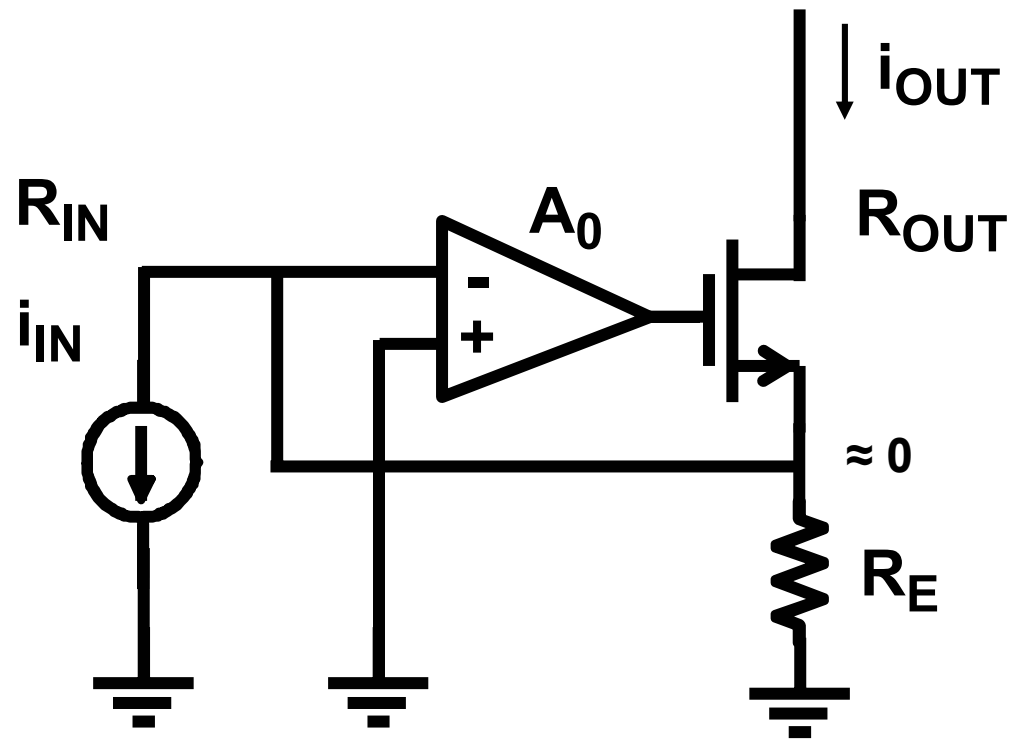

$$R_E > 1/g_m$$

$$A_I = 1$$


$$LG = A_0$$

$$R_{IN} = \frac{1/g_m}{LG} \approx 0$$

$$R_{OUTOL} = r_o (1 + g_m R_E)$$

$$R_{OUT} = R_{OUTOL} LG \approx \infty$$

Ideal current mirror

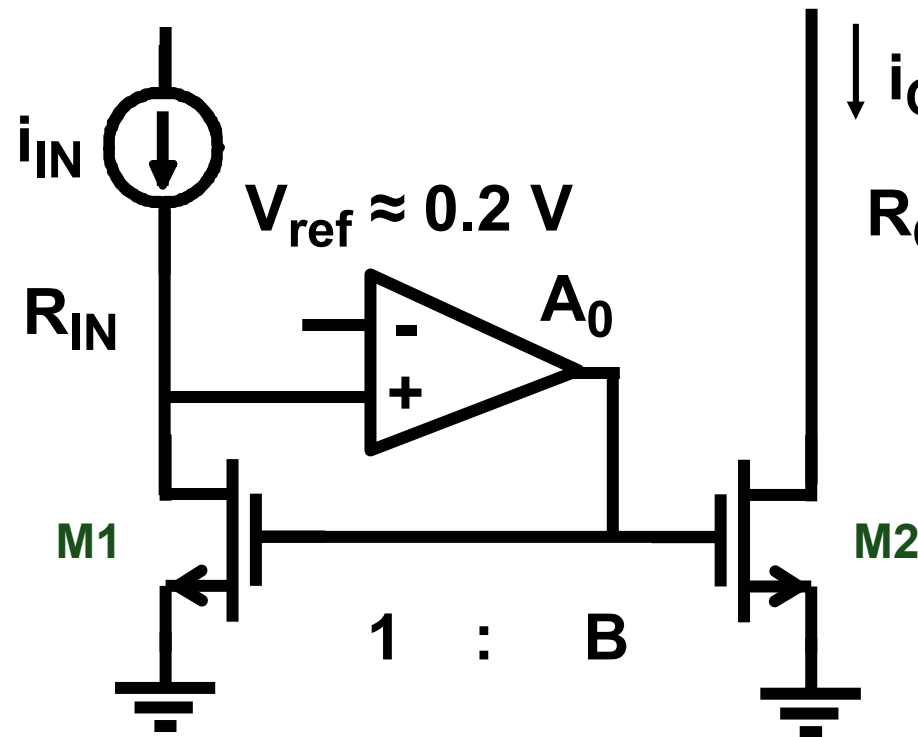

$$i_{OUT} = B i_{IN} \quad A_I = B$$

$$R_{OUT}$$


$$LG = g_{m1} r_{o1} A_0$$

$$R_{IN} = \frac{R_{INOL}}{LG} = \frac{1}{g_{m1} A_0} \approx 0$$

$$R_{INOL} = r_{o1}$$

$$R_{OUT} = r_{o2}$$

Gain boosting

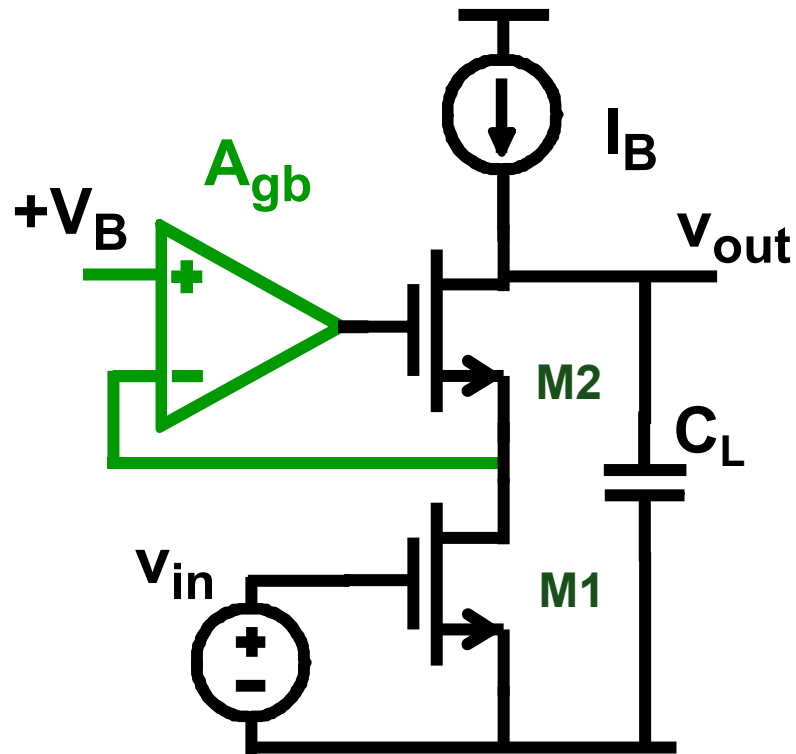

$$LG = A_{gb}$$

$$R_{E2} = \frac{1/g_{m2}}{LG} \approx 0$$


$$R_{OUTOL} = r_{o2} (1 + g_{m2}r_{o1})$$

$$R_{OUT} = R_{OUTOL} LG \approx \infty$$

$$A_v = A_{gb} (g_m r_{DS})_1 (g_m r_{DS})_2$$

Hosticka, JSSC Dec.79, pp. 1111-1114; Sackinger, JSSC Febr.90, pp. 289-298;
Bult JSSC Dec.90, pp. 1379-1384

Linear laser diode driver

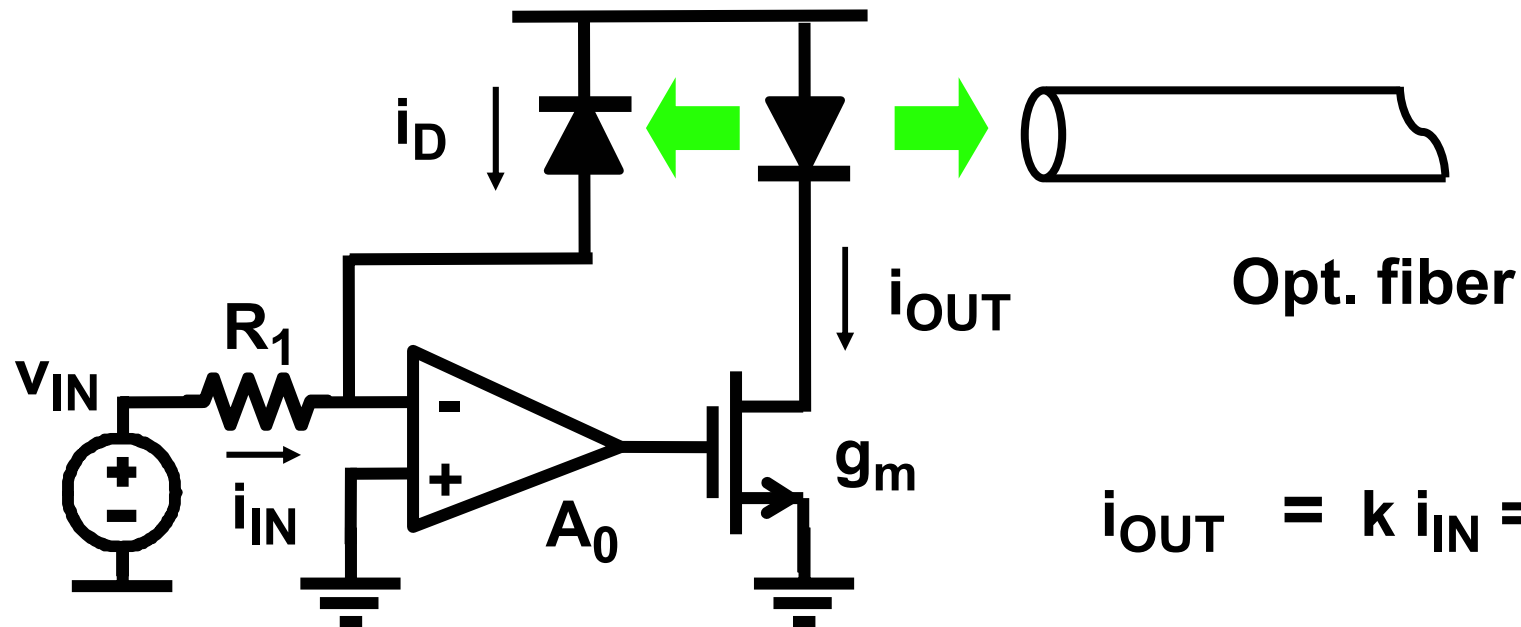

$$i_D = \frac{i_{OUT}}{k}$$


$$i_{OUT} = k i_{IN} = k \frac{V_{IN}}{R_1}$$

$$LG = \frac{g_m A_0}{k}$$


Table of contents

- Introduction
- Shunt-shunt FB for Transimpedance amps.
- Shunt-series FB for Current amplifiers
- Transimpedance amplifiers for
low noise and high frequencies

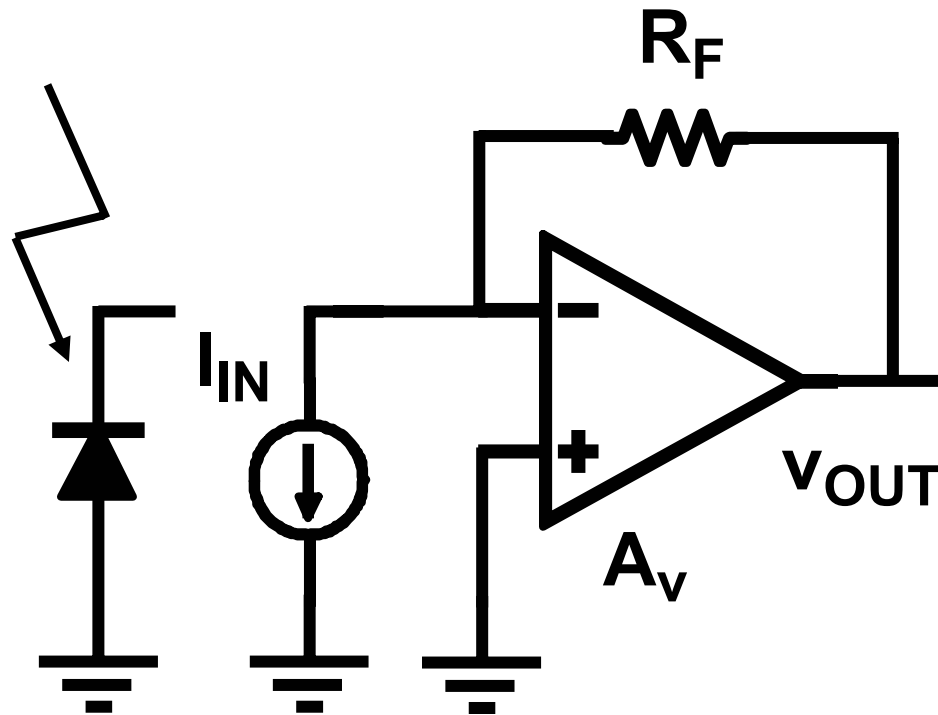Optical receiver : Current or voltage amplifier




$$V_{OUT} = R_F I_{IN}$$

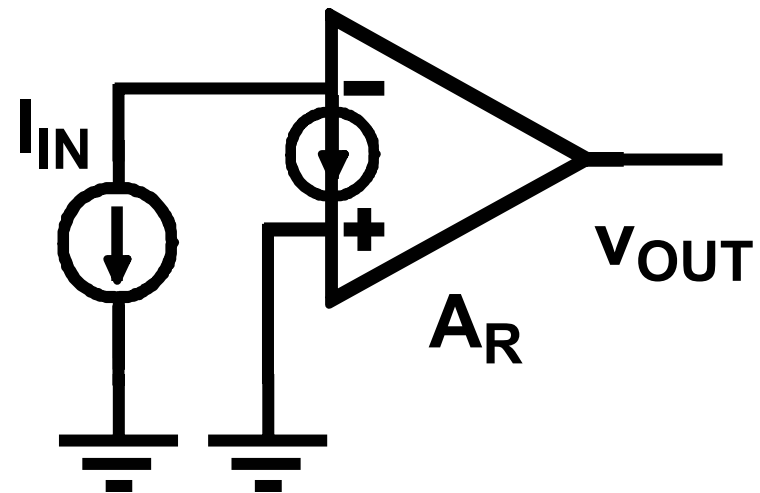

$$V_{OUT} = A_R I_{IN}$$

Current detector with voltage amplifier

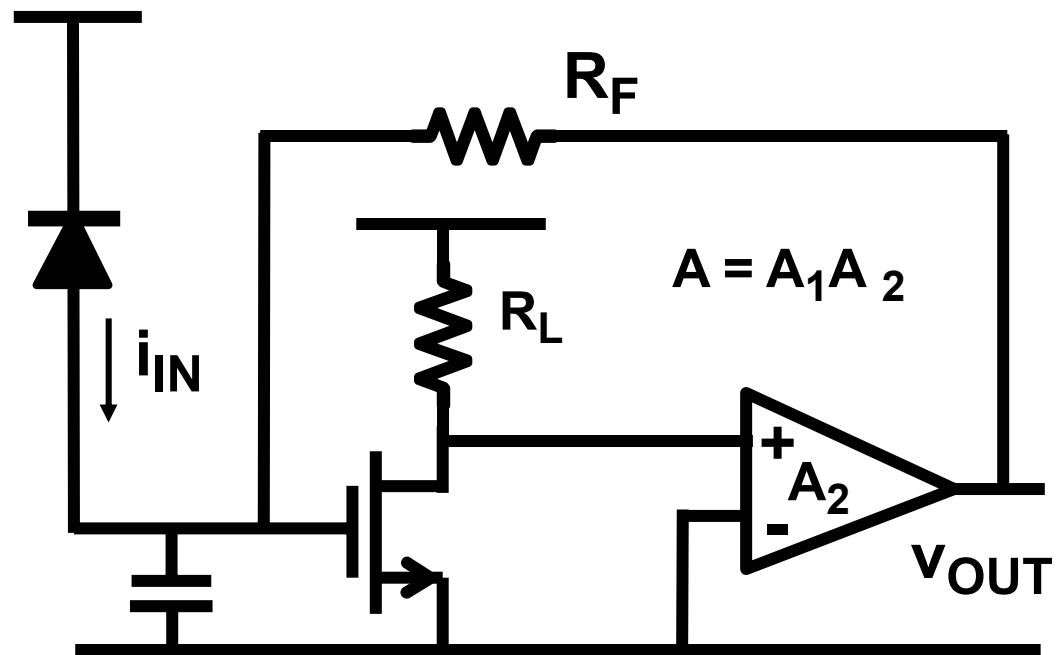

$$C_P = C_D + C_{GS} \quad A_1 = g_m R_L$$

Noise matching : $C_D = C_{GS}$


$$\frac{V_{IN}}{i_{IN}} = \frac{R_F}{A_1 A_2} \frac{1}{1 + R_F \frac{C_P}{A_1 A_2} s}$$

$$\frac{V_{OUT}}{i_{IN}} = R_F \frac{1}{1 + R_F \frac{C_P}{A_1 A_2} s}$$

$$T = \frac{A_1 A_2}{1 + R_F C_P s}$$

$$A_R \text{ BW (THz}\Omega) = \frac{A_1 A_2}{2\pi C_P}$$

Current detector with voltage amplifier

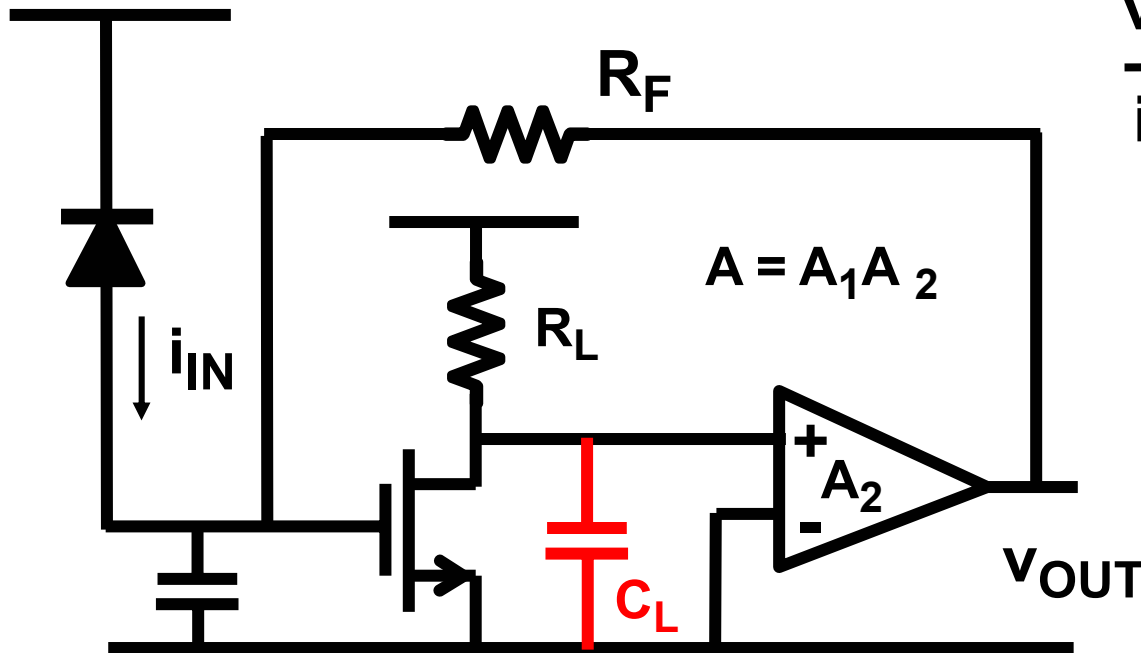

$$\frac{V_{IN}}{i_{IN}} = \frac{R_F}{A_1 A_2} \frac{1 + R_L C_L s}{1 + as + bs^2}$$

$$a = \frac{R_F C_P}{A_1 A_2}$$


$$b = \frac{R_F C_P R_L C_L}{A_1 A_2}$$

$$C_P = C_D + C_{GS} \quad A_1 = g_m R_L$$


No peaking if $R_L < \sqrt{\frac{R_F}{4g_m A_2} \frac{C_P}{C_L}}$

$$\frac{V_{OUT}}{i_{IN}} = R_F \frac{1}{1 + as + bs^2}$$

BW in voltage/current amplifier

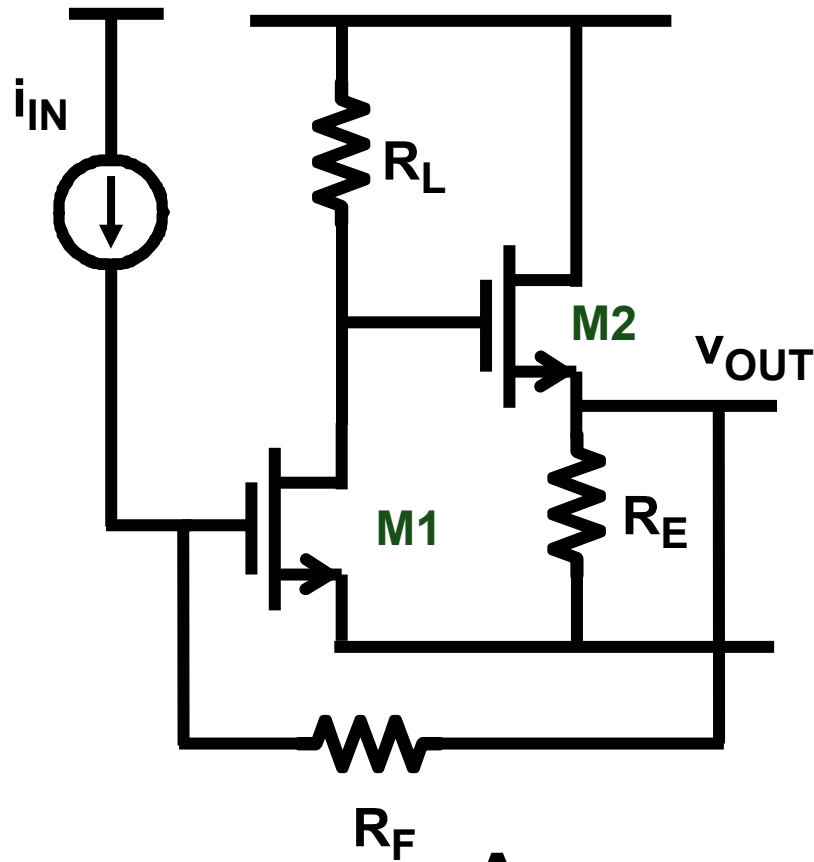

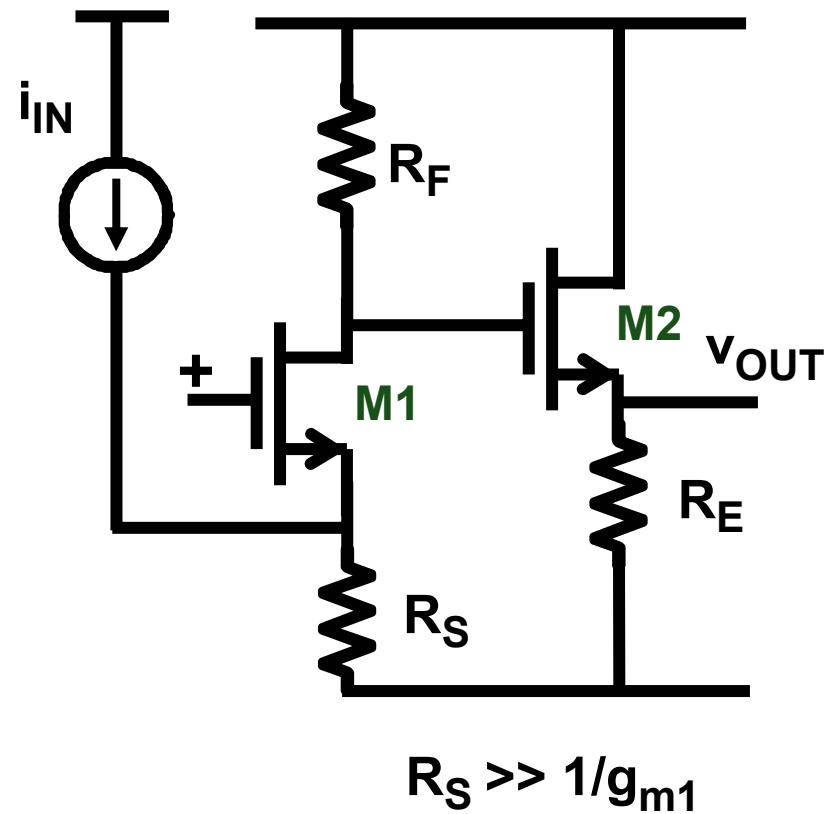
$$BW = \frac{A_{v1}}{2\pi R_F (C_{GS1} + C_D)}$$



$$BW = \frac{1}{2\pi R_F (C_{GD2} + C_{DB1})}$$

Current detector with input cascode

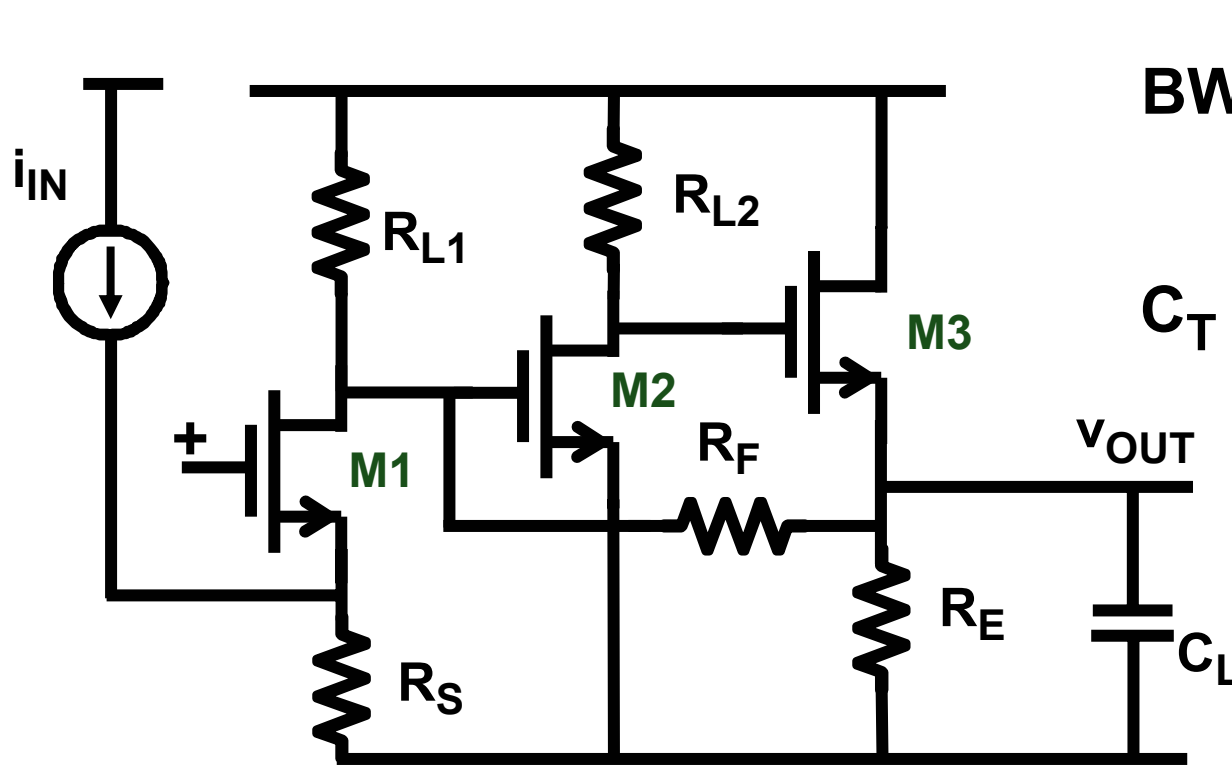

$$BW = \frac{A_{v2}}{2\pi R_F // R_{L1} C_T}$$

$$C_T = C_{GS2} + A_{v2} C_{GD2}$$

$$A_{v2} = g_{m2} R_{L2}$$


$$V_{OUT} = R_F i_{IN}$$

$$R_{OUT} = \frac{1/g_{m3}}{A_{v2}}$$

Z_{IN} independent of f ! $R_S \gg 1/g_{m1}$

Vanisri, etal, JSSC June 95, pp. 677-685

Current detector with regulated cascode

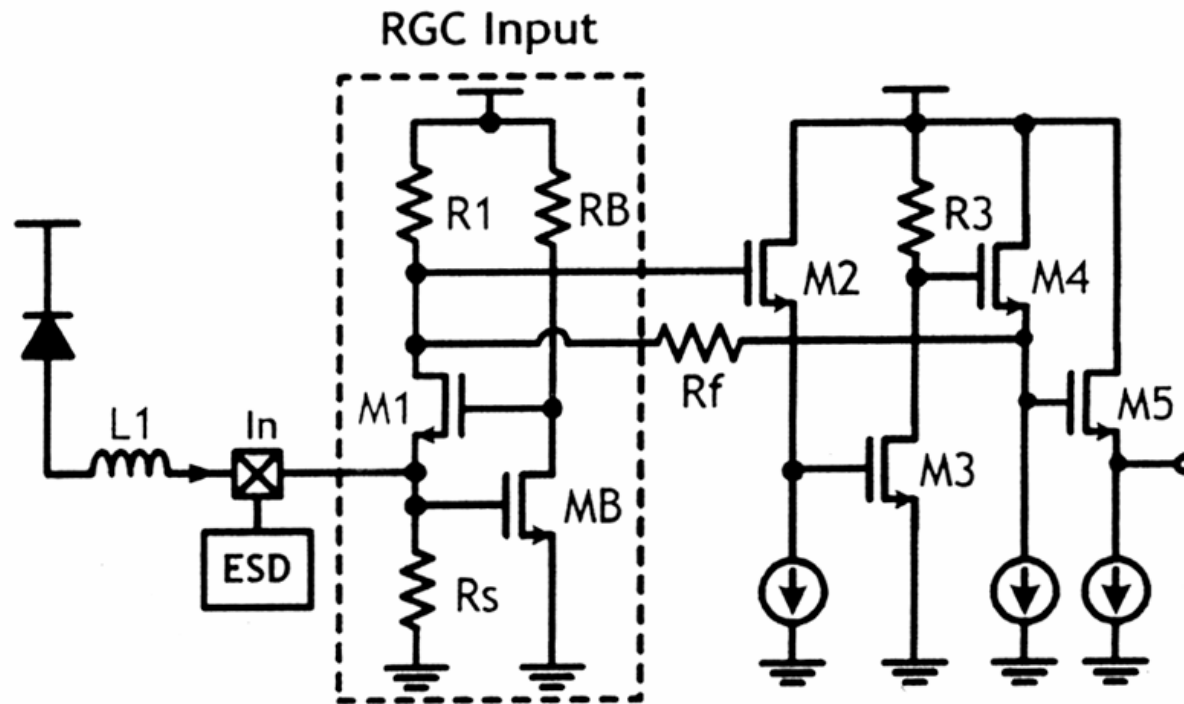

5 V 17 mA

$C_D = 0.5 \text{ pF}$

$R_F = 800 \Omega$


$BW = 1 \text{ GHz}$

$g_{mB} = 3 g_{m1}$

BW independent of C_D ! Current noise : R_S & $R_F // R_1$

Park, JSSC Jan. 04, 112-120

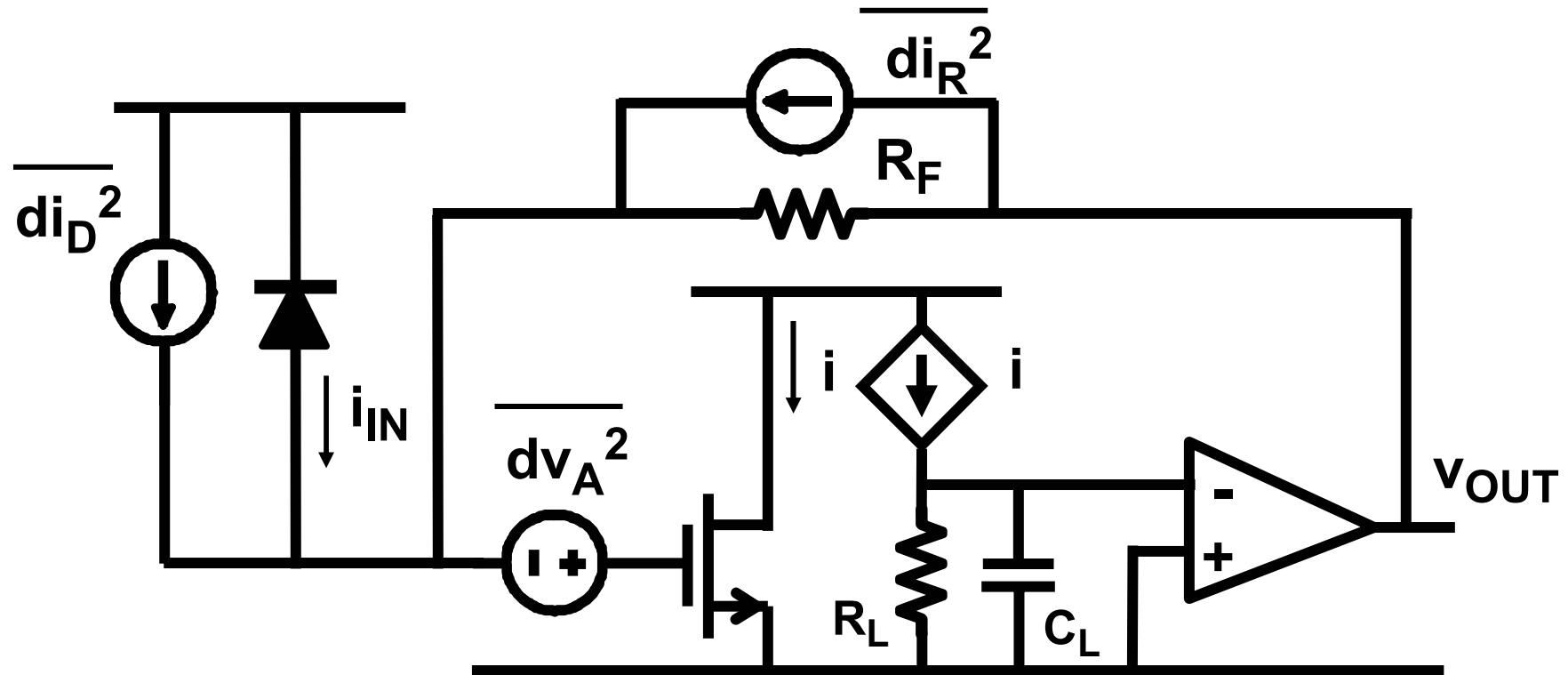Noise sources of detector voltage amplifier




$$\overline{di_D^2} = 2qI_D df$$

$$\overline{di_R^2} = \frac{4kT}{R_F} df$$


$$\overline{dv_A^2} = 4kT \left(\frac{2/3}{g_m} \right) df$$

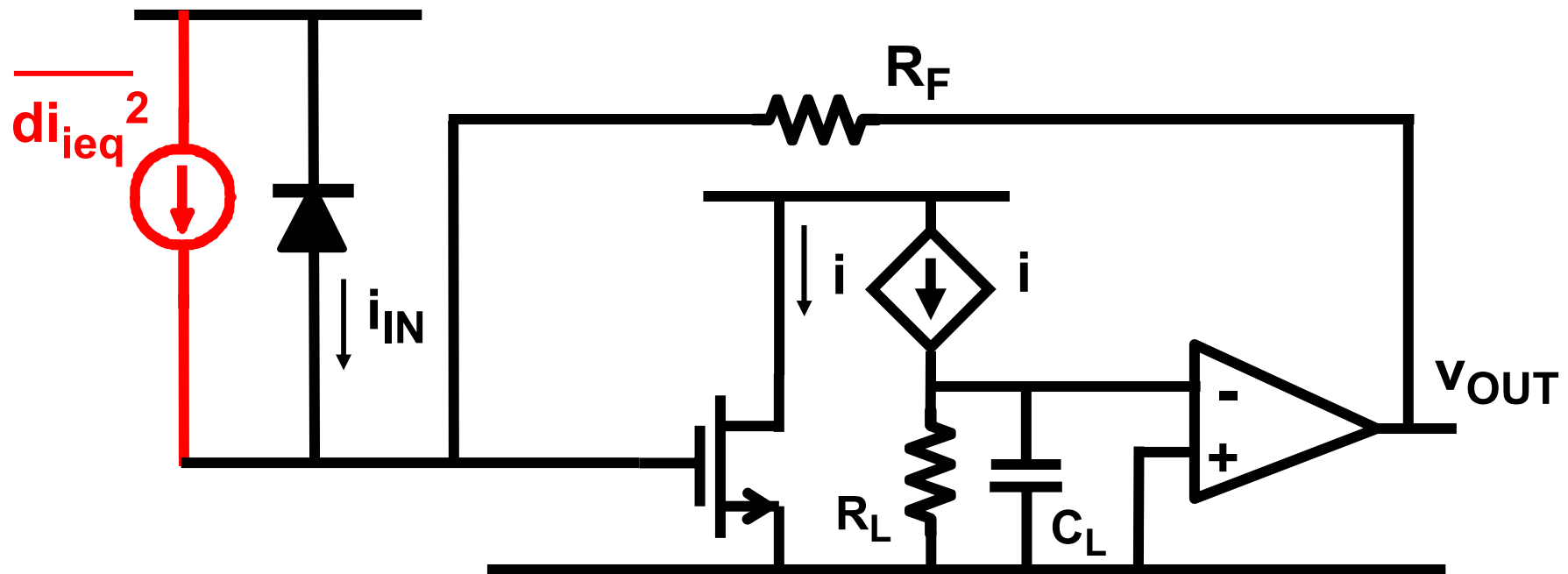Noise density of detector voltage amplifier



$$\overline{di_{ieq}^2} = \overline{di_D^2} + \overline{di_R^2} + \frac{\overline{dv_A^2}}{R_F^2} \approx \overline{di_D^2} + \overline{di_R^2} \quad \text{if } R_F > \frac{2/3}{g_m}$$

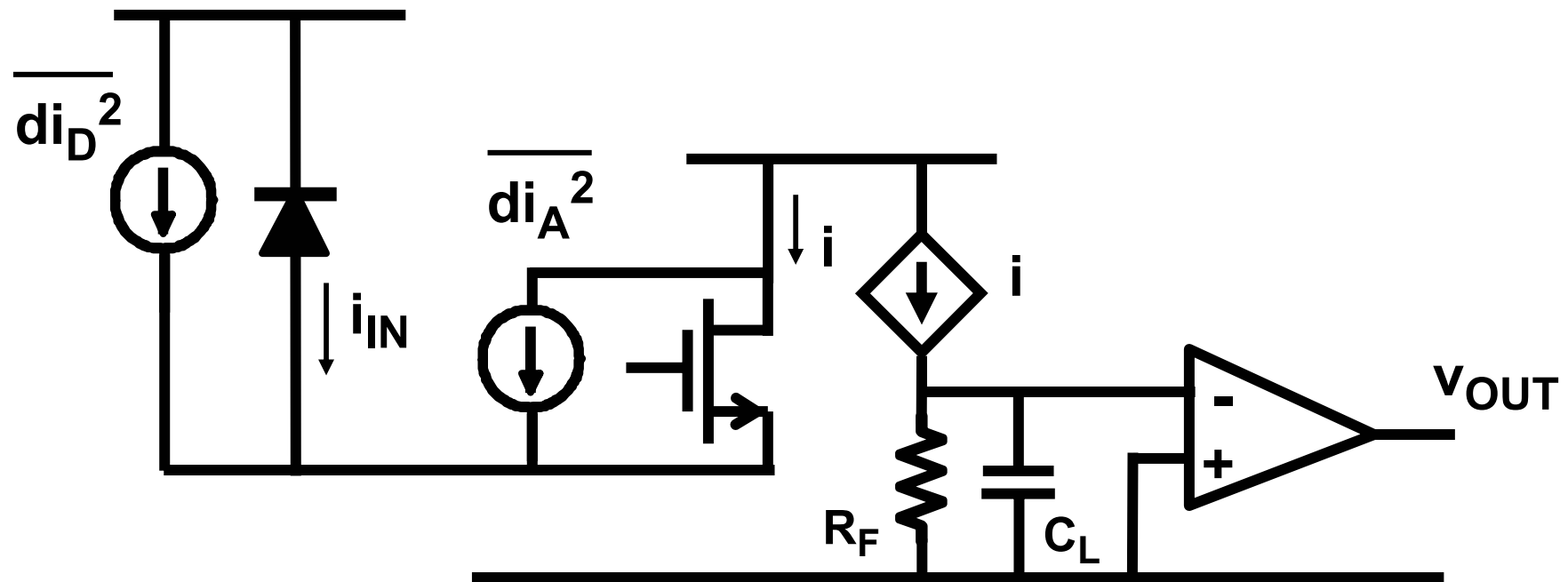
Noise sources of detector current amplifier



$$\overline{di_D^2} = 2q I_D df$$

$$\overline{di_A^2} = 4kT \frac{2}{3} g_m df$$

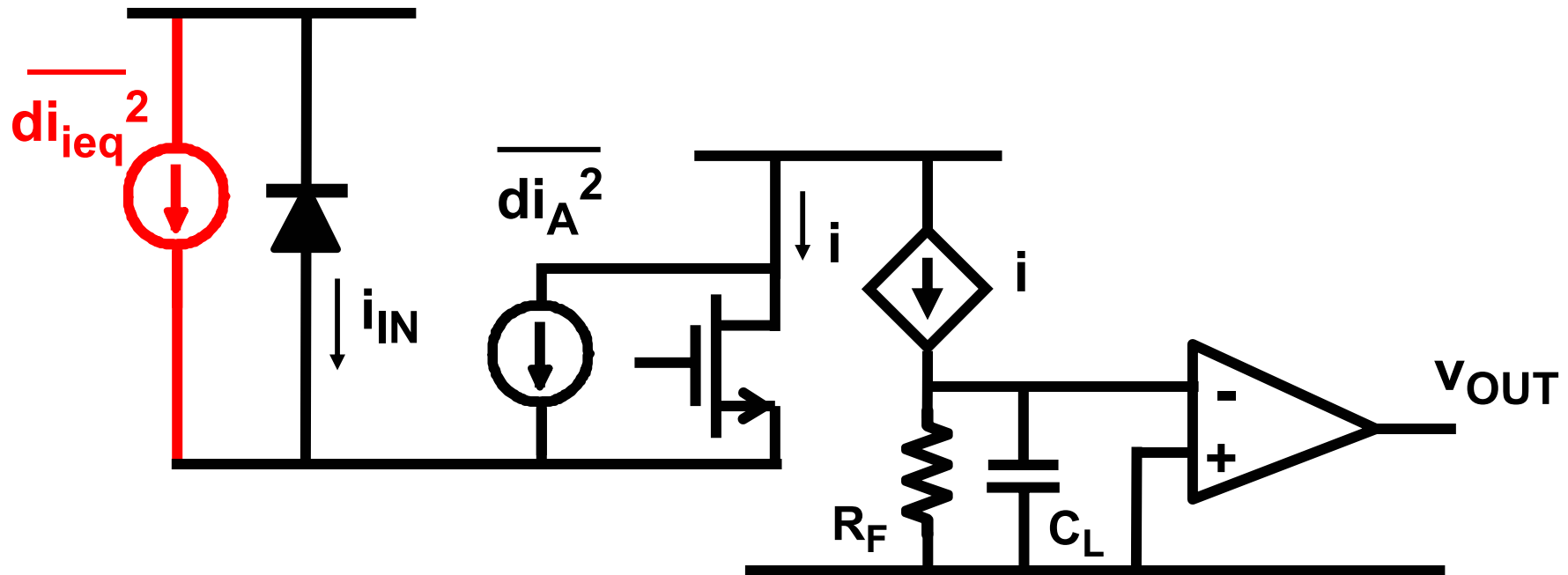Noise density of detector current amplifier



$$\overline{di_{ieq}^2} = \overline{di_D^2} + 4kT \frac{2}{3} g_m df \quad \text{is transistor noise !}$$

Comparison of noise densities

Voltage amp.: $\overline{i_{IN}^2} = \overline{di_R^2} = \frac{4kT}{R_F} df$

Current amp.: $\overline{i_{IN}^2} = \overline{di_A^2} = 4kT \frac{2}{3} g_m df$

 Voltage amplifier better when $R_F > \frac{3}{2} \frac{1}{g_m}$

Comparison of integrated noise

Large I_D : $\overline{i_{IN}^2} = \overline{di_D^2} \left(BW \frac{\pi}{2} \right)$


Small I_D :

Voltage amp.: $\overline{i_{IN}^2} = \overline{di_R^2} \left(BW \frac{\pi}{2} \right) = \frac{kT}{R_L} \left(\frac{R_L}{R_F} \right)^2 \frac{g_m}{C_P}$

Current amp.: $\overline{i_{IN}^2} = \overline{di_A^2} \left(BW \frac{\pi}{2} \right) = \frac{2}{3} \frac{kT}{R_F} \frac{g_m}{C_L}$

 Voltage amplifier better when $R_F > \frac{3}{4} R_L$

CMOS photodiode amplifier

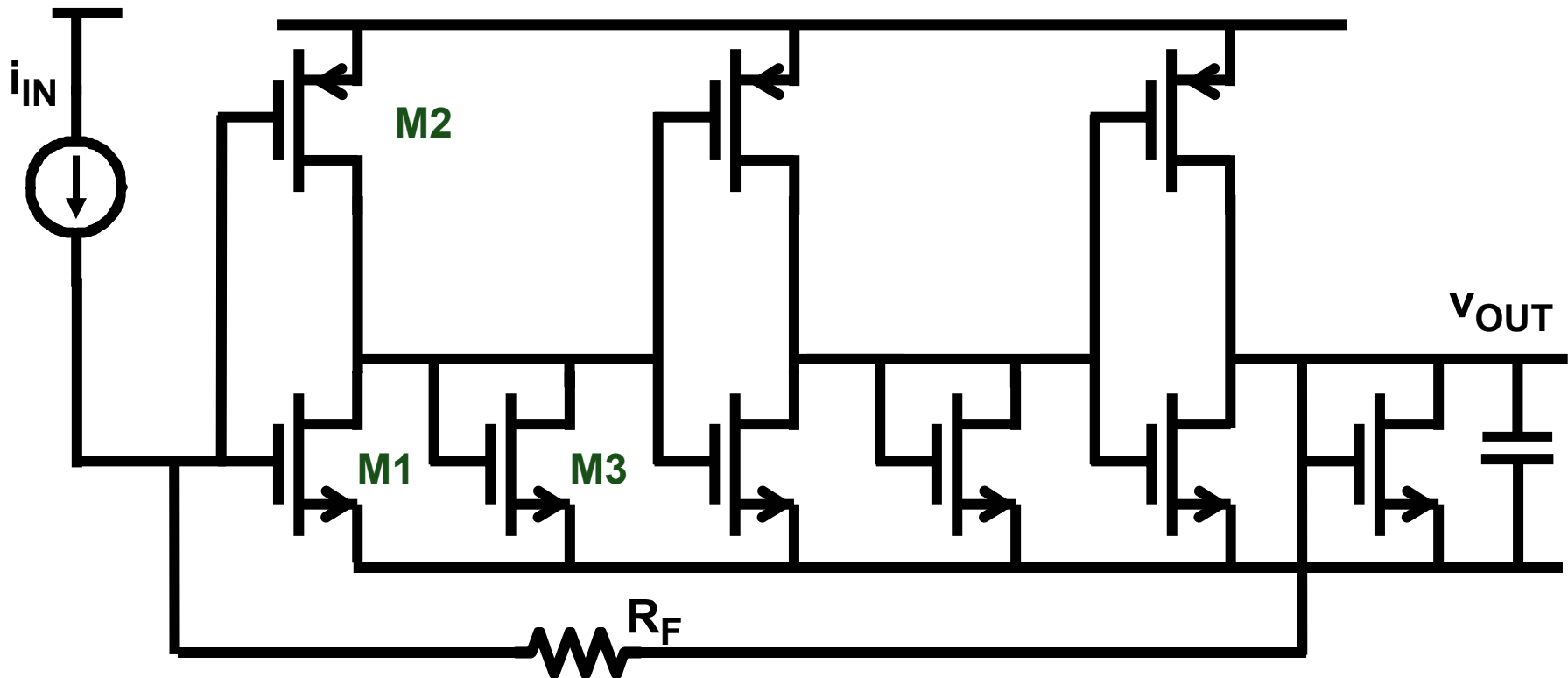


$150 \text{ k}\Omega \times 120 \text{ MHz} = 18 \text{ THz}\Omega$
450 MHz per cell

0.5 pA/ $\sqrt{\text{Hz}}$

Ref. Ingels, JSSC Dec 1994, 1552-1559

CMOS wideband amplifier cell

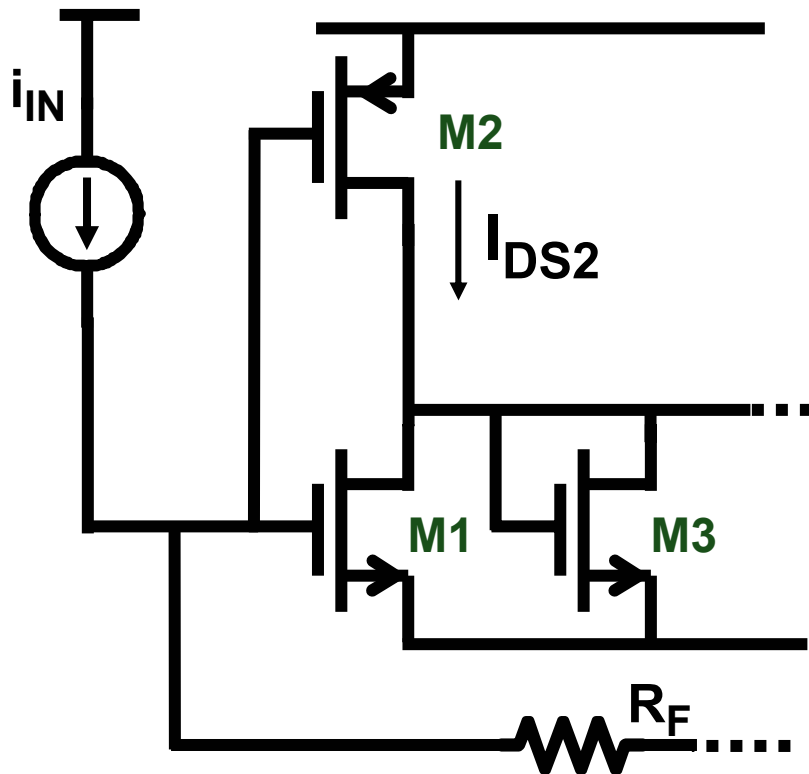

M_1 & M_3 : same V_{GS} & V_{DS}

$K'_n \approx 2K'_p$

All L are L_{min}

$$A_v = \frac{g_{m1} + g_{m2}}{g_{m3}}$$


$$g_m = 2 \sqrt{K'_n I_{DS} W/L}$$

$$I_{DS1} = \lambda I_{DS2}$$

$$I_{DS3} = (1 - \lambda) I_{DS2}$$

$$V_{GS1} = V_{GS3} : W_3 = W_1 \frac{1 - \lambda}{\lambda}$$

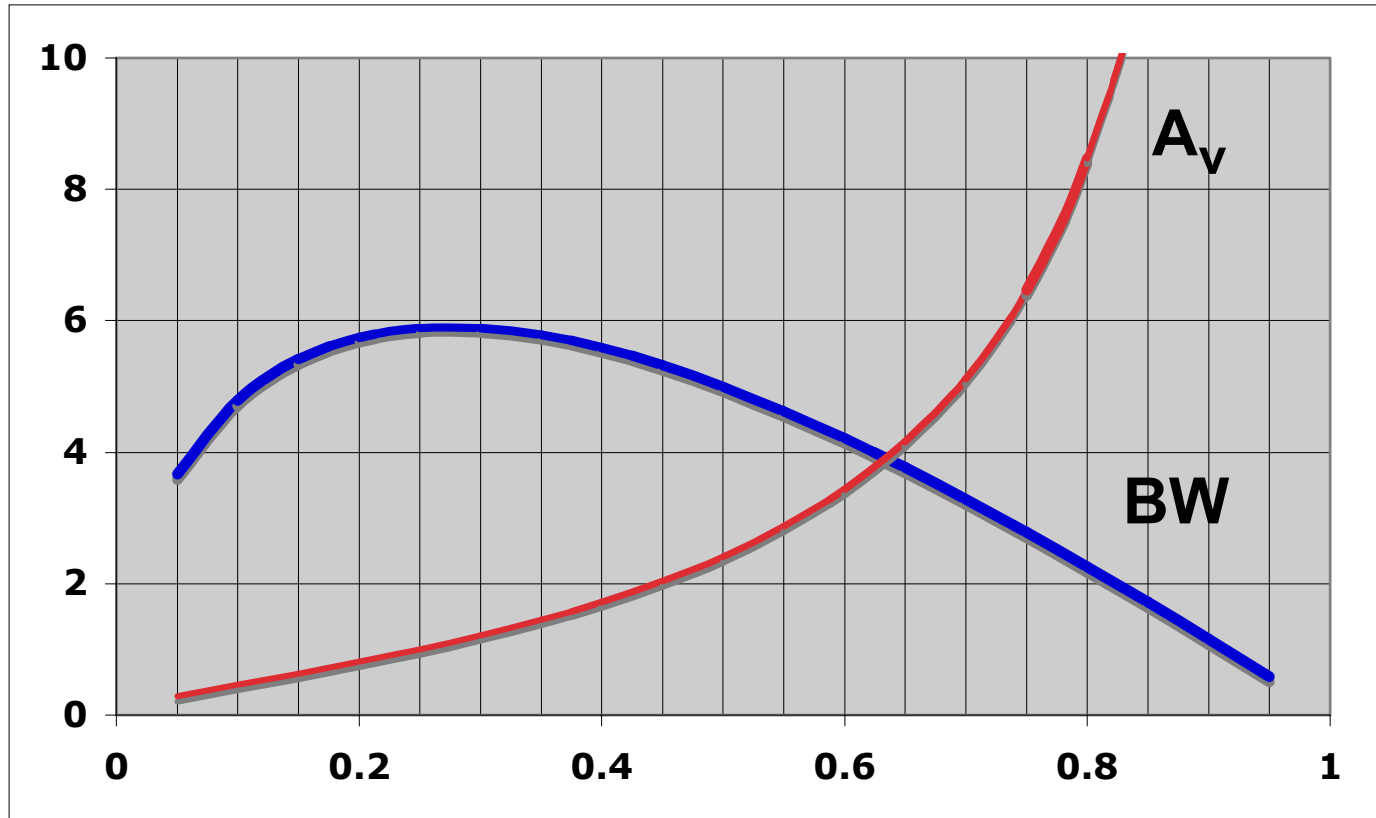CMOS wideband amplifier : gain and bandwidth



$$\frac{\lambda}{1 - \lambda} \left(1 + \sqrt{\frac{W_2}{2\lambda W_1}} \right)$$

$$BW = \frac{g_{m3}}{2\pi C_n}$$

$$\sim \frac{(1 - \lambda) \sqrt{\lambda W_1}}{W_1(2 - \lambda) + \lambda W_2}$$


$$W_1 = 2$$

$$W_2 = 4$$

$$C_n = C_{DB1} + C_{GS3} + C_{DB3} + C_{DB2}$$

$$C_{DB} \approx C_{GS} \approx kW \quad k \approx 2 \text{ fF}/\mu\text{m}$$

Integrated resistor

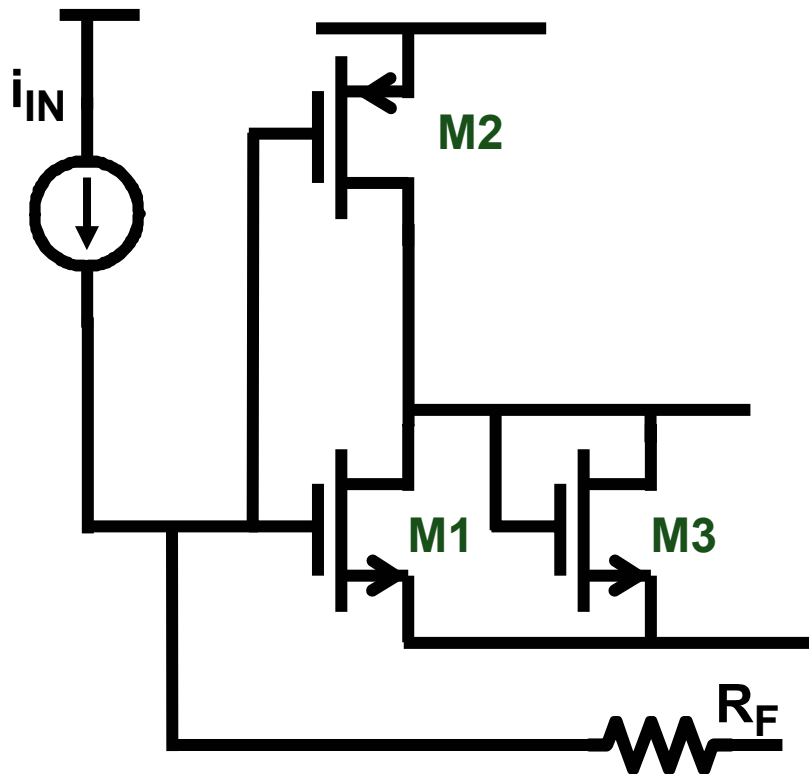

R_F ? Poly R : large size : large L
distributed C :
45° phase shift at 100 MHz

$$f_{-3dB} = \frac{1}{2\pi} \frac{2.43}{R_S C_0 L^2}$$


R_S = sheet res. (Ω / □□)

C₀ = unit cap. (F/cm²)


MOST : W = 1.3 μm & L = 1 μm
allows dynamic compression

Glaser; IC Engineering
Add.Wesley, p.132

Gain compression

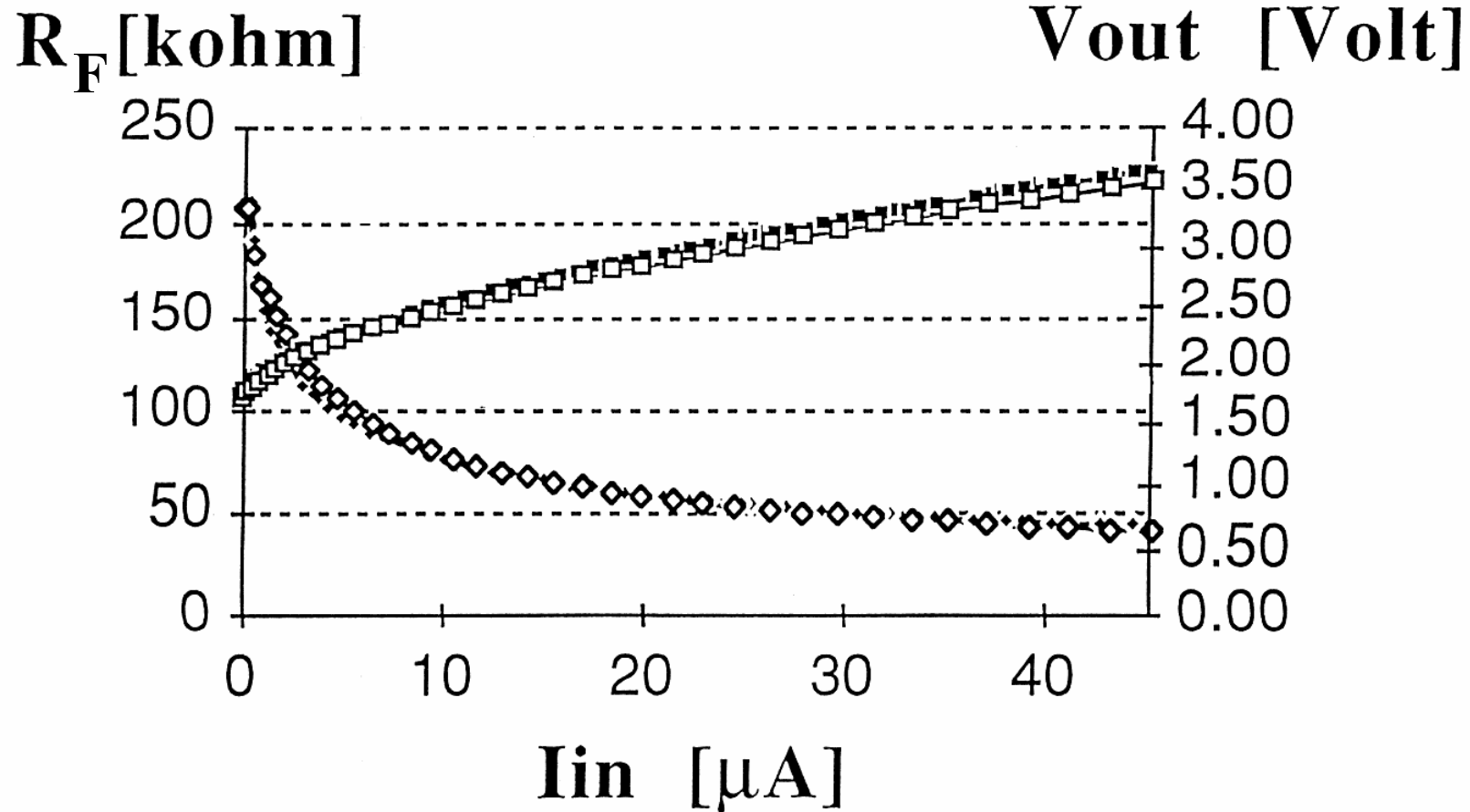

1 Gb/s 1 k Ω transimpedance stage

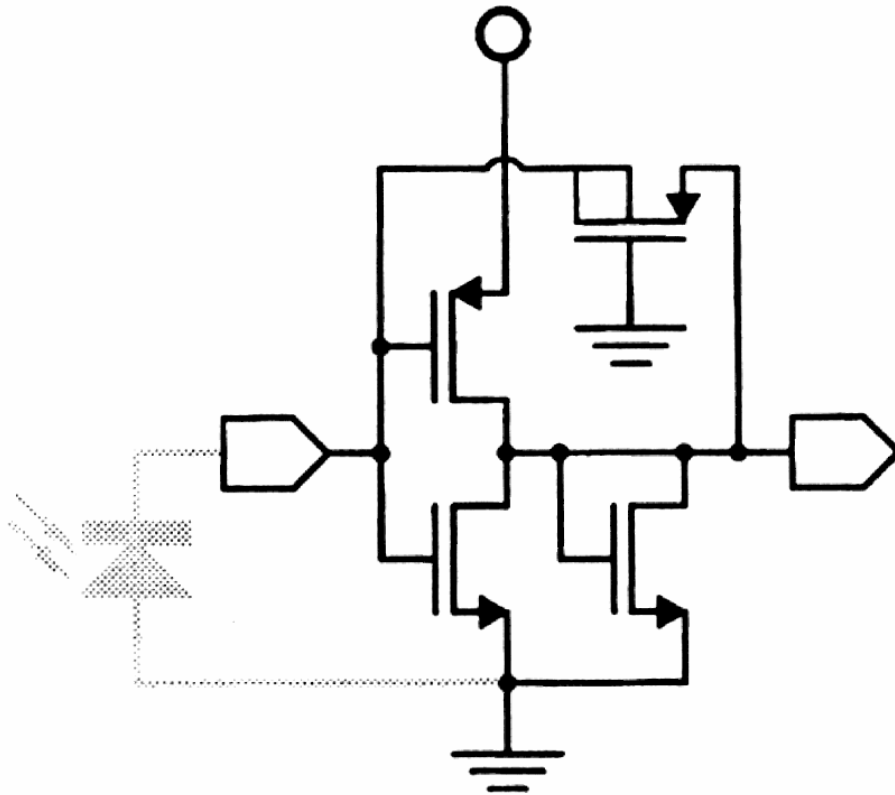

pMost vs nMOST :

**nMOST R increases for
larger diode currents !
pMOST gives compression !**

$$C_d = 0.8 \text{ pF} \approx C_{GS}$$

Capacitive noise matching !


BW = 500 MHz

5 mA (5V)

0.7 μm CMOS

Ref. Ingels, JSSC July 1999, 971-977

High-frequency Resistance R_F

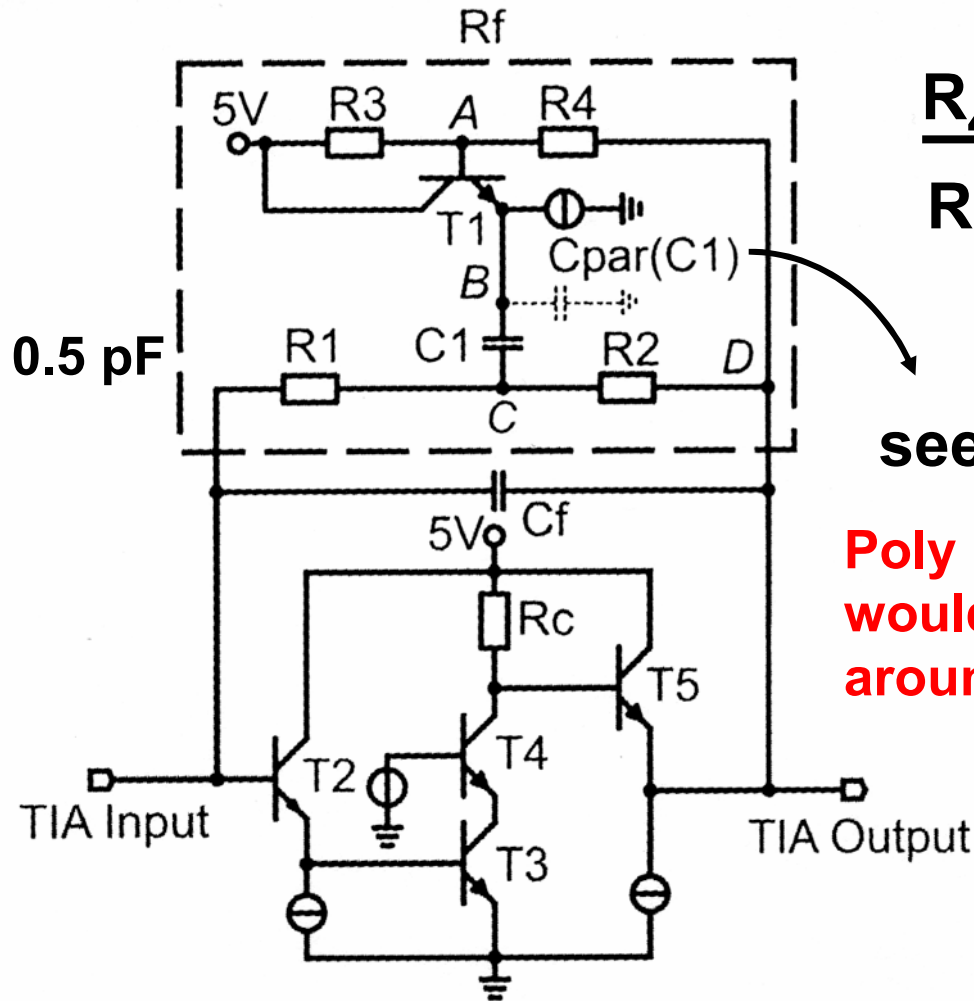

$$\frac{R_4}{R_3} = \frac{R_2}{R_1} = 2$$

$$R_1 + R_2 = 200 \text{ k}\Omega$$

$$R_3 + R_4 = 4 \text{ k}\Omega$$

sees $1/g_{m1}$

$$C_d = 0.1 \text{ pF}$$

**Poly $R_F = 200 \text{ k}\Omega$
would cut off
around 67 MHz !**

$$180 \text{ k}\Omega \quad 380 \text{ MHz}$$


$$68 \text{ THz}\Omega$$

$$14 \text{ mA (5 V)}$$

$$0.6 \mu\text{m BiCMOS}$$

Seidl, ISSCC 04, 470-471

BICMOS transimpedance amplifier

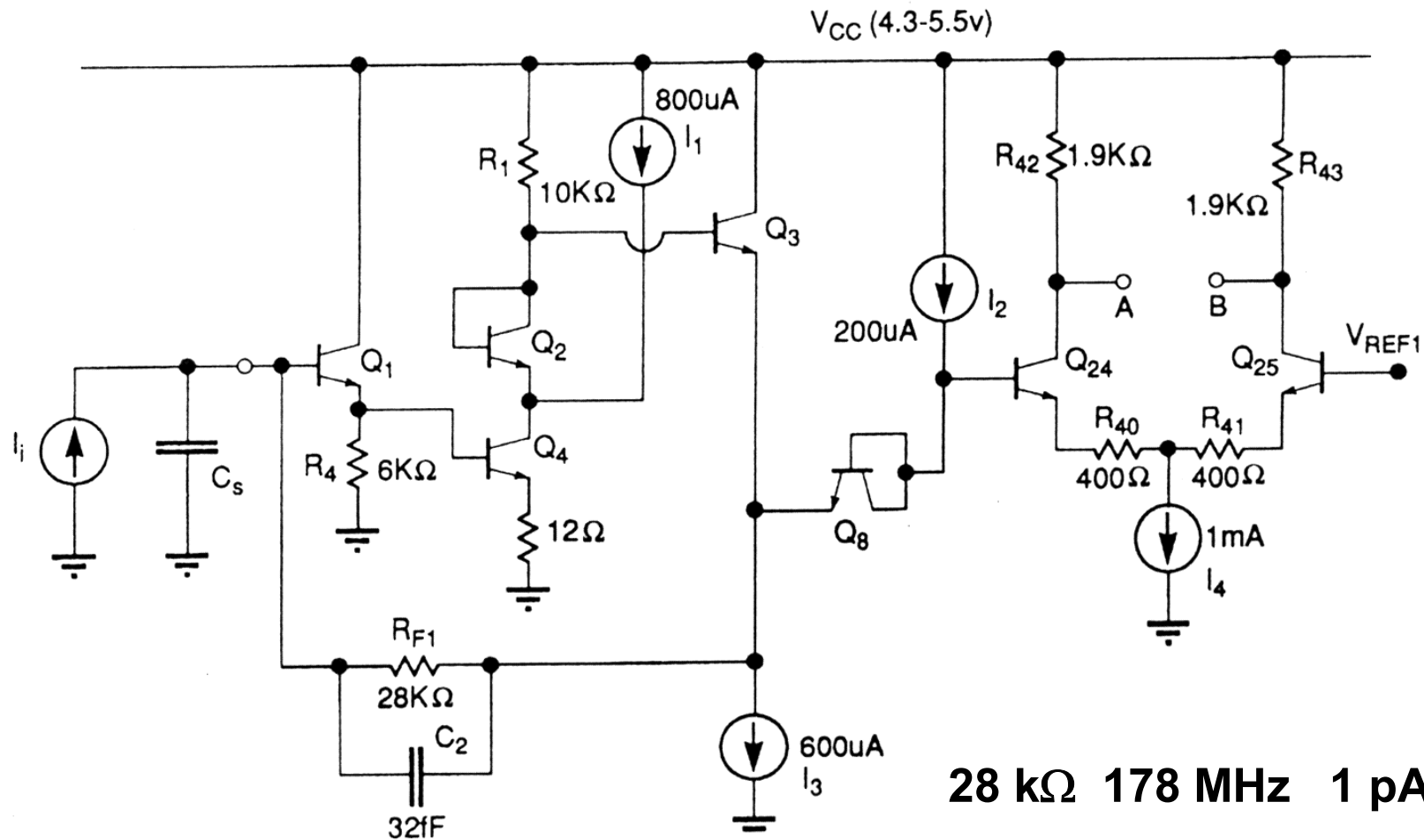


178 MHz

28 kΩ 178 MHz 1 pA/√Hz

Ref.Meyer, JSSC June 1994, 701-706

BICMOS transimpedance amplifier

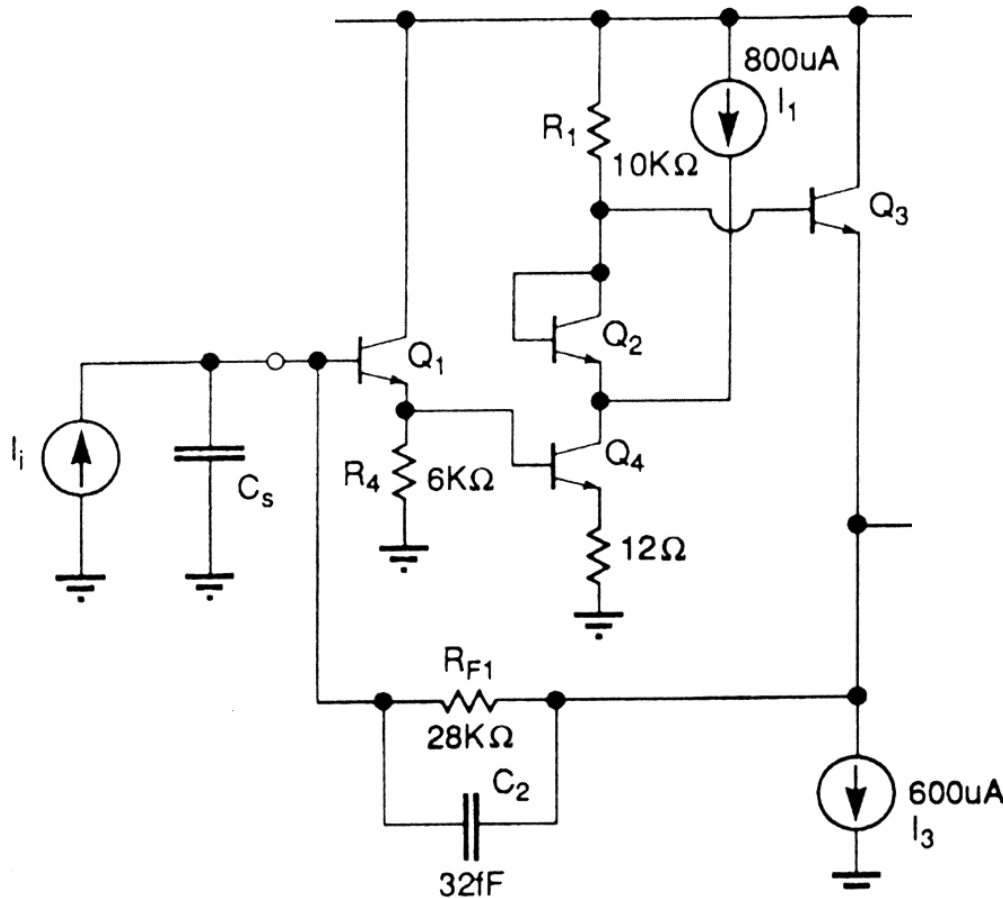

178 MHz

$$A_v = \frac{R_1 // \dots}{12 + 1/g_{m4}} = \frac{5 \text{ k}\Omega}{12 + 28} = 125$$

$$R_i = \frac{R_{F1}}{1 + A_v} = 240 \Omega$$

$$C_i = (1 + A_v) C_2 = 4 \text{ pF}$$


$$\overline{di_i^2} = 2qI_{B1}df + \frac{4kT}{R_{F1}} df$$

$$= (0.4 + 0.6)10^{-24} \approx 10^{-24} \text{ A}^2/\text{Hz}$$

28 kΩ 178 MHz 1 pA_{RMS}/√Hz

Ref.Meyer, JSSC June 1994, 701-706


Low-voltage transimpedance amplifier

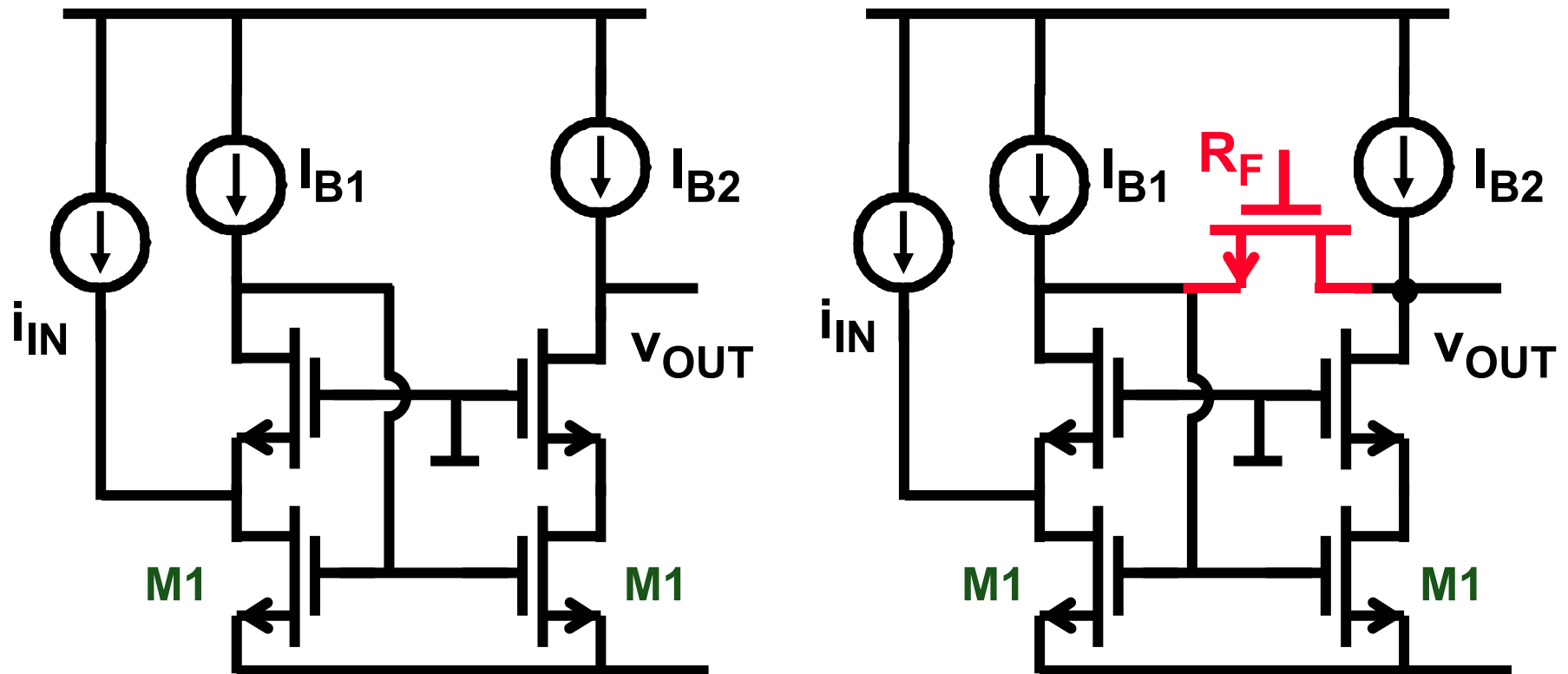

$$\text{If } R_F > 1/g_{m1} : v_{OUT} = - R_F i_{IN}$$

Ref. Phang, Johns, ISSCC 2001, 218-219

75 Mb/s optical receiver in CMOS

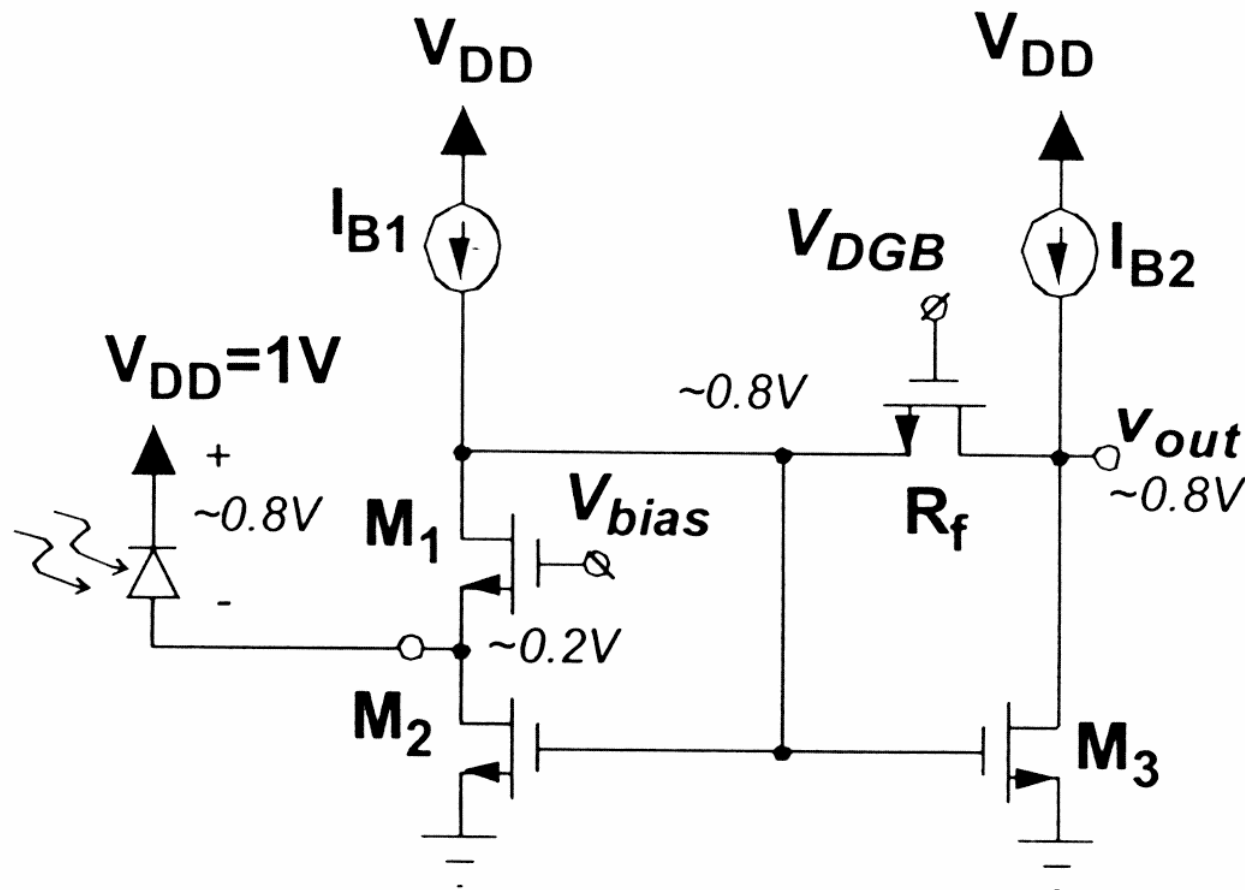

$C_d = 1 pF$

(40 μA)

2.4 $k\Omega$

45 MHz

75 Mb/s


11 pA_{RMS}/\sqrt{Hz}

0.35 μm CMOS

1 V (1 mA)

Ref. Phang, ISSCC 2001 218-219

GaAs 10 Gb/s receiver

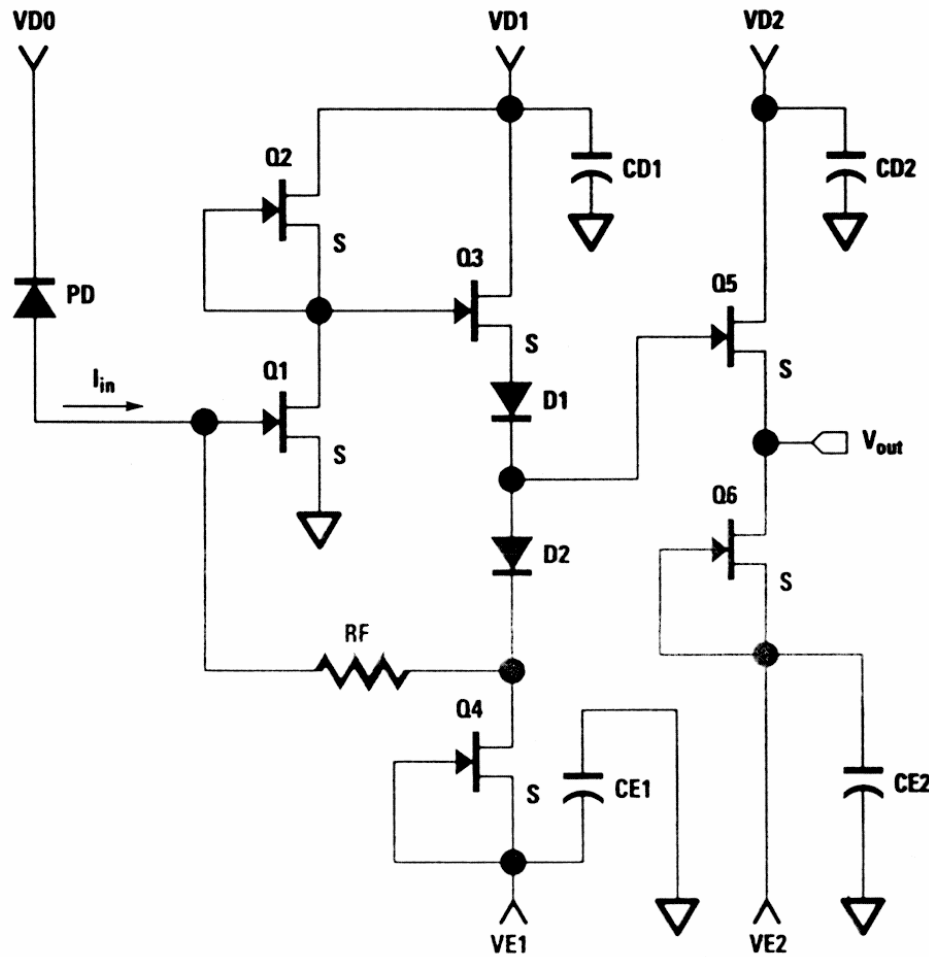

**HP - GaAs MODIC :
depletion nMOST's**

560 V/W

**flip-chip PD :
-3 dB at 7.2 GHz
10 pA/ $\sqrt{\text{Hz}}$**

**wire bond :
-3 dB at 4.2 GHz
20 pA/ $\sqrt{\text{Hz}}$**

Table of contents

- **Introduction**
- **Shunt-shunt FB for Transimpedance amps.**
- **Shunt-series FB for Current amplifiers**
- **Transimpedance amplifiers for
low noise and high frequencies**