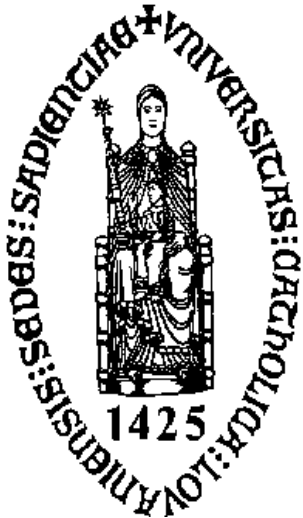

Offset and CMRR : Random and systematic



Willy Sansen

KULeuven, ESAT-MICAS

Leuven, Belgium

willy.sansen@esat.kuleuven.be


 


Table of contents

- **Random offset and $CMRR_r$**
- **Systematic offset and $CMRR_s$**
- **CMRR versus frequency**
- **Design rules**
- **Comparison MOST and bipolar transistors**


Ref: Pelgrom, JSSC Oct.1989, 1433-1439
Croon, JSSC Aug.02, 1056-1064
Croon, Springer, 2005

Definition of offset

 



Offset voltage v_{os}

Gain error with offset

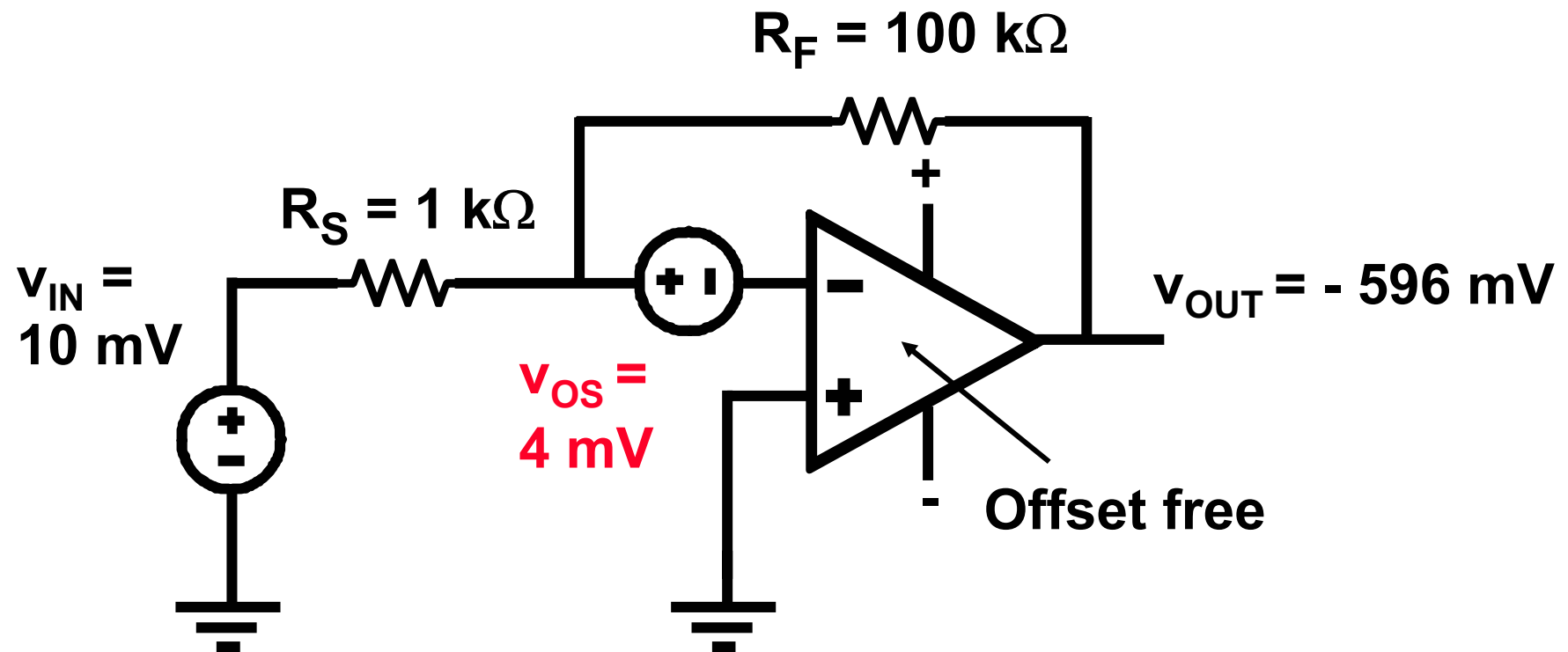


The gain is 59 instead of 100 !

Yield of n-bit flash-ADC with offset

  

Ref: Pelgrom, IEDM 1998, pp.789.

Random offset : mismatches

 

$$I_{DS} = K' \frac{W}{L} (V_{GS} - V_T)^2$$

$$\sigma_{\Delta V_T} = \frac{A_{VT}}{\sqrt{WL}}$$

$$A_{VT} \sim t_{ox} \sqrt[4]{N_B}$$


Ref: Keyes, JSSC Aug. 1975, 245-247
Shyu, JSSC Dec 1984, 948-955
Lakshmikumar, JSSC Dec 1986, 1057-1066
Pelgrom, JSSC Oct.1989, 1433-1439
Croon, JSSC Aug. 2002, 1056-1064

$$A_{VT} \approx 5 \text{ mV}\mu\text{m}$$

for $0.25 \mu\text{m}$ nMOST

+50 % for pMOST

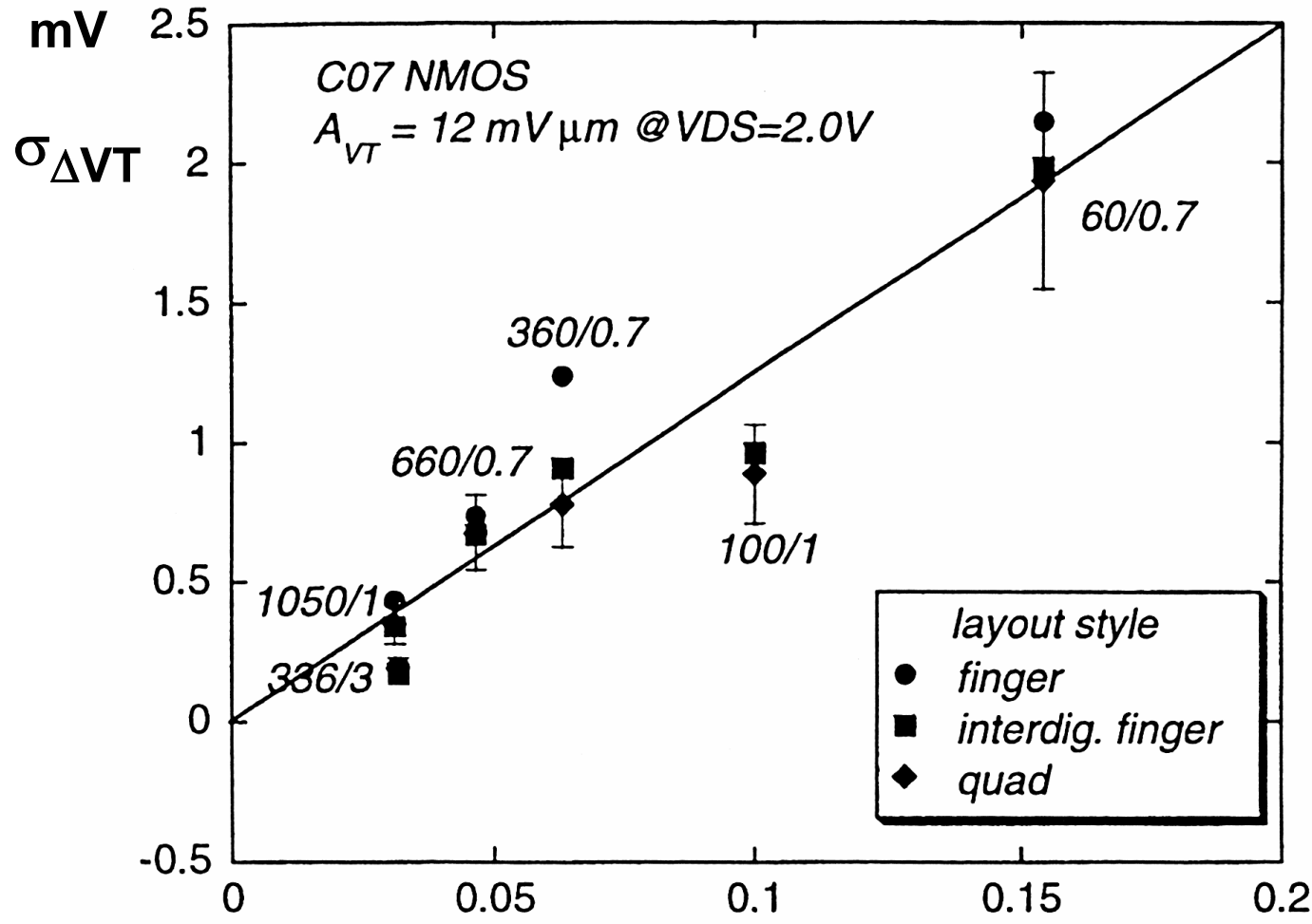Threshold voltage sigma $\sigma_{\Delta V_T}$




$$\sigma_{\Delta V_T} = \frac{A_{VT}}{\sqrt{WL}}$$

$\sigma(\Delta V_T) \approx 2 \text{ mV}$
 $W/L = 60/0.7 \mu\text{m}$
 in $0.7 \mu\text{m}$ CMOS

$$1/\sqrt{WL}$$

1/ μm

Threshold voltage mismatch A_{VT}

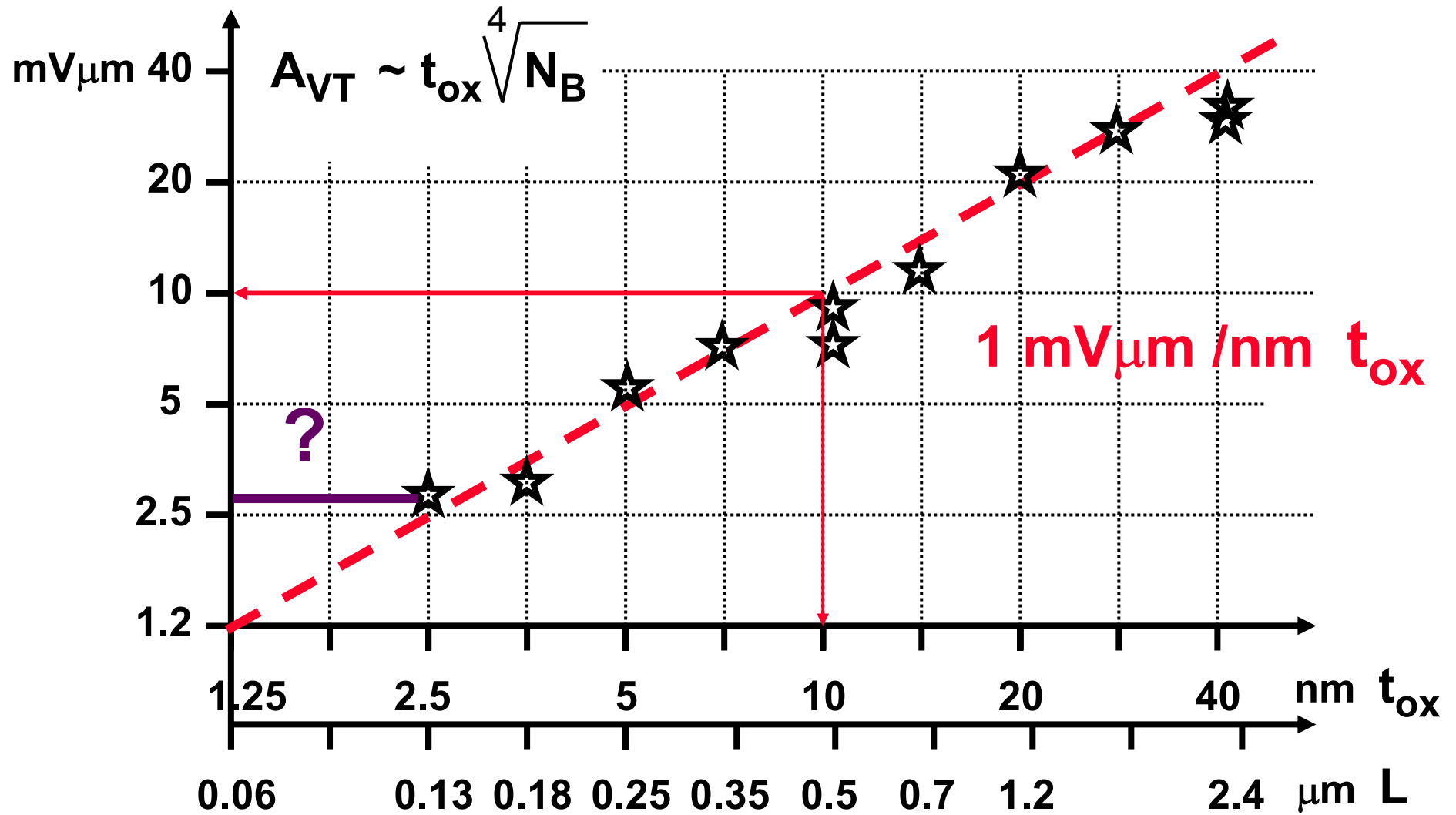

Random offset : mismatches

$$\frac{\Delta K'}{K'} = \frac{A_{K'}}{\sqrt{WL}}$$

$A_{K'} \approx 0.0056 \mu\text{m} \quad +50 \% \text{ for pMOST}$

$$\frac{\Delta W/L}{W/L} = A_{WL} \sqrt{\frac{1}{W^2} + \frac{1}{L^2}}$$

$A_{WL} \approx 0.02 \mu\text{m} \quad +50 \% \text{ for pMOST}$

$$\frac{\Delta \gamma}{\gamma} = \frac{A_{\gamma}}{\sqrt{WL}}$$

$A_{\gamma} \approx 0.016 \mu\text{m} \quad -25 \% \text{ for pMOST}$


Negligible if $B = S$

Ref.: Pelgrom : JSSC Oct.1989, pp.1430-1440

Mismatch coefficients for nMOST

Techno L (μm) t_{ox} (nm)	2.5 50	1.2 25	0.7 15	0.5 11	0.35 8	0.25 6
A_{V_T} (mV μm)	30	21	13	7.1	6	\Rightarrow 0
A_{W_L} (% μm)	2.5	1.8	2.5	1.3	2	\Rightarrow 1.8
S_{V_T} (mV/mm)	0.3	0.3	0.4	0.2		
S_{W_L} (%/mm)	0.3		0.2	0.2		

Random offset in differential pair

 

$$v_{od} = \Delta R_L \frac{I_B}{2}$$


$$v_{os} = \frac{v_{od}}{g_m R_L}$$

$$v_{os} = \frac{\Delta R_L}{R_L} \frac{I_B}{2g_m}$$

$$v_{os} = \frac{\Delta R_L}{R_L} \frac{V_{GS} - V_T}{2}$$

Ref.: Laker, Sansen : Design of analog ..., MacGrawHill 1994

Random offset in differential pair

 


$$v_{OS} = \Delta V_T + \frac{V_{GS} - V_T}{2} \left(\frac{\Delta R_L}{R_L} + \frac{\Delta K'}{K'} + \frac{\Delta W/L}{W/L} \right)$$

⇒ small $V_{GS} - V_T$

Ref.: Laker, Sansen : Design of analog ..., MacGrawHill 1994

Random offset in current mirror

 


$$\frac{\Delta I_{out}}{I_{out}} = \frac{\Delta V_T}{(V_{GS} - V_T)/2} + \frac{\Delta K'}{K'} + \frac{\Delta W/L}{W/L}$$

⇒ large $V_{GS} - V_T$

Ref.: Laker, Sansen : Design of analog ..., MacGrawHill 1994

More offset in current mirror

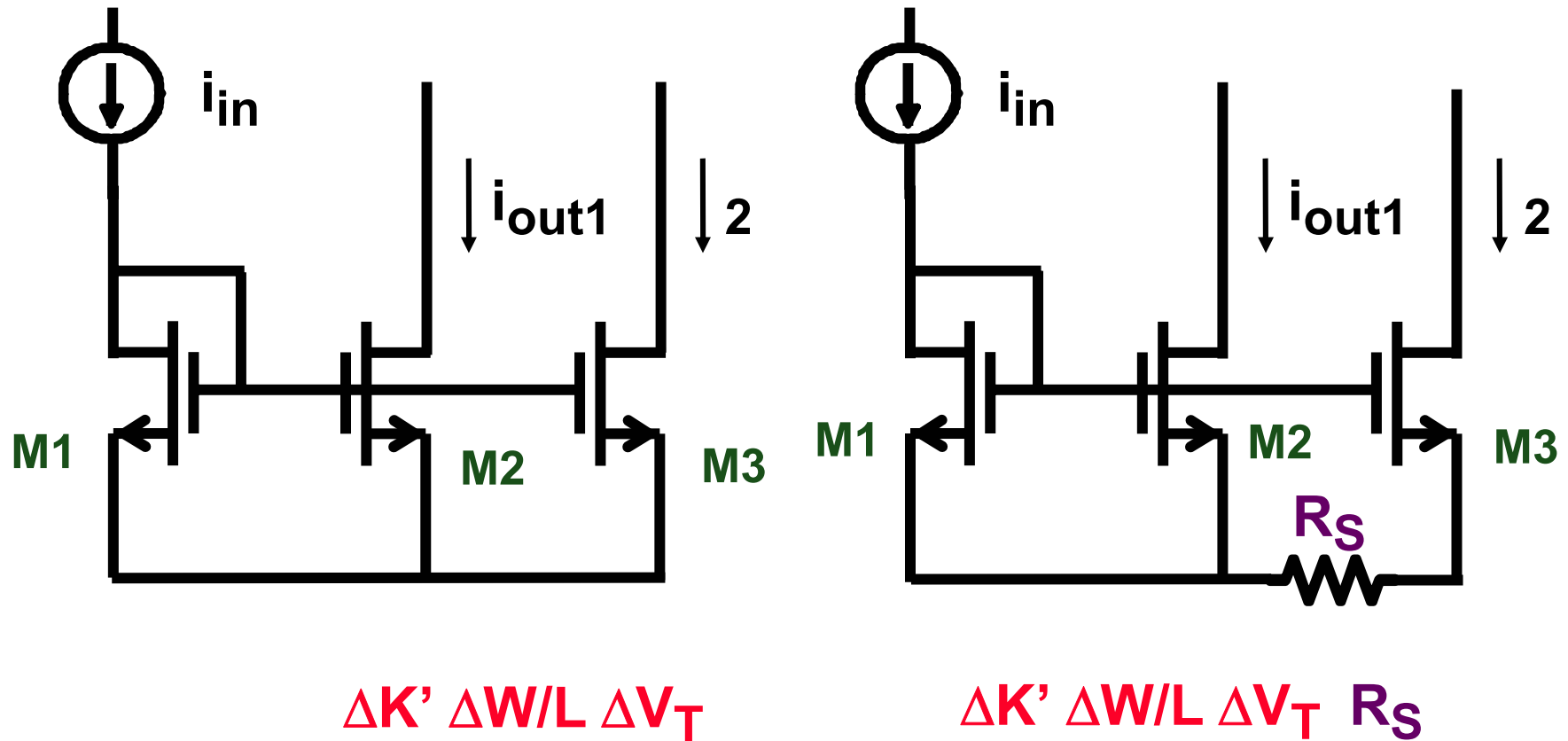

Mismatch in drain current

$$I_{DS} = \frac{\beta}{2} (V_{GS} - V_T)^2 \qquad \beta = \frac{K'}{n} \frac{W}{L}$$



$$\frac{\Delta I_{DS}}{I_{DS}} = \frac{\Delta\beta}{\beta} - \Delta V_T \frac{2}{V_{GS} - V_T}$$

$$\sigma^2 \left(\frac{\Delta I_{DS}}{I_{DS}} \right) = \sigma^2 \left(\frac{\Delta\beta}{\beta} \right) + \sigma^2 (\Delta V_T) \underbrace{\frac{4}{(V_{GS} - V_T)^2}}_{\frac{1}{(nkT/q)^2}} \quad \text{in wi}$$


$$\left(\frac{g_m}{I_{DS}} \right)^2 \quad \text{in general}$$

Mismatch in drain current for w_i and s_i
  
$$\sigma^2 \left(\frac{\Delta I_{DS}}{I_{DS}} \right) = \sigma^2 \left(\frac{\Delta \beta}{\beta} \right) + \sigma^2 (\Delta V_T) \underbrace{\frac{4}{(V_{GS} - V_T)^2}}_{\text{in si}} \quad \text{or} \quad \underbrace{\frac{1}{(nkT/q)^2}}_{\text{in wi}}$$



Random CMRR in differential pair -1

 

$$v_{od} = A_{dd} v_{id} + A_{dc} v_{ic}$$


$$v_{oc} = A_{cd} v_{id} + A_{cc} v_{ic}$$

$$A_{dd} = \left. \frac{v_{od}}{v_{id}} \right|_{v_{ic} = 0} = g_m R_L$$

$$A_{dc} = \left. \frac{v_{od}}{v_{ic}} \right|_{v_{id} = 0} \approx 0$$

$$CMRR = \frac{A_{dd}}{A_{dc}} \approx \infty$$

Random CMRR in differential pair -2

 

$$A_{dc} = \left. \frac{v_{od}}{v_{ic}} \right|_{v_{id} = 0} \neq 0$$


$$v_{ic} = v_{inc} \Rightarrow i_c = \frac{v_{inc}}{R_B}$$

$$v_{od} = \Delta R_L i_c / 2$$

$$A_{dc} = \frac{\Delta R_L}{2 R_B}$$

$$\text{CMRR} = \frac{2 g_m R_B}{\Delta R_L / R_L}$$

Random CMRR in differential pair -3

 

CMRR =

$$\frac{2 g_m R_B}{\frac{2 \Delta V_T}{V_{GS} - V_T} + \frac{\Delta R_L}{R_L} + \frac{\Delta K'}{K'} + \frac{\Delta W/L}{W/L}}$$

Relation random offset and CMRR

$$v_{OSr} = \Delta V_T + \frac{V_{GS} - V_T}{2} \left(\frac{\Delta R_L}{R_L} + \frac{\Delta K'}{K'} + \frac{\Delta W/L}{W/L} \right)$$

$$CMRR_r = \frac{2 g_m R_B}{\frac{2 \Delta V_T}{V_{GS} - V_T} + \frac{\Delta R_L}{R_L} + \frac{\Delta K'}{K'} + \frac{\Delta W/L}{W/L}}$$

$$v_{OSr} CMRR_r = \frac{V_{GS} - V_T}{2} 2 g_m R_B = I_B R_B = V_E L_B = 5 \dots 15 V$$

$$v_{OSr} CMRR_r = 10 V$$

Relation random offset and CMRR

$$v_{OSr} \text{ CMRR}_r \approx V_{E}L_B \approx 10 \text{ V} \quad (\sim L_B)$$

10 mV 60 dB \approx 10 V as for MOSTs

1 mV 80 dB \approx 10 V as for Bipolar transistors



10 μ V 120 dB \approx 10 V with trimming : with laser
with Zener zap
with fusible links

Low offset = High CMRR

Table of contents

- Random offset and $CMRR_r$
- Systematic offset and $CMRR_s$
- $CMRR$ versus frequency
- Design rules
- Comparison MOST and bip.transistors


Systematic offset in current mirror

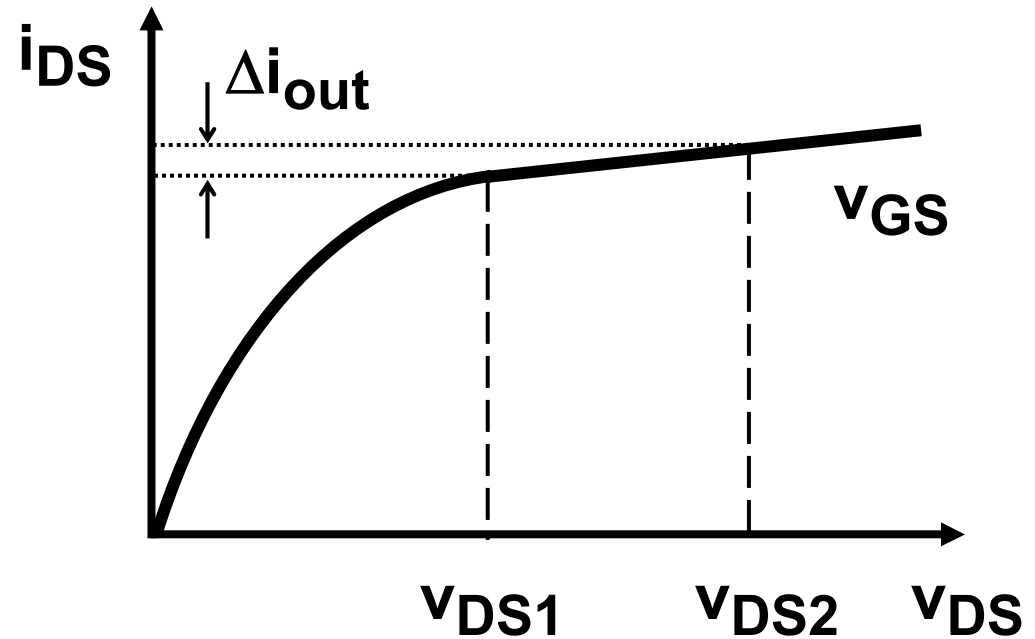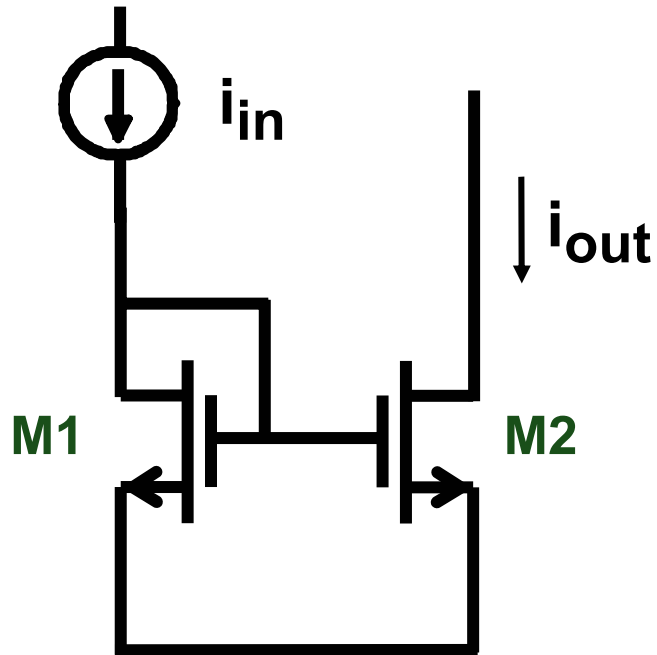


~~$\Delta K' \Delta W/L \Delta V_T$~~

$$\frac{\Delta i_{out}}{i_{out}} = \frac{v_{DS2} - v_{DS1}}{V_{E}L_2}$$

Systematic CMRR in differential Pair - 1

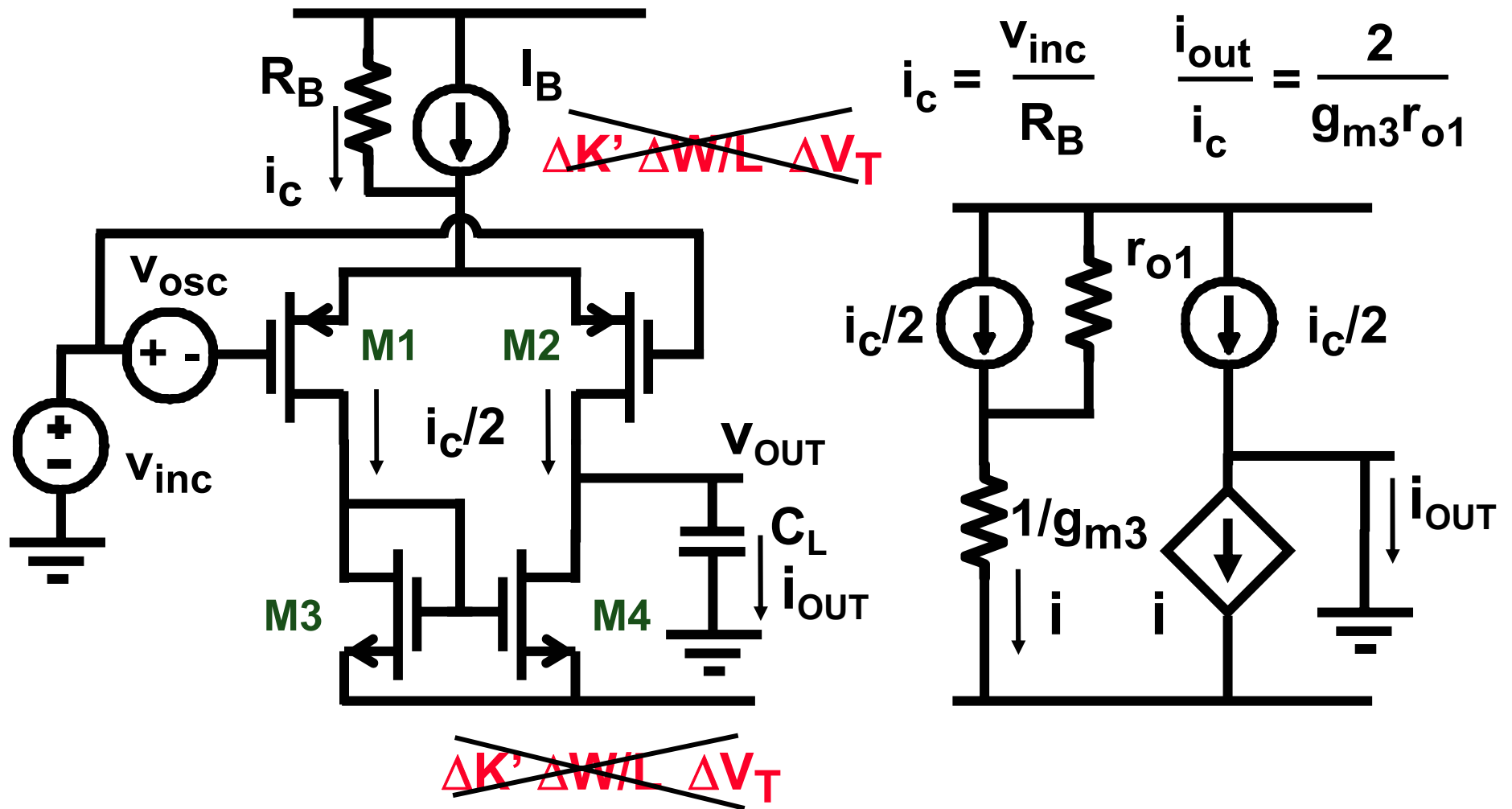

Systematic CMRR in differential Pair - 2

 

$$\frac{i_{out}}{v_{inc}} = \frac{1}{R_B} \frac{2}{g_{m3}r_{o1}}$$

$$\frac{i_{out}}{v_{osc}} = g_{m1}$$

$$\frac{i_{out}}{v_{inc}} = \frac{A_{dc}}{A_{dd}} = \frac{1}{CMRR_S}$$



v_{ind} (indicated by an arrow pointing to v_{osc})

Systematic CMRR in differential Pair - 3

$$\frac{\frac{i_{out}}{V_{inc}}}{\frac{i_{out}}{V_{osc}}} = \frac{V_{osc}}{V_{inc}} = \frac{A_{dc}}{A_{dd}} = \frac{1}{CMRR_s}$$



$$CMRR_s = \frac{1}{2} g_{m1} R_B g_{m3} r_{o1}$$

$$CMRR_s V_{osc} = V_{inc}$$

  


Total CMRR
  
$$\frac{1}{\text{CMRR}} = \frac{1}{\text{CMRR}_r} + \frac{1}{\text{CMRR}_s}$$



Offset Miller CMOS OTA

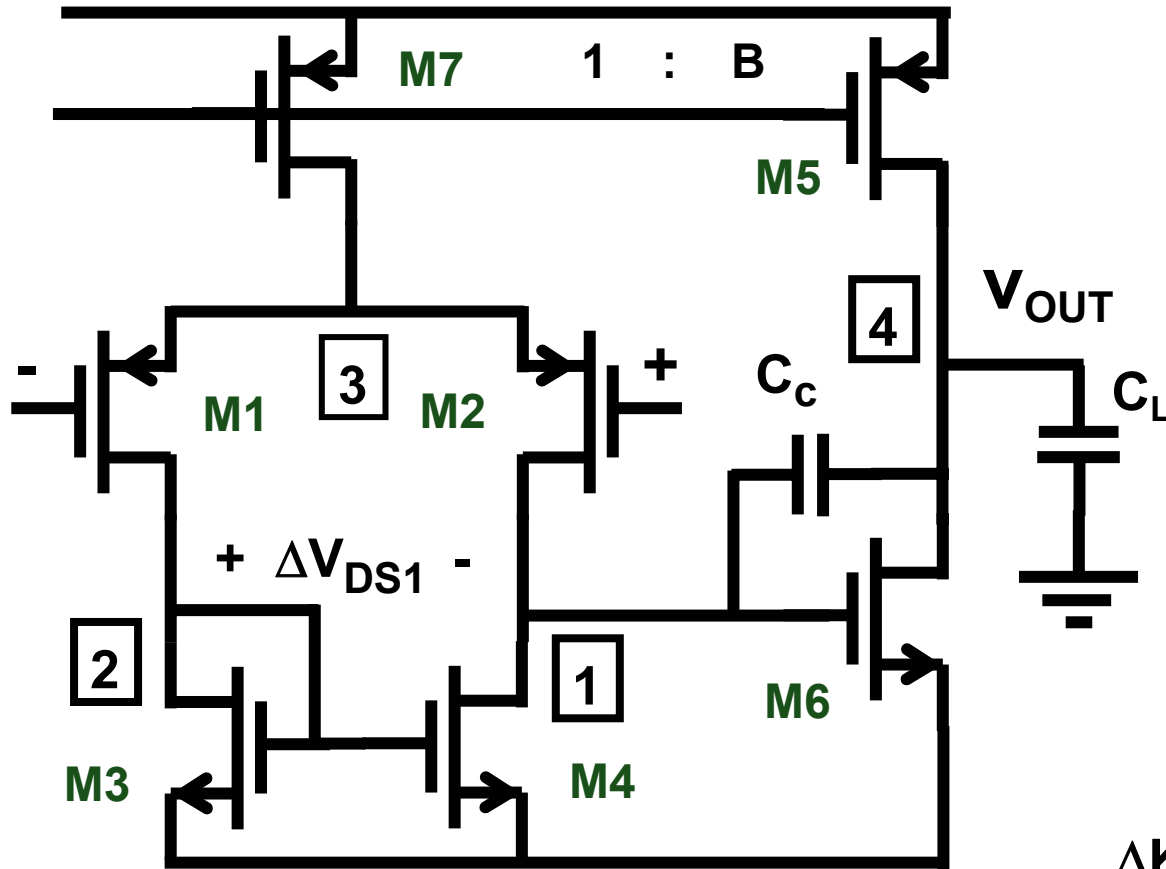

$$A_{v1} = g_{m1} r_{o2} // r_{o4}$$


$$v_{OS} = \frac{\Delta V_{DS1}}{A_{v1}} +$$

$$\Delta V_{T1} + \frac{g_{m3}}{g_{m1}} \Delta V_{T3}^* +$$

$$+ \frac{V_{GS1} - V_T}{2} S$$

$$S = \frac{\Delta K'_n}{K'_n} + \frac{\Delta K'_p}{K'_p} + \frac{\Delta W/L_1}{W/L_1} + \frac{\Delta W/L_3}{W/L_3}$$

Offset Folded cascode CMOS OTA

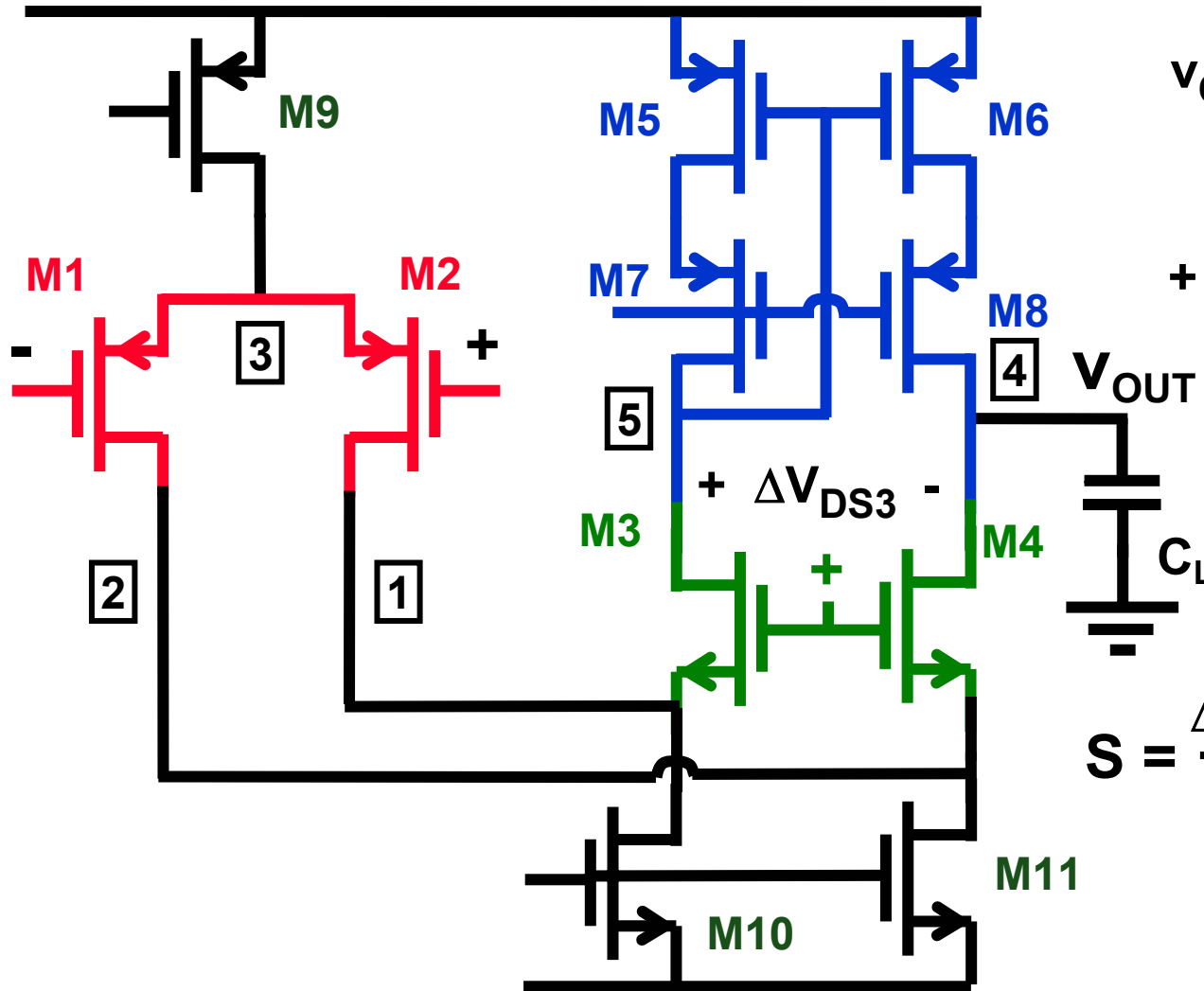

$$v_{OS} = \frac{\Delta V_{DS3}}{A_v} + \Delta V_{T1} + \frac{g_{m6}}{g_{m1}} \Delta V_{T5} + \frac{g_{m11}}{g_{m1}} \Delta V_{T11}^*$$

$$+ \frac{V_{GS1} - V_T}{2} S$$

$$S = \frac{\Delta K'_n}{K'_n} + \frac{\Delta K'_p}{K'_p} + \frac{\Delta W/L_{1,6,11}}{W/L_{1,6,11}}$$

Table of contents

- Random offset and $CMRR_r$
- Systematic offset and $CMRR_s$
- **CMRR versus frequency**
- Design rules
- Comparison MOST and bip.transistors

Ref.: Laker, Sansen : Design of analog ..., MacGrawHill 1994

CMRR vs frequency

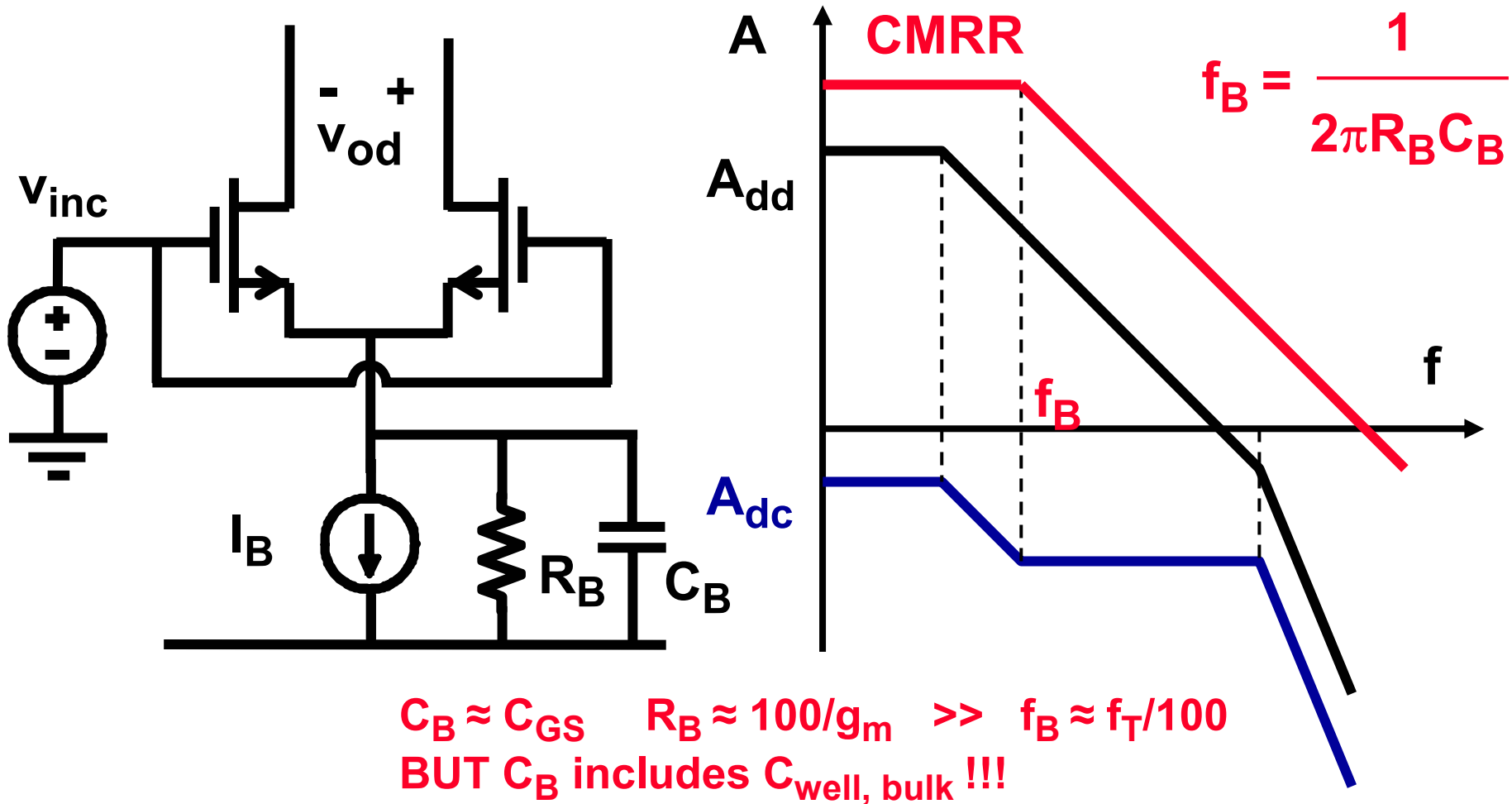


Table of contents

- Random offset and $CMRR_r$
- Systematic offset and $CMRR_s$
- $CMRR$ versus frequency
- Design rules
- Comparison MOST and bipolar transistors

Layout rules for low offset

1. Equal nature


2. Same temperature
3. Increase size
4. Minimum distance
5. Same orientation
6. Same area/perimeter ratio
7. Round shape
8. Centroide layout
9. End dummies
10. Bipolar always better !

Hastings,
“The Art of Analog Layout”
Prentice Hall 2001
R. Soin, ..”A-D Asics, .. ”
Peregrinus, 1991

Layout rules for low offset

1. Equal nature
2. Same temperature
3. Increase size
4. Minimum distance
5. Same orientation
6. Same area/perimeter ratio
7. Round shape
8. Centroide layout
9. End dummies
10. Bipolar always better !

On same isotherm

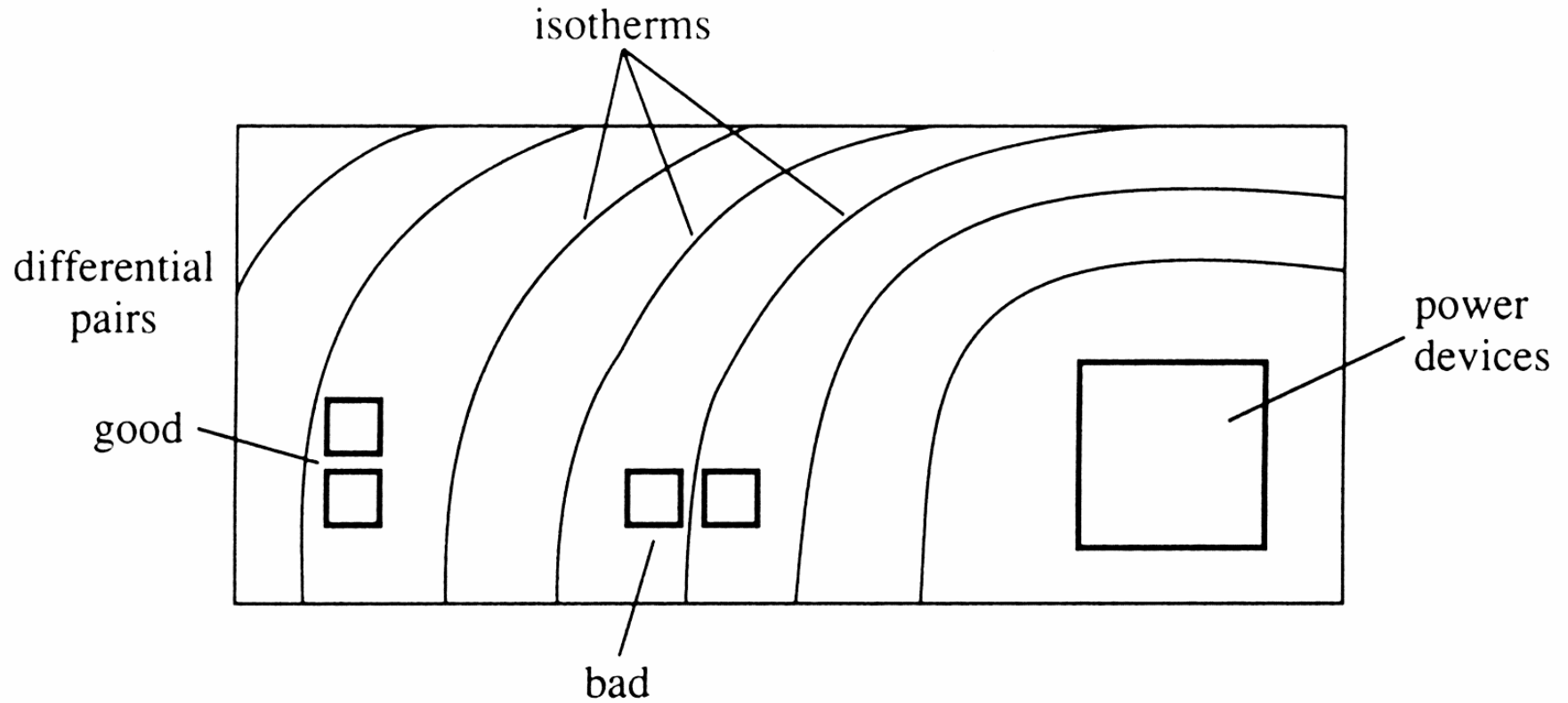


Solomon, JSSC Dec 74, 314-332

Layout rules for low offset

1. Equal nature
2. Same temperature
3. Increase size
4. Minimum distance
5. Same orientation
6. Same area/perimeter ratio
7. Round shape
8. Centroide layout
9. End dummies
10. Bipolar always better !

Layout resistor

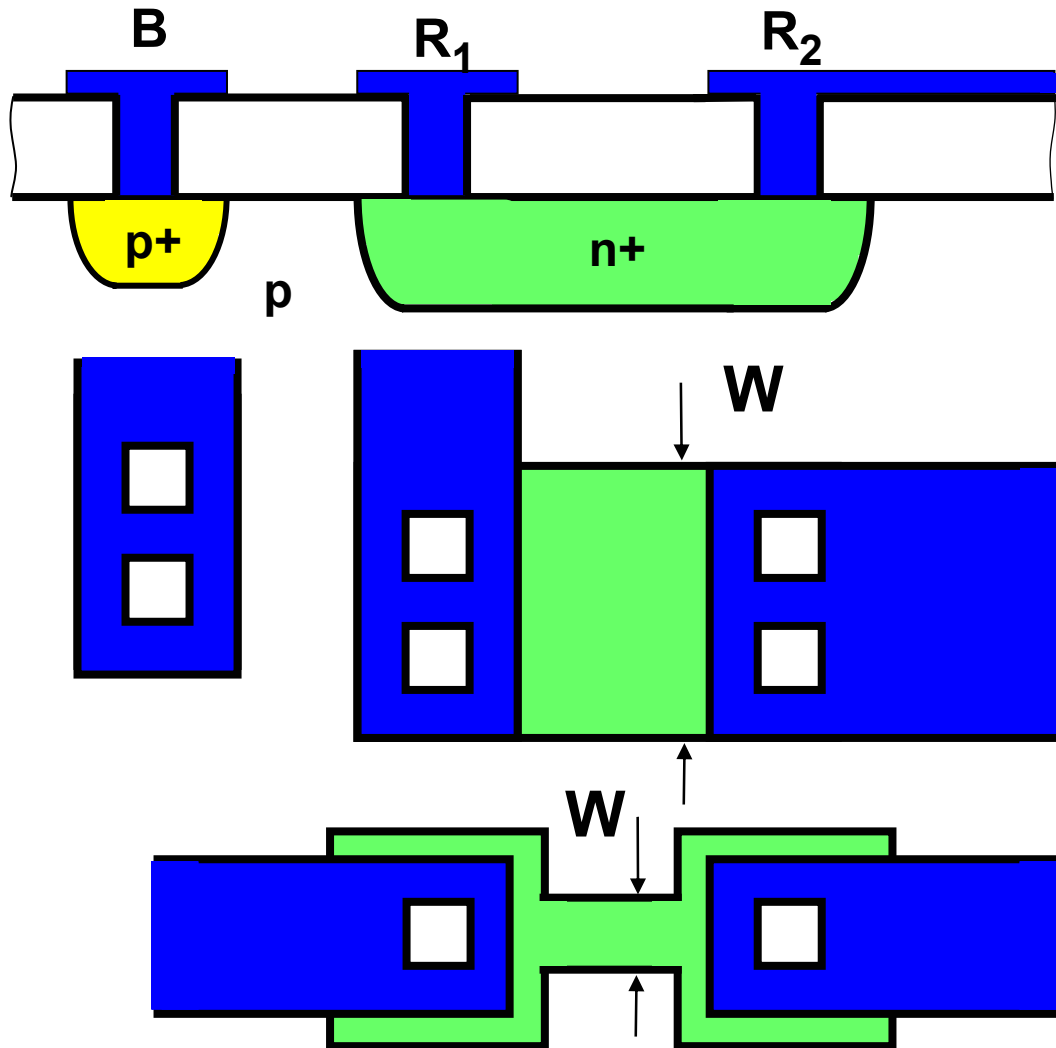


Source/drain
diffusion
resistor
in CMOS

Ref.: Laker, Sansen :
Design of analog ...,
MacGrawHill 1994
Table 2-6

Table resistors


Process	Type	$\rho \square$ Ω/\square	absolute accuracy percent	temperature coefficient percent/ $^{\circ}\text{C}$	voltage coefficient percent/V	breakdown voltage V
Bipolar	base diffusion	150	10	0.12	2	50
	emitter diffusion	10	20	0.02	0.5	7
	pinch resistance	5 k	40	0.33	5	7
	epi layer	1 k	10	0.3	1	60
	aluminum	50 m	20	0.01	0.02	90
	ion-implantation	2 k	1	0.02	0.2	20
	ion-implantation	200	0.3	0.02	0.05	20
CMOS	S/D diffusion	20-50	20	0.2	0.5	20
	well	2.5 k	10	0.3	1	20
	poly gate	50	20	0.2	0.05	40
	poly resistance	1.5 k	1	0.05	0.02	20
	aluminum	50 m	20	0.01	0.02	90
Thin film	NiCr(Ta)	200	1	0.005	0.005	90
	aluminum	50 m	20	0.01	0.02	90

Mismatch vs size for resistors


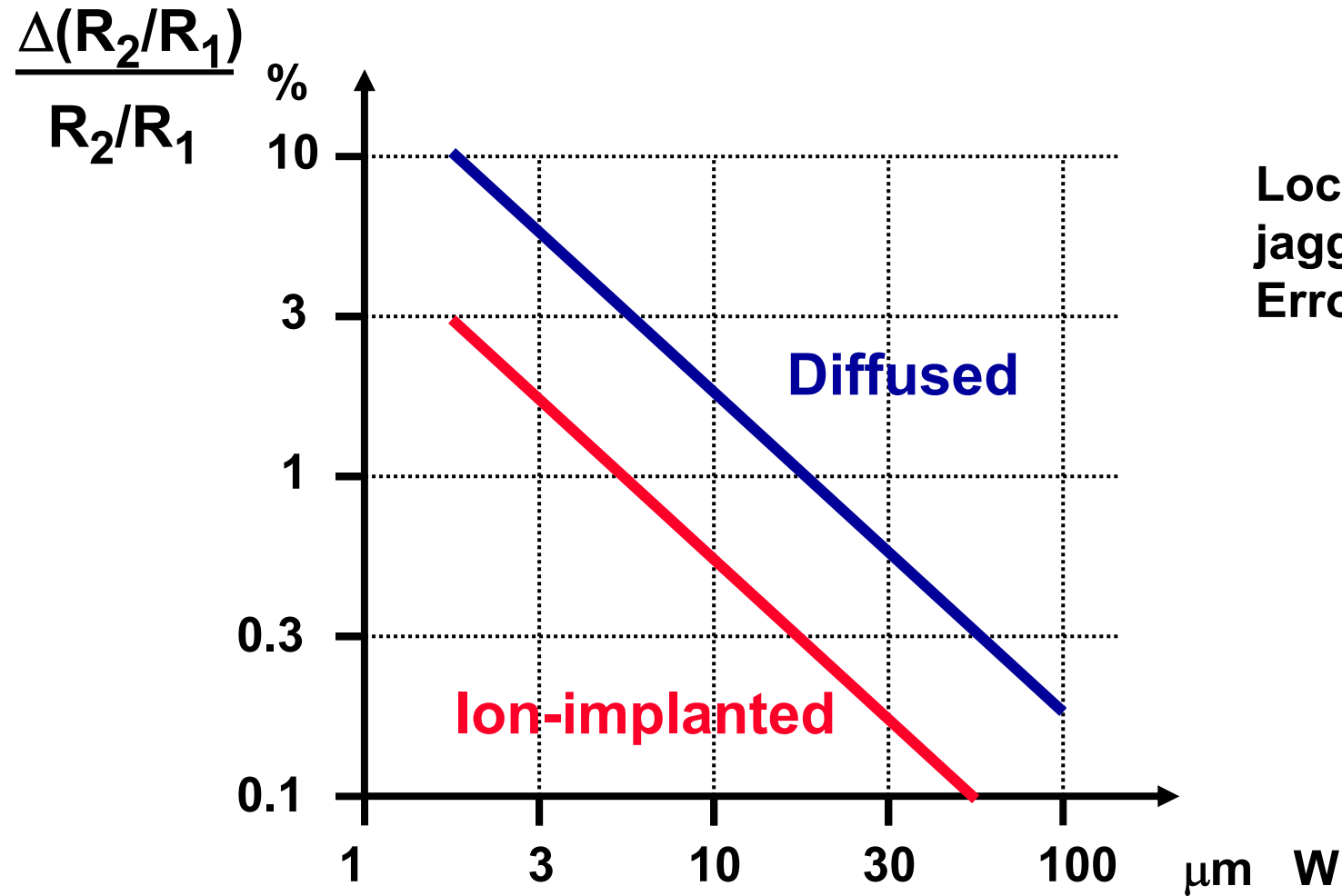


Local errors :
jagged edges, ..
Error $\sim 1/\text{size}$

Layout capacitors

 

Poly to S/D capacitor

  

Poly to poly capacitor


$$C_{\text{par}} \approx \frac{1}{6 \dots 15} C_{\text{pp}}$$

Table capacitors

Process	Type	C nF/cm ²	absolute accuracy percent	temperature coefficient percent/°C	voltage coefficient percent V	breakdown voltage V
Bipolar	C_{CB}	16	10	0.02	2	50
	C_{EB}	50	10	0.02	1	7
	C_{CS}	8	20	0.01	0.5	60
CMOS	$C_{ox}(50\text{ nm})$	70	5	0.002	0.005	40
	$C_{m,poly}$	12	10	0.002	0.005	40
	$C_{poly,poly}$	56	2	0.002	0.005	40
	$C_{poly,substrate}$	6.5	10	0.01	0.05	20
	$C_{m,substrate}$	5.2	10	0.01	0.05	20
	$C_{poly,substrate}$	6.5	10	0.01	0.05	20

**Ref.: Laker, Sansen :
Design of analog ...,
MacGrawHill 1994
Table 2-7**

Mismatch vs size for capacitors

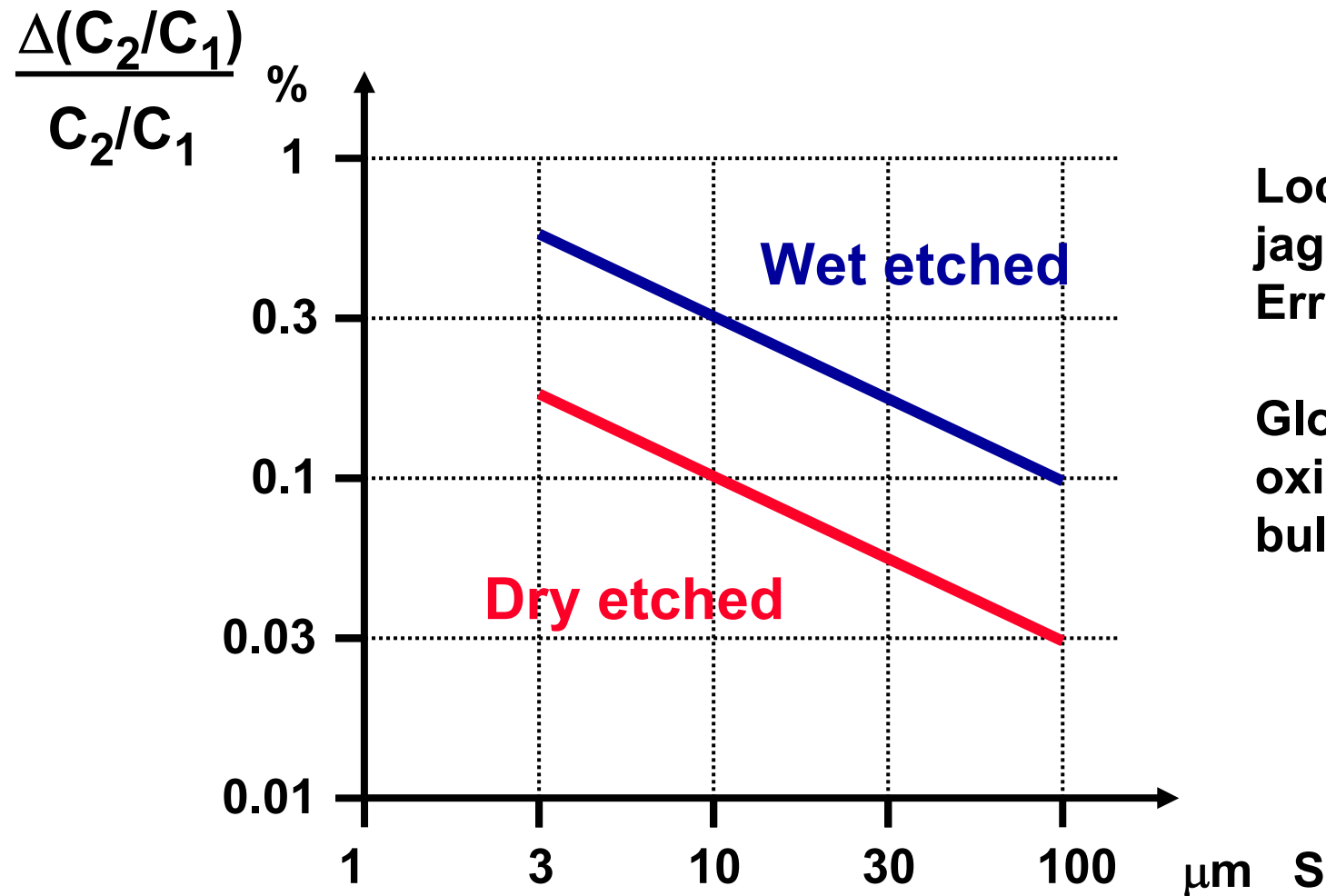

Local errors :
jagged edges, ..
Error $\sim 1/\text{size}$

Global errors :
oxide thickness,
bulk doping, ..


Layout rules for low offset

1. Equal nature
2. Same temperature
3. Increase size
4. Minimum distance
5. Same orientation
6. Same area/perimeter ratio
7. Round shape
8. Centroide layout
9. End dummies
10. Bipolar always better !

Layout rules for low offset

1. Equal nature
2. Same temperature
3. Increase size
4. Minimum distance
5. Same orientation
6. Same area/perimeter ratio
7. Round shape
8. Centroide layout
9. End dummies
10. Bipolar always better !

Matching of transistor pairs

 

Bad

Better


Better

Layout rules for low offset

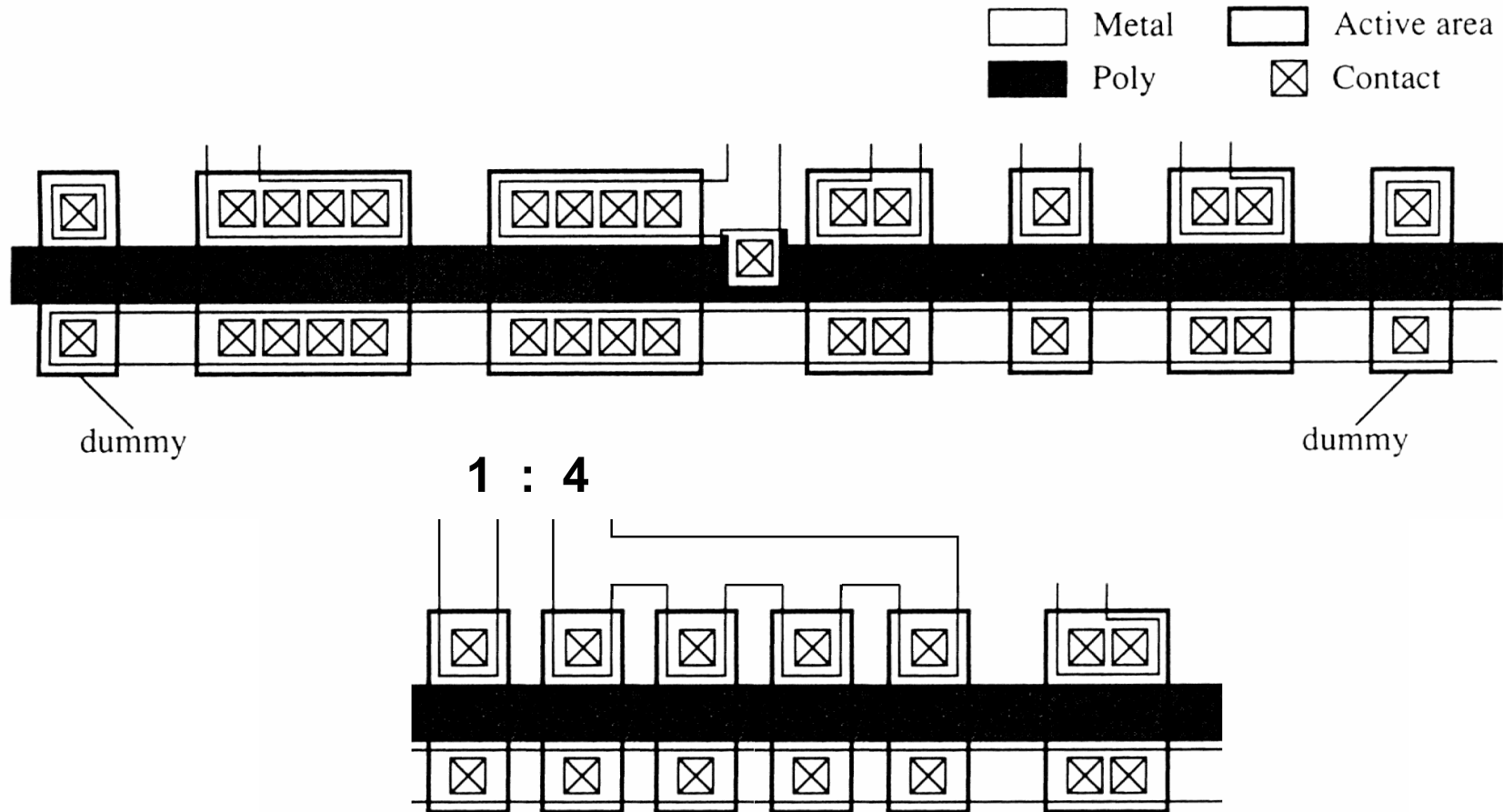1. Equal nature
2. Same temperature
3. Increase size
4. Minimum distance
5. Same orientation
6. Same area/perimeter ratio
7. Round shape
8. Centroide layout
9. End dummies
10. Bipolar always better !

Matching of current mirrors

Current mirror 4:4:2:1:2 with end dummies.




Layout rules for low offset





1. Equal nature
2. Same temperature
3. Increase size
4. Minimum distance
5. Same orientation
6. Same area/perimeter ratio
7. Round shape
8. Centroide layout
9. End dummies
10. Bipolar always better !


Layout rules for low offset

1. Equal nature
2. Same temperature
3. Increase size
4. Minimum distance
5. Same orientation
6. Same area/perimeter ratio
7. Round shape
8. Centroide layout
9. End dummies
10. Bipolar always better !

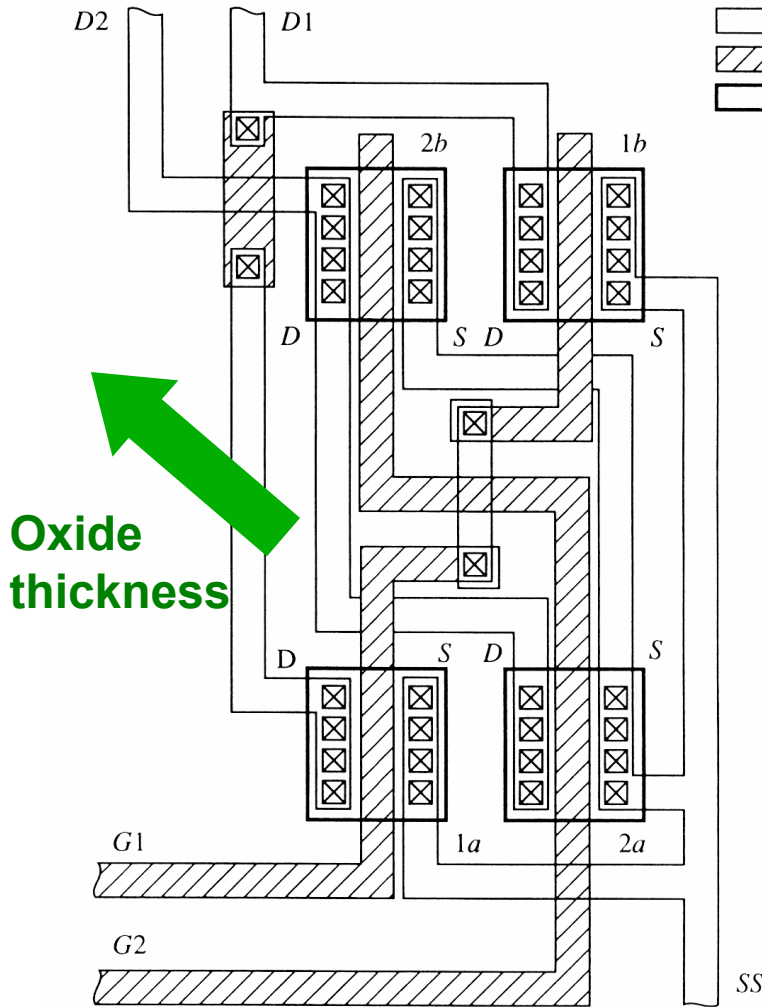Cross-coupled differential pair

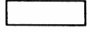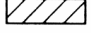

 
-  Metal
-  Poly
-  Active area
-  Contact



Less sensitive
to global variations :
Oxide thickness
Substrate doping level

.....

Centroide layout of capacitors

 

Ratio:

1

2

4

8


16

Layout rules for low offset

 
1. Equal nature
2. Same temperature
3. Increase size
4. Minimum distance
5. Same orientation
6. Same area/perimeter ratio
7. Round shape
8. Centroide layout
9. End dummies
10. Bipolar always better !

Matching of current mirrors

Current mirror 4:4:2:1:2 with end dummies.



Layout capacitance ratio

 

Ratio $7/2 = 3.5$

Courtesy Vittoz

Layout rules for low offset

1. Equal nature
2. Same temperature
3. Increase size
4. Minimum distance
5. Same orientation
6. Same area/perimeter ratio
7. Round shape
8. Centroide layout
9. End dummies
10. Bipolar always better !

Table of contents

- **Random offset and $CMRR_r$**
- **Systematic offset and $CMRR_s$**
- **CMRR versus frequency**
- **Design rules**
- **Comparison MOST and bipolar transistors**

Offset of MOST and bipolar transistors

MOST :
$$v_{OS} = \Delta V_T + \frac{V_{GS} - V_T}{2} \left(\frac{\Delta R_L}{R_L} + \frac{\Delta K'}{K'} + \frac{\Delta W/L}{W/L} \right)$$

Bipolar :
$$v_{OS} = \frac{kT}{q} \left(\frac{\Delta R_L}{R_L} + \frac{\Delta I_S}{I_S} \right) \text{ is much smaller !!}$$


1) no V_T

2) $kT/q \ll (V_{GS} - V_T)/2$


3) Drift decreases with v_{OS} :
$$\frac{\Delta v_{OS}}{\Delta T} = \frac{v_{OS}}{T}$$

Bipolar : Base current !

Bias or base currents

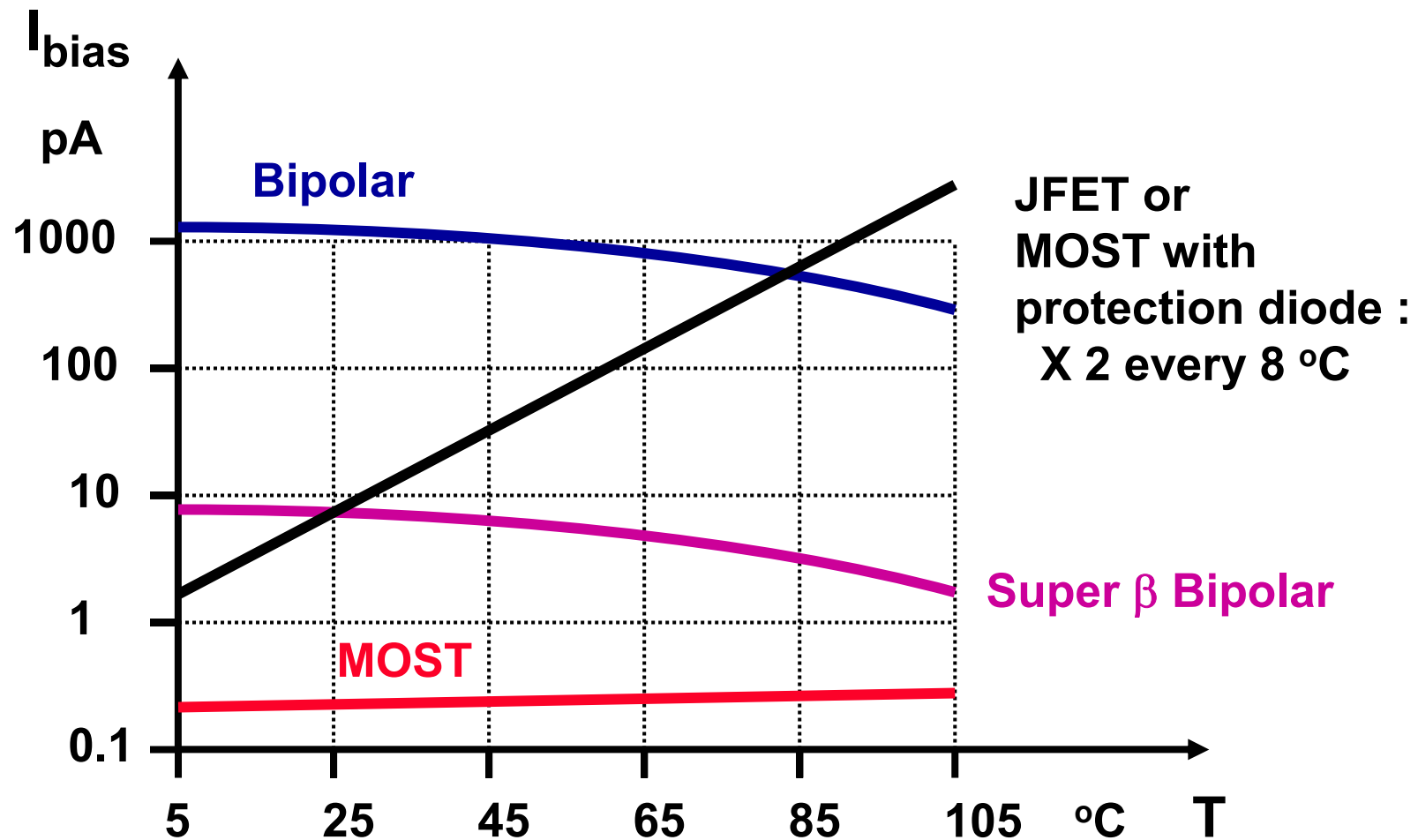


Base current compensation

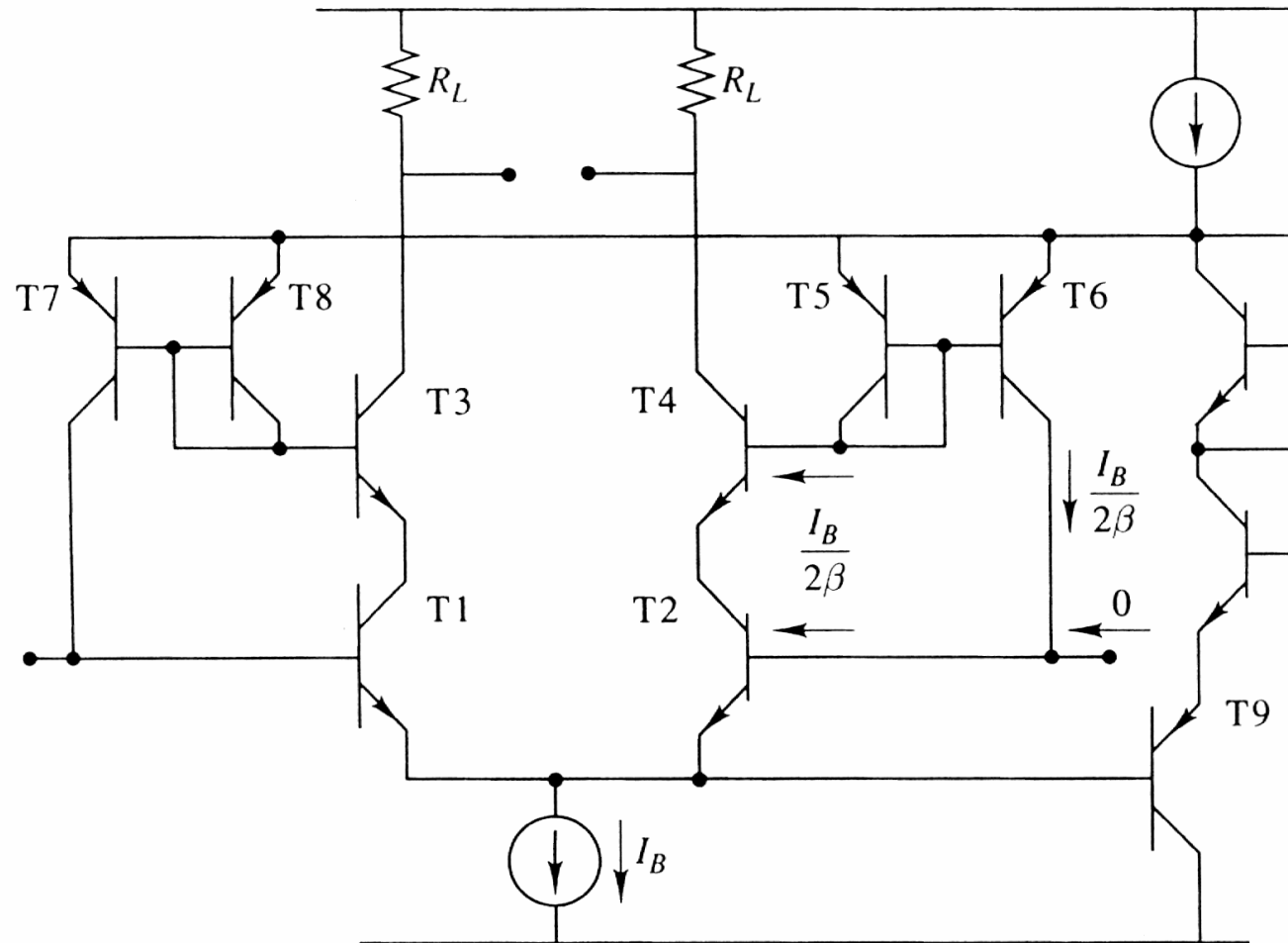


OP07

Common-mode base current compensation

OP27

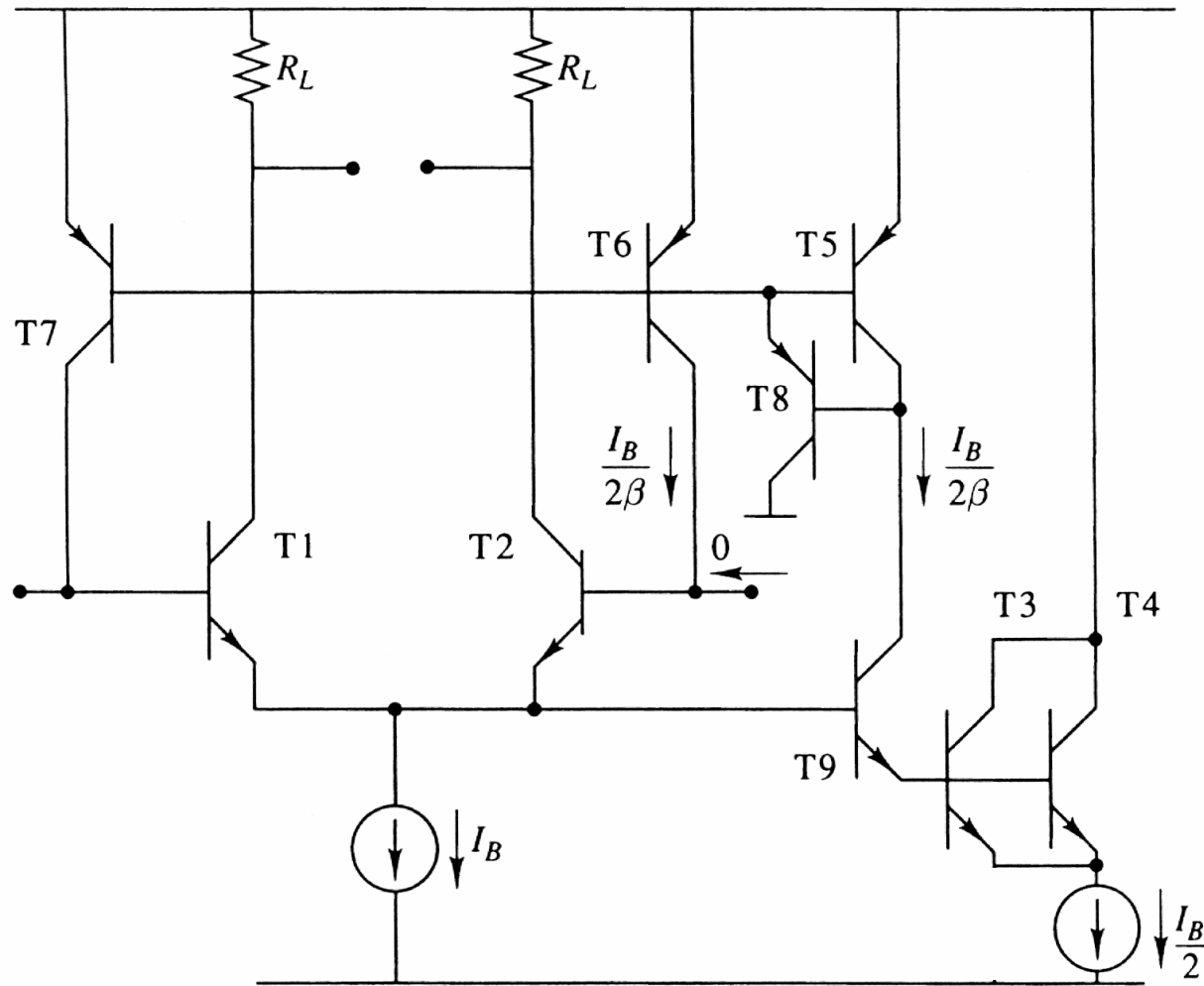

Tracking base current compensation

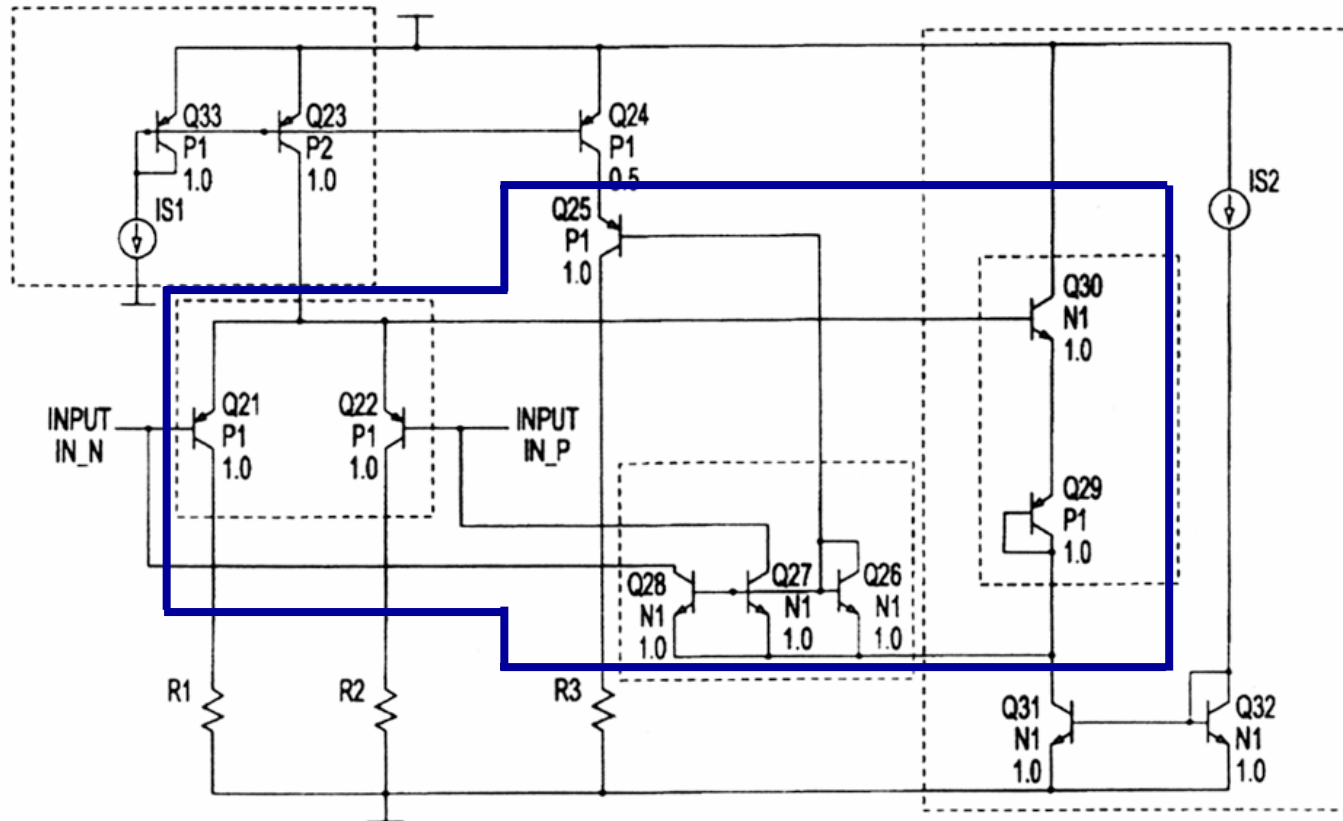


Q29 & Q30 provide a voltage clamp to track the input bias currents for changes in CM input voltage.

Ref. Gross, JSSC, Feb. 2004, 404.



OP-97 : input current compensation

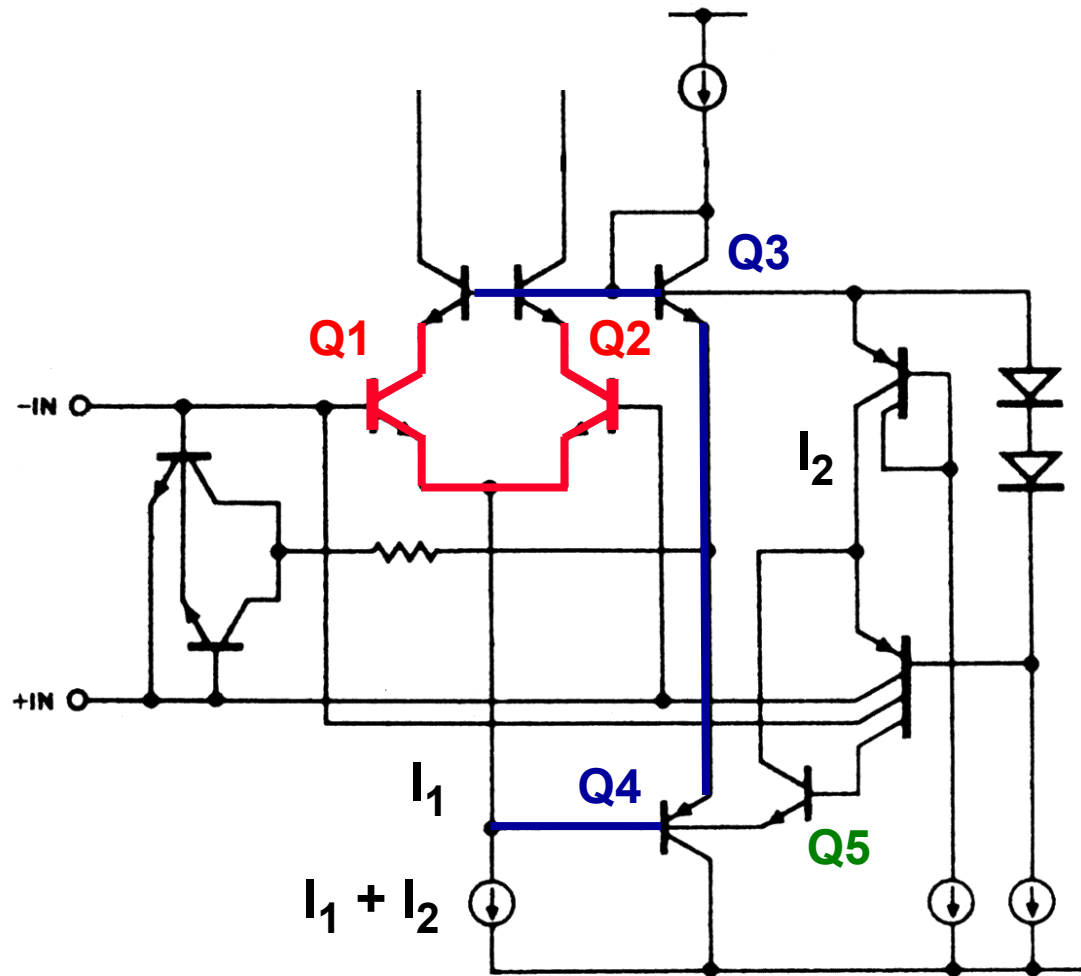

Low input currents
because
super- β transistors
at the input !

Require low V_{CE} !

$$V_{CE1,2} = V_{BEon} \approx 0.7 \text{ V}$$

Limits because of device mismatch

$$\frac{1}{(\text{Accuracy})^2} \approx \sigma^2 \left(\frac{\Delta I_{DS}}{I_{DS}} \right) \approx \frac{4 A_{VT}^2}{WL (V_{GS} - V_T)^2}$$

$$\text{Speed} \approx f_T = \frac{2 I_{DS}}{2\pi WL \frac{2}{3} C_{ox} (V_{GS} - V_T)}$$

$\frac{V_{DD}}{2}$

$$\frac{\text{Speed} \times (\text{Accuracy})^2}{\text{Power}} = \frac{1}{C_{ox} A_{VT}^2} \sim \frac{1}{t_{ox}}$$

= Technological constant

Limits because of device noise

$$S/N = \frac{V_{pp}^2 / 2}{4kT R BW}$$


$$S/N = \frac{V_{pp}^2 / 8}{kT / C}$$

$$P_{min} = \frac{V_{pp}^2}{R}$$

$$P_{min} = V_{DD} BW V_{pp} C$$

$$P_{min} \approx 8kT BW S/N$$

Noise versus mismatch for high DR

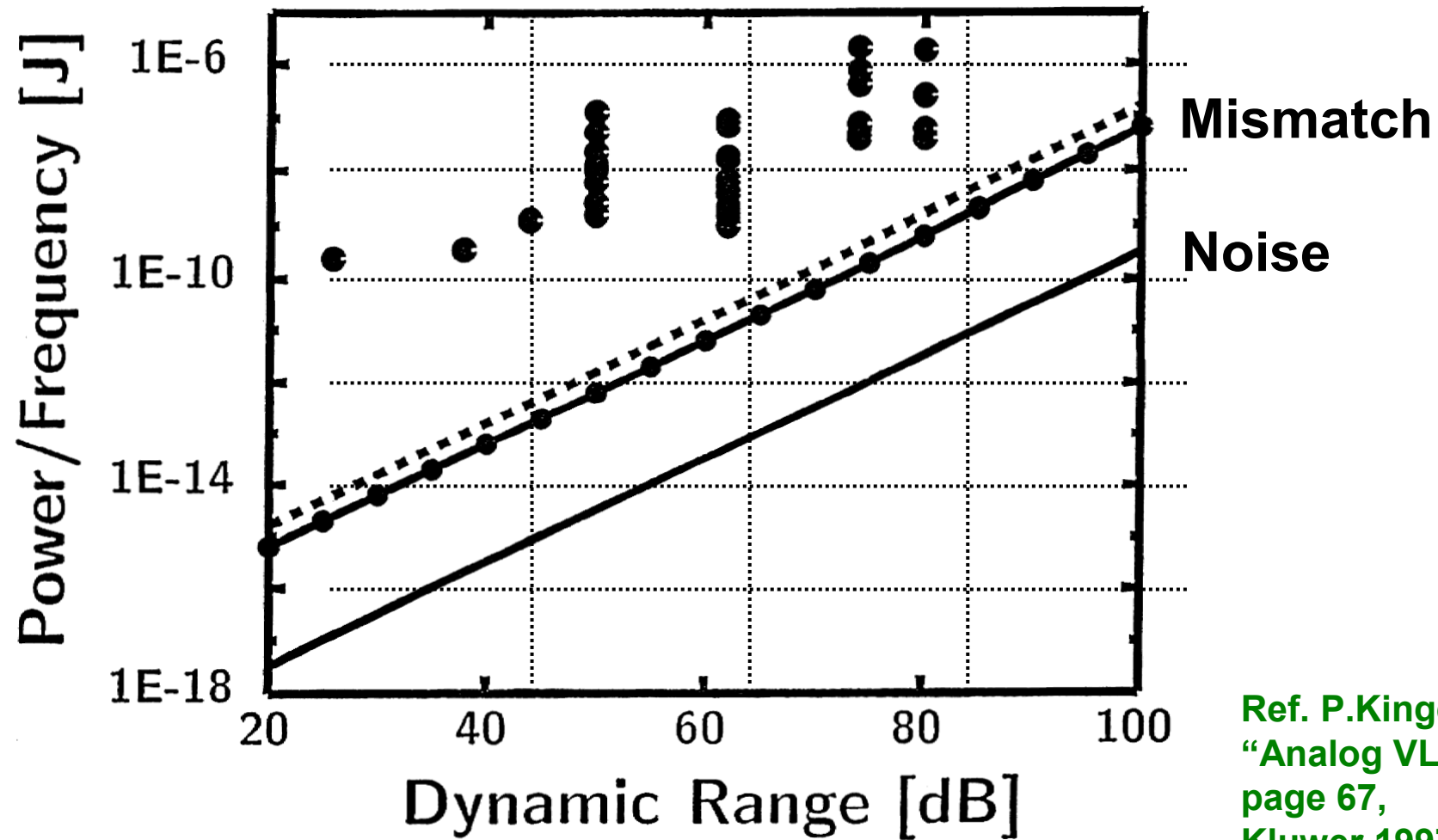

Ref. P.Kinget, ...
"Analog VLSI .."
page 67,
Kluwer 1997.

Reduced DR in deep submicron CMOS

 


Table of contents

- **Random offset and $CMRR_r$**
- **Systematic offset and $CMRR_s$**
- **CMRR versus frequency**
- **Design rules**
- **Comparison MOST and bipolar transistors**

Ref: Pelgrom, JSSC Oct.1989, 1433-1439
Croon, JSSC Aug.02, 1056-1064
Croon, Springer, 2005