
## <u>Crystal Oscillators - Layout Recommendations (specific examples)</u>

#### Example for a MSP430F123 oscillator layout:

- □ Crystal as close as possible at XIN/XOUT terminals.
- Separate GND below the crystal and load capacitors connected to the Vss terminal.
- Load capacitors grounded to the separate GND.
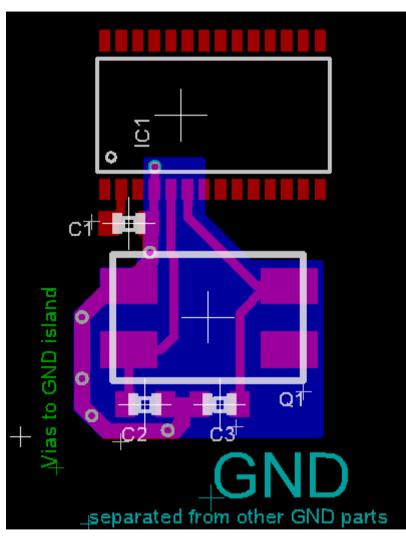
#### Support:


- Application report covering all oscillator related topics is in work.
- The App.Rep. will also give tested layout examples for every specific MSP430 package.



### <u>Crystal Oscillators - Layout Recommendations (specific examples)</u>
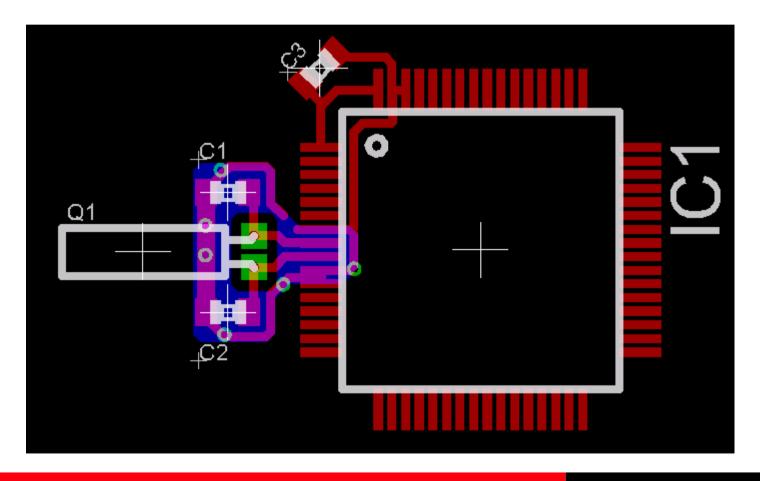
#### Example for a MSP430F413 oscillator layout:


□ Utilizing the nc spare pins beside the XIN/XOUT.



## <u>Crystal Oscillators - Layout Recommendations (specific examples)</u>
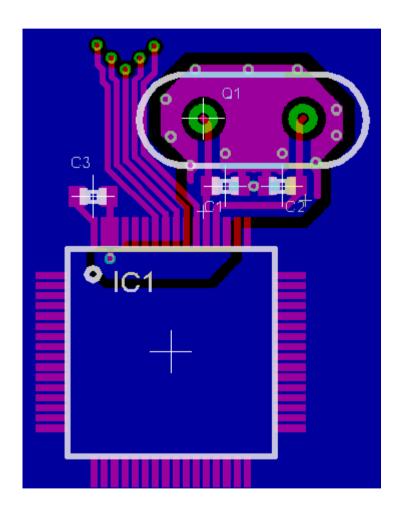
# Example for a MSP430F13x/14x XT2 oscillator layout:

- Distance between crystal an oscillator pins as short as possible
- ☐ Separate GND
- Load not absolutely balanced, can be compensated by C1/C2 adaptation.



TEXAS INSTRUMENTS