

CPE/EE 421 Microcomputers


WEEK #10

Interpreting the Timing Diagram


The 68000 Read Cycle

Timing Diagram of a Simple Flip-Flop


Idealized form of the timing diagram

 


Actual behavior of a D flip-flop

 

General form of the timing diagram

 

 An alternative form of the timing diagram



U A H


U A H

The Clock

- A microprocessor requires a clock that provides a stream of timing pulses to control its internal operations
- A 68000 memory access takes a minimum of eight clock states numbered from clock state S0 to clock state S7



Alan Clements

5

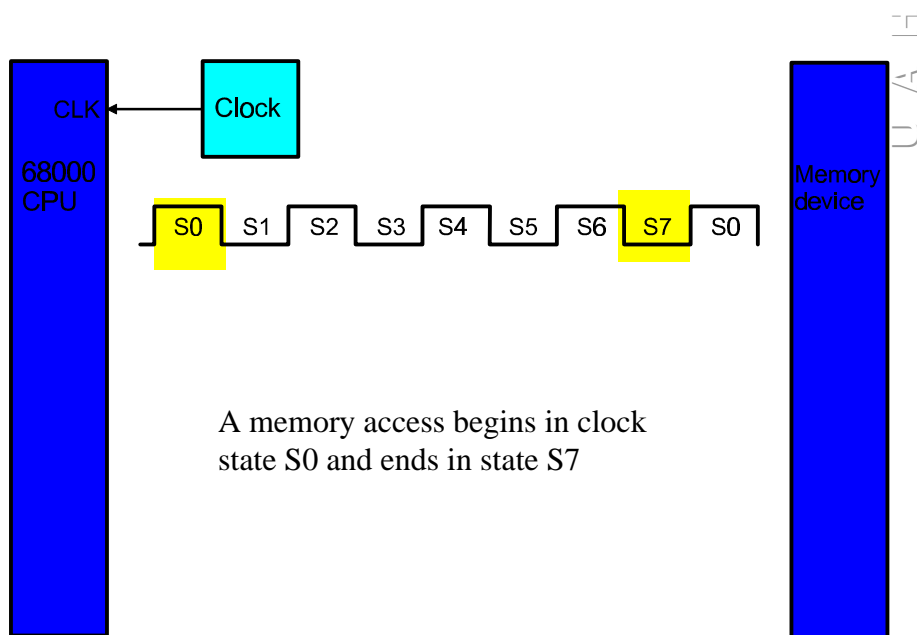

Alan Clements

6

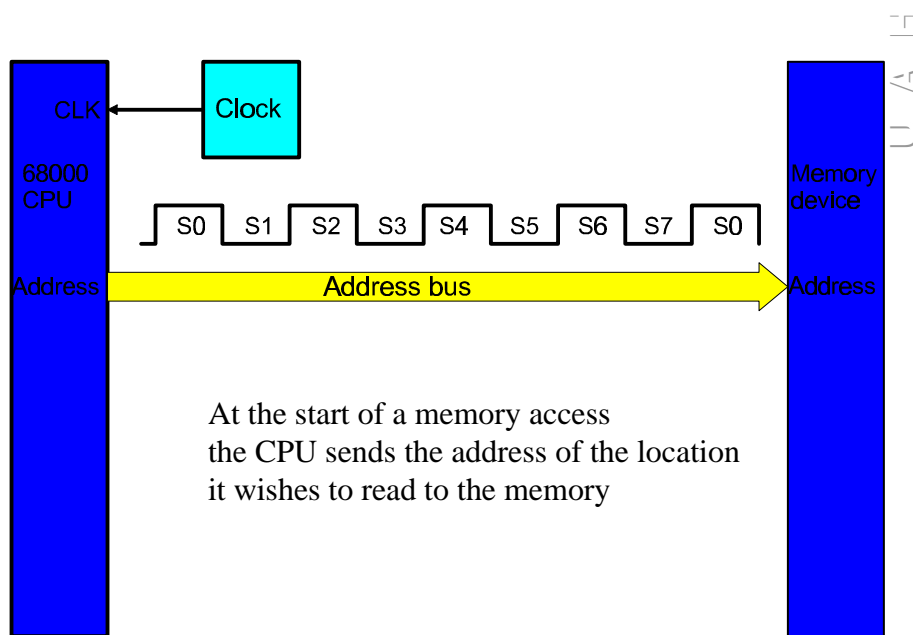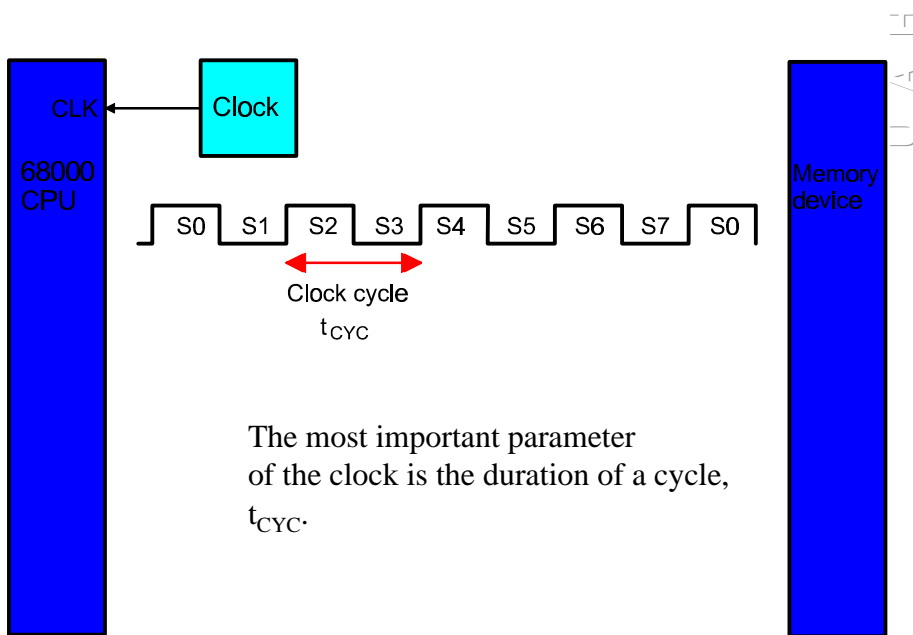


Address Timing

- We are interested in **when** the 68000 generates a new address for use in the current memory access
- The next slide shows the relationship between the new address and the state of the 68000's clock


Alan Clements

9

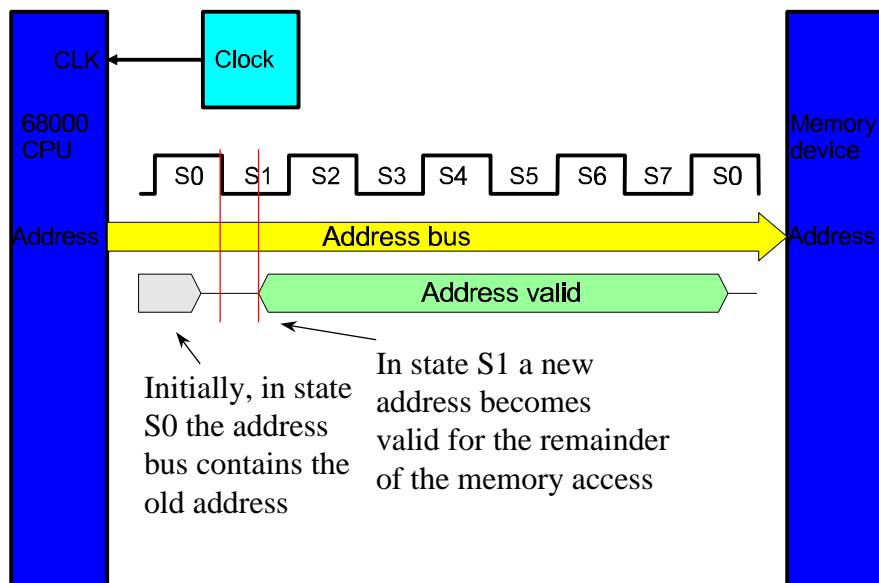



Alan Clements


10

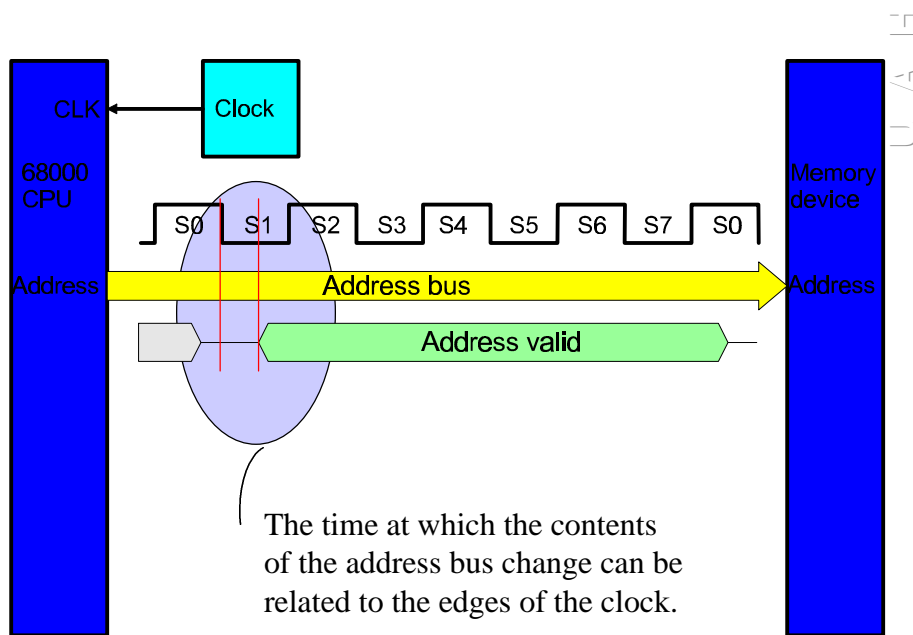

Address Timing

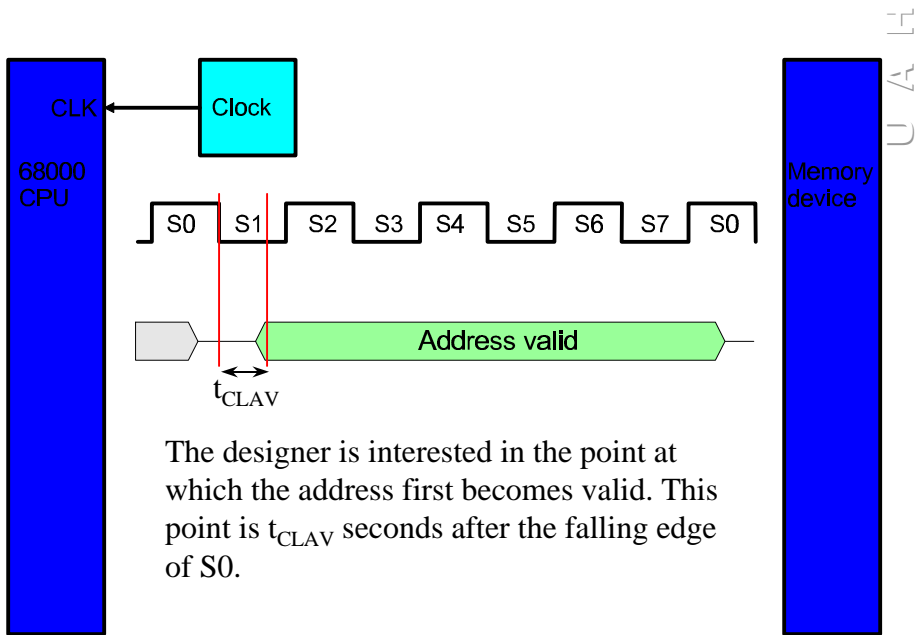
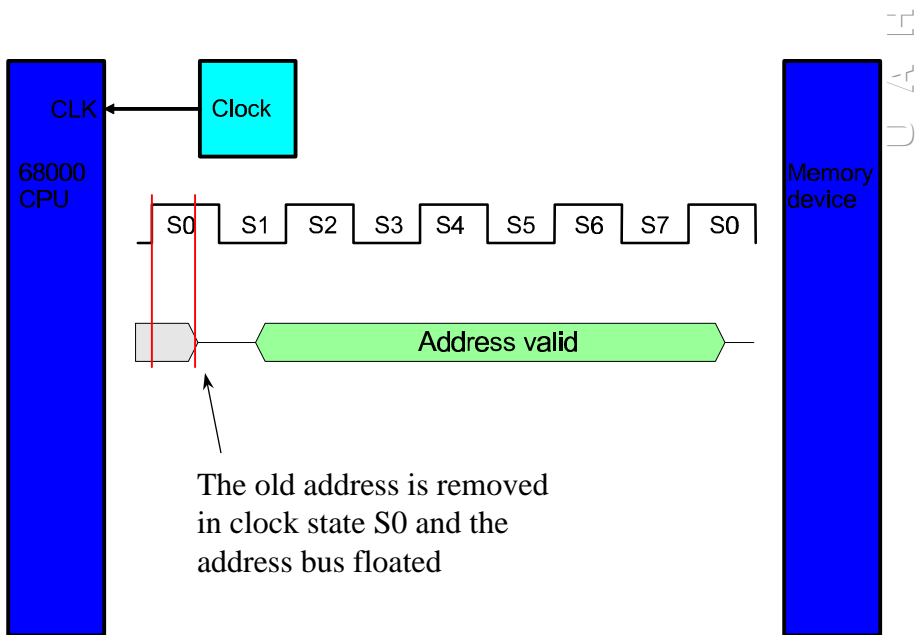
- Let's look at the sequence of events that govern the timing of the address bus
- The "old" address is removed in state S0
- The address bus is floated for a short time, and the CPU puts out a new address in state S1



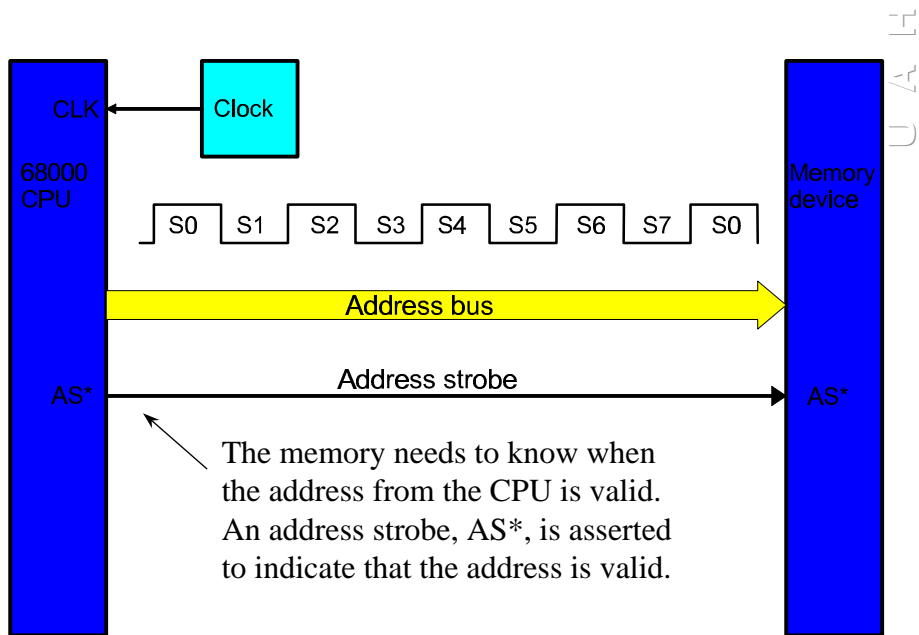

Address and Address Strobe

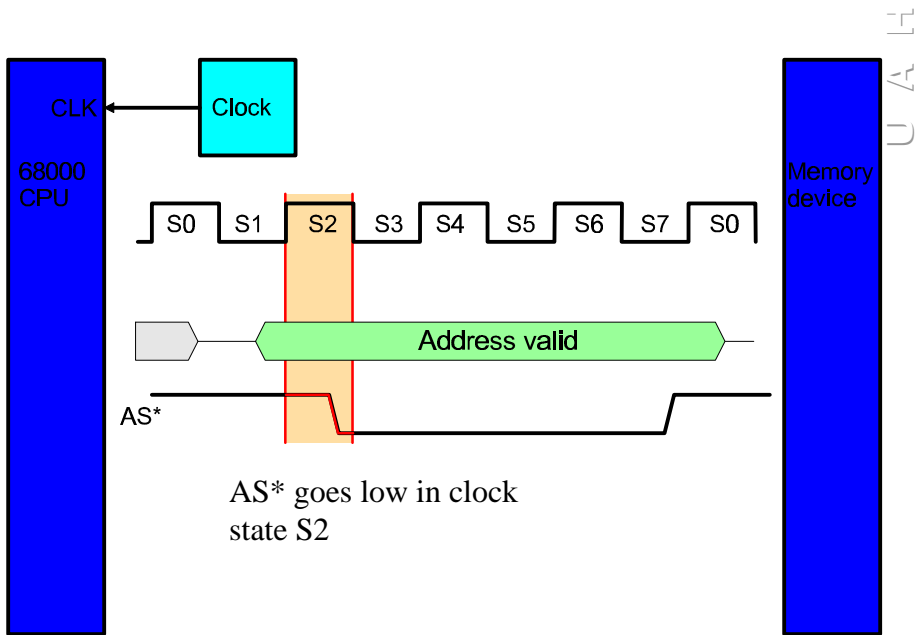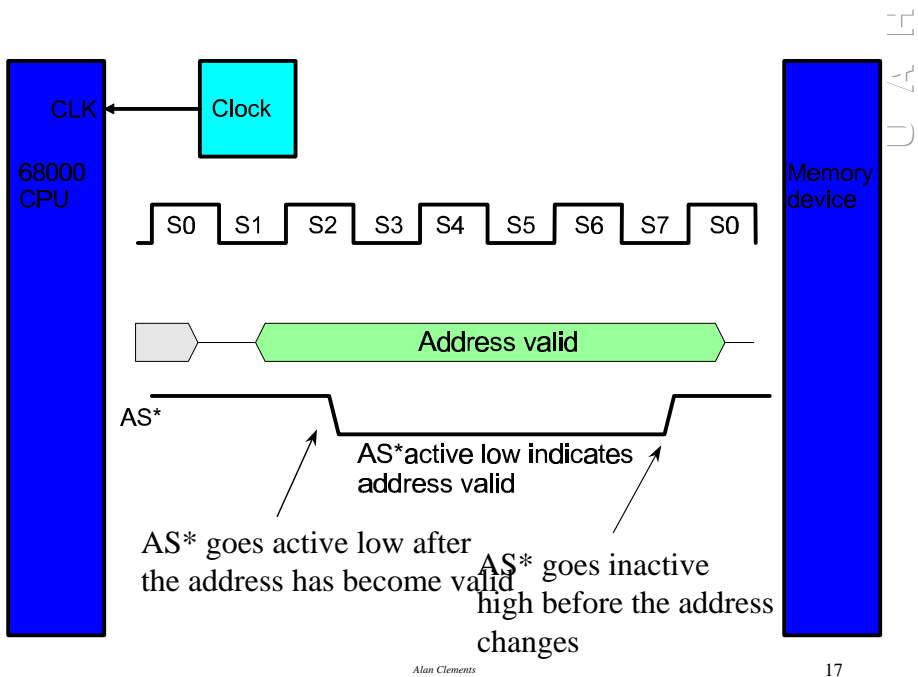- We are interested in the relationship between the time at which the address is valid and the time at which the address strobe, AS*, is asserted
- When AS* is *active-low* it indicates that the address is valid
- We now look at the timing of the clock, the address, and the address strobe




The Data Strobes

- The 68000 has two data strobes LDS* and UDS*. These select the lower byte or the upper byte of a word during a memory access
- To keep things simple, we will use a single data strobe, DS*
- The timing of DS* in a read cycle is the same as the address strobe, AS*

Alan Clements

19

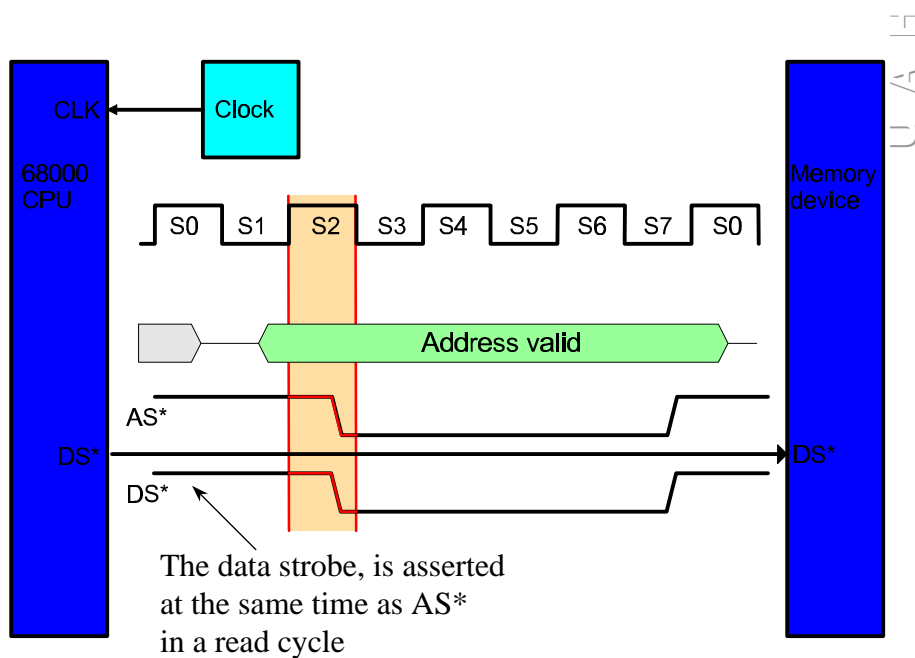

Alan Clements


20

The Data Bus

- During a read cycle the memory provides the CPU with data
- The next slide shows the data bus and the timing of the data signal
- Note that valid data does not appear on the data bus until near the end of the read cycle

Alan Clements

21

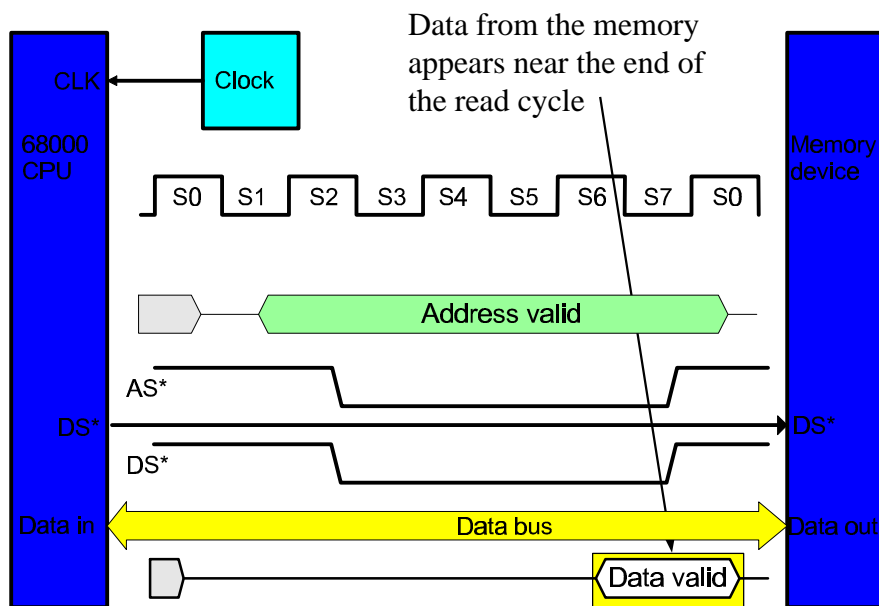

Alan Clements


22

Analyzing the Timing Diagram

- We are going to redraw the timing diagram to remove clutter
- We aren't interested in the signal paths themselves, only in the relationship between the signals


Alan Clements

23

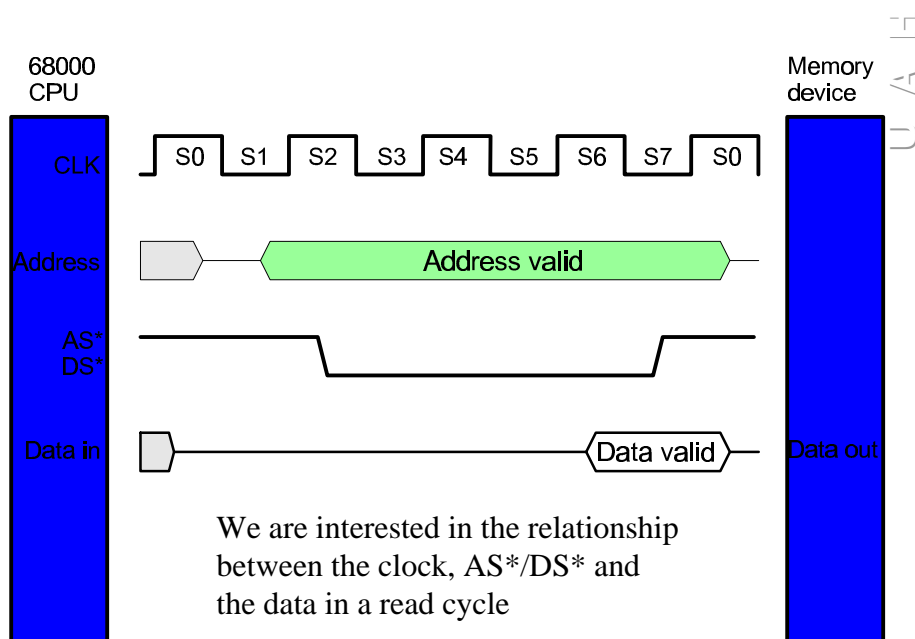


Alan Clements

24

 

Alan Clements

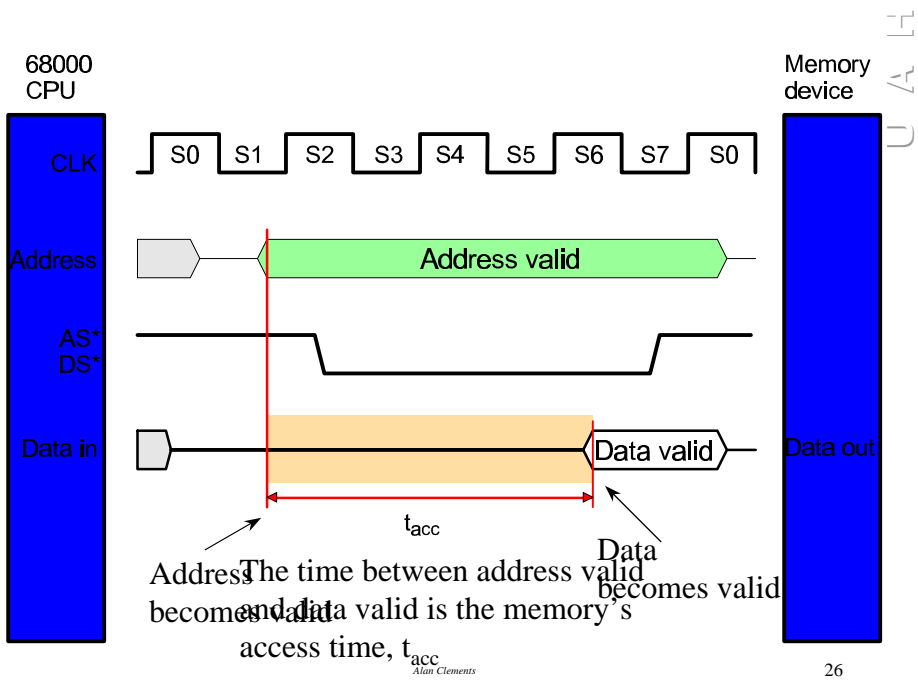


Alan Clements

Calculating the Access Time

- We need to calculate the memory's access time
- By knowing the access time, we can use the appropriate memory component
- Equally, if we select a given memory component, we can calculate whether its access time is adequate for a particular system



Alan Clements


27

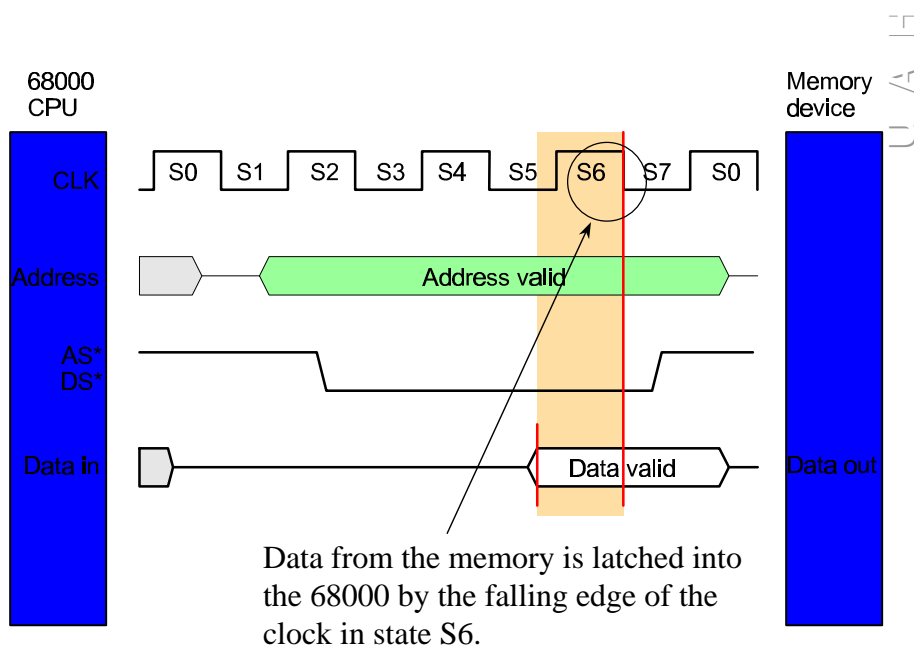

Alan Clements


28

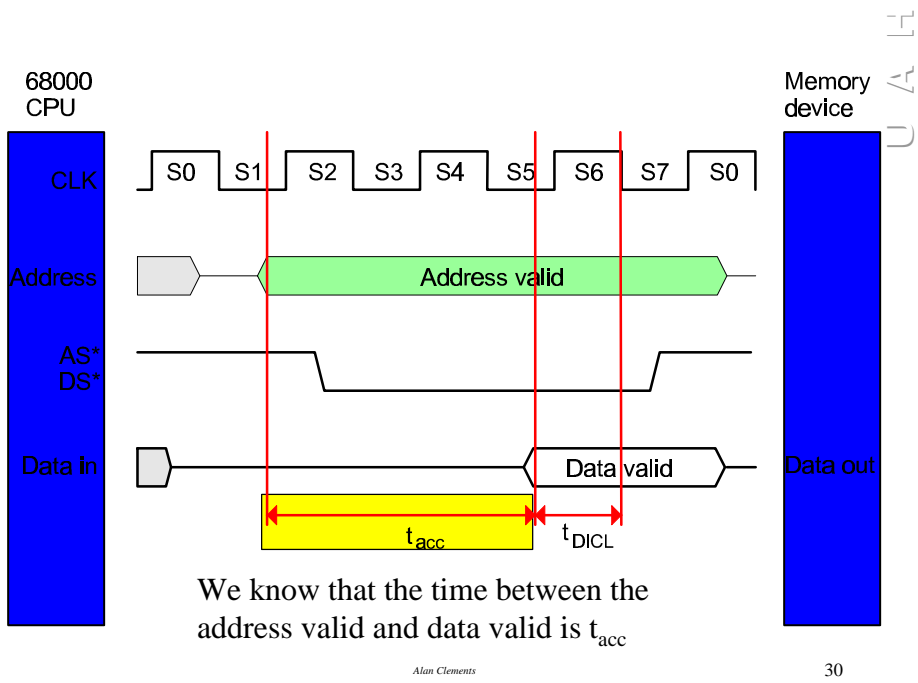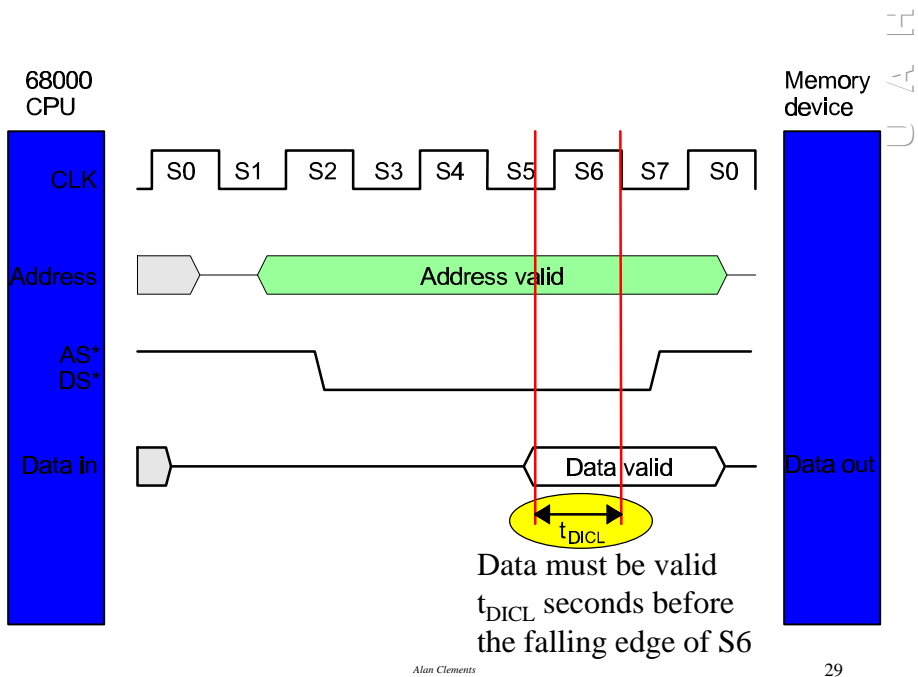

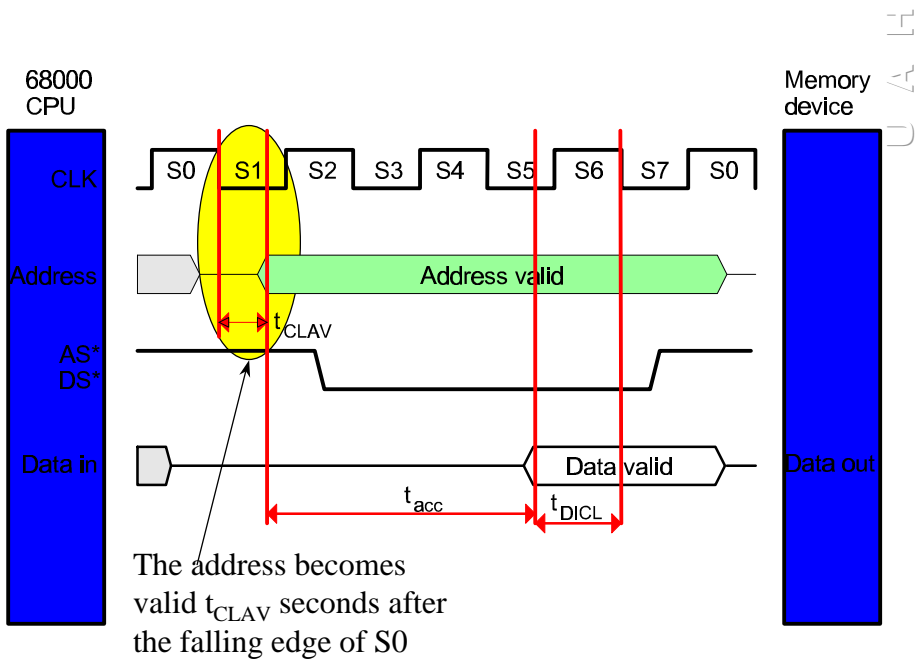


Alan Clements

31

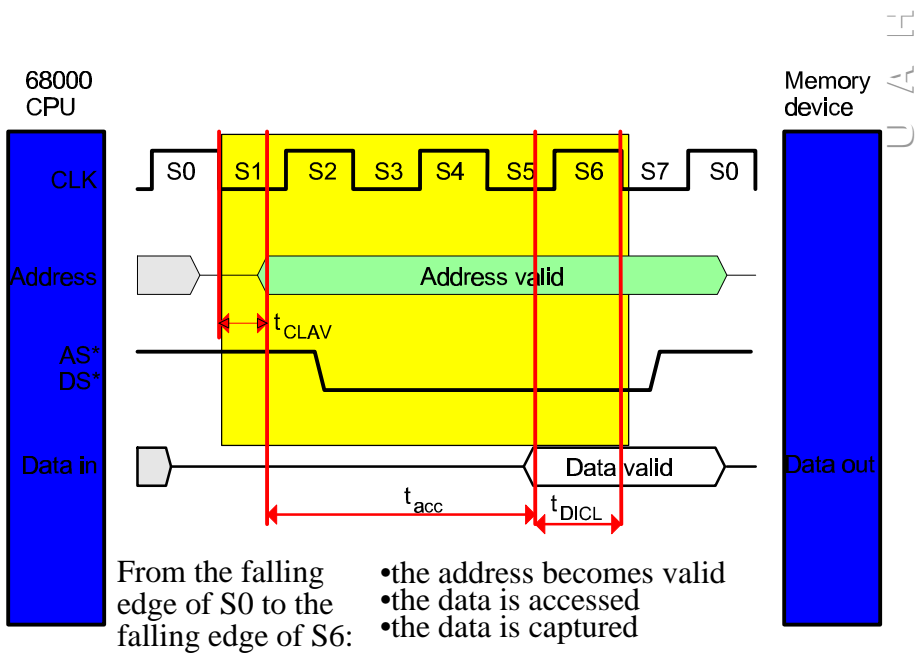


Alan Clements

32

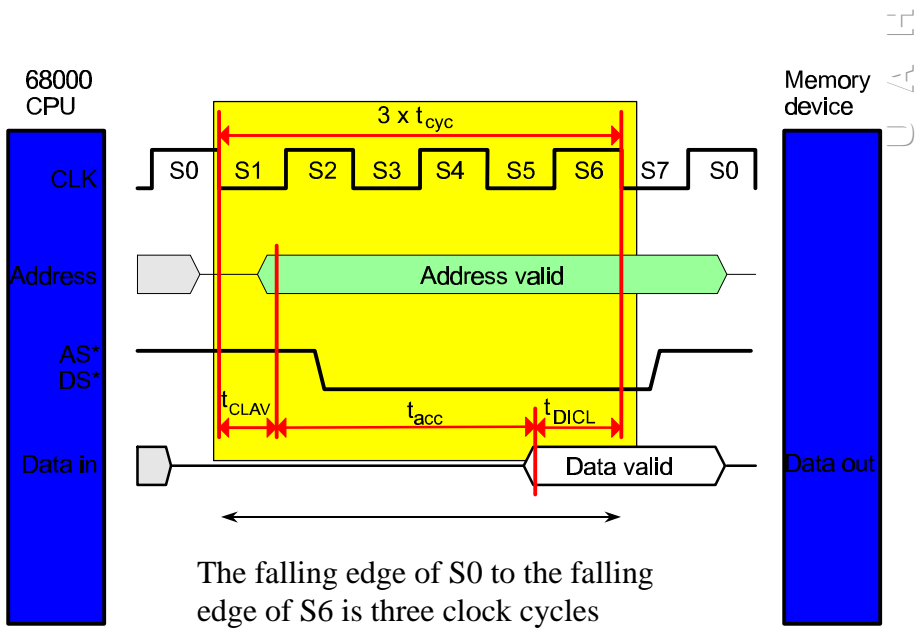

Alan Clements

33

 

Alan Clements

34

Timing Example

- 68000 clock 8 MHz $t_{\text{CYC}} = 125 \text{ ns}$
- 68000 CPU $t_{\text{CLAV}} = 70 \text{ ns}$
- 68000 CPU $t_{\text{DICL}} = 15 \text{ ns}$
- What is the minimum t_{acc} ?
- $3 t_{\text{CYC}} = t_{\text{CLAV}} + t_{\text{acc}} + t_{\text{DICL}}$
- $375 = 70 + t_{\text{acc}} + 15$
- $t_{\text{acc}} = 290 \text{ ns}$